

# ELECTRONICS

Australia

HIFI  
NEWS

MARCH, 1976  
AUST \$1.00\* NZ \$1.00



IBM scanning electron microscope

**BUILD OUR SIMPLE, NEW ELECTRONIC ORGAN!**  
**ALSO: TOUCH-CONTROLLED TABLE LAMP,**  
**NOVEL "LEDS AND LADDERS" GAME OF SKILL,**  
**FUNCTION GENERATOR USING A SINGLE IC**





## HOW DOES \$189\* SOUND? SUPERB!

The Sony PS2350 is a magnificent belt-driven turntable totally new in design and materials. The plinth is made of Sony's revolutionary new material BMC (bulk moulding compound), which is almost 100% acoustically dead. The 30 cms aluminium diecast platter and 4-pole hysteresis synchronous motor significantly reduce wow and flutter to under 0.06% (wrms) S/N ratio 63dB. The PS2350 has rubber disc supports to insulate the disc from vibration (a real hassle with conventional turntables). Here are a few of the PS2350's superb features: hydraulic cueing device, auto tone-

arm return, magnetic cartridge, reject mechanism and of course all the care and precision that people who understand good Hi-Fi have come to expect from Sony.

The price? \$189! Have a listen to the Sony PS2350 — we think you'll agree it's superb.

\*recommended retail price.

## "IT'S A SONY"

Hear the difference research makes

GAC.S.7611

For your nearest stockist call SONY Sydney 2.0221 Canberra 95.2100 Melbourne 874.8222 Brisbane 44.4488 Adelaide 268.3444 Perth 81.3422






# ELECTRONICS Australia


Australia's largest-selling electronics & hi-fi magazine

VOLUME 37 No 12

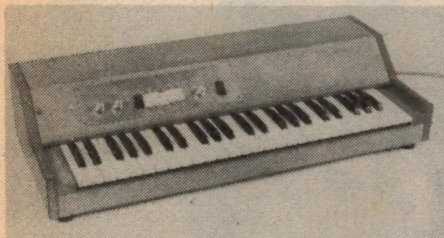

With this issue, we commence description of an easy-to-build, low-cost electronic organ that should suit beginner and enthusiast alike. The basic unit features 4-octave compass, two-speed vibrato of adjustable depth, pitch control, and four stops. Details on page 34.

## Coming next month!

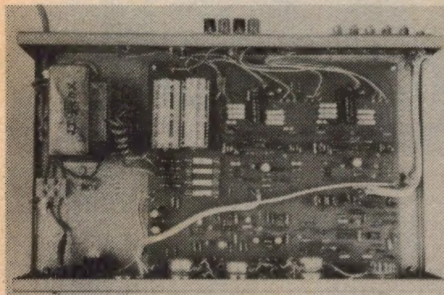

Don't miss the next issue in which we feature the first article on the exciting new Playmaster Twin Twentyfive stereo amplifier. It is really easy to build, all on a single PCB and uses readily available parts. Make sure you get your own copy!

## On the cover

Electron beam technology has been extensively developed at IBM Corporate Research Division, both to increase the resolving power of electron microscopes and to fabricate ultra-small devices. Shown here is the image produced by a surface scanning microscope whose novel design permits resolution of details 20-30 Angstroms in size, about three times smaller than can be seen with previous instruments. (Photo courtesy IBM Australia.)

## CONTENTS—MARCH, 1976

### world of electronics and hi-fi

- 3 Editorial: TV programs & advertising revisited
- 7 Hi-Fi News:  
*A portable radio "that costs the earth"—Toshiba-EMI integrated stereo—Pioneer headphones—Cantata cassettes—Semi-automatic turntable from Apan*
- 12 Developing a new recording tape
- 17 Review: Yamaha TC-800GL stereo cassette deck
- 21 Review: Sony ST-4950 FM tuner
- 28 The impact of radio on the maritime services
- 32 Optical fibre techniques in avionics data transmission
- 74 Forum: Time is running out for BC band DX

### projects and technical

- 34 At last: an electronic organ that's easy to build
- 40 Build this novel 'LEDs & ladders' game
- 46 When considering loudspeaker enclosures . . . how tight is "airtight"?
- 48 'Magic' table lamp uses low-cost touch switch
- 56 Crystal-locked converter for the LF and VLF bands
- 64 Simple function generator based on a single IC
- 68 DSB transmitter from junk-box parts
- 78 The serviceman: Batteries—and international standards
- 80 What's new in solid state: More on opto-coupler uses
- 84 Build your own electrostatic loudspeaker Pt 2
- 89 Circuit and design ideas:  
*Application for 74C14 CMOS Schmitt trigger—Try this IF noise limiter—Automatic brightness for digital clock—General purpose amplifier uses uA741cIC—Brake light warning indicator*
- 92 Introduction to digital electronics: Logic circuit "families"
- 96 Electronics Australia data: Disc records—new and old
- 97 Electronics Australia data: the frequency spectrum—2
- 98 Practical electronics demonstration: The bistable multivibrator
- 100 Index to Volume 37
- 108 New products:  
*CL8963/H Doppler alarm from ED&S—Elega DR-196C headphones—New supplier for transformers and metalwork—Function / sweep generator Collet knobs—Miniature relays—E-Z-Hook range*

### regular features

- 24 News highlights
- 102 Record reviews—classical
- 104 Record reviews—devotional, popular, jazz
- 112 Letters to the Editor
- 114 Book reviews
- 117 The amateur bands
- 121 Shortwave scene
- 123 Information centre
- 126 Marketplace—classified
- 128 Index to advertisers





# PHILIPS



## A screwdriver and about 1/2 an hour is all you need to build this 40 watt Philips speaker system.

Philips make it easy and inexpensive for you to own a professional speaker system. Assemble it yourself in about 30 minutes and you have 40 watt (RMS) capacity speakers to complement your hi-fi gear.

The AD8K40 Speaker Kit includes:

- 2 pre-cut, pre-finished wood grain cabinet enclosures with pre-painted baffle boards.
  - 2 mounted grill cloths with pre-painted baffle boards. • 2 x 8" woofers. • 2 x 1" dome tweeters.
  - 2 x 2-way crossover networks with leads and fastons fitted.
  - Innerbond lining. • Wood screws.
  - Wood glue. • Caulking compound.
- Plus full assembly instructions.

For further information contact  
ELCOMA  
Electronic Components and Materials,  
P.O. Box 50,  
Lane Cove N.S.W. 2066.  
Or phone 42 1261 or 42 0361  
Branches in all States.

# ELCOMA

153-111





## Editorial Viewpoint

### TV programs & advertising—revisited

Some 15 months ago in this column I was critical of the TV programs being broadcast for children, and of the advertising with which they were heavily laced. I also expressed misgivings about the possible long-term effects of this material on the psychological development of our children, pointing out how little we really know as yet about the effects on either children or adults of audio-visual violence, or the emotion manipulating techniques used by advertisers.

Not surprisingly, these comments drew fire from people within the commercial TV and advertising industries. The main point made by the apologists was that I was not qualified to pass judgement upon TV programming or advertising, because I was not an "expert"—i.e., someone working in their industries. When this patently invalid argument was challenged, they fell back on the time-worn excuse that "we only give the public what it wants".

There are so many flaws in this argument that at the time I found it very difficult to believe it was being offered seriously—let alone sincerely. For a start, the rating system used to determine "what the public wants" at best only indicates how the public chose between the limited material which has already been broadcast; it gives no real indication of the material they would appreciate or benefit from in the future, if given a real choice.

Unfortunately despite the weak arguments of the apologists, it soon became clear that critics of the system like myself were simply voices in the wilderness. Nothing seemed likely to be done, and since then I had given up the subject as a lost cause.

It was therefore with great interest and satisfaction that I read the recent report on this same subject by two researchers at the Sydney Teachers College. As I mention in the review of this report on page 114 of this issue, it lends considerable weight to the view that we need to know much more about TV and its effects upon the young mind.

I hope this report meets with the interested reception it deserves—not just from broadcasting authorities, administrators, and researchers in education and sociology, but from those to whom programming and advertising should be of direct concern: parents. I hope also that the points it raises are given careful consideration by the ABCB committee currently looking into revision of the regulations concerning TV programming and advertising.

In the meantime, those who are concerned about programs and advertising can help influence the eventual outcome by acting individually. Not just by the direct method of "channel selector censorship", but also by registering complaints with the stations, the advertisers and the ABCB whenever they see objectionable or suspect material.

If you don't do this, you can hardly complain if nothing much is done.

—Jamieson Rowe

#### EDITOR-IN-CHIEF

Neville Williams  
M.I.R.E.E. (Aust.) (VK2XV)

#### EDITOR

Jamieson Rowe  
B.A. (Sydney), B.Sc. (Technology, NSW)  
M.I.R.E.E. (Aust) (VK2ZLO/T)

#### ASSISTANT EDITOR

Philip Watson  
A.M.I.R.E.E. (Aust.) (VK2ZPW)

#### SCIENCE FEATURES

Greg Swain, B.Sc. (Hons, Sydney)

#### PRODUCT REVIEWS

Leo Simpson

#### TECHNICAL PROJECTS

David Edwards, B.E. (Hons, Tasmania)  
Ian Pogson (VK2AZN/T)

#### GRAPHICS

Robert Flynn

#### PRODUCTION

Ross Tester

#### ADVERTISING MANAGER

Selwyn Sayers

#### CIRCULATION MANAGER

Alan Parker

ON SALE THE FIRST MONDAY OF EACH MONTH.

Printed by Dalley-Middleton-Moore Pty Ltd, of Wattle St, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

\*Recommended and maximum price only.

#### Editorial Office

12th Floor, 235 — 243 Jones Street, Broadway, Sydney, 2007. Phone 2 0944. Postal Address: PO Box 163, Beaconsfield 2014.

#### Advertising Offices

Sydney — 57-59 Regent St, Sydney 2008. Phone: 699 3622.

Representative: Narcisco Pimentel.

Melbourne — 392 Little Collins St, Melbourne, 3000. Phone: 67 8131.

Representative: Keith Watts

Adelaide — Charles F. Brown & Associates Ltd, 168 Melbourne St., North Adelaide 5006

Representative: Tom Duffy 267 4377

Perth — 454 Murray Street, Perth 6000.

Representative: Jack Hansen 21 8217.

#### Subscriptions

Subscription Dept, John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001.

#### Circulation Office

21 Morley Ave, Rosebery, Sydney 2018. Phone 663 3911

#### Distribution

Distributed in NSW by Sungravure Pty Ltd, 57-59 Regent St, Sydney; in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 101-105 Weymouth St, Adelaide; in

Western Australia by Sungravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 22 Argyle St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.

#### Copyright. All rights reserved

Devices or arrangements shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice to patent rights.

All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia.



...re speakers you can really play with. Models are available with high or low resonance cones for use with electric guitars or as bass or wide-range speakers in hi-fi stereo systems.

CFL\* cones developed by Plessey and ferrite magnets provide improved frequency response, efficiency and reliability under the highest loadings.

In any application where you have high power inputs and you want high power and quality output, The Plessey C12P is supreme.

Full construction details for suitable enclosures for the C12P range are available on request.

Look for the Plessey CFL sticker—your guarantee of a speaker with exceptional performance characteristics.

Models and Frequency Response


Plessey C12P—Guitar, 55Hz-10kHz,

C12P—Woofer, 35Hz-10kHz,

C12PX—Wide range, 35Hz-13kHz.

C12PX—Guitar, 55Hz-13kHz

\*CFL with Plessey controlled fibre length cone.

**PLESSEY** 

# Power to play with.

**New high performance 12" speakers with CFL cones and 30 watts RMS.**


Plessey Australia Pty. Limited  
Components Division  
The Boulevard, Richmond.  
Victoria. 3121

Melbourne 423921 Brisbane 708097  
Sydney 720133 Perth 687111  
Adelaide 2236294



**Distributors & Stockists:** N.S.W. Lawrence & Hanson Pty. Ltd., Martin De Launay Pty. Ltd., Dick Smith Wholesale Pty. Ltd. VIC. Lawrence & Hanson Pty. Ltd., Radio Parts Pty. Ltd. W.A. Atkins Carlyle Ltd. QLD. The Lawrence & Hanson Electrical Co. (Qld.) Ltd. S.A. Gerard & Goodman Pty. Ltd. TAS. W. & G. Genders Pty. Ltd. N.Z. Plessey (N.Z.) Limited, Rata Street, Henderson, Auckland. In all states, Kits-Sets (Aust.) Pty. Ltd.



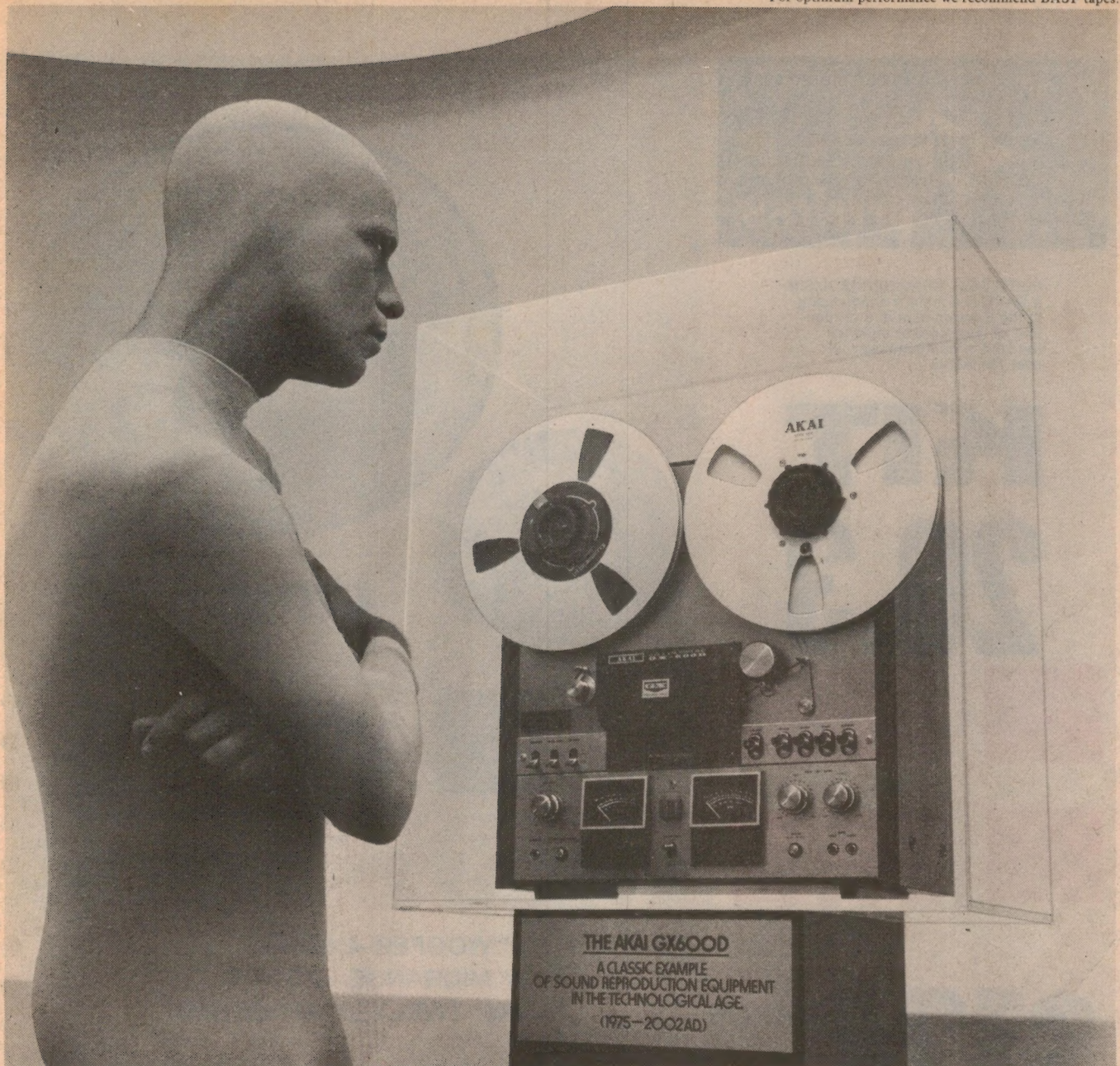

## Its rewards might be in another place and time, but yours are here and now.

The GX600D tape deck illustrated above is one of our top models. It retails around \$770. That's a lot. But the GX600D is a lot of tape deck. It's totally professional in every function. Recording, dubbing, mixing, playback.

Yet the controls are beautifully simple. After all, we want to give you good times. Not hard times.

It comes, like all AKAI hi-fi equipment distributed by AKAI Australia, with our Complete Protection Plan\*. Which simply

means 12 months full parts and labour warranty on all Tape Equipment, 2 years full parts and labour warranty on all Amplifiers, Turntables and Speakers and a lifetime warranty on all GX Tape Heads.

If you're still thinking about the price, think about this: sure, we could have compromised and saved a hundred. But we can't see any future in that.

The AKAI Hi-Fi Professionals are: **NEW SOUTH WALES — SYDNEY CITY AND METROPOLITAN.** Sydney: Douglas Hi-Fi, 338 George Street; Duty Free Travellers Supplies, 400 Kent Street; European Electronics, 187 Clarence Street; Instrol Hi-Fi, Cnr. Pitt & King Streets; Magnetic Sound Industries, 32 York Street; Jack Stein Audio, 275 Clarence Street. **Bankstown:** Selound Hi-Fi, Cnr. North Terrace & Apian Way. **Burwood:** Electronic Enterprises, 11 Burwood Road; Edge Electrix, 31 Burwood Road. **Concord:** Sonarta Music Services, 24 Cabarita Road. **Cremorne:** Photo Art & Sound, 287 Military Road. **Crows Nest:** Allied Hi-Fi, 330 Pacific Highway. **Hurstville:** Hi-Fi House, 127 Forest Road. **Liverpool:** Miranda Stereo & Hi-Fi Centre, 166 Macquarie Street. **Miranda Fair:** Miranda Hi-Fi & Stereo Centre, Shop 67, Top Level. **Mona Vale:** Warringah Hi-Fi, Shop 5, Mona Vale Court. **Parramatta:** Gramophone Shop, Shop 151, Westfield Shoppingtown; Selound Hi-Fi, 27 Darcy Street. **Roselands:** Roselands Hi-Fi, Gallery Level. **South Hurstville:** Selound Hi-Fi, 803 King George's Road. **Summer Hill:** Fidelia Sound Centre, 93B Liverpool Street. **Sutherland:** Sutherland Hi-Fi, 5 Boyle Street. **Waitara:** Hornsby Hi-Fi, 71 Pacific Highway. **Westleigh:** Sound Incorporated, 16 Westleigh Shopping Centre. **NEW SOUTH WALES COUNTRY.** **Albury:** Haberecht's Radio & TV, 610 Dean Street. **Bega:** Easdowns, 187-191 Carp Street. **Bowral:** Fred Hayes, 293 Bong Bong Street. **Broken Hill:** Pee Jay Sound Centre, 364 Argent Street. **Gosford:** Gosford Hi-Fi, 163 Mann Street; Miranda Stereo & Hi-Fi Centre, Cnr. Donnonson & Baker Streets. **Moss Vale:** Bourne's Merchandising, 1 White Street. **Newcastle:** Ron Chapman Hi-Fi, 880 Hunter Street; Eastern Hi-Fi, 519 Hunter Street. **Nowra:** Nowra Hi-Fi, Shoalhaven Arcade. **Taree:** Taree Photographics, Graphic House, 105 Victoria Street. **Wagga Wagga:** Haberecht's Radio & TV, 128 Baylis Street. **Wollongong:** Hi-Fi House, 268 Keira Street; Selound Hi-Fi, 2-6 Crown Lane. **A.C.T. Civic:** Allied Hi-Fi, 122 Bunda Street. **Fyshwick:** Allied Hi-Fi, 3 Paragon Mall, Gladstone Street. **QUEENSLAND.** **Brisbane:** Chandler's, 120 Edward Street; Chandler's, 399 Montague Road, West End; Stereo Supplies, 95 Turbot Street; Tel Air Electronics, 187 George Street. **Nambour:** Custom Sound, Currie Street. **Mt. Isa:** The Sound Centre, West Street. **Rockhampton:** Chandler's, 144 Alma Street. **Southport:** Stokes Electronics, Scarborough Street. **SOUTH AUSTRALIA.** **Adelaide:** Ernsmiths, 48-50 King William Street; Flinders Trading Co., 55 Flinders Street; Sound Centre 2001, 115 Gouger Street. **Blackwood:** Blackwood Sound Centre, 4 Coromandel Parade. **Glenside:** Steiner Electronics, Conygham Street. **Moana:** Bob Carmen, 185 Commercial Road. **VICTORIA.** **Melbourne:** Douglas Hi-Fi, 191 Bourke Street; Pantiles Hi-Fi, Cnr. Flinders Lane & Elizabeth Street. **Warrnambool:** A. G. Smith, 159 Liebig Street. **WESTERN AUSTRALIA.** **Perth:** The Audio Centre, 883 Wellington Street. **Calista:** Hub Hi-Fi, Kwinana Hub, Gilmore Avenue. **East Victoria Park:** Japan Hi-Fi, 889 Albany Highway. **Nedlands:** Audio Distributors, Broadway Shopping Centre, Broadway. **Midland:** Midland Audio, 16B Great Northern Highway. **Mosman Park:** Audio Distributors, 14 Glyde Street. **W.A. COUNTRY.** **Bunbury:** Aabel Music, 130 Victoria Street. **Kalgoorlie:** Hambley's Hi-Fi, Shop 13, Central Arcade, Hannan Street. **TASMANIA.** **Burnie:** James Loughran & Sons, 29-31 Wilnot Street. **Hobart:** Quantum Electronics, 181 Collins Street. **Launceston:** Wills & Co., 7 Quadrant. **NORTHERN TERRITORY.** **Darwin:** Pfitzners Music House, Smith Street.

\*The Complete Protection Plan does not cover equipment purchased outside Australia.

# AKAI

The name you don't have to justify to your friends.


70621





PEERLESS FABRIKKERNE A/S is a DANISH company specialising in the development and production of loudspeaker units for the High Fidelity industry all over the world.

# KIT 20.3

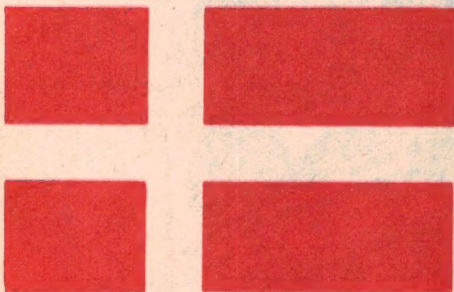

# \$124

PER PAIR


SPEAKER KITS ONLY  
NO TIMBER

CROSSOVER FREQ.	1500 & 6000 CPS
POWER HANDLING	50 WATTS RMS
POWER REQUIREMENT	6 WATTS RMS
FREQ. RESP.	55-20,000 CPS
CABINET SIZE	20 LITRES



8" WOOFER—L 825WG  
5" MIDRANGE—650 MRC  
2 1/4" TWEETER—MT225 HFC

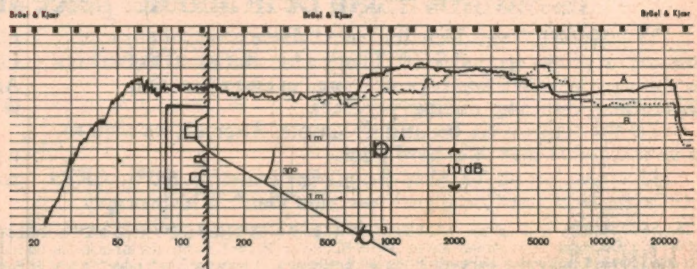
Sound pressure response curve for system 20-3.



Curve A: Axial pressure response frequency characteristic measured as per DIN 45500.  
Curve B: Corresponding curve measured 30° from axis (normal listening direction by stereo).

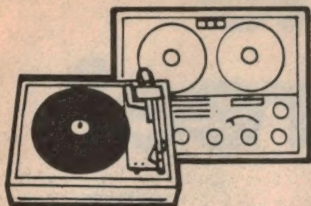Danish HI FI Southern Cross Plaza 638930 and Burke Road, Camberwell 824839 Melbourne. Convoy Technocentre Woolloomooloo 3582088 Sydney.  
Danish HI FI Mount Lawley 710100 Perth. Brisbane Agencies Audio Centre Fortitude Valley 219944 Brisbane.





# Hi Fi News

## A portable radio "that costs the earth..."

The above heading is neither critical of a product, nor is it original. It has been adopted by National Panasonic as a marketing slogan for their latest model the RF-8000: "A portable radio that costs the earth... But it gives you the world". At a recommended retail price of \$2,700, the first part of the slogan, at least, needs no further justification!


by NEVILLE WILLIAMS

Apart from their hifi products, National Panasonic are well known for their transistor portables, ranging from very small personal compacts to ambitious and expensive multiband portables. But it is safe to say that few enthusiasts will have envisaged or expected anything as pretentious—or as costly—as the new RF-8000.


It would surely represent some kind of an ultimate to the DX enthusiast.

Instead of the more usual three or four bands, the RF-8000 offers no less than 24, ranging in coverage from 150kHz to 230MHz, and distributed over two separate tuning dials.

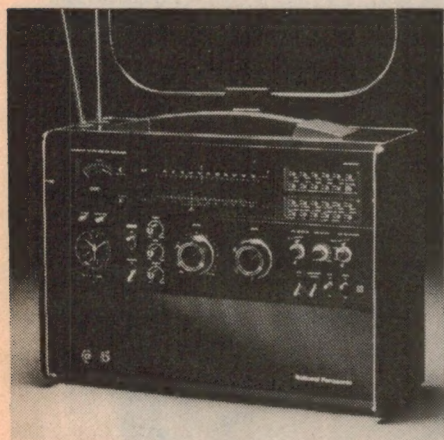The first group of bands cover long-wave, medium-wave, 8 VHF bands and 2 that are commonly used for marine weather broadcasts. In the second group are 12 short-wave bands, each 1MHz wide, and each with a substantially linear



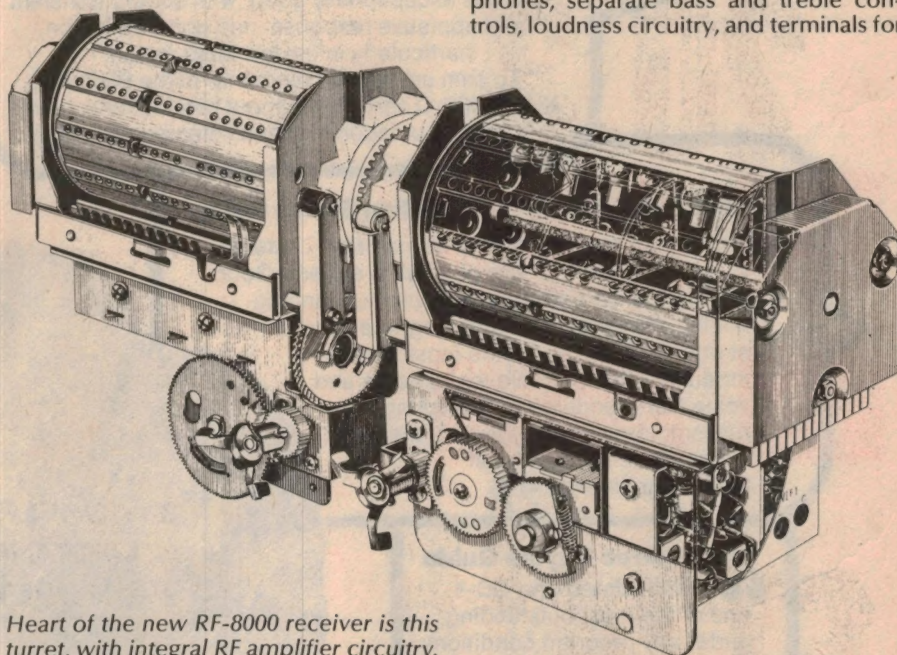Early pictures of the RF-8000 convey the impression of just another gimmicky portable. Only later does it become evident that it is possibly the most elaborate and expensive consumer portable radio ever devised!



Heart of the new RF-8000 receiver is this turret, with integral RF amplifier circuitry.

tuning scale. Not only does the receiver cover the various bands, but it can be switched for a variety of modes, AM, FM, SSB and CW. According to the manufacturers, the general performance must be equated, not to portable receivers as such, but to communications style equipment.

An in-built crystal calibrator is provided, which allows the dial to be set more precisely so that SW frequencies can be read off to an accuracy of at least 5kHz.

From the point of view of the user, band selection is the easiest yet to operate. The user merely presses the button and waits for a few seconds for the internal mechanism to respond. The digitally controlled system rotates the drums separately, as necessary, and illuminates a LED indicator to show that a particular dial is the one now in operation. Contacts in the turret system are gold-plated.

In the interests of efficiency and best signal/noise ratio, the SW and VHF bands have their own RF amplifier stages, built right into the turret sections.

The bandspread short-wave section uses the well known Collins approach: a double-change superhet, with a separate crystal for each band. This ultimately feeds into a 455kHz IF system with a 10-stage ceramic ladder type filter offering two stages of selectivity, multi-mode reception, amplified AGC, sideband selection, etc.

The VHF section can operate as a single change superhet into a conventional 10.7MHz IF system for wideband FM with AFC and squelch. However, it can be switched through the 455kHz IF system for narrow band operation (60dB down at 15kHz).

At the output end, the RF-8000 employs a 5-stage wide-range amplifier (50Hz to 20kHz) with provision to drive two built-in 7 x 4in loudspeakers or phones, separate bass and treble controls, loudness circuitry, and terminals for

auxiliary input, record output and external loudspeaker.

In keeping with the likely needs of the complete DX enthusiast, the RF-8000 also has its own in-built precision clock, based on a tuning fork and operating from its own 1.5V battery.

For portable use, the receiver operates from 8 "D" size torch cells, giving a nominal output voltage of 12V. However, it can operate from an external DC supply or from AC mains. In the latter case, the supply voltage available to the audio amplifier rises to 16V, with a consequent increase in available power output.

What about antennas? Integral with the receiver are 3 ferrite core antennas, one each for long-wave, medium-wave and marine band. These can be used in conjunction with a rotatable (360-degree) frame antenna for increased indoor directionality and sensitivity. A 2-rod telescopic antenna is provided for



# We're #1—and the critics totally agree!

## **HIRSCH-HOUCK LABS... Stereo Review**

“The Pickering XUV/4500-Q is obviously one of the best phono cartridges presently available. There are few stereo cartridges that can outperform it in any of its individual characteristics, and we know of none that could be said to be a better stereo/CD-4 pick-up.”

## **B. V. PISHA... Audio Magazine**

“The Pickering XUV/4500-Q ranks among the top cartridges for stereo, SQ, QS and CD-4. The sonic clarity is exceptionally good, with superb transient and applause response, and good definition, particularly in the low bass region.”

“To sum up, we can recommend the Pickering XUV/4500-Q cartridge without reservations, based upon our laboratory and listening tests.”

## **MAURICE HOLTHAM... Canadian Stereo Guide**

“In fact the reproduction of all material... stereo, CD-4 and matrix... was absolutely superb. Good recordings were reproduced with outstanding fidelity and clarity, and tracking was secure at one gram with even the most heavily modulated bands. Solo instruments and voice were rendered with exciting realism; large orchestral and choral works came through in all their magnificence.”

## **Hi-Fi Stereo Buyers Guide**

“In both stereo and CD-4 one of the most outstanding under any program conditions. Sound so clean and crisp it almost hurts.”

“This pickup is a perfect example of why measurements cannot truly express the sound quality from a transducer; though the measurements are good, the sound quality was rated by the entire listening panel as superb.”



The specifications of the XUV/4500-Q are so exciting that we hope you will write to



*“for those who can hear the difference”*

**Fred A. Falk & Co. Pty. Ltd.**

P.O. Box 34 Rockdale, N.S.W. 2216, Australia Tel. 597-1111

**Fountain Marketing Limited** P.O. Box 5029 Auckland, New Zealand Tel. 763-064

Reprinted by permission of Audio, Canadian Stereo Guide, Hi-Fi Stereo Buyers Guide and Stereo Review Magazines.



VHF, while external 75 and 300-ohm antennas can also be connected.

Needless to say, all this does not come in a pocket-size case. The RF-8000 is "portable" in the sense that it can be carried from place to place as a self-contained unit but it measures 512 x 361 x 213mm (just over 20 x 14 x 8in) and weighs 21kg (46+ pounds) without batteries!

Local distributor for National Panasonic is Haco Distributing Agencies Pty Ltd, of 57-69 Anzac Pde, Kensington, NSW 2033. They do not expect to sell large numbers of the RF-8000 in Australia, nor can they afford to have too many of them sitting around on display shelves. But they can supply further details to genuinely interested readers.

## TOSHIBA-EMI

A new integrated stereo system, combining AM/FM stereo radio tuner, pre-amplifier, power amplifier, turntable deck and a high performance cassette tape deck in one compact unit has been announced by Toshiba-EMI (Australia) Pty Ltd.

Named the Stereo Music Centre SM-3200, the unit is attractively styled in a slim line walnut case with easily located front panel controls.

The radio tuner provides for both VHF FM/stereo and medium-wave AM reception. There is also a long-wave band, but this is of little practical value in Australia. According to manufacturer's literature, "better than average sensitivity and selectivity ratings ensure good quality reception even from distant stations or under crowded channel conditions". The frequency ranges are FM stereo: 88-108MHz, AM: 525-1605kHz (MW) and 150-380kHz (LW).

The SM-3200 may be used with a variety of speakers. Impedances of 4, 8 or 16 ohms can be readily accommodated, and 12 watts RMS per channel is available to provide adequate power for most listening purposes. Separate treble and bass controls are featured and total harmonic distortion is claimed to be no

# TOSHIBA-EMI INTEGRATED STEREO



The new "Stereo Music Centre SM-3200" by Toshiba-EMI combines turntable, cassette player and twin microphones with AM/FM tuner, full preamplifier and power amplifier circuitry and twin loudspeaker systems.

greater than 1.0% at full rated output.

While essentially a two-channel system, a built-in speaker matrix enables the SM-3200 to give four channel effects using an extra pair of speakers. These may also be placed in a separate room and switched (by a front panel push-button) to give normal stereo listening from either the main or alternate speakers.

The turntable is a 2-speed semi-automatic unit, using a 4-pole synchronous motor, with belt drive to a die-cast alloy turntable. An S-shaped arm is used, giving inherent dynamic balance, fitted with standard removable head-shell, an interchangeable MM-type cartridge and diamond stylus.

A feature of the cassette tape recorder

is the Dynamic Noise Limited (DNL) system. Operating only on playback, DNL greatly reduces background tape hiss, and can be switched in or out, as required, by a simple push-button control. Unlike Dolbyised systems with their specific record/playback requirements, DNL can be used on all cassettes – pre-recorded or otherwise.

Chromium dioxide tapes and the more usual ferric oxide varieties can be used with the recorder, which is equipped with specially hardened permalloy heads to ensure maximum resistance to wear. The recorder operates at 4.8 cm/sec and has a 4-track/2-channel stereophonic system incorporating individual left and right record level controls.

As well as the usual twin level-meters and three-digit tape counter, the recorder contains a number of additional features including an instantaneous 'pause' control, front-panel microphone sockets and a noise-suppression switch for reducing high frequency noise when recording from radio.

A headphone jack is included on the unit front panel, while connection facilities at the rear include two-channel 'AUX' amplifier input jacks, two-channel 'tape-out' jacks, speaker terminals, and FM and AM antenna jacks. Accessories available include speakers, headphones, microphones, FM antenna and a spindle adapter for 45rpm, 7-inch records. Dimensions of the SM-3200 are 690mm wide x 170mm high x 380mm deep.

Further details are available from Toshiba-EMI (Australia) Pty Ltd, 301 Castlereagh St, Sydney 2000.



Pioneer's new "Monitor 10" headphones feature high sensitivity, often desirable for use with tape decks, preamplifiers, etc. The drivers use mylar diaphragms.



Also designed for high sensitivity, these new Pioneer SE-255 headphones combine performance with economy. Driver diaphragms are carbon fibre blend.



## PIONEER HEADPHONES

Two new headphones released by Pioneer Electronics Australia Pty Ltd both offer exceptionally high sensitivity. This sensitivity means that the user can connect them directly to a tape deck, tuner or pre-amplifier and expect high level musical reproduction.

The first of Pioneer's new headphones is the "Monitor 10" and is designed for professional type monitoring of tape recording sessions and the like, or for providing "the ultimate" in private stereo listening.

Pioneer's Marketing Services Manager, Mr Doug Bell says that the Monitor 10 uses a well tested but new polyester material for the large 57mm (2¼") cone drivers. Called mylar, this ultra-thin stiff material helps reproduce crisp tonal differences over the entire frequency range with very low distortion.

Another feature of the Monitor 10 is the unique mounting of the headphone diaphragms, which are housed in specially designed earcups. This prevents any significant leakage of sound radiation.

The other headphones released by Pioneer exploit the advantages of the newly developed speaker cone material called Carbon Fibre Blend.

Commenting on the new SE-255 headphones Mr Bell said: "When translated into performance this space age material enables the speaker cones to produce crisp natural sound reproduction of any part of the frequency spectrum".

Recommended retail prices for the new headphones are approximately \$60 for the Monitor 10 and approximately \$30 for the SE-255.

For further information: Mr Noel Brown, Pioneer Electronics Aust Pty Ltd, 178-184 Braeside Rd, Braeside, Vic.



*Just released in Australia, the Apan Model BRC-233 semi-automatic turntable features belt drive operation, an independent hydraulic cue facility, an S-shaped tone arm with plug-in headshell, and adjustable anti-skating. A magnetic cartridge and the timber base and perspex cover are included in the recommended retail price of \$159.00. Further information is available from Ralmar Agencies Pty Ltd, 71-73 Chandos St, St. Leonards, NSW 2065.*

## CANTATA CASSETTES

By the time this issue appears on sale, a new range of prerecorded cassettes will have made their appearance on the Australian market. Under the "Cantata" label, the cassettes are being produced in Sydney by KGC Laboratories for Convoy International Pty Ltd. They will be distributed to resellers throughout Australia by Goldring Sales and Service Pty

Ltd, and can be ordered by local record shops.

Where a supply difficulty is encountered, the cassettes can be obtained — or ordered directly — from Edels Pty Ltd, 437 George St, Sydney 2000.

In discussing the project with an E.A. representative, Malcolm Goldfinch, Convoy's Managing Director, said that the objective was to provide customers with a range of pre-recorded cassettes offering better quality than is normal in the popular field. To this end, the cassettes are recorded on to TDK Dynamic tape, using the Gauss System facilities at KGC Laboratories.

The cassettes are all "Dolbyised" so that, by playing them back on decks switched to "Dolby", a significant improvement in signal/noise ratio will be realised.

Where the playback deck is not fitted with Dolby facilities, there are two options. The first is to turn the treble control down slightly to preserve the best subjective frequency balance, and this will give some discrimination against noise. On the other hand, in a noisy vehicle or environment, the cassette may best be played "straight", in which case the inherent treble boost to low level passages may well make for easier listening.



*A group of three of the new Cantata cassettes, typical of the twenty or so titles available as we go to press. We plan to review them progressively through the year. From the currently available titles, Cantata appears to be favouring MOR (middle of road) sound — a description that might be somewhat inappropriate for automotive use!*





**The new Apan BRA 121 Series 4000.  
Integrated hydraulic cue device. Semi-automatic.  
4 channel ready. Servo assisted.**

The top of the range semi-automatic. Strobe edge aluminium turntable. Electronically controlled A.C. servo assisted motor rear mounted. An incredible wow and flutter of 0.08%. Superior Jelco MC 14D cartridge 4 channel ready. For full 4 channel CD 4 sound, change the stylus to Jelco ND-IX or slip in the complete Jelco 4C-IX cartridge.

You can't go past the Apan BRA 121 Series 4000.  
Ask your dealer to show you.



**Raimar Agencies,**  
71-73 Chandos Street,  
St. Leonards.  
N.S.W. 2065  
Telephone 439-4352.  
Agents and distributors  
throughout Australia.

Also available  
BMU 121 Manual  
BRU 121 Semi-Automatic  
BFU 121 Fully Automatic

**apan**



# Developing a new recording tape\*



by DAVID R. MILLS

Enthusiasts tend to become understandably confused by all the talk of new tape formulations. While this article deals specifically with a new Ampex mastering tape, discussions of the factors involved and decisions that had to be taken parallel those for other tapes aimed at the consumer market.

The goal of any audio mastering system is the faithful recording, storage and reproduction of sound without losing its quality and without adding anything to it. Tape is the storage medium on which magnetization patterns are analogs of the sound—the level of magnetization being proportional to the instantaneous sound intensity.

The limits of a tape's performance are the level of output as a boundary condition on the high side and the level of bias noise as a limit on the low side. The total recording capability of the tape is defined as the region between these limits.

While it is theoretically possible to improve system performance either by increasing the tape's output capability or by reducing the level of tape noise, in a practical sense, the only real option is to increase output while maintaining noise at a low level.

Actual recording equipment is itself somewhat noise limited and, while the system noise of good machines is below the tape noise, it is not so low that a significantly lower noise tape could be used to advantage. In addition, there appears to be no magnetic material currently

available which could lower tape noise significantly without creating other performance problems.

To improve the storage medium (tape) without making significant changes in the other elements of the system, it is therefore necessary to increase the tape's capacity for magnetization or, more precisely, its remanence. Also, since the recording process is most effective in the longitudinal direction, it is the longitudinal magnetization which must be increased.

When a significant increase in a tape's capacity for magnetization in the longitudinal direction has been achieved the tape will have the capability to record sound at higher levels without distortion and without a noticeable increase in bias noise. If this is the only change in the tape, the increased output will be realised by increasing the record level; the only other adjustments are those required to recalibrate the meters. Provided the machine is not limited in record current or output handling capacity, the benefits of such a new tape would be immediately apparent on an existing system.

Having reduced the design problem to that of developing a higher output tape to perform in an otherwise fixed system, our next objective was to define the level of improvement which we could

David Mills, 38, is manager of audio tape development at the Ampex Tape Laboratories in Redwood City, Ca. He holds a degree in chemical engineering from Purdue University and has been involved in research and development in the area of tape recording since 1965. Research on GrandMaster tape has been in train since 1972, paralleling the development of high energy cassette tape.


realistically expect to achieve. After an analysis of available materials and technology, we set ourselves the following goals (relative to Ampex 406/407):

1. A 3 to 4dB improvement in signal-to-noise ratio.
2. No change (increase) in the bias current requirement.
3. No change in the erasure properties.
4. No change in equalisation characteristics.


These goals, when translated to the specific magnetic design requirements, meant that we had to accomplish an increase in the magnetic remanence of the tape from a current value of 1100 Gauss to a value exceeding 1500 Gauss. This had to be accomplished without degrading any of the other properties expected in modern recording tapes.

Figs. 1-3 show the evolution of mastering tape through three generations in purely magnetic terms. The hysteresis loop, obtained by subjecting a sample of tape to an oscillating magnetic field and measuring the corresponding change in magnetization, provides a graphic representation of its magnetic recording potential.

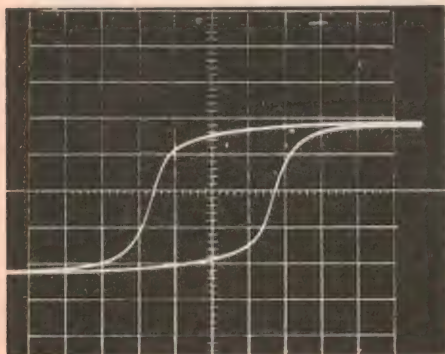
The loop is bisected horizontally by the zero magnetization axis and vertically



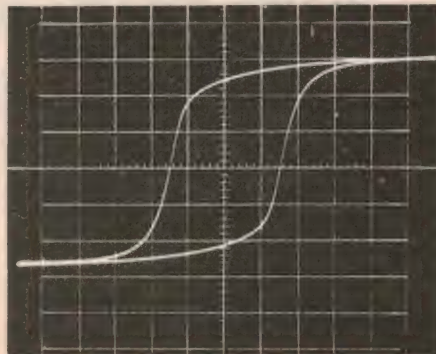These three curves illustrate progress which has been achieved by technological development of the type described in this article. Fig. 1 (left) depicts early mastering tape (circa 1965)



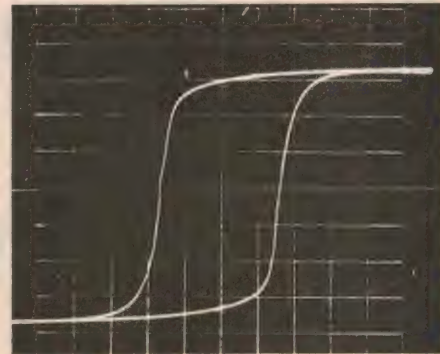with MPVC ca 40%, coercivity 330 Oe, remanence 850 Gs, squareness 0.8 and S/N ratio 66dB. Five years later (Fig. 2) MPVC ca is 50%, coercivity 300 Oe, remanence 1140 Gs, squareness 0.8, S/N



70dB. With the new GrandMaster tape (Fig. 3, right) MPVC ca is 60%, coercivity 325 Oe, remanence 1560 Gs, squareness 0.91, and S/N 74dB. The result: reduced tape distortion at any given output.

\*By arrangement with Ampex Australia Pty Ltd. Condensed from an article in "Recording Engineer Producer".



## METHODS OF INCREASING REMANENCE



Fig. 4

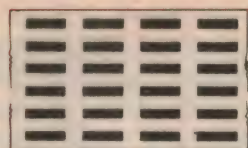


Fig. 5



Fig. 7



Fig. 6

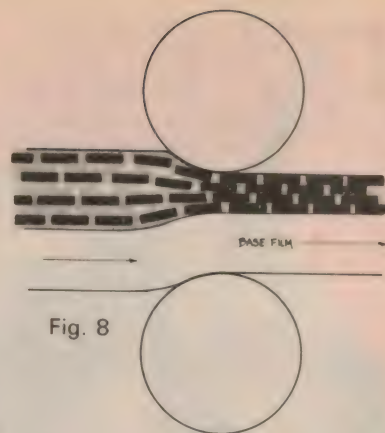
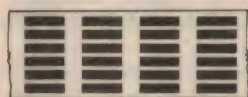


Fig. 8

Assuming the use of a particular type of magnetic coating, the problem of achieving increased remanence is largely a physical one—packing more aligned particles into a coating of acceptable thickness. See text for details.

by the zero field axis. The greater the vertical extension of the loop, the greater the output potential of the tape. The wider the loop, the more difficult it is to magnetize (and demagnetize) the tape.

Specifically, the remanence is defined as the level of magnetization at the point where the loop intersects the vertical axis. The coercivity is the level of field where the loop intersects the horizontal axis.

The coercivity is the field necessary to cause significant magnetization changes and this determines the bias current required for optimum recording and, to some extent, the difficulty of erasure. The objective of our development program was to raise the remanence significantly without making any change in the coercivity.

As Fig. 3 shows, the magnetic formulation finally adopted caused the loop to have high squareness—the hysteresis loop is extremely rectangular. This gives higher remanence by virtue of better loop shape, but it has the additional effect of reducing tape distortion at any given output and reducing the difficulty of erasure.

In short, the three curves show the progress, magnetically, from the original mastering tapes to the “state-of-the-art” GrandMaster. Remanence and then squareness were greatly increased while coercivity was held constant to maintain machine compatibility.

Getting back to fundamentals, the

remanence of a tape can be increased in the following ways:

1. Use a magnetic material which has a higher intrinsic magnetization than iron oxide. (Fig. 4).

2. Increase the thickness of the coating—increase amount of magnetic material (Fig. 5).

3. Pack more magnetic material into a given tape coating—increase proportion of magnetic material (Fig. 6).

4. Increase the amount of magnetic material which is aligned in the preferred direction—increase orientation (Fig. 7).

Although these four methods are all valid, only the last two could be considered in this case.

The use of material with higher intrinsic magnetization was ruled out because the bias currents required for the known materials having higher magnetization are beyond the capability of existing studio machines. The two materials which can be considered in this case, chromium dioxide ( $\text{CrO}_2$ ), and magnetite ( $\text{Fe}_3\text{O}_4$ ), offer only modest improvements in intrinsic magnetization (12-15%) accompanied by serious deficiencies in either chemical stability, coercivity (high bias) and/or cost.

Increasing the magnetic coating thickness provides higher remanence potential because more magnetic oxide is present in the vicinity of the head at any given instant. However, the standard reel configurations make it impossible to increase the oxide thickness significantly

without also either reducing the length of the tape or decreasing the base film thickness.

Any reduction in base film thickness would be accompanied by a decrease in the physical strength of the tape and by an increase in the susceptibility to print-through.

The shortening of the standard tape lengths is not desirable, although situations could be envisioned where this approach could be used. Problems might be encountered, however, in ensuring flat response at high frequency if the coating were too thick.

**REMANENT MAGNETIZATION:** The two techniques which we utilized for increasing the remanent magnetization capability of the new tape were to increase the volumetric loading of magnetic material in the coating (without increasing thickness) and to increase the level of particle orientation in the longitudinal direction. Increased volumetric loading can be achieved in two ways:

1. Formulate the coating so that the magnetic material is a larger fraction of the total coating layer. In the formulator's terminology, this means increasing the

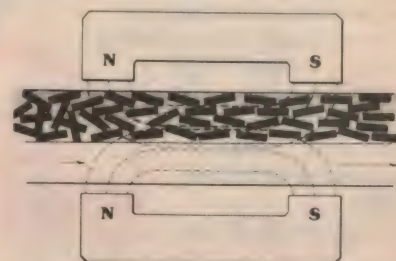


Fig. 11

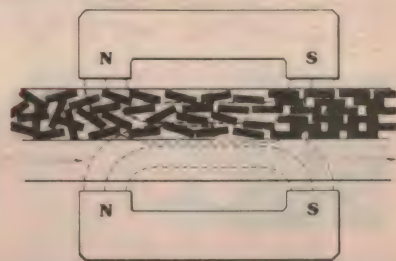


Fig. 12

## WAYS TO IMPROVE PARTICLE ORIENTATION

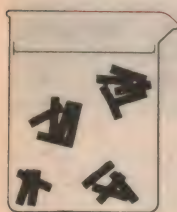


Fig. 9

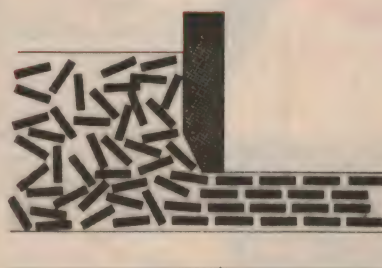


Fig. 10

Adequate particle orientation starts with the mix (Fig. 9 above) but involves application, the use of a magnetic field and the choice of orientable particles.





# WHOPPERS

## (2 1/2")

## SULCO

will give you  
the right

## DRILL

The design and construction of these drills are the result of continuing tests . . . extreme accuracy is their outstanding feature . . . from wire sizes in straight shank jobbers' drills through to taper length and taper shank models for numerical control machine drilling . . . the drill you can rely on is . . .



A comprehensive range of  
**DRILLS, REAMERS,  
END MILLS, CARBIDE TOOLS,  
SCREW EXTRACTORS, TOOL BITS and SPECIAL TOOLS**

also available **EX-STOCK** from



469 PACIFIC HIGHWAY  
ARTARMON N.S.W.  
Tel: 424214

## A new recording tape

magnetic pigment volume concentration (MPVC). In the case of the new tape, the MPVC was increased by about 10%.

In order to do this, the binder system, which is the matrix that contains and supports the magnetic oxide, must be strengthened and improved. If this is not done, serious problems of coating durability will develop, giving rise to oxide shed and head clogging, as well as storage stability problems.

Early binder systems (ca. 1965-1970) were capable of MPVC's in the 35 to 40% range. The class of binders used in the current generation products is capable of MPVC's from 45 to 50%, primarily through the use of cross-linking binder components.

The Grandmaster product achieves its further increase in MPVC to the 55 to 60% range by improvements in basic binder properties and through the reduction of additives which contribute neither magnetic nor binder properties to the coating. As an example, the use of a conductive carbon back coating on the tape permits additional magnetic oxide to be put in the magnetic coating since the carbon, which would otherwise have occupied 4 to 8% of the oxide volume, is relocated to the back of the tape.

2. Increase the density of the oxide coating by high-pressure calendering (Fig. 8). Although the coating is formulated to provide a certain theoretical oxide density, the actual coating contains microscopic voids which cause the magnetic density to be lower than this theoretical value. If the dried but uncured coating is passed between a steel roll and a hard, yet compliant roll at high temperature and pressure, a significant densification/thickness reduction takes place which essentially eliminates the coating voids. This permits the application of initial coating thicknesses which would exceed the full-reel limits at the standard length specifications and then employs hard calendering to compact the coating to obtain correct total tape thickness.

**PARTICLE ORIENTATION:** Improved particle orientation can be obtained in several ways:

1. Proper dispersion of oxide in the binder system (Fig. 9).
2. Proper adjustment of the rheological characteristics of the fluid coating during application—flow orientation (Fig. 10).
3. Passing the coated tape through an appropriate longitudinal magnetic field while the coating is in the fluid state (Fig. 11).
4. Utilization of a "highly-orientable" magnetic oxide particle in the formulation—HOP (Fig. 12).

It can be assumed that all commercially available tapes have undergone an optimization phase in which Item 1 through 3 have been carefully established to give maximum tape performance. However, until recently there were no gamma ferric particles which could be said to fall in the highly-orientable category. Now there are several.

By selecting an HOP material, it is possible to increase hysteresis loop squareness (a measure of magnetic orientation) from a typical value of 0.80 to values in excess of 0.90. This has a direct effect on the output sensitivity of a tape but it has an even more significant effect on its distortion properties. This is an improvement which manifests itself as a reduction in third harmonic distortion at any operating level. It permits higher recording levels and lower distortion on the tape at any given recorded level. Ultimately, it extends the useful operating range of the tape since it is the onset of distortion and not the absolute saturation point of a tape which defines its limit of usable output.

This is shown in the accompanying input-output curves which clearly reflect the improved linearity and increased output at low and high frequencies of Grandmaster compared with 406/407 (Fig. 13). The farther the output curve follows the 45° line, the lower the distortion characteristics of the tape. Also, the higher maximum values result in greater tape headroom or saturation capability.



**ELECTRICAL PERFORMANCE:** The design objective in developing this new tape has necessarily been oversimplified but, in fact, many properties were carefully balanced in arriving at the final product. Two sets of curves (Fig. 14) show the complete audio recording characteristics of the two generations of mastering tape. The curves depict six recording parameters which change with bias current.

Note that on both tapes, the output sensitivity at low and high frequency reaches a maximum at a given bias setting and falls off at lower or higher settings. Also note that the third harmonic distortion reaches a minimum on both tapes at another bias point and increases if the bias setting is raised or lowered. Weighted noise remains relatively constant with bias on both tapes.

The optimum bias setting is a compromise which balances highest output against lowest distortion and flattest response. The choice, for both tapes, is the point at which the distortion is at its minimum and the output is 1.0dB below its peak at 10kHz. This optimum point is exactly the same for both tapes and can be arrived at by overbiasing 1.0dB at 10kHz. Close comparison of the two sets of curves shows the improvements realized in this new tape — increased sensitivity throughout the audio frequencies, low distortion and slightly reduced noise.

#### INPUT-OUTPUT CHARACTERISTICS

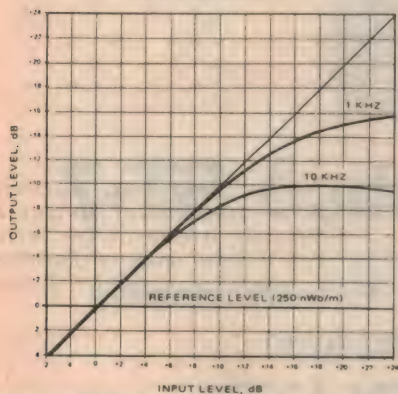
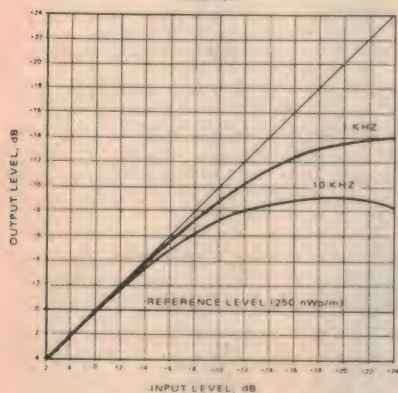


Fig. 13: Reflecting the result of the work described by the author, the lower curve for GrandMaster tape offers a significant improvement over the earlier 406/407 generation.

## EFFECT OF BIAS ON RECORDING PARAMETERS

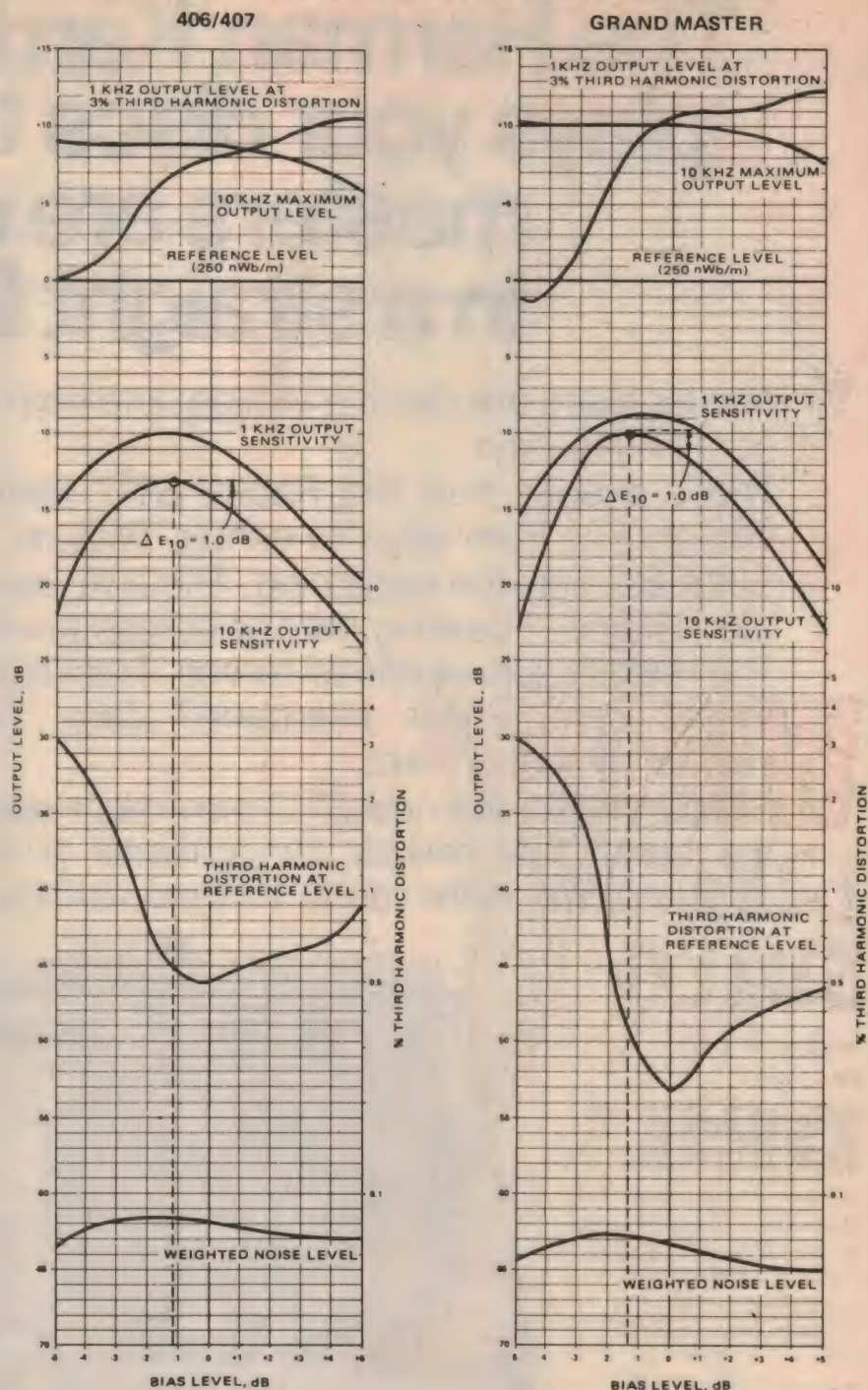


Fig. 14: These two sets of curves indicate the complete audio recording characteristics of two tape generations. Optimum HF bias remains unchanged but every individual performance area shows some improvement.

**MACHINE ADJUSTMENT:** The result of this development is a tape which can provide 4.0dB of increase in signal-to-noise ratio if used properly. Assuming that a machine is set correctly for the current generation of mastering tape (specifically Ampex 406), the following changes should be made:

1. Increase record level 2.0dB. This increased input level plus the increased sensitivity gives a level on the tape which is 3.0dB higher than 406.
2. Reduce reproduce level 3.0dB to

adjust for the higher level on the tape. Because of the improved distortion properties of the tape, this higher level on the tape will have the same third harmonic distortion as 406 did at a level 3.0dB below this point.

Now, without having changed bias, the new tape is being recorded at the same distortion level as before but the apparent noise on playback is 4.0dB lower than with 406 due to its 1.0dB lower intrinsic noise and the 3.0dB lower playback gain.




# The Harman Kardon ST-7 plays your discs the way masters are cut. In a straight line.

Master discs are cut in a straight line from edge to center. With no tracking error.

That's exactly how the Rabco ST-7 plays your record. In a straight line from edge to center. With no tracking error.

But that's only the beginning. The arm, carried by the remarkable "rolamite" bearing, moves across the disc in a straight line. The result is a cascade of zeroes. Tracking error? Zero. Skating force? Zero. Stylus overhang? Zero. Vertical force? Zero. Horizontal force? Zero.

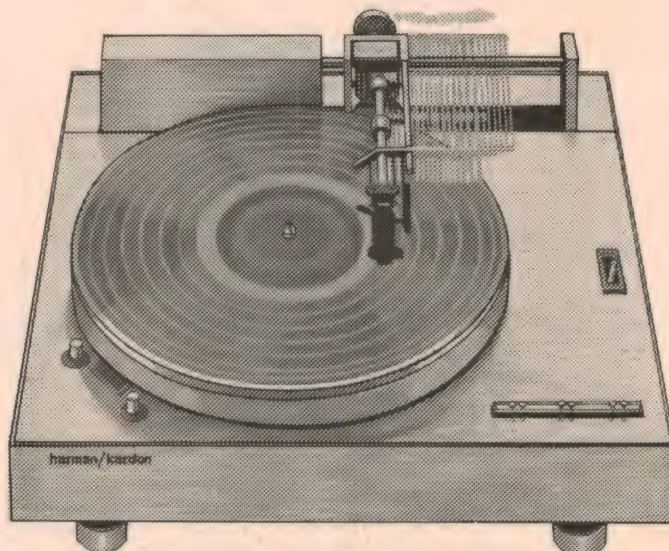Simply stated, the new ST-7 provides a way of playing music in the home that makes conventional pivoted arm turntables obsolete. We invite you to a demonstration.



## The harman/kardon Rabco ST-7

The Rabco ST7 is available from fine High Fidelity dealers around Australia. Ask for specifications from:

**HARMAN AUSTRALIA PTY LTD**

**PO Box 6, Brookvale 2100. NSW. Ph 939-2922**



## Yamaha TC-800GL stereo cassette deck

Much of today's high fidelity equipment looks very similar in appearance to the layman, but that problem does not occur with the Yamaha TC-800GL. It was conceived and styled by an Italian industrial designer, Mario Bellini whose signature appears on the control panel.



Whether or not the styling of the Yamaha TC-800GL attracts or repels you, it does have a number of advantages such as excellent visibility. The angled control deck can be easily viewed from any angle in the listening room. And the cascade of controls from top to bottom has a certain compelling logic. But the appearance is in no way related to the other products in the Yamaha high fidelity range.

And for those who cannot understand how a cassette deck can have its weight-distribution so arranged that it will sit in that slanted mode, we can now reveal the truth. The deck has a fold-out prop on its underside, to stop it from reverting to the horizontal position of its forebears!

The case is all plastic, with a charcoal coloured velvety scuff-resistant finish. The finish does not show finger-marks and is a good background for the screen-printed lettering of the various labels and controls. The underside of the deck has a compartment to accommodate nine C-size flashlight cells to render the unit free of mains-power. The deck may also be powered from a car battery.

Six rocker buttons are used to control the transport mechanism. These have a

slightly different layout from that on most cassette decks, although this does not seem to pose any difficulties. The buttons have a fairly heavy action which can be a problem for those who are not heavy-handed.

No less than seven slider controls are featured in the cascading display. At the top is the pitch control which has a detent position in the centre of its travel to provide the correct speed. Range of speed control is about plus and minus 3% so the calibrations to plus and minus 5

are perhaps a little inappropriate.

Below the pitch control are individual sliders for playback level, and microphone and line mixing. We found that the slider controls did not have a pleasant feel when being operated and the serrations on the slider "pads" were too sharp and rough for comfort. One good point though — Yamaha have taken pains to ensure that the slider elements are well sealed against dust and dirt. Overall travel of the sliders is 45mm.


Five push-buttons are provided above the slider controls for Memory, Limiter, Dolby NR, FeCr and Power. The Memory feature is the same as on other cassette decks in that it allows a cassette to be rewound to a preset "000" setting on the revolution counter whereupon the mechanism stops automatically. The Limiter is also similar to other decks in that it acts to compress recording levels when they rise above 0dB. The Limiter has low distortion and Fast attack and slow decay times.

Readers will note that there is a button to provide optimum conditions for the new Ferrichrome tape but Cr02 does not seem to be mentioned. This is because the TC-800GL is one of the few cassette decks available which automatically senses the presence of a Cr02 cassette and change the necessary circuits for optimum conditions.

The metering facilities are unusually comprehensive. Notice that the meters are calibrated over a range of 46dB— from minus 40 to plus 6. Most cassette decks only design to provide meters with half that range, and often the calibrations mean very little. However, the meter calibrations on the TC-800GL are notable for their accuracy as well as their range.


In addition, there are no less than four LEDs, two per meter to give further indication of signal conditions. Red LEDs are used to indicate peaks in excess of 0VU while green LEDs (which may not be visible in our illustration) start to glow at minus 7dB below 0VU and are fully alight at minus 3dB. Thus by following the manual instructions on the use of the meters and LEDs it is possible to obtain near-optimum recording levels.

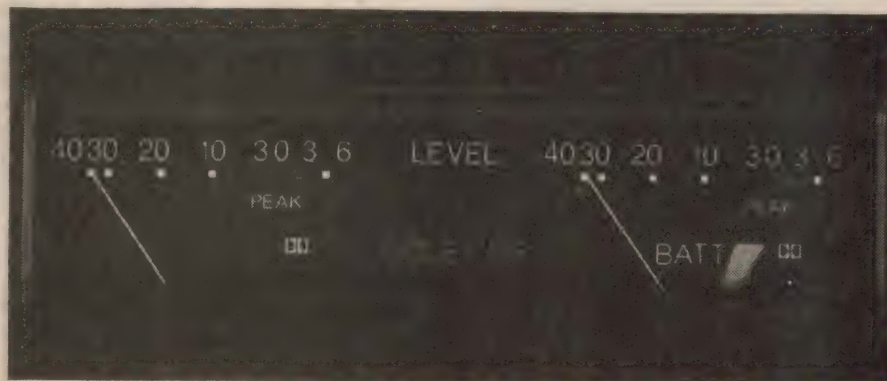The underside of the case is removable to reveal an interior that is crowded with circuitry, as is the case with most



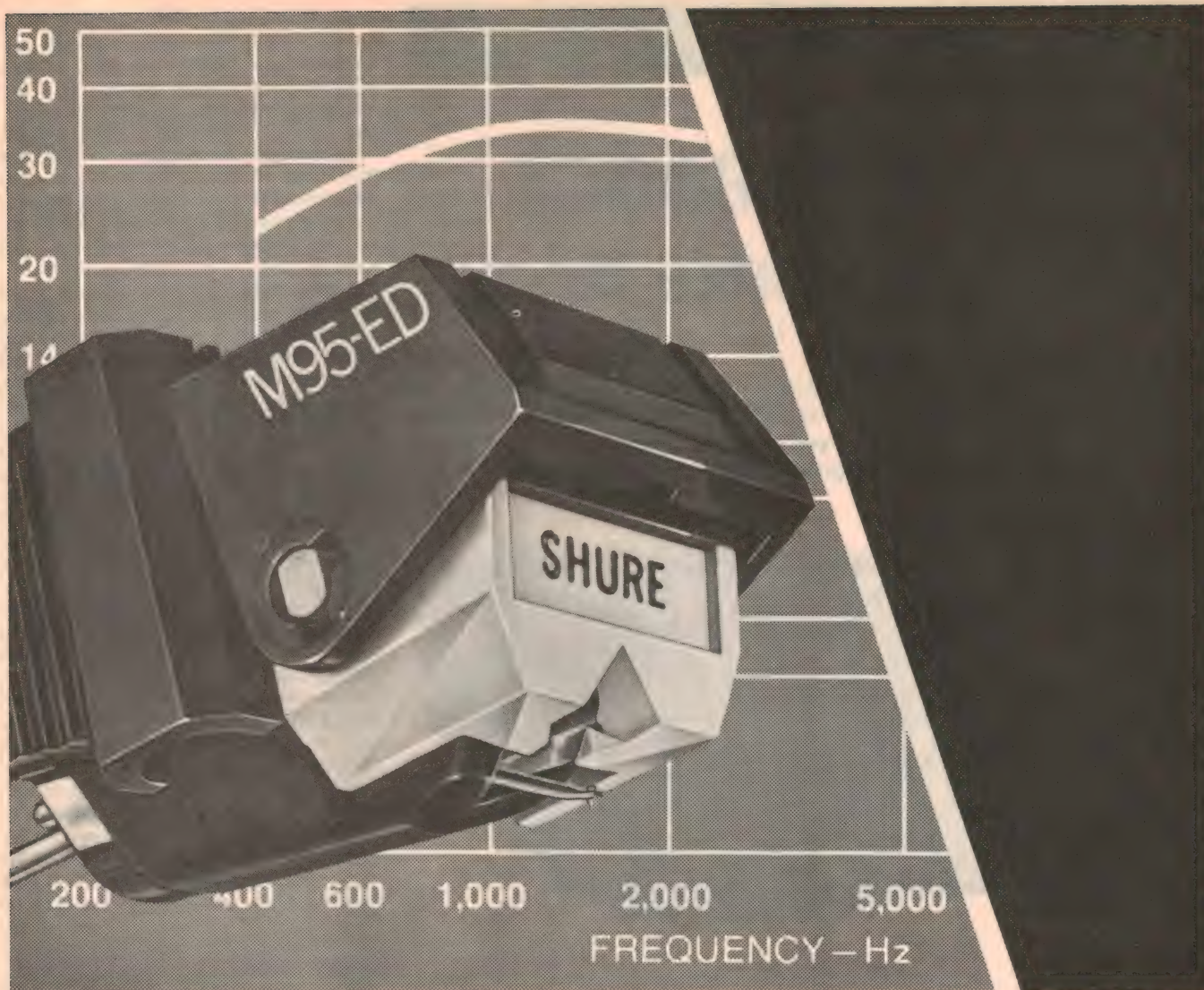Notice that the meters are calibrated from minus 40 to plus 6.





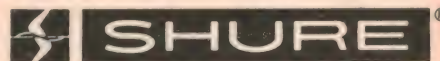
## M95ED: A Significant Technological Innovation



Shure now introduces a superb, moderately priced pick-up cartridge with a performance second only to the renowned V-15 Type III. The technologically advanced electromagnetic structure with a newly designed pole-piece virtually eliminates hysteresis loss. The frequency response from 20 to 20,000 Hz remains essentially flat. Operating at extremely light tracking forces of between  $\frac{3}{4}$  and  $1\frac{1}{2}$  grams, the exceptional trackability of the M95ED enables it to trace the very high recorded velocities encountered on many modern recordings with the result that in addition to providing faithful reproduction of the recorded sound, stylus and record wear are reduced to minimum proportions. The M95ED: A notable addition to the Shure range with a performance never before available at such a competitive price.

Distributed in Australia by  
**AUDIO ENGINEERS PTY. LTD.**  
 342 Kent Street, Sydney. Write for catalogue.






**AUDIO ENGINEERS (Vic.)**  
 2A Hill Street  
 THORNBURY. 3071. Vic.

**RON JONES PTY. LTD.**  
 57 Castlemaine Street,  
 MILTON. 4064. Qld.

**ATHOL M. HILL PTY. LTD.**  
 1000 Hay Street,  
 PERTH 6000 W.A.




## YAMAHA TC-800GL

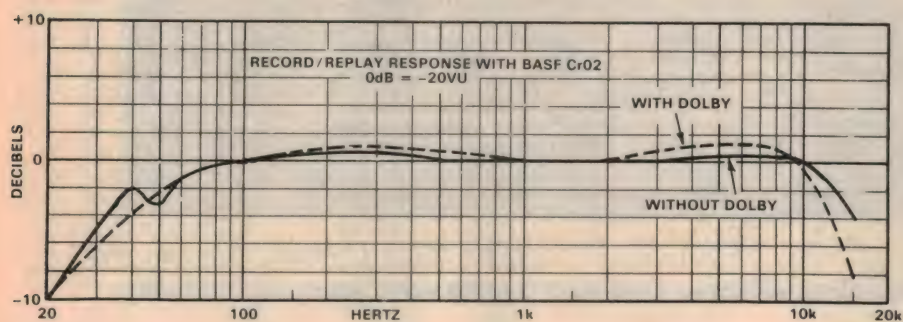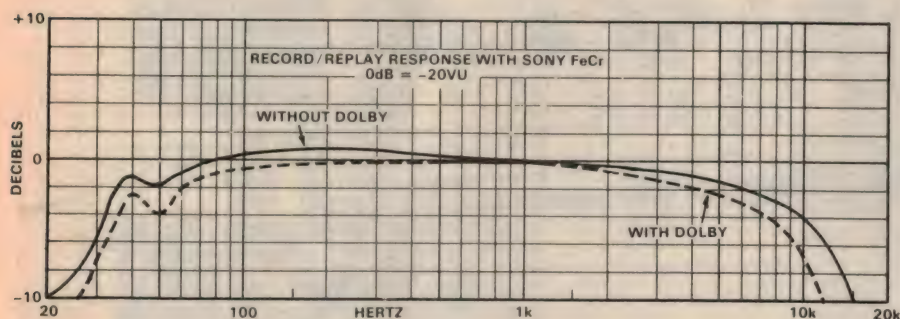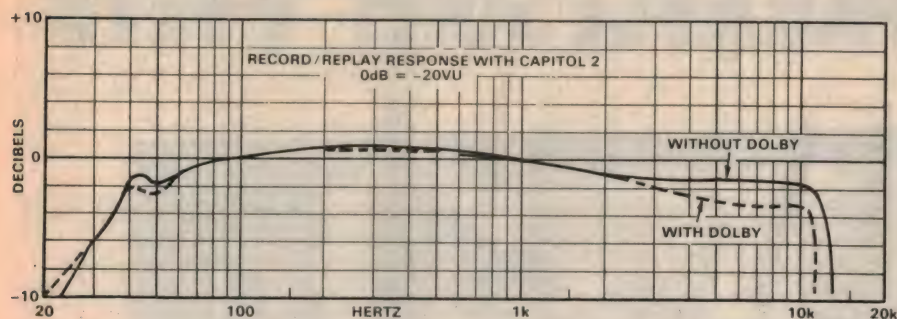

cassette decks. Several integrated circuits are employed. For example, the microphone input preamplifiers are low noise ICs, as are the meter and LED drive circuits. The Dolby circuitry also uses an IC, the NE545B manufactured by National Semiconductors. Changes to bias, metering and equalisation circuitry to accommodate the different tape types is accomplished by switching transistors rather than a large multi-contact switch.

The unit reviewed had a removeable two-core mains flex fitted with a two-pin plug. Since other Yamaha equipment is supplied with the correct mains cord and plug we assume that the local distributor will at least fit a three-pin mains plug.

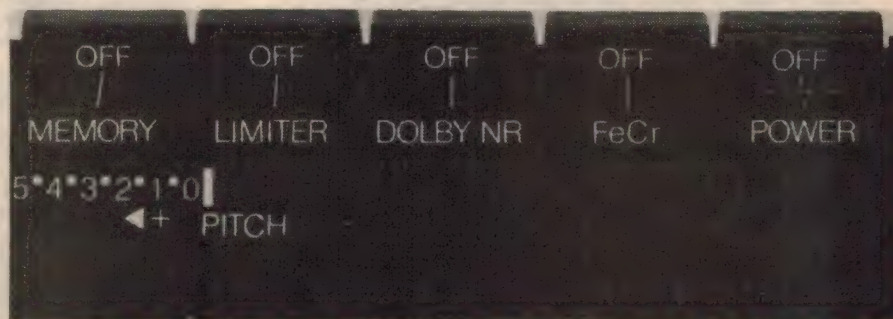The biggest problem we found with the deck was that of loading and unloading cassettes. We found cassettes difficult to load – pushing the cassette into the carrier clicked it into place, but spring tension pushed it out slightly so that the cassette fouled the locating pins when the lid carrier was closed. And when the Eject button was pushed, the deck uner-



No switch is provided for Cr02 cassettes as these are sensed automatically.

ringly fired the cassette onto the floor. This was probably due to maladjustment as it seemed to worsen as our tests proceeded.

Frequency response test results are shown in the accompanying graphs. These are taken at the usual level of minus 20dB below 0VU are quite typical of many cassette decks in this price range. As is usually the case, the frequency response was not quite as

extended nor as linear when Dolby noise reduction was employed.

Harmonic distortion is quite low even at levels well above 0VU and typical measurements yielded results of the order of 1%. Signal-to-noise ratio was 50dB which improved to 52dB with Dolby in use although this measurement does not take into account the normal attenuation above 5kHz so the audible result is rather better than the results indicate.

Clearly Yamaha could have improved frequency response and signal-to-noise ratios but this would mean a worsening of the harmonic distortion figures. We rate the specifications compromise as being a good one, and indicative of conservative design rather than "spec chasing".

Separation between channels was very good and ranged from better than 40dB at 100Hz and 1kHz to better than 30dB at 10kHz. Meter response was also very good with the minus 3dB indication at 16kHz.

Very low figures are claimed for wow and flutter performance but we found it quite dependent on the vagaries of cassettes. We were able to obtain a best measurement of 0.13% DIN, which is very good although this result could not be expected with most cassettes.

Sound quality on playback was generally good although not up to the ultimate standards set by some very expensive decks on the market. During headphone listening we noted that hum was audible during quiet passages but this did not occur on playback via an amplifier and loudspeakers.

In summation, we must rate the Yamaha TC-800GL as being a good all-round performer with most unusual styling and features, some of which space prevents us from detailing. In view of its

performance and features, the price is not unreasonable in these times of generally inflated prices.

Recommended retail price of the Yamaha TC-800GL is \$398 including sales tax. Further information may be obtained from hifi retailers or from the Australian distributors, Rose Music Pty Ltd, 17-23 Market Street, South Melbourne or interstate offices. (L.D.S.)



# THE INCOMPARABLE SONY 'V-FETS'



**Sony's TA Series – A new breed of amplifiers so advanced they lift world standards in fidelity.**

SONY research takes the art of solid-state amplification a giant leap forward. Now amplifiers offer all the true warmth and brilliance of the classic vacuum tube without any of its drawbacks. In fact, Sony's V-FETs are the biggest thing in stereo hi-fi since the vacuum tube.

Tubes are inefficient, they deteriorate and wear out. They also require an output transformer to drive speakers. And there's no way they can be set up in true complementary circuits with true wave form symmetry.

Sony's V-FET amplifiers overcome all that with high current utilization ratio and uniform thermal flow for exceptionally stable operation under greatly varying conditions.

## **"Watts per dollar" is no longer the test**

Amplification goes into a new era, a "V-FET Era" with Sony's new TA series. Both the TA4650 and TA5650 give great power and superb natural fidelity, with literally dozens of applications and facility features, typical of Sony design ingenuity.

To list a few:  
Complete FET protection circuits which prevent circuitry or speaker damage, professional controls designed for utmost accuracy and precision, including

instant 20db muting volume control and level control memory. Tape monitor and dubbing facilities are thoroughly professional and very comprehensive as are the rear panel connection facilities.

The TA5650 boasts a powerful 50W RMS per channel power output, frequency response 10 Hz – 100KHz and a harmonic distortion figure of 0.05% (at rated output). Truly a magnificent performer. From only \$559.\*

The TA4650 delivers a linear smooth 30W RMS per channel, frequency response 10Hz – 100KHz, harmonic distortion an amazing low 0.05%. From only \$439.\*

Whatever your demands, the new SONY V-FET Amplifiers deliver a superb performance with looks to match. Naturally they're perfectly compatible with SONY's new range of space-age Hi-Fi equipment.

If you're into sound, you must be into SONY.

\*Recommended retail price.

# **"IT'S A SONY"**

**Hear the difference research makes**

GAC.S.76

For your nearest stockist call SONY Sydney 2.0221 Canberra 95.2100 Melbourne 874.8222 Brisbane 44.4488 Adelaide 268.3444 Perth 81.3422



## Sony ST-4950 FM Tuner

One of the trends with FM tuners is to package them in larger chassis, larger in fact than many stereo amplifiers. Here is one of the new models from Sony, the ST-4950, which matches the new range of V-Fet stereo amplifiers.

Dimensions of the Sony ST-4950 are 462 x 331 x 168mm (W x H x D) including knobs, rear terminals and feet. An extra 150mm is required at the rear of the chassis to enable the bar antenna to be swung through a maximum arc of 90 degrees for best AM reception. Mass of the unit is 8.6kg.

Size and styling of the unit combine to give an impression of sizeable mass. Two meters are employed, one for AM and FM signal strength while the other is a centre-indicating type for FM tuning accuracy. A long linear tuning scale combined with the large fly-wheel assisted tuning knob makes tuning very easy. A red LED doubles the visible length of the dial pointer when a station is tuned in, so that combined with the meter indications there is no mistaking stations when tuning across the dial. Dial calibrations are very accurate, to within better than 50kHz.

There is a large push-button for Power and three smaller buttons for AFC, Hi-blend and Multipath. The AFC button is normally deactivated when station tuning but in practice with the ST-4950 it does not really matter. The AFC does not have the tenacious action found on some tuners, whereby the pointer can be moved half-way across the dial before the AFC finally "lets go" of a strong station with all the reluctance of a cow pulling its foot out of a bog.

The Hi-blend button is the same as found on other tuners and is used to reduce high frequency noise on weak stereo signals. It effects a slight reduction in the high frequency response and a

quite drastic reduction in separation between channels at high frequencies.

A three-position Function switch provides FM stereo, FM mono and AM reception modes. Terminals are provided on the rear panel for 75 ohm coaxial

controls for the variable audio output levels.


Sony fit a detachable three-core power flex fitted with the correct three-pin mains plug for the Australian market. The fact that the chassis and one side of the signal circuitry are tied to mains earth results in an earth loop problem for some amplifiers, but there was no problem with a companion Sony TA-5650 V-Fet stereo amplifier which we had on test at the same time. (This amplifier will be reviewed next month.)



cable and 300 ohm ribbon antennas as well as a long-wire AM antenna which is used where the bar antenna does not suffice. RCA sockets are provided for fixed and variable audio outputs and the mono output from the discriminator. In addition, there are two screwdriver preset

path display on an oscilloscope. However, the multipath button on the front panel is more useful as far as most listeners are concerned. When this button is depressed in the presence of multipath reception conditions the signal-strength meter responds to the audio amplitude of the audio signal. The instruction manual clearly indicates how the signal strength should be maximised while minimising multipath reception by careful antenna orientation. With this procedure it is a straightforward task to obtain the most distortion-free FM reception.

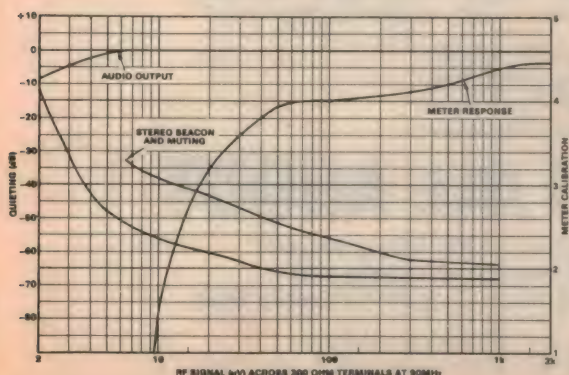As can be seen from the photograph of the interior, most of the circuitry is accommodated on a large PC board which, at 385mm wide, is one of the largest we have seen in a high fidelity component. A six-section tuning gang is mounted on the FM front-end PC board. Two sections



At left are the quieting characteristics for the ST-4950. Also included is the meter response versus signal strength.



# AMPLIFIERS EXPLAINED:



## **KA-1200G\*\***

Power Output: 13 + 13 watts RMS into 8 ohms load at 1,000 Hz. Both channels driven. Total Harmonic Distortion: 0.8% at rated power into 8 ohms load. Power Bandwidth: 20 Hz to 40,000 Hz.


**\$180.00\***



## **KA-1600G\*\***

Power Output: 23 + 23 watts RMS into 8 ohms load at 1,000 Hz. Both channels driven. Total Harmonic Distortion: 0.8% at rated power into 8 ohms load. Power Bandwidth: 20 Hz to 40,000 Hz.

**\$285.00\***

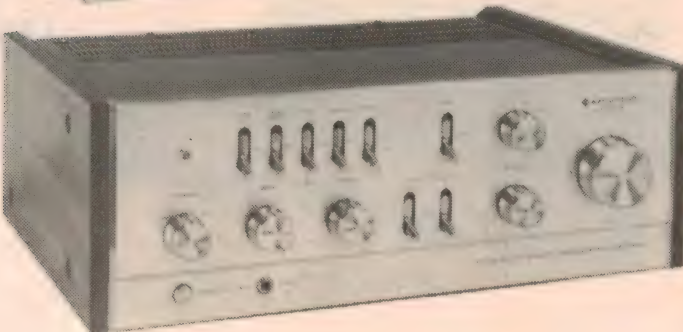

## **KA-4006\*\***

Power Output: 32 + 32 watts RMS into 8 ohms load at 20 Hz-20,000 Hz. Both channels driven. Total Harmonic Distortion: 0.5% at rated power into 8 ohms load. Power Bandwidth: 8 Hz to 45,000 Hz.

**\$399.00\***

\*Recommended Retail Price.

\*\*Averaged manufacturers' specifications subject to change without notice.

The amplifier is the heart of a hi-fi system. It takes the electronic signals from your programme source and boosts them sufficiently to enable the speaker to convert them to actual sound. The amplifiers above are examples of good amplifiers. They aren't cheap, but nor is any good hi-fi component. Their specifications are their credentials. If you understand them, you'll know just how good they are. If you're a bit lost with the specifications, we have just the thing: "The New, Improved, Updated, More Detailed Hi-Fi Explained in Simple Language by Kenwood Booklet". It will make these specifications much clearer. Because when you know more about good hi-fi, you'll be better able to appreciate Kenwood hi-fi.



# **KENWOOD**

## WHAT GOOD HI-FI IS ALL ABOUT

We want you to know what good hi-fi is all about, so we are giving you our booklet absolutely free. It is a complete dictionary of hi-fi terms and explanations, available at your nearest hi-fi specialist, displaying the Kenwood sign.

Distributed and serviced in Australia by Jacoby Mitchell Company.  
Head Office: 215 North Rocks Road, North Rocks, N.S.W. 2151. Telephone: 630-7400



## SONY ST-4950

are used for the mixer and local oscillator of the AM tuner circuitry.

Integrated circuits are used for the IF amplifiers and the multiplex decoder while the remainder of the circuitry employs discrete semiconductors. Total semiconductor count is 3 IC's, 4 FETs, 23 transistors and 20 diodes and two LEDs.

Most of the performance specifications are summarised in the two graphs. These curves are for 100% audio modulation and pilot level of 10%. The meter response to signal strength is very non-linear and is virtually saturated (at a reading of about 4.5) for signals of 1mV or so.

Frequency response is within  $\pm 1\text{dB}$  from 20Hz to 15kHz and separation between channels was also very good: approaching 40dB over most of the audio range. Suppression of 19kHz and 38kHz residual signals was excellent at 62dB. Ultimate quieting level was 68dB, which is also the residual noise level in the muted condition.

Harmonic distortion was not quite as good as the specification with readings of just over 0.2% in mono mode and .33%, 0.3% and .37% in stereo at 100Hz, 1kHz and 6kHz respectively.



While the overall performance in the FM mono and stereo modes is undeniably good, the AM performance is lamentable. For example the audio bandwidth is only of the order of 2kHz. One can obtain better from a \$10 portable! How manufacturers can continue to provide such woeful AM performance at such prices is hard to credit. It is akin to selling a colour TV receiver that only receives one channel in colour and the rest in B & W!

It would seem that if manufacturers are not willing to accept the challenge of designing an AM section of reasonable performance, then they should omit the facility altogether. This is a general criticism applied to all manufacturers, of course. And it is not sufficient to reply that AM programs do not warrant high quality reception. If overseas journals are correct, it would appear that many FM stations overseas are content with low standards anyway and that there are many high-quality AM stations. Why not make the effort to obtain good reception from both?

Aside from our major criticism regarding AM reception, it is difficult to fault the ST-4950. It is clearly well-designed and assembled meticulously.

Recommended retail price of the Sony ST-4950 is \$389 including sales tax. Further information can be obtained from high fidelity retailers or from the Australian distributors, Sony Kemtron Pty Ltd, 453 Kent Street, Sydney, NSW 2000. (L.D.S.)

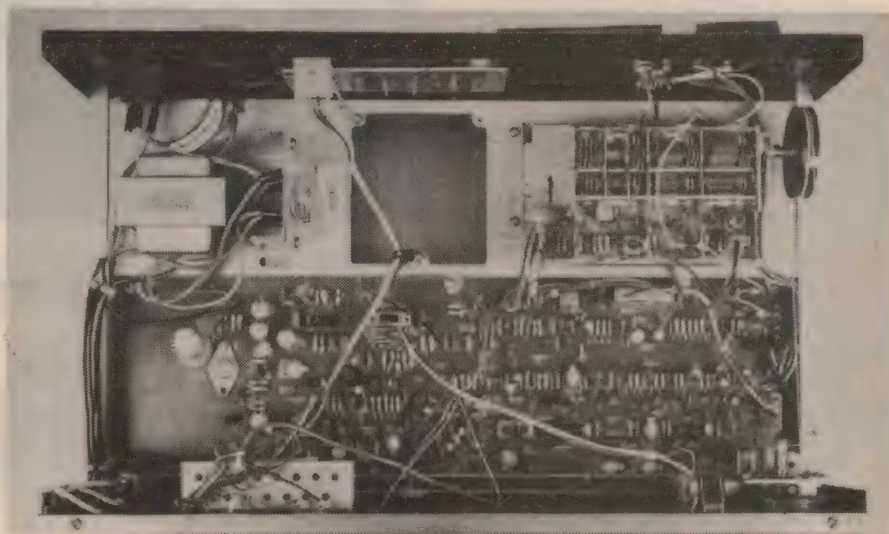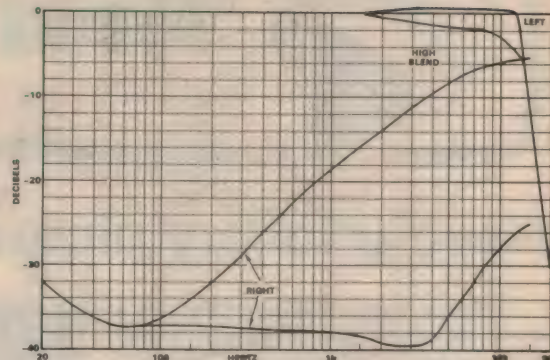*These curves show the frequency response and separation between channels and shows the effect of the Hi-blend switch.*



## Cordless Soldering.. With the Wahl ISO-TIP

for electronic circuitry

Rechargeable battery electric soldering tools

Complete freedom from cords, transformers, power points, plugs. The Wahl ISO-TIP soldering tool is light (170g), slim, powerful: suitable for tag soldering, printed circuits & miniature components.

- Heats in 5 seconds
- Up to 150 joints per charge
- Long life ni-cad batteries
- Choice of quick-change tips
- No leakage or induced current
- Exclusive 'lock-off' switch
- Spotlight illuminator
- Vehicle adaptor available

\* Approval No. V/74394/7578

From trade houses or

**ROYSTON ELECTRONICS**

22 Firth St., Doncaster, Vic., 3108.

VIC: 848 3777 QLD: 52 3166


N.S.W.: 709 5293 S.A.: 42 6655

RE757 W.A.: 81 5500

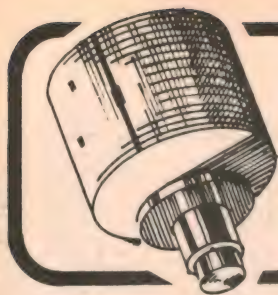
\* Automatically recharges when placed in stand.







## News Highlights

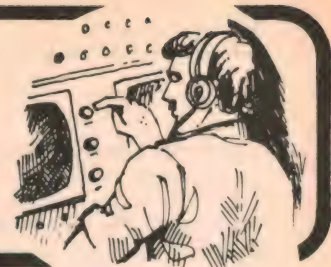

### Revolutionary picture transmission system

A picture transmission system and a new visual display system, both described as "revolutionary", have been developed at the University of Western Australia. The inventors, Professor John Ross (psychology) and computer technologist Monte Sala, developed the new systems out of fundamental research being carried out by Professor Ross and his colleagues on the human eye and visual perception.


The new picture transmission system enables rapid transmission of photographs, maps and other graphic material by cable or by radio. In terms of cost, speed, reliability and resistance to interference, the system is believed to be vastly superior to any presently available. It is also claimed to provide the first "natural" means of computer picture storage.

The conventional method of transmitting a picture is to send it as a frame broken down into a series of lines. Transmission starts at the top left hand corner of the frame and continues line by line until the picture is completed at the bottom right hand corner. The system devised by Professor Ross and Mr Sala differs in that random scan patterns are used to convey the information.

For purposes of transmission, the picture is broken down into thousands of individual picture elements which are transmitted one by one in a random sequence. An addressing system, devised by Mr Sala, defines the location of each element within the picture. The inventors claim that each picture element is addressed at a cost of one bit of information per element.

At the receiving end, the picture elements are re-assembled by detecting the address bits, determining the correct location for each picture element, and locating it accordingly. In interference-free conditions, the prototype machine will receive a picture over a voice-quality channel in less than 3 seconds.

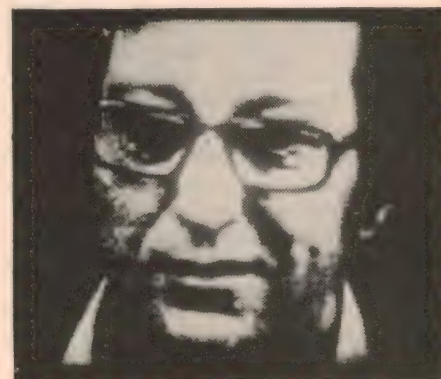The new technique has several inherent advantages over more conventional transmission techniques. In particular, it offers greater immunity to interference. Interference to the signal train will only affect individual picture elements, and because these will be randomly distributed in the picture the effects will be less noticeable to the observer.



Photograph at left shows image of Professor Ross 'coming up' on the screen, while at right is the final picture. Although the developmental system displays identification quality half tones, high quality transmission is feasible.

Other features are the ability to transmit at variable speeds, and the capacity of the receiver to start building the picture from any point. And because the system is inherently digital, pictures may be stored by computer on any convenient mass storage device.

The new visual display system, known as the Betagraph, utilises a remarkable capacity of the human visual system recently discovered by Professor Ross. This capacity is used in the Betagraph to cause the viewer to see a picture which is not objectively present.

By way of analogy, the principle of the Betagraph can be illustrated by considering a car moving behind a picket fence. While it has long been appreciated that


the image which the eye sees is based on scanty information, namely the pattern of light and colour appearing through the cracks between the pickets, it is now known that the eye's ability to construct a picture of the car is very highly developed.

In the Betagraph, the display consists of widely spaced columns of LEDs which may be considered as corresponding to the cracks in the fence. When these LEDs are turned on and off in appropriate sequences, the eye sees, not vertical columns of dancing light, but a moving image which appears to fill the space between the light columns.

The material displayed may consist of text and pictures, and messages may be as long as required. Movement may be in either direction. The display can be computer controlled as part of a network, or can be driven from a standard cassette recorder.

The great advantage of the Betagraph is the small number of light sources required in comparison with conventional displays. This makes the unit very efficient in terms of the components required and in terms of power consumption. Immediate applications include the display of information in public places such as airport terminals, and as desk-top units to display messages to individuals in large organisations.

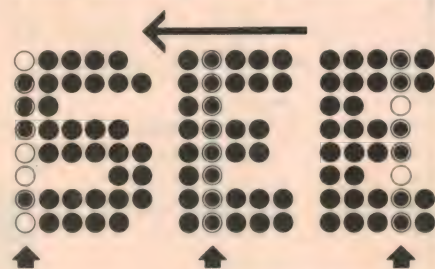The picture transmission system and the Betagraph were developed by the University in association with Deltec, a Perth electronics firm. Patents are held by the University.



Solid circles represent the Betagraph image. Only the solid circles enclosed by line circles are actually objectively present as lights 'on', the open circles representing lights 'off'. A suitably programmed pattern of lights in the columns indicated by the arrows causes the image to move across the entire visual field.



## Post Office meter monitors telephone use

Telecom Australia has approved a new meter which will enable subscribers to monitor charges for calls dialled from their telephones. The new meter, known as the Telemeter, is being introduced to meet a growing demand for this facility, and will progressively replace an existing meter.

Two types of Telemeter are available:

- a "Private Meter" which simply registers and accumulates meter pulses in unison with the exchange meter, and which is primarily intended for use in private homes and small businesses; and
- a "Control Meter" which must be reset after each STD or local call is made before further calls can be made. This facility is expected to make the unit attractive for shops, cafes, motels etc where proprietors are prepared to make a telephone service available to customers on a charge-per-call basis.

Rental for the private meter has been set at \$12 per year, with no installation fee. For the Control Meter, a standard installation charge of \$20 applies, while rental has been set at \$48 per year. Inquiries show that there is likely to be a very strong demand for both meter types.

## Miniature digital compass developed by AWA

A miniature digital compass, developed for Australia's defence forces, has attracted wide interest in Britain and the United States.

The compass, measuring only 65mm x 50mm and weighing 130g, uses modern integrated optoelectronics to achieve outstanding accuracy with rugged construction and low cost. It was developed by the Microelectronics Division of Amalgamated Wireless (Australasia) Ltd with support from the Australian Government.


Based on the north-seeking principle, the digital compass operates by means of a photoelectric cell reading the movements of a transparent, coded compass card or disc. This disc is attached to a dual-magnet assembly mounted on a shock-proof, single-pivot bearing.

An infra-red LED illuminates the disc through a collimating lens to produce a shadow of the code pattern on a 10-element, monolithic photo-diode array. The IC converts this information into a digital data stream to give a 4-digit numeric readout on the associated display unit. The readout is expressed in degrees relative to magnetic north.

Although designed specifically for use in Australian defence and scientific applications, the new compass is suitable for a range of other uses. These include marine and land vehicle navigation, surveying and remote monitoring.
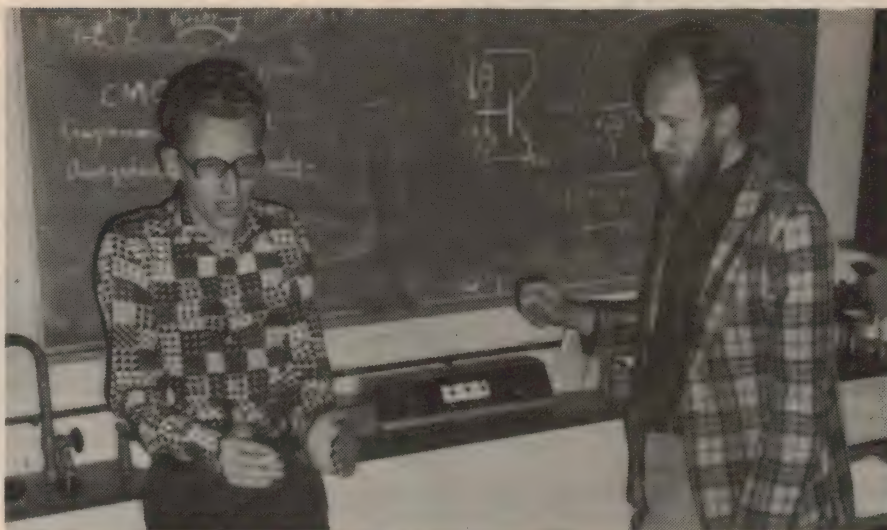
## Award to Philips scientists for I<sup>2</sup>L

*... new technology looks set to eclipse CMOS*



Mr C. Hart (left) and Mr A. Slob of Philips Research Laboratories, Eindhoven.

Mr C. M. Hart and Mr A. Slob of Philips Research Laboratories in Eindhoven, The Netherlands, were awarded the 1975 Achievement Award from the American magazine "Electronics" for their invention of integrated injection logic, or I<sup>2</sup>L. The award was shared with two German employees of IBM, Mr H. Berger and Mr S. Weidmann, who independently produced the same invention at about the same time.

Known alternatively as MTL (for merged transistor logic), I<sup>2</sup>L makes it possible to put a much larger number of logic circuits onto a single chip than was previously possible with bipolar techniques. Advantages of the comparatively new technology are such that it looks as

though it will become the preferred LSI technology, eclipsing MOS and CMOS technologies.

In the past few years, I<sup>2</sup>L has contributed greatly in solving the problems met in the design of increasingly larger integrated circuits. It is easier to make than either TTL or CMOS; its gates and other elements are between 4 and 10 times smaller than those of either TTL or CMOS; it has the speed of TTL, but uses less power than CMOS; and it will operate at supply voltages down to about 1V.

In addition, I<sup>2</sup>L offers the IC designer greater freedom of layout. For a more detailed description, readers are referred to the December 1975 issue of EA.

## New aids for the blind: electronic calculators . . . ... and a paper money identifier

The American Foundation for the Blind has announced the development of two electronic calculators—one with a braille output and the other with a voice output—plus a paper money identifier to aid the blind.

The braille calculator consists of a standard five-function calculator which was modified by the foundation's engineering division to incorporate a single braille readout cell. Within the cell is a 2 x 3 matrix array of solenoid actuated pins. These are activated to give the appropriate readout in braille one decimal place at a time. A control feature enables the user to regulate the speed at which the braille digits follow each other.

The audible readout calculator was developed for the foundation by Telesensory Systems Inc. of Palo Alto, California. Designated Speech Plus, the unit has a

24-word vocabulary built into a speech-generating custom ROM IC that announces every entry and result. It has six basic functions, including square root and percent, automatic constant, a change of sign key, a floating decimal point, and an eight-digit visual display. Results are repeated at the press of a switch.

The pocket-sized paper-money identifier uses an infrared sensor to detect the dark and light areas of a bill of any denomination, and emits a low-pitched tone for dark areas and a higher-pitched tone for light areas. An instructional tape recording is supplied with the device to teach the operator to identify the tone pattern that is characteristic of a particular denomination. The unit, developed from NASA's biomedical-application program, is now manufactured by EMR Ltd, Los Angeles.



## NEWS HIGHLIGHTS

### 22kV "zap" for Sydney's gas pipeline



One essential procedure involved in pipelaying on the Moomba to Sydney natural gas pipeline is the test and repair of any defects found in the coating on the 34-inch diameter pipes.

The 1300km long pipeline being built by The Pipeline Authority is scheduled to bring natural gas to Sydney in April, 1976.

Pictured is the test equipment that has been 'walked' over 800km from Mt. Hope near Cobar, in Central NSW since construction began in early 1974.

The testing machine incorporates a circular spring, to which a 22,000V charge is applied. A lead from the portable battery/transformer unit is attached to one end of the pipe in contact with the steel.

If there are imperfections in the coating, the electric charge jumps the gap between the spring and the steel pipe, and a warning device in the unit beeps loudly. Workmen then patch the coating before the pipe is lowered into the trench.

### Calculator doubles as a ballpoint pen

Hosiden Electronics, Japan, has claimed a world first with the development of an 8-digit calculator which doubles as a ball-point pen. Dubbed the "Calcu-pen", the unit is to be exported to the US market where it is expected to be a popular gift item.

In size and shape the Calcu-pen resembles an ordinary ball-point pen, being just a little larger in diameter. The body of the pen contains the display, together with five key switches. These incorporate the calculating figures, four basic arithmetic signs, percent and clear signs, and a decimal point. The key switches move in four distinct directions, vertically and horizontally, enabling the required function or number to be selected.

Hosiden is a company specialising in the manufacture of keyboard switches and other components for calculators. The Calcu-pen is a result of the company's technological research, although the LSI circuitry is supplied by Sharp Corporation.

### Local thick film circuits in AWA-Thorn colour TVs

Hybrid Electronics Australia Pty Ltd has announced the successful development of reflow soldering techniques for thick film circuits.

Making the announcement, Wal Berryman, General Manager of Hybrid Electronics, said that these developments had enabled colour TV modules to be made in Australia for local manufacturer AWA Thorn. The modules developed include vertical amplifiers, oscillators and colour convergence circuits.

Solder reflow of standard components on to thick film resistor networks often provides the best cost-reliability optimisation for high-volume consumer and industrial electronics requirements. While not as dense in packaging as the conventional hybrid chip and wire approach, the advantages are significant in many product areas.

### New RCA satellite for US communications

A new era in US communications history was begun recently with the launch of a new communications satellite—the RCA Satcom 1—from the Kennedy Space Center.

The new satellite is the first of three that RCA will operate as part of its Satcom domestic communications system, designed to provide telephone, video and data services to customers throughout the US. The spacecraft, now in geosynchronous orbit 36,000km above the equator, was scheduled to commence operational service in February.

Satcom 1 is the most advanced communications satellite ever put into commercial service. It has 24 independent communications channels or transponders, double the capacity of previously launched satellites of a similar nature. Each transponder is capable of handling 1,200 voice grade channels, one colour television transmission, or more than 60 million bits per second of digital data.

Initial satellite operations will be

through nine existing RCA earth stations, with emphasis on Alaska services. These services include critical satellite operation for Alaska pipeline communications. An additional twelve RCA standard stations and up to sixty small earth stations are scheduled for operation with the RCA Satcom System in 1976.

### Local telecom industry wants Govt. action

The win by the Liberal-National Country Party in the Federal Election has sparked strong optimism that the telecommunications manufacturing industry in Australia will be revitalised. This was stated in a recent press release issued on behalf of the Australian Telecommunications Development Association (ATDA).

The chairman of ATDA, Mr T. E. Hodgkinson, commented: "We in the telecommunications and electronics manufacturing business were one of the first cabs off the rank to be hit by the low-protection policies of the previous Federal Government; so it is reasonable to suppose that we can



Mr T. E. Hodgkinson


expect some early relief, some real support for local industry in a nationally important field."

Industry leaders are vitally concerned that the new Government take swift and decisive action to revive the industry before it loses its base as a viable entity.


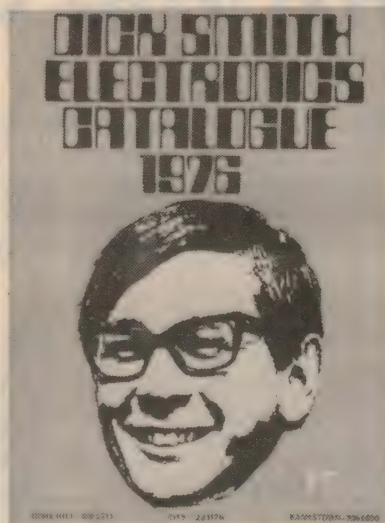
# FREE Next Month

NEW ENLARGED  
84 PAGE  
DICK SMITH  
CATALOG/MANUAL.  
NORMALLY 75c. BUT  
FREE IN APRIL  
ISSUE OF  
ELECTRONICS  
AUSTRALIA.  
ORDER YOUR COPY  
NOW!



In addition to all the usual features and projects in April's issue, we will be presenting a completely new edition of the famous Dick Smith Catalog. The catalog will have 84 pages instead of 64 with many new products for the hobbyist, professional, audiophile, amateur, etc. Anyone remotely interested in electronics needs the catalog. It will have a special data section too! Previous editions of E.A. containing catalogs have rapidly sold out. So to avoid disappointment reserve your copy at your local newsagent NOW. Limited quantities of the new catalog will be available direct from Dick Smith at 75c each. But don't miss out, get your copy FREE in April issue.

84 pages of Hi Fi, Audio, Tapes, Car Radios, Intercomms, Mics, Calculators, Amps, Kits, Speakers, Amateur Radio, Books, Instruments, T.V. Antennas, Games, Transformers, Components, Tools, Hardware, Relays, Semiconductors, Data, etc, etc.

## DON'T MISS OUR APRIL ISSUE

How far has soldering tool technology advanced?

### CONTROLLED POWER at the touch of a button!

**DUOTEMP.** Slim, light, with dual thermal-power capacities. Idles all day on half wave power, at optimum PCB soldering temperature, without over heating.

For fast heat-up —  
For long sequences or heavy joints, a touch of the sensitive button converts it to full wave. Power is instantly doubled. Temperature is maintained while soldering.

This is made possible by the high thermal efficiency of the Adcola design.  
Fast heat-up and tip temperature recovery. Regulated temperature. Long element life.

## ADCOLA

STILL SETTING THE PACE IN  
SOLDERING EQUIPMENT



## DUOTEMP

Today's standard in soldering tools for printed circuits and sensitive micro-electronic components.

### OTHER MODELS

There's an even more advanced model, with sensitive in-handle electronic circuitry for feed-back temperature control. It's called Thermatic.

**THERMATIC**

For occasional use, we recommend the high efficiency single temperature Adcola Standard.

**STANDARD**

3  
SIZES  
IN EACH  
MODEL



# The impact of radio on the maritime services

One of Guglielmo Marconi's principal concerns was to use wireless to end the isolation of ships at sea. In 1900 he formed a company with that express purpose in mind—a company that has since given 75 years of maritime service and is now a recognised world leader in this field. This article briefly traces through those 75 years of service, highlighting events of significant historical interest.

Seventy-five years ago, Guglielmo Marconi formed The Marconi International Marine Company on the very day that he celebrated his own 25th birthday—25th April 1900. The object of the company was to enable shipowners to rent wireless apparatus, the services of operators and the use of Marconi shore stations, so ending the isolation of those at sea. The services still operate today, though the shore stations in Britain are now under Post Office control.

In 1900, the year of his dramatic bridg-

ing of the Atlantic with Morse code transmissions, Marconi started to establish a network of permanent wireless stations specifically for maritime communication. Stations were built that year on the British and Irish coasts and in Belgium and Germany, while US stations on the Nantucket lightship and at Siasconnet were made available, and a station at Bell Isle in the Gulf of St Lawrence was nearing completion.

By the end of 1901, not only had the British and Italian Navies adopted the

'new device' but so too had the first British merchant ship, a number of foreign merchant ships, and the Cunard liners, "Lucania" and "Compania".

The value of Marconi's invention as a life-saver was established beyond question in 1909 when the wireless-equipped White Star liner "Republic" collided with the Italian ss "Florida". Before long, ships were converging on the scene in response to the wireless distress signals. For his devotion to duty during this traumatic experience, the Marconi radio operator Jack Binns assured himself of a place in the annals of maritime history.

Jack Binns, Marconi Wireless Operator, received an inscribed watch to mark his devotion to duty when the "Republic" and the "Florida" collided off the coast of America. Guglielmo Marconi made the presentation.



Above, Dr Crippen is led off the ss "Montrose" by Inspector Dew, following a wireless message from the captain of the ship to Scotland Yard. Photo at left shows early radio transmission and direction finding equipment installed on board a lifeboat.



as told by  
the Marconi Company

During the first decade of the company's life, the number of wireless-carrying ships increased steadily, but it was the part that wireless played in the arrest of the notorious murderer, Dr Crippen, that supplied the drama. Captain Kendall of the "Montrose", suspecting that Dr Crippen and his mistress, Ethel le Neve, were aboard his ship bound for Canada, signalled New Scotland Yard by wireless and, on arrival in Canada, they were taken into custody by fast-travelling Inspector Dew of the Yard.

In 1912 came the tragic "Titanic" disaster. Those who survived owed their lives to wireless and to the devotion and bravery of the Marconi Marine radio officers, one of whom, 'Jack' Phillips, died at his post.

During the First World War, the company trained 3,300 operators for mercantile marine service, and 180 of its own radio operators lost their lives at sea. As often happens in time of war, technological progress hotted up. Radio direction finding was brought to a fine art, and the range of a ship's wireless telegraphy station was increased to between 2,000 and 3,000 miles. Wireless telephony too made headway, culminating in a large scale demonstration in 1920, when delegates of the Empire Press Union on board ss "Victorian" held wireless telephone conversations over distances in excess of 1,000 miles. The new Marconi direction finder was also demonstrated on this voyage, and within six years was adopted by over 200 ships.

Another war-time development to go into wide use was the Marconi auto-alarm which, unlike many wireless devices, actually enabled some ship-owners to cut down on expenses, as it performed the task of two wireless watch-keepers—formerly mandatory on certain ships.

The '20s also saw the introduction of sound reproducing equipment on board ships, and the 'Marconi Band Repeater', through its microphone, amplifier and loudspeakers, brought live and gramophone music to entertain those at sea.

Meanwhile, the fishing industry had not been slow to follow the example of the deep sea vessels, and by the late '20s, 191 trawlers and drifters carried company equipment. By 1930, the newly-developed Marconi echometer was bringing valuable underwater information, including fish locations, to trawlermen, as does its descendent today, the echosounder.

Two years after Guglielmo Marconi's death in 1937, Marconi Marine was again heavily committed to war work, provid-



Above, the ss "Lucania", the first Cunard ship to be fitted for transmitting and receiving wireless messages. She sailed on her first voyage with the apparatus on board on 15 June 1901. Below is the wireless room of a liner of 1912.





# radio parts GROUP

OUR NEW COMPREHENSIVE TRADE CATALOGUE IS BEING DISTRIBUTED NOW!!

For an Annual Subscription of \$15.00 (Postage and Packaging Included) You Can : —

- Increase Efficiency and Keep up with Inflation by Quoting Accurately
- You Won't Waste Time by Requesting Telephone Quotes, because our Prices Remain Firm for the Month of Issue.
- You Will Receive Information on New Lines, Manufacturers Surplus Stocks, Specials, The Stock Situation on Semi-Conductors and Valves.
- Each Section will be Renewed with New Information and New Lines Periodically.



CODE	DESCRIPTION	T	P	A	R	TR
2849 2625	METERS	8	1			9.60
2849 2657	METERS	8	1			9.60
2849 2673	METERS	8	1			9.60
2849 2689	METERS	8	1			9.60
2849 2697	METERS	8	1			9.60
2705	METERS	8	1			9.60
2721	METERS	8	1			9.60
2737	METERS	8	1			9.60
2849 2785	METERS	8	1			9.60
2849 2801	METERS	8	1			9.60
2849 2817	METERS	8	1			9.60
2849 2833	METERS	8	1			9.60
2849 2849	METERS	8	1			9.60
2849 2881	METERS	8	1			9.60
2849 2897	METERS	8	1			9.60
2849 2913	METERS	8	1			9.60
2849 2929	METERS	8	1			9.60
2849 2945	METERS	8	1			9.60
2849 2961	METERS	8	1			9.60
2849 2977	METERS	8	1			9.60
2849 2993	METERS	8	1			9.60
2849 3009	METERS	8	1			9.60
2849 3025	METERS	8	1			9.60
2849 3041	METERS	8	1			9.60
2849 3057	METERS	8	1			9.60
2849 3073	METERS	8	1			9.60
2849 3089	METERS	8	1			9.60
2849 3105	METERS	8	1			9.60
2849 3121	METERS	8	1			9.60
2849 3137	METERS	8	1			9.60
2849 3153	METERS	8	1			9.60
2849 3169	METERS	8	1			9.60
2849 3185	METERS	8	1			9.60

**Radio Parts GROUP**

AFTER HOURS ORDERS TELEPHONE 328 2224  
 REGISTERED OFFICE: 562 SPENCER ST., WEST MELBOURNE 3003  
 TELEPHONE 329 7888 TELEX 32980  
 SOUTHERN DEPOT: 1103 DANDENONG RD., EAST MALVERN TELEPHONE 211 8122

TO: RADIO PARTS GROUP, P.O. Box 124, North Melbourne, 3051, Victoria.

Please Send me Your Comprehensive Catalogue and Price Service for the Period of 12 Months

Enclosed is my Cheque / Money Order / Order Number (if Account Customer) for ..... copies at \$15.00 Each.

Name: .....

Company Name: .....

Address: .....

PLEASE PRINT CLEARLY TO ENSURE CORRECT MAILING.

E.A.3.76



At right, Empire Press Union delegates sailed to Canada in 1920 in the liner "Victorian". Marconi wireless telephony kept her in touch for practically the whole voyage, and concert programs were exchanged with the shore while in mid-ocean.



ing radio personnel for the British Merchant Navy and equipment for both British and allied shipping, and moving service depots along the line of battle for the benefit of ships coming into port.

After the war, Marconi Marine decided to direct the radar experience gained by The Marconi Company to the design of completely new equipment for peacetime shipping. In 1946, the first Radiolocator went on exhibition and a radar school was established in Chelmsford to train both shore and sea staff.

In its Jubilee year, 1950, the company received orders for re-equipping all the lighthouses and radio beacons round the coast of Britain. The following year it supplemented the already comprehensive Marconi Marine installation of the "Gothic" which, as the floating headquarters for the Commonwealth tour of the Queen and the Duke of Edinburgh, had to meet excessive communication demands.

Notable in the '50s was the increasing use of VHF for maritime purposes. The company was ready to meet the demand with a new range of equipment, exploiting, in the late years of that decade, the advantages of the single sideband mode of operation, which has led directly to Omega, automatic Loran, selective calling and automatic error correcting systems that ensure accurate telex communication.

In the mid-'60s a vast new market for Marconi Marine opened up with the arrival of the first North Sea drilling rig. Over the years requirements have advanced from simple radiotelephone links with the shore to specially designed ISB (independent sideband) equipment providing simultaneous radiotelephony and teleprinter transmission.

1970 saw another piece of history being made when Dallas Bradshaw of Marconi Marine became the first woman radio officer to go to sea in the British Merchant Navy. The '70s have also seen the introduction of Marconi Marine electronics officers and the expanding use of the company's equipments, which include a variety of on-board entertainment systems and the spectacular, fully automatic anti-collision radar, 'Predictor'.

Since 1900, the company has led the way in marine electronics. A Queen's Award winner for export achievement, it offers to ships of all nationalities the widest range of electronic equipment available from any one company. 2



"King's Grey" wireless room—a typical trawler installation of the '20s.



The radio room of a modern trawler. The Polish-built Boyd Line "Arctic Buccaneer" has a complete Marconi Marine communications station.

Reprinted from the Marconi publication "Aerial", by arrangement.



# Optical fibre techniques in avionics data transmission

The importance of suitable data transmission to the success of an overall avionics system has long been recognised. During the past decade, the Flight Automation Research Laboratory of Marconi-Elliott Avionic Systems Limited has included a team specifically briefed to investigate such data transmission requirements for avionic systems. One of the techniques investigated over the last five years is the transmission of data using fibre optics as the transmission medium.

by **TREVOR A. MORGAN, B.Sc (Hons.)\***

In general, fibre optic transmission systems may utilise either single or multi-mode waveguide. For single mode systems waveguide attenuations as low as 2dB/km with bandwidth capabilities of 10M bits/s/km have been reported. However, systems employing such fibres require a laser source and accurate optical connections (laser-to-fibre, fibre-to-fibre) for the launching and maintenance of mode propagation. This latter requirement may be acceptable for telecommunications where a cable is rarely disconnected, but is not suitable for avionic systems where maintenance requirements dictate the use of easily separable units.

Multi-mode waveguides are commercially available with attenuations of less than 100dB/km (20dB/km have been reported), and with bandwidth capabilities of 500Mbits/s. A broad range of off-the-shelf electro-optical devices in the

form of light emitting diodes, photodiodes and avalanche photodiodes are available for use with such fibres. Single fibres may be used but the connector tolerances are eased by using a bundle of fibres (20–100) which also permits a certain amount of fibre damage without the total loss of transmission.

The efforts of the Flight Automation Research Laboratory have therefore been concentrated on multi-mode bundle systems using light-emitting diodes (LEDs) and p-i-n photodiodes for point-to-point transmission of digital signals. The input logic signal is modulated into a return-to-zero format, the duty ratio of which is dependent upon:

- the LED characteristics in terms of optical rise and fall times and maximum mean current permissible, allowing for life and temperature degradation;
- the maximum attenuation between LED and photodiode due to optical cable and connectors;
- the radiation levels at the photodiode

to give the necessary signal-to-noise ratio to meet error-rate requirements in conjunction with the design complexity of the receiver in terms of bandwidth and overall gain.

The resulting modulation is input to a current amplifier, the output of which drives the LED in the forward bias mode. The output radiation from the LED is normally coupled into the fibre optic bundle by locating the polished fibre end in close proximity to the LED.

The resulting combination is usually a bulky and inefficient lens. However, special communications devices similar to the Burrus diode devices are now being constructed with large diameter fibre tails. The output from these devices is coupled into the fibre bundle using a fibre bundle connector which can give as little as a 3db power loss across the interface. For fully practical systems, taking into consideration maintenance and installation requirements, this solution is preferred.

The same problem exists at the receiver end and the same provisos apply. The losses, however, at this interface are reduced by using large area chip devices.


The received signal is seen as a low-level current from the photodiode. Typical conversions are 0.5A/W for p-i-n photodiodes and 80A/W for avalanche photodiodes. The avalanche device unfortunately requires an accurately controlled bias voltage, which causes considerable design problems when dealing with an operating temperature range of  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$ .

There are several methods of achieving current-to-voltage conversion at the head amplifier. Systems have been built in the laboratory using either a transimpedance amplifier, or by driving a load resistor with the photocurrent and amplifying the resulting voltage signal with a voltage amplifier.

Output from the head amplifier is input to a level detector, the output of which is a transistor transistor loop (TTL) level signal. This signal is demodulated back to the original form input at the transmitter.

The techniques described have been used in the development of several systems over the past years. These are briefly outlined in the following paragraphs:

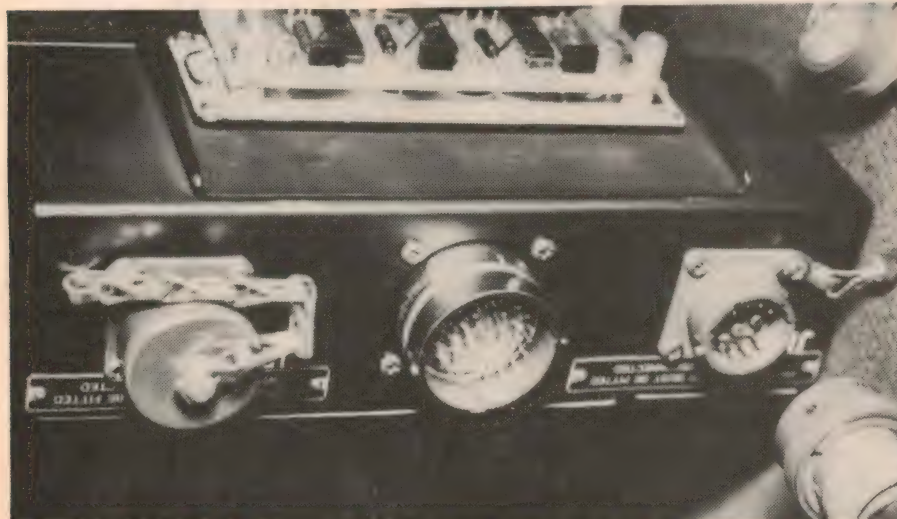(1) A multiplexed data transmission system capable of multiplexing analog and digital information to a maximum of 300 channels. The multiplexed data is



*This optical coupler unit forms part of the new digital Flight Control Electronics System for the Boeing YC-14 Advanced Medium STOL transport aircraft. Main advantages include complete electrical isolation and no EM interference.*



transmitted serially over two fibre optic channels, 20 metres in length and at a rate of 100kbits/s. The received light input is reconstituted and demultiplexed to its original form. This system was built under contract to the U.K. Ministry of Defence and was successfully operated in flight in 1971 and 1972.

(2) A 75-metre, 5Mbits/s airborne computer optical link was developed for the Ministry of Defence in 1973. The system was built using 400dB/km fibres, a large diameter chip LED, and an avalanche photodiode. Automatic rear mounted rack connectors interface transmitting and receiving devices with the fibre bundles. The system allowed the asynchronous transfer of stored data from one computer to the other and vice versa and replaced a point-to-point wiring system requiring approximately one hundred, 70-metre lengths of triple twisted cable.

(3) During the course of a Ministry of Defence sponsored research programme into failure survival digital flight control systems, a quadruplex, high integrity, flight control system demonstration rig was developed using a self-clocking fibre optic data transmission system between channels. The optical system was used to crossfeed data between channels for signal consolidation and fault detection. Each channel provides three 2Mbits/s optical data outputs into fibre bundles which connect to the optical inputs of each of the other channels.

A practical realisation of this prototype was seen in Marconi-Elliott's high integrity digital flight control electronics system recently built for the Boeing YC-14 Advanced Medium STOL transport. In this system, optical data transmission is used to compare command signals between the redundant lanes.

The use of fibre optics in such a system offers the following advantages over similar systems employing conventional electrical data transmission:

- Complete electrical isolation precludes the propagation of electrical faults from one channel to another, thus maintaining high integrity and also reducing the risk of induced electrical fires and other catastrophic damage.
- No errors are introduced into the system via the transmission medium from electro magnetic interference.
- Possibility of high bit rates without fear of radiation incompatibility with other systems.
- Reduced risk of system re-design due to incompatibility during the aircraft system integration stage.

The examples given demonstrate the practicability of optical data transmission in avionics. The efforts of the research team are now directed towards consolidating the techniques and experience gained to produce practical optical transmission systems compatible with normal aircraft and manufacturing techniques. 2



## -that's where the money is!

Stott's course is totally comprehensive — and includes both sophisticated electronic equipment and project materials you need to gain a thorough understanding of servicing techniques.

Divided into three self-contained sections, the course covers:

Part 1 — Introduction to Electronics (theory and practice)

Part 2 — Monochrome Television Receivers


Part 3 — Colour Television, including processing circuitry, service techniques, fault tracing and trouble shooting techniques.

Like all Stott's courses, you work with your own instructor who is an expert in this exciting and rewarding field, at your own pace, in your own home.

If you are a beginner, Stott's will teach you everything you need to know concerning television principles and receiver circuitry.

If you are already working in the field, or have completed some studies in electronics, you may be eligible to enter the course at an advanced stage. Whether your aim is to enter the TV service industry or whether you wish to gain a thorough understanding of television theory and servicing as an aid to sales experience, this is the course which will help you make it!

Other electronics courses offered by Stott's include:  
Radio for Amateurs — Amateur Operator's Certificate  
For full information mail this coupon today:

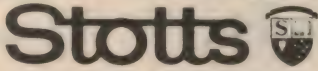	
TECHNICAL CORRESPONDENCE COLLEGE The name to trust in correspondence education Please send me, without obligation, full details of the following courses:	
Stott's undertake that no sales counsellor will call.	
Mr., Mrs., Miss	Age
Address	
Postcode	
159 Flinders Lane, Melbourne. 383 George Street, Sydney. 290 Adelaide Street, Brisbane.	66 King William St. Kent Town, S.A. 89 St. George's Terrace, Perth. P.O. Box 3396, Singapore 1.
STC815	EA 3 76



# At last: an electronic organ that's easy to build!

Building an electronic organ is now a far less daunting job than it was even a year or two ago, thanks to the advances made in IC technology. This is the first of a short series of articles written to show you how to take advantage of the new technology—first in building a basic minimum-cost single manual organ, and then in expanding on the simple design to produce more pretentious instruments.

by JAMIESON ROWE

Sooner or later many electronics enthusiasts seem to develop an interest in building an electronic organ. Perhaps this is because such a project offers not only the usual challenge of building a piece of equipment and getting it going, but also the opportunity to acquire an instrument for family entertainment and enjoyment—and hopefully at an attractive price.

In an effort to satisfy this interest among our readers, EA has published in the past a number of articles on electronic organs and organ building. Noteworthy among these were the articles of May-June 1955 by R. A. B. Tarrant, and those of November 1961-August 1962 by present Editor-in-Chief Neville Williams describing the Stromberg-Playmaster organ. Since then there have been other articles dealing with various aspects of organs such as reverberation units and vibrato modulators, together with descriptions of small "toy" instruments.

Since the description of the Stromberg-Playmaster organ we have not attempted to describe another "serious" instrument, however, despite indications that there existed plenty of potential reader interest in such a project. One reason for this was that many of the essential parts were in poor and unreliable supply—keyboards, for example.

Another reason was that the cost of commercial instruments had fallen to the level where it would be very difficult to achieve any worthwhile saving by the do-it-yourself approach—particularly when a full-scale organ project tends to involve a great deal of time and effort; far more than many would-be builders expect.

These reasons made it very difficult to justify either our own development of an organ project, or the publication of articles encouraging readers to commit their time and money.

Just recently, we became aware that this situation has begun to change for the

better, once more as the result of developments in integrated circuit technology. It is now possible to generate all of the notes required even for the various pitches of a pretentious organ, using a mere handful of ICs and other components on a single modest-sized printed circuit board (PCB). And the resulting note generator needs no tuning as such, the note relationships being locked permanently in a very close approximation of the tempered musical scale.

As many will appreciate immediately, this represents a most dramatic advance over what has been possible in the past. It means that now the note generator can not only be far simpler and easier to build, but also vastly easier to get going and maintain. There is no need for the initial tuning hassle which presented a major hurdle to constructors in the past, nor will there be any need for retuning

later on.

There is also a cost advantage, at least as far as the note generator itself is concerned.

As soon as we realised the possibilities in this direction, we decided to re-examine the idea of an electronic organ project. And the prospect certainly looked more promising than before, mainly because of the developments with regard to the note generator. But there were still problems to be overcome.

The main hassle concerns keyboards. These have always been a problem; in the past those keen to build an organ generally had to obtain an old harmonium keyboard, and spend much time and effort in adding suitable switch contacts. This perhaps added to the challenge for the real fanatics, but understandably it provided a stumbling-block to deter almost everyone else.

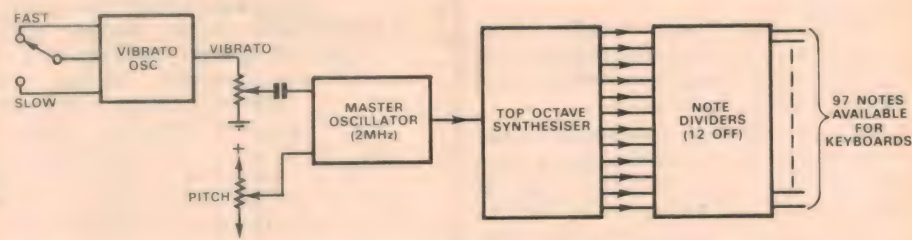


FIG. 1

PLAYMASTER 760 ORGAN—NOTE GENERATOR—BLOCK DIAGRAM

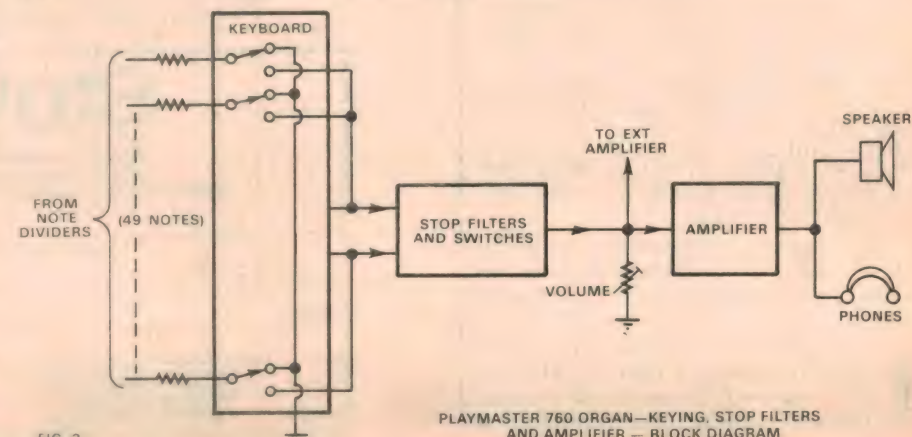



FIG. 2

PLAYMASTER 760 ORGAN—KEYING, STOP FILTERS AND AMPLIFIER—BLOCK DIAGRAM





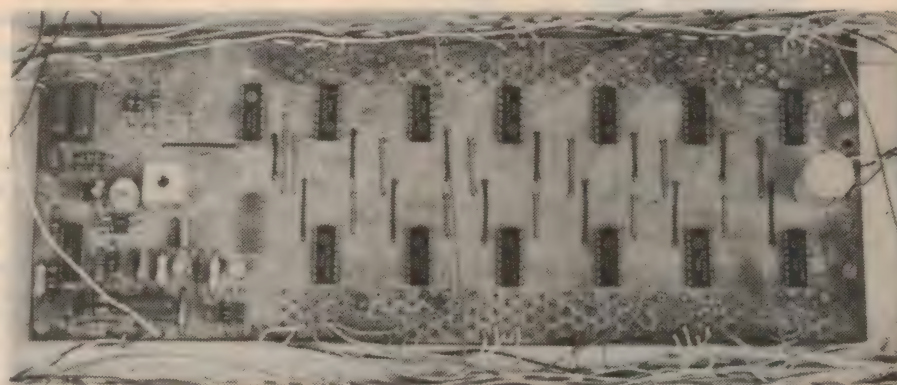*Above is the simple organ, photographed before it was completed by the addition of a lettered front panel and music rack. Below is a view of the note generator board, which actually provides all 97 notes required for quite pretentious organs.*



In the case of the Stromberg-Playmaster project, moulded keys were available at the time, along with keyboard frames and matching hardware to provide suitable switches of the single-pole variety. This allowed constructors to assemble an attractive keyboard with only a moderate amount of effort. Unfortunately most of the hardware for that project has long since dried up, although we understand that quantities of the original fully-moulded keys (less the switches) are available at 10c per key from the firm Electronic Arts, of 126 Bombay Street, Lidcombe NSW 2141. These may provide a solution for those with the necessary time and patience.

The ideal solution would be completely assembled keyboards, preferably with multi-pole switches fitted to each key, so that the builder would not be involved in a lot of tedious and rather fiddly assembly work. Such keyboards appear to be available from time to time overseas, although they are not really easy to come by even in Japan or the USA. And they are not cheap when you can get them—which is hardly surprising, as their assembly involves a fairly high labour content.

After a good deal of enquiry locally, we have been able to nominate only one firm able to offer virtually immediate supply of assembled keyboards. The firm is Dick Smith Electronics, and the keyboard they can supply is a very nicely made 4-octave unit with single pole switches. This is quite adequate for a small organ, and although its modest compass and switching limitations make it less than ideal for more elaborate instruments, there are now ways of getting around most of the limitations.

Other keyboards more suitable for larger instruments may possibly become available later but, for the present, it would appear that these are likely to be the only keyboards available for the immediate future. They are available at a price which although not cheap, is at the same time not unreasonable. Bought

separately it will cost you \$97.50 including sales tax, although Dick Smith Electronics tell me they hope to whittle this down when the keyboard is bought as part of an organ kit.

In view of the availability of these keyboards, we decided to go ahead with a new organ project—hence this article and those which are planned to follow.

Please note, however, that the approach we will be adopting is intended to be of maximum help to the largest number of interested hobbyists—often with little or no previous experience building electronic organs. The designs presented are not intended primarily for the committed organ enthusiast wishing to produce a “no holds barred” juggernaut, although some of the modules should be of considerable interest to such people.

We are first of all going to describe a very simple and minimum-cost single manual organ—as shown in the pictures. This incorporates a complete note generator module which takes full advantage of current IC technology. The note generator module is in fact directly suitable for use as the heart of far more pretentious instruments, and in later articles we plan to tell you how to either

upgrade the simple organ or build a more elaborate instrument from scratch.

Presenting the new note generator initially as part of a very simple organ makes sense, because it is just such a project which it will benefit most. Not only this, but the resulting organ is so delightfully easy to build that we believe it offers an ideal way for those with no previous experience to “get started”.

By the way, don't think that the simple organ is a mere toy. It has an entirely practical 4-octave compass, two-speed vibrato of adjustable depth, a split keyboard facility, control of absolute pitch over a range of  $\pm 3\%$  (to allow playing with other instruments), and four stops which are capable of a surprising range of different tone colours at the basic 8ft pitch.

In short, we have designed the simple organ with care so that despite its modest pretensions it should be capable of entirely musical and satisfying performance. As such it should be very suitable for the beginner to learn the rudiments of organ playing, or as a low-cost practice instrument for the professional organist.

The main advantage of the simple



**KEF**  
the speaker  
engineers

**KEF**  
speaker  
systems

**KEF**  
speaker  
units

**KEF**  
speaker  
kits

Distributed by Audioson International Pty. Ltd.

Sydney 938 1186 Melbourne 329 6066 Adelaide 337 7000 Perth 25 9993

## ELECTRONIC ORGAN

organ compared with similar small organs available commercially is that it may be readily expanded into a more pretentious instrument, if and when you so desire.

As a matter of interest, we estimate that a kit of parts for the basic organ as described should be in the order of \$170, which compares quite well with commercial mini-organs.

At the heart of the basic organ is the note generator module, as already noted. The block diagram for this module is shown in Fig. 1, with the remaining sections required for the simple instrument shown in Fig. 2. As you can see, the note generator consists of four main sections: a vibrato oscillator, a master note oscillator, a top octave synthesiser and a group of 12 note dividers—one for each note of the tempered musical octave.

It is the last two of these main sections,

the top octave synthesiser and the note dividers, that represent the most dramatic changes from previous organ techniques. The top octave synthesiser consists of a single IC, which simultaneously divides a single input signal from the master oscillator by 12 different ratios to provide the 12 notes of the uppermost octave on a 2ft organ stop.

These 12 notes are then taken by the note dividers, and each one is divided by two the appropriate number of times, to provide the notes of all the lower octaves. In the case of all of the notes except C, this involves 7 divisions by two, to give a total of 8 octave versions of each note. An additional division is required for C, because 9 octave versions of this note are required—one at the top of each octave, and a final one at the bottom of the very lowest octave.

A single IC is used to provide all 7 of the binary divisions for each note—that is, one IC for each of the 12 note dividers, or 12 divider ICs in all. An additional IC is used to provide the eighth division for

### Organ terminology explained . . .

For those unfamiliar with organ terminology, many organs have facilities to sound a number of different notes — either singly or together — when each key is pressed. The organ is said to be sounding in "unison" or 8ft pitch when pressing each key results in the same note which would be produced by pressing the corresponding key of a piano. The term "8ft" comes from pipe organ practice, where the largest member of a rank of open pipes sounding this pitch has a speaking length of approximately 8 feet.

If the note produced when a key is pressed is an octave lower than the note in 8ft pitch, the organ is said to be sounding in 16ft pitch. Similarly if the note is an octave higher than the note in 8ft pitch, this is described logically as 4ft pitch. If it is two octaves higher, this is described as 2ft pitch. Some instruments are capable of sounding notes three octaves higher, or in 1ft pitch.

In addition to providing such facilities for sounding notes which are related to unison pitch by integral octaves, more pretentious organs may be capable of sounding other notes which although harmonically related are not separated by whole octaves. These are described generally as "mutation" pitches, and are designated by fractional footages such as 2- $\frac{2}{3}$ ft, 1- $\frac{3}{5}$ ft, 1- $\frac{1}{3}$ ft, and more rarely 5- $\frac{1}{3}$ ft and 10- $\frac{2}{3}$ ft.

The important point to grasp about the various pitch facilities which may be provided on an organ is that they are not mutually exclusive. Although it is usually possible to use any pitch singly, and this is often done, they may also be used together in various combinations to achieve interesting or musically satisfying results.

Control of the various pitches is usually achieved by the stop knobs, tablets, rockers or drawbars, along with the control of tone colour. This is done by providing the various tone colours in various pitches. Thus a theatre-type organ may provide the flute-like tibia tone colour in various pitches, with tablets marked "Tibia 8ft", "Tibia 4ft", "Tibia 2ft" and so on. Similarly a classical-type organ may provide the traditional diapason tone colour in a range of pitches, although here the rockers or drawstop knobs may be given names like "Diapason 8ft", "Principal 4ft", Twelfth 2- $\frac{2}{3}$ ft" and "Fifteenth 2ft".

The same applies to the tone colours based on imitation of string and other orchestral instruments, although here the stop names tend to vary more with pitch — the idea being to suggest various instruments. Thus a stop tablet providing string tone in 8ft pitch may be labelled "Gamba 8ft" or "Salicional 8ft", but another providing string tone of 4ft may be marked "Violin 4ft" or "Salicet 4ft". Similarly the equivalent of an 8ft stop control marked "Oboe 8ft", in 16ft pitch may have the marking "Bassoon 16ft".

Organ keyboards designed for playing with the hands are known as "manuals", while a keyboard for playing with the feet is a "pedalboard". The number of keys provided on a manual or a pedalboard is known as its "compass". Concert organs have a manual compass of 61 notes (5 octaves) and a pedalboard compass of 32 notes (2½ octaves), but smaller organs may have a reduced compass for both manuals and pedalboard.







## JUST A SAMPLE FROM OUR LARGE RANGE OF CCTV PRODUCTS



**2 1/3" VIDICON CAMERA**  
\*\$143.50

RF/Video Output, Vidicon Racking  
Also  
5" Viewfinder Cameras  
1" Vidicon Low Light Level Cameras  
Silicon Diode Cameras



**9" HIGH RESOLUTION  
MONITOR** \*\$126.00

Suitable CCTV, Computer Terminals etc.  
Also 15" monitor \$145.00  
12" receiver/monitor (modified for VTR) \*\$145.00




**SCANNER 24V AC with  
Autoscan** \*\$111.30  
\*\$160.00 (c/w control)

Also complete range Pan/Tilt Units, light & heavy duty.



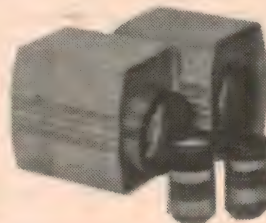**CAMERA WALL/CEILING MOUNT**  
C/W Pan/Tilt Head \*\$11.55




### LENSES—

Length	
Motorised Zoom	
F1.6/16mm	
1-9	*\$17.42
10-24	*\$16.00
F1.3/8mm	
1-9	*\$35.00
10-24	*\$30.50



**HIDDEN CAMERA  
ENCLOSURE**

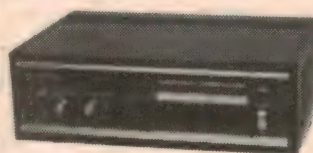c/w 6" speaker  
60 x 36 x 22 \*\$51.00  
45 x 30 x 22 \*\$43.00



**AUDIO VISUAL  
COMMUNICATOR**  
4.4W amplifier  
5 pos. video/  
audio switcher  
\*\$125.00

(use with hidden camera enc.)

PA SPECIAL		
10 watt horn		\$10.50
15 watt horn		\$19.50
60 watt amplifier	\$111.00	20 watt horn \$23.75
30 watt amplifier	\$84.50	25 watt horn \$23.80
15 watt amplifier	\$47.00	30 watt horn \$35.80
(sales tax included)		

### TRADE ENQUIRIES WELCOME

\*plus 15% Sales Tax if applicable



CONTACT US FOR COMPLETE PRODUCT AND  
TECHNICAL INFORMATION

**DYNETICS PTY. LTD.**

425E PENNANT HILLS RD., PENNANT HILLS, SYDNEY 2120  
02-848-9055

SOLE AUSTRALIAN AGENTS VICON INDUSTRIES INC. U.S.A.

## ELECTRONIC ORGAN

used. A value of .082uF gives the usual "fast" vibrato rate of 7Hz, which is changed to the slow "chorus" rate of about 1Hz by using two additional 0.33uF capacitors to give a total of 0.74uF.

The oscillator does not give a sinewave output; in fact it can deliver either a square or a triangular wave, depending upon which output is used. However by using the triangular wave and passing it through a simple R-C filter which is switched to suit the two speeds, we obtain an approximate sinewave output which in terms of vibrato cannot be distinguished from a true sinewave.

The signal from the RC filter is taken to a 100k linear pot, which becomes the vibrato amplitude control. The degree of vibrato may thus be varied from zero (i.e., no vibrato at all) to maximum—about  $\pm 1$  semitone, which should be more than adequate.

The vibrato signal from the pot is AC coupled to one input of a third op-amp element of the LM3900 IC. This element is used as a unity gain buffer, driving the two varicap diodes to modulate the frequency of the master oscillator.

The second input of the buffer is taken to the pitch control, which is a 15k linear pot connected in series with two limiting resistors across the 12V supply rail. Varying the pot thus alters the quiescent DC bias applied to the buffer op-amp, and its output accordingly follows suit to vary the quiescent reverse bias on the varicaps. Hence the average frequency of the master oscillator may be varied, to move the pitch of the entire instrument. The range provided is about  $\pm 3\%$ , which should be more than enough to allow the organ to be matched to an existing piano or other fixed-pitch instrument.

The complete 97-note generator circuitry is built on a single PC board which measures 280 x 106mm, and is coded 76/EO2(G). Patterns for the PCB are available from our Information Service, although ready-made boards should be available from the usual suppliers.

The wiring diagram for the note generator board is shown in Fig. 4. As you can see, there are surprisingly few components involved, despite the fact that the generator provides all of the notes required for even quite pretentious organs. Each of the 97 note outputs is provided with three terminal pads, to facilitate multiple connections with larger organs.

You may have noticed already that the PC pattern obviously provides for an additional IC, yet no device is shown in that position. The additional device is a 4016A quad switch, which may be used in conjunction with the currently unused half of the 4013A device for stop combination switching in more elaborate





Wiring up the note generator board should be fairly straightforward using Fig. 4 as a guide, even for those with little previous experience building electronic projects. The main thing is to use a small soldering iron, to avoid overheating the components or the PC board, and to make sure that you wire in the IC's and other polarity-sensitive components the correct way around.

- Wire all other components onto the board before these ICs, including all of the wire links.
- Make sure the soldering iron tip and barrel are reliably earthed.
- Connect the earthy supply lead of the board to the same earth, before soldering in the MOS ICs, and until all are soldered in place.
- Handle the ICs as little as possible before fitting them to the board.
- Solder the earthy and positive supply pins of each IC to their PC pad before soldering the other pins.

A further point to note is that the nominal "earth" pin of the 50242 top octave synthesiser IC is not earthed directly, but is brought out to the side of the board and marked "-0.7V". It is necessary to peg the Vdd level of this device at a slightly more negative potential than the earth line of the note dividers, to ensure reliable drive to these ICs. This is because the top octave synthesiser is a P-channel MOS device, while the dividers use CMOS technology.

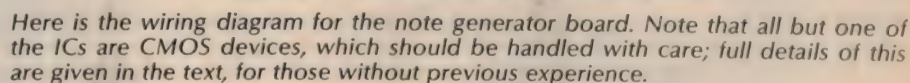No circuit diagram has been given for the top octave synthesiser and divider sections of the note generator module, as these consist of little more than the ICs involved. The only other components are



A parts list for the note generator module is given in this article for the benefit of those wishing to "get started" with construction. The parts needed for the remainder of the simple organ will be given in the second of these articles. 



# Build this novel 'LEDS & ladders' game!

Here is a low cost pocket-sized electronic game that will test your patience and sense of timing. Seemingly simple, you may find to your dismay that literally hours of practice are required before you can "reach the top".

by DAVID EDWARDS

As you can see from the photographs, our new game consists of a small box, fitted with two switches, sixteen small light emitting diodes (LEDs), and an illustrated front panel. The illustration is a schematic drawing of a well, with a ladder reaching from the bottom to the top. The LEDs are arranged on the rungs of the ladder, representing successive foot positions as the ladder is climbed. The topmost LED, which is a different colour to the other ones, is on the ground at the top of the well.

When the POWER switch is pressed, the bottom LED commences to flash at a two second rate. The object of the game is simply to make the LED climb the ladder, by appropriate manipulation of the CLIMB button. Success is signified when the different coloured LED at the top is illuminated.

The trick in the game is that the CLIMB switch can only be operated when a LED is on. When this condition is satisfied the LEDs illuminate in turn, to simulate the effect of a light climbing the ladder.

If, however, the CLIMB switch is pressed when no LED is illuminated, the player is surprised and infuriated to find that when a LED comes on again, he is back at the bottom of the well. Of course, the device is scrupulously fair, so that even if the switch is only pressed for the shortest of times, back to the bottom he goes!

So, having limbered up his wits, as well as his switch operating finger, our player attacks the infernal machine again. With his eye glued to that first LED, and his finger poised, he waits for that light to come on. Flash!, the LED emits, his finger stabs the button, and the LED commences to climb!

One! two! three! four LEDs emit in turn, the button is released, and a fraction of a second later, the LED goes out. With bated breath, our player scans the LEDs, and is rewarded by seeing the fourth LED come on again. Once more he stabs at the button, once again the LED commences to climb.

Some time later, the fifteenth LED casts a ruddy glow over the perspiring face of

our player, who decides to stop for a short time to wipe his brow. Those last few steps had seemed to be harder to climb than the earlier ones, in fact, he'd only just managed to go from the fourteenth to the fifteenth rung in one go.

Directing his attention back to the game, our hero is horrified to find that he's slipping back down the ladder, now only the fourteenth LED is alight. Desperately, he punches mindlessly at the button, the LED climbs up higher, just reaches the top, and then goes out. And he's still pressing the switch!

With a heart-rending groan, he releases it, and then watches dejectedly as the lowest LED flashes merrily. Some minutes later, he musters his courage, and once more commences to climb.

Just in case you're wondering whether or not it is possible to reach the top, we can assure you that it is. In fact, the little man at the top is waving to show you that he managed it, so don't lose heart and give up.

*You can see from this illustration how we have arranged the LEDs on the ladder rungs. The one at the top is a different colour, to signify success. Instructions detailing how to play are included on the front panel.*

Turning now to the circuit diagram, we can examine its various sections, and see exactly how the game operates. The 555 type IC functions as an astable multivibrator. The frequency of operation is determined by the two 100k resistors and the 10uF capacitor. The diode connected between pins 6 and 7 serves to make the mark/space ratio unity, while the 0.01uF capacitor connected to pin 5 ensures reliable triggering.

The output from the timer is obtained at pin 3, and is in the form of a square-wave with an amplitude only slightly less than the supply voltage. The CLIMB push-button connects this pin to a large electrolytic capacitor, via a diode/resistor network.

If the CLIMB button is pressed when the voltage on pin 3 is high, the diode is reverse-biased, and the 470uF capacitor is charged via the 6.8k resistor. When the button is released, the capacitor commences to discharge through the 1M and 390k resistors. However, the time-constant is very long, of the order of 10 minutes, so that for the moment we will assume that the capacitor retains its charge indefinitely.

However, if the CLIMB button is pressed when the voltage on pin 3 is low, the diode is forward biased, and the capaci-









# JUST ARRIVED! NEW MODEL 'COMMUNICATOR' V.H.F. ALL- BAND



**RADIO  
SENSATION**

WARNING: DO NOT CONFUSE  
WITH SIMILAR LOOKING RECEIVERS  
WITH ONLY LIMITED COVERAGE.

Dick Smith is Proud to bring you  
a VHF receiver that covers  
ALL AUSTRALIAN bands.  
54 to 220 MHz.

- \* EXCLUSIVE SIGNAL STRENGTH  
INDICATOR HELPS TUNING.
- \* LATEST MILITARY-LOOK FINISH  
IN BLACK, GREY, GREY/GREEN  
WITH WHITE LETTERING.
- \* MULTISECTION AERIAL.

- COVERS THE FOLLOWING BANDS:
- \* AM - This is the standard Broadcast Band.
  - \* 54 - 88 - TV, Fire Brigade, Ambulance,  
Police, Business Radios etc.
  - \* 88 - 108 - FM Band. Listen to all the  
new FM Broadcasts.
  - \* 108 - 136 - AIR. All Aircraft, Jumbos,  
Towers etc.
  - \* 135 - 174 - Amateurs, Marine VHF,  
Harbour Control, Ambulance,  
Fire Brigade, Police, Taxis,  
Road Patrols etc.

**FREE: EXCLUSIVE V.H.F. STATION  
GUIDE ONLY FROM US**

**\*Specially  
designed for Australia  
\*Opens NEW listening  
realms \*Complete  
VHF coverage**

**\*16transistors.  
\*15diodes.  
\*2rectifiers,  
\*1varistor.**

**\$49.00**

**Free DELIVERY AND  
INSURANCE ANYWHERE  
IN AUSTRALIA.**  
(includes batteries)



**Portable Fluro Lantern**

All purpose, portable fluro lantern that operates from  
either six "D" size batteries or can be plugged into  
your car cigarette lighter. Complete with all  
attachments including wall brackets. Ideal to use in  
home, garage, camping, boating, fishing, caravans,  
emergency motor repairs, etc. Good bright light.  
Weather and dust proof.

Cat. X1091 ..... \$15.95




**\$9.75  
CARAVAN, CAR, BOAT, LIGHT**

Easily plugged into car or boat cigarette lighter. Perfect for use off  
12 volt circuit in caravan. Operates from 12 volt DC battery. Has  
transistorised circuit protected by a diode against reverse connection.  
Compact, attractive, practical design with 8 watt fluorescent  
12 inch tube. Normally sells for \$15.50 NOW ONLY \$9.75

# SOUND LEVEL METER

Every  
member  
of the  
Noise  
Abatement  
Society  
should  
have  
one!

**\$47.50**

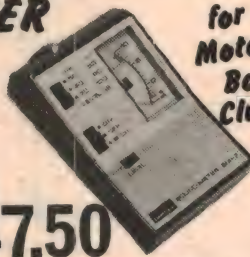

A must  
for all  
Motor  
Boat  
Clubs

SM7 Latest addition to our instrument range, the SM7  
is ideal for office, factory and many other uses. Fully  
solid-state and miniaturised for convenience. 6 ranges  
cover 40 to 110db. Uses 'A' weighting network. Taut  
band type meter movement graduated from -10db to  
+10db with battery check. Mic is electret type and  
covers 30-8000 Hz. 150 hour battery life. Measures  
10.6 (L) x 6.6 (W) x 3.6 (H) cm. and weighs only 150g.  
Complete with free earpiece for checking sound being  
monitored. This is a full 6 range instrument (most  
have only 5). Cat. Q1530 ..... Only \$47.50



**'LIP-STICK'  
ALARM**

**\$3.98**

A Lipstick size tube that lets  
off an ear-splitting wail when  
pressed. Fits into pocket or  
purse. Protect your wife or  
lover with this alarm.  
Bargain at only \$3.98



**PERSONAL  
TORCH  
ALARM**  
**\$3.98**


A powerful torch which  
doubles as an ear-splitting  
alarm. Operates from three  
penlight cells. A must for  
the wives or girlfriends  
car.  
Excellent Value \$3.98



**SALE SPECIAL**

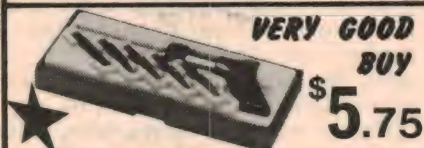**\$4.25**

This kit comprises a ratchet handle and four screwdriver  
blades (two slotted and two phillips). The handle is a  
specially designed pistol grip to give maximum power.  
Packed in an attractive presentation case. \$4.25




**VERY GOOD  
BUY**

**\$5.75**

This kit consists of a special ratchet pistol grip handle  
and five screwdriver blades (three slotted and two  
phillips). The blades are held in place by an exclusive  
MAGNETIC chuck so you can change blades in an  
instant. Very good value at only \$5.75

# PLAY YOUR OWN TV GAMES TONIGHT

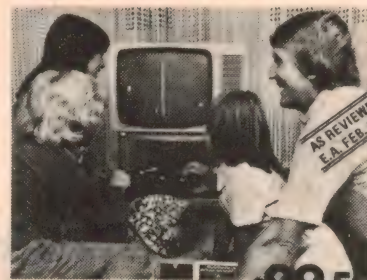

AS REVIEWED IN  
E.A. FEB. 1976

**\$99.50**

VIDEO GAME OLYMPIC:  
Play Tennis - Wallgame - Find the Gap - Grabbit - Trapper  
Moving Target..... ONLY \$99.50  
VIDEO GAME Mk1:  
Play Squash - Tennis - Football with dribbling and tackling.  
Great fun for the whole family..... GOOD BUY AT \$139.50  
Mk111 KIT: Build your own for the low amount of \$89.50  
\*SIMPLY PLUG INTO TV ANTENNA SOCKET.  
No modifications needed. Ideal for parties. Compact unit.  
Please include \$5.00 for Packing and Postage.  
CALL IN FOR A DEMONSTRATION GAME!




**FIRE  
EXTINGUISHER**  
**\$5.25**

A must for all workshops, cars, boats, caravans  
home etc. Particularly suitable for electrical,  
kerosene and petrol fires where the use of  
water would be dangerous. Bracket for wall  
mounting supplied at no extra charge.  
Is your life worth \$5.25
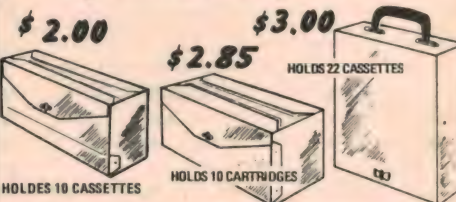
# VINYL CASSETTE & CARTRIDGE HOLDERS!

Don't leave your valuable cassettes or cartridges lying  
around to gather dust or be damaged. Available in a wide  
range of colours. Made from strong attractive vinyl.



**\$2.00**

**\$2.85**

**\$3.00**

HOLDS 22 CASSETTES

HOLDS 10 CASSETTES

HOLDS 10 CARTRIDGES

# Keep Your Car Clean

DON'T SLING YOUR CASSETTES AROUND  
IN THE CAR

Dick offers an under-dash cassette holder  
moulded in black plastic with clear front lid.  
Holds ten cassettes and cases complete with  
bracket and labels.

This unit saves the inconvenience  
of searching for your  
favourite cassette.

**\$3.99**



**EXTRA  
SPECIAL**

**\$7.50**

This twelve piece kit comprises four screwdriver blades  
(two slotted and two phillips) a socket shaft and six  
commonly used metric sockets, as well as the ratchet  
pistol grip handle. Fantastic Value at only \$7.50

NEW 84 PAGE CATALOGUE IN THE  
APRIL ELECTRONICS AUSTRALIA  
Yes a completely new and larger edition  
of the world famous catalogue will be  
presented FREE in April E.A. so book  
your copy NOW. The enlarged catalogue  
will feature many new products - Hi Fi  
- Kits - Tools - Books - Instruments  
- Amateur Gear - Components -  
Semiconductors etc. etc. They're all in  
the new catalogue. The issue must be a  
sell out and there won't be very many  
over runs.  
SO ORDER YOUR COPY NOW.



**DICK SMITH**

**ELECTRONICS CENTRE**  
Head Office & Mail Orders

162 Pacific Highway Gore Hill  
N.S.W. 2065 tel: 439 5311  
telex: AA 20036  
cables: DIKSMIT Sydney

Shop hours:  
Mon-Fri 9-5.30 Sat 9-12.

Also at **CITY 125 York St**  
tel: 291126  
(Nr Town Hall)  
and **BANKSTOWN**  
361 Hume Hwy  
tel: 709 6600  
(Nr Chapel Rd)

**bankcard**  
welcome here



## LEDs & LADDERS



Although we stated earlier that the loading on the 470 $\mu$ F capacitor was negligible, this is not strictly so. The 1M and 390k resistors, in conjunction with the impedance presented by pin 11, as well as the leakage resistance of the electrolytic itself, combine to slowly discharge the capacitor. This discharge is most noticeable when the capacitor is highly charged, and accounts for the "slipping back" observed by our hypothetical player. This effect adds to the difficulty of the game.

The stabilised LED driving voltage is made available at pin 14, and is normally connected to pin 16 by a suitable resistor. We have included a transistor in series with a 10k resistor, and used the output of the 555 to switch the transistor on and off. This pulses the LEDs, eliminating the need for a separate flashing indicator.

As well as being economical in terms of components, this also means that a stabilised supply is not necessary. This is because the 555 and the UAA170 both use fractions of the supply voltage as their references, making frequency and comparator switching levels independent of supply variations. As the LEDs are driven from a constant voltage source, their intensity does not change with supply voltage either.

We have used eight 1.5V penlight cells to power the circuit, giving a nominal 12V supply. The batteries are mounted in two 4-way holders, as shown in the photographs. The average current drain of the complete circuit is about 25mA, giving an estimated life of 40 hours.

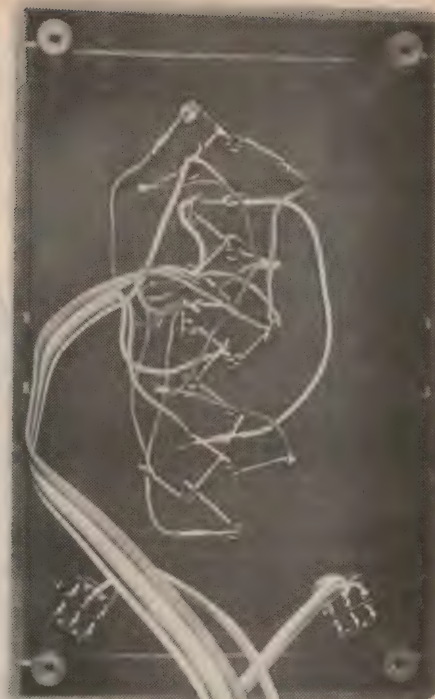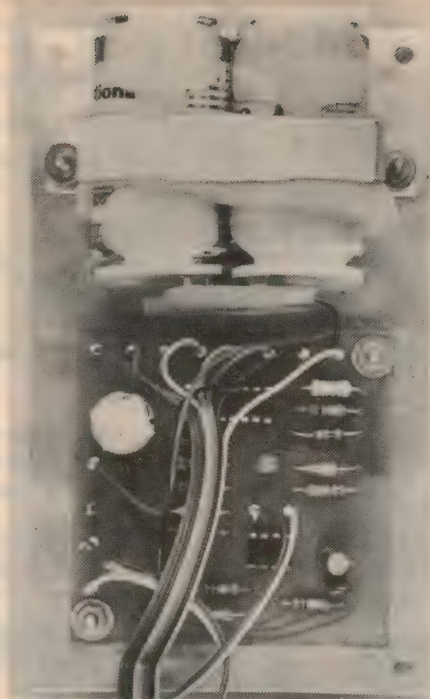If required, it would be possible to fit a small transformer and rectifier/filter assembly in place of the batteries, although the initial cost would be much higher. The voltage applied to the circuit must be kept below 16V, to prevent damage to the ICs.



These two photographs give a clear picture of the internal construction, including details of how the LEDs are wired together.

Construction of the game is quite simple, as all major components except the LEDs are mounted on a printed circuit board (PCB). This measures 71 x 71 mm, and is coded 76g3. We recommend the use of PCB stakes for all external connections to the PCB. Fifteen are required.

We mounted the game in a standard plastic utility box, measuring 159 x 96 x 50mm, fitted with an aluminium lid. We used the box upside down, which necessitated filing off the moulded-in feet on the bottom. We made a front panel from photo-sensitive aluminium, and used this as a template for drilling the required holes for the LEDs and switches.

We expect that component suppliers

will be able to supply suitable front panels. Alternatively, dyeline prints are available from our Information Service. These may be used to make bromide prints by the contact method.

The LEDs are simply pushed into suitable holes. If necessary, mounting clips can be used, or they may be simply glued in position. Arrange them so that the anodes and cathodes are all oriented in similar fashion, as this will facilitate wiring them up. If desired, the top LED can be a different colour, to signify success.


The choice of the switches poses a slight problem. Matching push-operated switches, such as we used, are obtainable, although they are expensive. If required, non-matching switches could be used, e.g., a slider type for the power switch, and an economy push-button for the climb switch.

The completed circuit board is fastened to the lid of the box using machine screws and nuts. The batteries are held in position with a small clamp fashioned from aluminium.

The wiring from the PCB to the LEDs and switches is best done with rainbow cable, as this makes for easy identification of the different leads. Complete the interconnections between the LEDs first, using the circuit diagram as a guide, and then connect them to the PCB.

Construction is then complete, and you can attempt to climb the ladder. If the LEDs do not come on in order, it is likely that the connections to them are in error. Any LEDs failing to emit will probably have anode and cathode transposed.

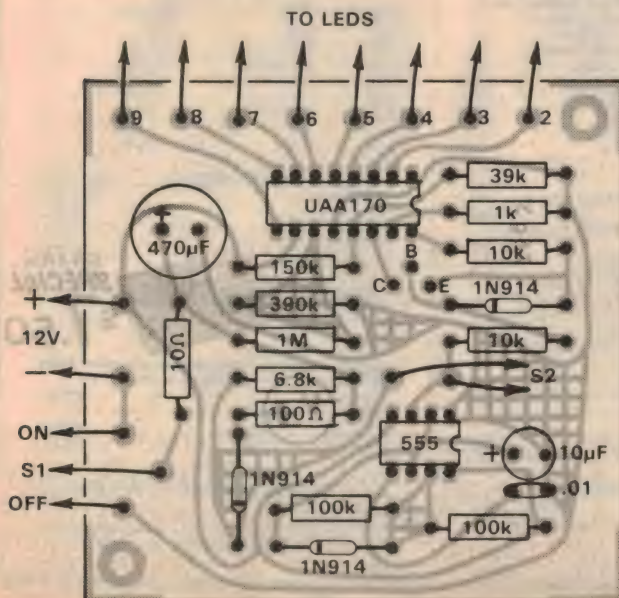Once you have mastered the necessary skills, and can climb to the top of




The numbered connections at the top correspond to the pin numbers of the UAA170. Refer to the main circuit diagram for details of the wiring required to the LEDs.


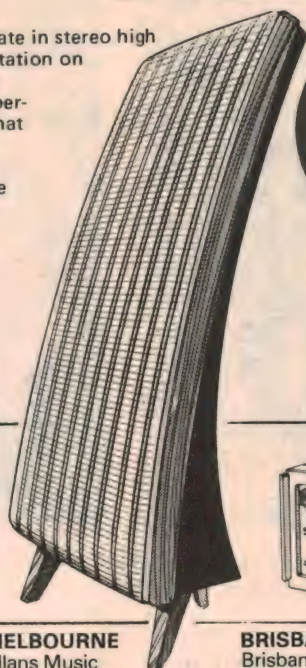
# For the closest approach to the original sound.....

The sound of QUAD is the ultimate in stereo high fidelity. QUAD has built its reputation on producing the finest high fidelity equipment in the world. It is so perfectly engineered and balanced that it is, without doubt, the closest approach to the original sound. The only way to really appreciate the reality of QUAD is to listen to it. And you are invited to do just that... at leading high fidelity retailers throughout Australia.



# QUAD

Australian Agent:

**BRITISH MERCHANDISING PTY LTD.**  
49 - 51 York St., Sydney. Telephone 29 1571.

Below, left to right: QUAD electrostatic loudspeaker, QUAD 303 power amplifier, QUAD 33 control unit, QUAD FM3 stereo tuner.

Free literature is available on request from your local QUAD retailer or from the Australian Agent (address above right).



## SYDNEY

Arrow Electronics  
Douglas Hi Fi  
Instrol  
Kent Hi Fi  
United Radio Distributors

## MELBOURNE

Allans Music  
Beland Electronics  
Douglas Trading  
Myers  
Sound City

## BRISBANE

Brisbane Agencies  
Stereo F.M. Sound  
**CANBERRA**  
Duratone  
Pacific Stereo

## ADELAIDE

Blackwood Sound  
Challenge Hi Fi  
Sound Spectrum

## HOBART

Bel Canto  
Quantum

## PERTH

Alberts TV  
& Hi Fi Centre  
The Audio Centre

# ELECTROCRAFT PTY. LTD.

106A Hampden Rd.  
Artarmon, 2064  
Phone 411-2989

Distributors of Belling Lee, Channel Master, Ecrafft, Hills, HI.Q, Lab Gear, Kingray, Matchmaster. Largest range of aerial equipment in Sydney.

## TELEVISION AERIALS, DISTRIBUTION AMPLIFIERS, EQUIPMENT AND ACCESSORIES WHOLESALE, TRADE AND RETAIL SUPPLIED.

### ECRAFT

	Retail Price	
Neosid Balun 75/300 uncased	\$0.65	
O.S.A.B. Outside aerial balun	3.81	
6.SB 6ft. Balun Fly Lead	3.65	
P.S.B. Plug and Terminal Balun	2.53	
2.75.T/S 2-way 75 ohm Transformer Splitter box	4.41	
3.75.T/S 3-way 75 ohm Transformer Splitter box	8.41	
4.75.T/S 4-way 75 ohm Transformer Splitter box	8.94	
5.75.T/S 5-way 75 ohm Transformer Splitter box	12.66	
2.3T 2-way 300 ohm Splitter box	4.48	
3.3T 2-way 300 ohm Splitter box	5.86	
4.3T 2-way 300 ohm Splitter box	7.12	
Adjustable Low Band Attenuator	6.31	
10" diameter degaussing coil	24.00	

### TELEVISION AERIALS FOR COLOUR

#### HILLS

	Retail Prices		Retail Prices
EFC.1	\$24.17	215.8 EL	\$19.26
EFC.2	\$32.06	216.9 EL	\$24.10
EFC.3/24	\$46.65	CY7 Colinear	\$25.95
EFC.4/03	\$58.68	2010 Airways	\$42.50

#### CHANNEL MASTER

3111 Super Colarray	\$36.50	638.8 EL	19.26
3110.2 EL Colarray	22.75	257 Colinear	26.07
		361A 17 EL Crossfire	54.95

#### HI.Q SINGLE YAGI'S

CH.2 4EL	\$20.80	Gutter Clip Aerial 1 EL	8.90
CH.4 & 5 A 8 EL	27.74	Gutter Clip Aerial 2 EL	11.00

### COAXIAL CABLES

Attenuation per 100ft at 200 MHz  
Belden 9242 Double screened with  
Belden 9248 Duofoil and Braid  
TVM1A Concordia Copper Screened  
Hartland WH89 Copper Braid  
Hartland WH87 Copper Braid  
Hartland WH86 Copper Braid  
300 ohm Feeder Cable  
Open wire line 300 ohm  
Open wire line 300 ohm

	Reel Size	Price
4.0 dB	500 ft	\$42.28
3.1 dB	500 ft	58.61
4.4 dB	100 metre	30.15
3.3 dB	100 metre	36.92
6.0 dB	100 metre	26.56
6.5 dB	100 metre	19.25
1.8 dB	100 metre	8.80
1.5 dB	100 ft	9.90
1.5 dB	300 ft	29.80

### FILTERS

F75B Single Channel Low Band Filter	\$9.56
F75C Single Channel High Band Filter	\$19.12
F75D/A Low Band Filter	\$7.65
F75WN Filter for Chs. 3, 4, 5, 5A	\$10.91
F/Hi/Lo High-Low Twin Aerial Filter	\$14.53
F300A Single Channel Balanced Low Band Filter	\$5.58

### F.M. AERIALS

	Retail Price
Matchmaster	\$21.30
Hills 3 EL	11.17
HI.Q 4 EL	15.91
HI.Q Gutter Clip 2 E1	9.50

### TELESCOPIC MASTS

20 ft	\$19.30
30 ft	30.81
40 ft	42.06
50 ft	54.42
60 ft	58.00

### KINGRAY AMPLIFIERS

	Retail Price
D15/500 m/V	\$48.80
D30/500 m/V	57.95
D40/600 m/V	79.30
D12/1500 m/V	67.10
MH 20 Mast Head	64.63

### LAB GEAR AMPLIFIERS.


	Retail Price
VHF UHF Mast Head 22 dB	\$72.43
CM 6014/DA 20 dB	60.25
CM 6034/DA 4 outlets 8 dB each	54.90
CM 6036/DA VHF 30 dB UHF 28 dB	84.63
Televerta (VHF to UHF frequency converter)	67.48
Channel Master Telstar	58.91

### ALL TYPES OF HARDWARE IN STOCK


Wall brackets, chimney mts., J Brackets, Turn-buckles, Guy Rings and Guy Wire. All types of masts, etc.



## LEDs & LADDERS GAME

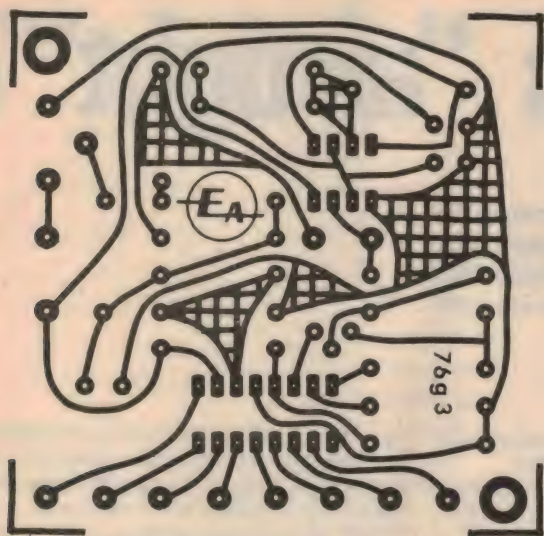

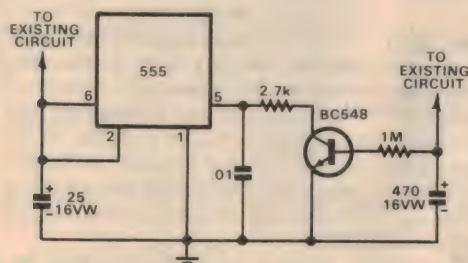Shown above is the PCB pattern, while to the right is a reproduction of the front panel. These are both full size, and can be copied if desired.



A simple modification to the game, as shown above, can make it very much harder to reach the top of the ladder.

the ladder in a dozen or so steps, a small modification can be made to make the game even harder to beat. By adding a single transistor and two resistors, the circuit can be modified so that the flashing rate becomes dependent on the amount of charge in the 470uF capacitor.

The accompanying diagram shows how this is done. The BC548 transistor is used as a variable resistance, loading down the control input of the 555 timer. As the voltage on the 470uF capacitor rises, the base current in the transistor increases, turning on the transistor.


This loads down pin 5, and changes the internal thresholds, so that the timing capacitor does not have to charge and discharge through the same voltage swing. This speeds the oscillator up, while maintaining the mark/space ratio at approximately unity.

Thus the LEDs turn on for shorter and shorter periods, making the task of climbing to the top of the ladder harder and harder as the climber approaches the top. The 1M base resistor serves to keep the transistor on the linear portion of its operating curve, while at the same time minimising loading.

The 2.7k resistor limits the maximum frequency of the 555. This value can be varied if required. With the value we have shown, we found that at the top of the ladder, the "on" pulses were a little too short for satisfactory operation, so we changed the 10uF timing capacitor to 25uF. This gave an acceptably wide "on"

pulse, while still making the task of climbing the ladder suitably difficult.

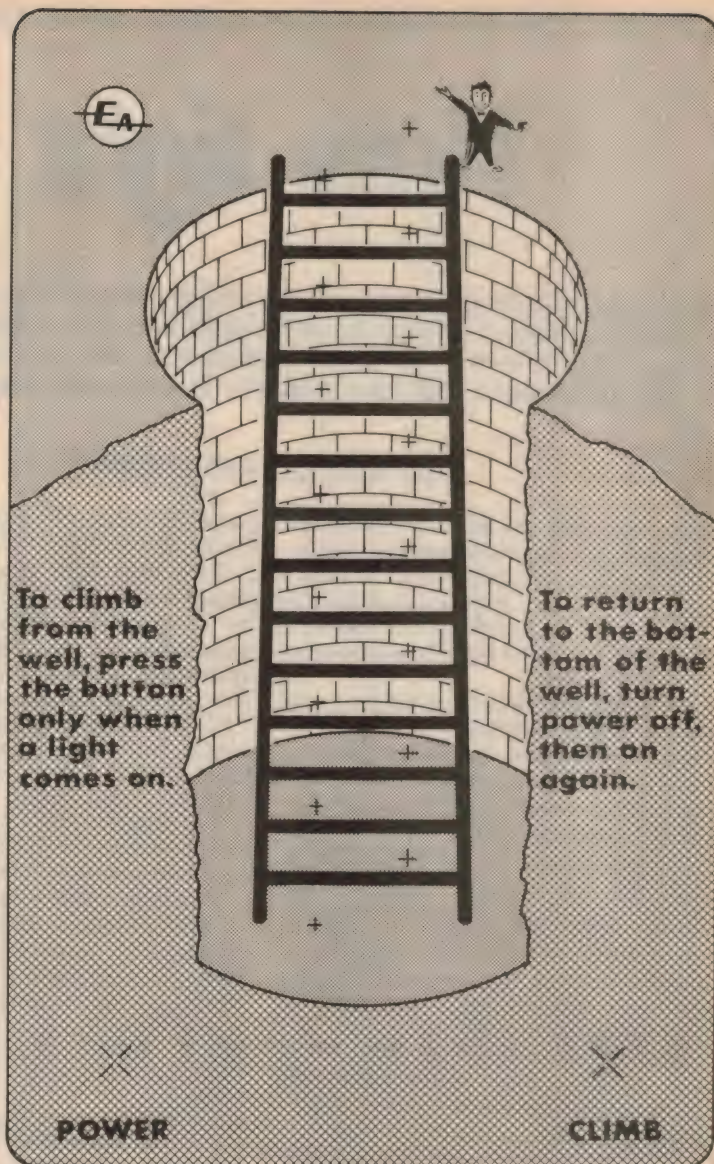No provision has been made on the PCB for these components. However, with a little care and ingenuity, they can be fitted to the pattern underneath the board. We will leave the exact details of this to individual constructors.



## THE VIDEO AND HI-FI CENTRE

We specialise in Video-Recording and colour TV's

Watch your favourite programme/film by recording with Video equipment.

For further details of our extensive range of Video equipment and colour receivers



Call at or telephone:

**THE VIDEO CENTRE**  
445 Oxford Street,  
Paddington. NSW 2021  
Tel: 31-2555



# How tight is "airtight"?

Almost as a matter of course, people who specify details of loudspeaker enclosures insist that they must be rigid and fully sealed against air leaks, apart from any deliberate vent or port. But just how important is this specification and how diligently should it be observed in practice?

by NEVILLE WILLIAMS

The question was asked in our recent Year Book and was answered in a matter-of-fact way—accurately but without any urgent conviction. Had we phrased the answer now, two or three months later, we might have been much more positive in our statements.

What happened in the meantime was that an engineer showed us the response curve he had plotted of an inexpensive, locally assembled vented system. The shape of the bass response caught our eye: Instead of holding more or less flat down to a discernable corner frequency, and then dropping away at something like 24dB/octave, it had a small hump at around 70Hz, followed by a slope to about 40Hz and a roll-off after that. It wasn't too bad a curve in terms of apparent response, but it was certainly not characteristic of the breed.

Thoroughly curious, we decided to take a closer look at the particular enclosure and were given a free hand to "have a go" at it.

Our first step was to plot an impedance curve—a much simpler procedure than measuring acoustic output but none-the-less indicative of what is going on. It is done by wiring a small value resistor (1 ohm or less) in series with the loudspeaker system and, while keeping the input to the speaker constant, measuring the voltage drop across the resistor with a millivoltmeter. By regarding this as proportional to the load current, it is possible to derive a figure for impedance relatively easily.

At 100Hz the impedance turned out to be 10 ohms—not at all an unlikely figure at this frequency for a nominal 8-ohm system. Below 100Hz, the impedance rose steeply to a broad peak embracing the 50-80Hz region and reaching about 30 ohms at between 60 and 70Hz. It then dropped to a trough of 18 ohms at 40Hz, climbing to another peak at about 28Hz. Superficially it was the classical shape of bass impedance curve except that the trough should have been about half the indicated value; in other words about 9 ohms!

As a back-up exercise, we managed to get hold of the other system in the pair and ran a similar test. It yielded much the


same curve but with an impedance at the enclosure resonance of 23 ohms!

The fact that the loudspeaker impedance looked like 18 and 23 ohms at the resonance of the system was an indication that the enclosures were not providing the proper acoustic load on the rear of the cone. Fairly obviously, the "Q" of both enclosures was much lower than it should have been, almost certainly accounting for the uncharacteristic acoustic output curve.

The hump at 70Hz would almost certainly be due to the resonance of the speaker itself in the confined enclosure.

What should happen below this region is that the port should contribute progressively more to the total acoustic output; radiating in phase with the loudspeaker. At enclosure resonance, output from the port is dominant and, ideally, sufficient to sustain the total response of the system at near reference.

At frequencies below enclosure

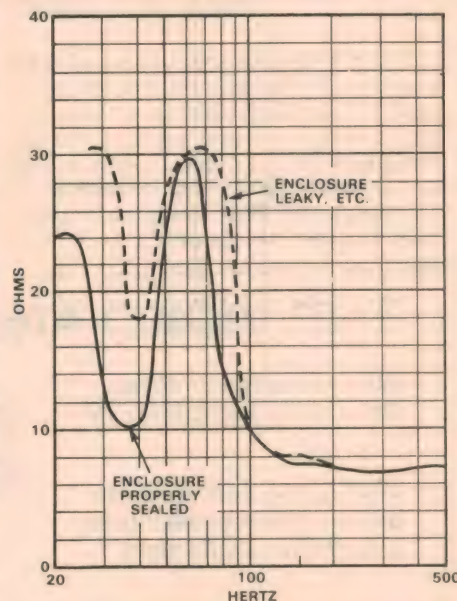

The bass end impedance of an inexpensive vented system before and after sealing. The curve includes the resistance of crossover inductor and connecting leads.

resonance, output from the port exhibits a change in phase so that, while it is still quite high, it tends to cancel rather than reinforce radiation from the cone. As a result, the response of the overall system should be sustained down to the enclosure resonance, thereafter falling away at a nominal 24dB/octave.

In the system under inspection, the designer had obviously aimed for an enclosure resonance of about 40Hz, a common design target which should cope with the frequencies contained in the vast majority of program material. For reasons that remained to be discovered, the enclosure was doing only half a job, contributing some strength to the 40Hz region but not enough to hold it up to reference. Hence the output curve which tended to straggle downwards from 70Hz.

There is a corollary to this: At system resonance, where most of the output is coming from the port, the excursion of the loudspeaker cone is minimal. From this flows the ability of a well-designed vented system to produce a generous bass output with minimal stress on the driver and, hopefully, minimal distortion and Doppler effect on higher frequencies. If the enclosure does not do its job, the user either puts up with the loss of response, or works the bass boost and speaker harder in an effort to make up the difference.

As it happened, visual inspection of the enclosures showed nothing obviously amiss, nor was there any obvious leak when the system was driven hard at 40Hz. We did notice that the internal cladding—1-inch Innerbond—was stapled rather loosely to the walls and somewhat radiused around the rear corners. It seemed possible that, if the Innerbond was unnecessarily occupying free space in the enclosure, or significantly moving with the air flow, it could be adding a significant loss component.

For the rest, the corners of the timberwork appeared to be mitred, flush and glued. The back was rebated, pinned and presumably glued snugly in position and, though unsupported, did not appear to be drumming unduly. The baffle was not bedded into caulk or foam but appeared



to fit snugly and tightly against cleats. The mid-range enclosure looked airtight, the bass driver was screwed down against its cork washer, and the tweeter (again without caulking) fitted snugly against the baffle surface.

It was not bad—but obviously not good either!

While it may have been interesting to work methodically through every joint and surface in order to apportion blame, it would also have been very time consuming. As a result, we decided to give the enclosures the full treatment and see how they measured up after that.

The internal cladding was stripped out and a cleat glued and screwed across the rear panel to stiffen it and divide it into two dissimilar areas. Cracks where the cleats abutted were filled with caulking compound glue, as appropriate, and a knob of non-hardening caulking compound was pushed over the rear of the connecting socket on the rear panel.

Then the cabinets were tilted back at 45 degrees and a line of PVC glue laid in the angle formed by the floor and back panel, the cleat and back panel, and the front cleat and floor. The glue was worked into the angle with a screwdriver and left to soak in and set overnight. It formed a quite obvious seal against any possible leakage in the joints so treated.

It took several such operations, plus the elapsed hours to run PVC into all the angles but, with the job done, we were sure that the enclosures themselves were really airtight.

further attention along the lines indicated.

Did our efforts make a difference?

Repeating the impedance curves under precisely the same conditions yielded a much narrower impedance peak for the speaker itself, centred on 60Hz, and an enclosure resonance dip bottoming at 10 ohms or less at 38Hz, which we subsequently discovered to be the design target.

Unfortunately, the year-end holiday shut-down forestalled any chance of repeating the actual response measurements but, if theory means anything, the output should likewise have been sorted out.

Certainly, on listening tests with sine-wave input, it was now smooth, solid and tight down to below 40Hz, with a corresponding bonus at the bass end of typical program material.

What comes out of this is plain enough. "Airtight" means exactly what it says in relation to a vented system, notwithstanding the presence of the port. And when the specification calls for lining to be pinned or glued firmly against the walls, it means "firmly". To disregard these matters is tantamount to setting up a critically tuned circuit, then carelessly wrecking it with resistive losses.

And what of fully sealed enclosures? Are they also critical?

Although it is not always realised, a practical sealed enclosure also relies on

a resonance effect—that of the driver itself, stiffened by the enclosed air behind the cone and damped, in part by the output impedance of the driving amplifier, and in part by any filling material specified for the enclosure.

Assuming that there is some constraint on enclosure volume, an optimum design will guide the system resonance to a selected frequency, and damp it to about unity "Q". The response curve should extend, substantially flat, or with a slight hump, down to the resonant frequency, rolling off thereafter at a rate of about 12dB/octave.

But, take that carefully designed system and lower the "Q" by over-filling the enclosure, or permitting air leaks, and the "corner" will disappear from the carefully tailored bass response curve, leaving it to trail away in an indeterminate fashion. In addition, there is every chance that air passing through the cracks will add its own hiss to the total sound.

Once again, "airtight" means ... airtight!

In practical terms, we have seen nothing to suggest that higher quality and higher priced enclosures from hifi specialist centres are suspect. We are not nearly so confident about economy systems and the kind of thing often put together by do-it-yourselfers. If you have any doubts at all about your own system, don't trust to appearances: buy a tube of PVC glue and a pack of adhesive foam and make sure!

## FIRMLY, THIS TIME

We then replaced the Innerbond but, this time, pinned it firmly back against the enclosure walls with a generous helping of upholstery tacks and drawing pins. In particular, we were careful to pin it down hard adjacent to the inner end of the vent tube. The vent tube itself was freed of any stray cardboard edges and for good measure, the ends were rounded with sandpaper and sealed with glue—this to silence any hisses which corners and fragments can cause when the tube is carrying high velocity air.

Next step was to obtain a 5-metre pack of 3/8-inch thick adhesive backed foam, which is available at most hardware stores as a draught excluder. (Engels No. 56.) This was located carefully along the cleats for the baffle to bed down against. A circle of the same material was also placed under the rim of the tweeter. The driver was left as it was, bedded down against its own cork gasket.

All this may sound like a rigmarole but it represents the difference between achieving an "airtight" condition or merely paying lip service to it. At the manufacturing stage the real thing will inevitably cost money, so that a "bargain" which merely looks the part may not be a bargain at all in the acoustic sense. Almost certainly it will need

## NOTICE TO ADVERTISERS

**Certain provisions of the Trade Practices Act 1974, relating to consumer protection place a heavy burden upon advertisers, advertising agents and publishers of advertisements.**

Section 52 of the Act imposes a general duty on everyone (individual and corporation alike) not to engage, in trade or commerce, in conduct that is "misleading or deceptive."

In addition Section 53 (read with Sections 6 (3) (c) and 79) makes it a criminal offence (punishable in the case of an individual by a fine of \$10,000 or 6 months' imprisonment and in the case of a corporation by a fine of \$50,000) for an individual or corporation to do any of the following in trade or commerce in connection with the supply or possible supply of goods or services or in connection with the promotion by any means (for example advertising) of the supply or use of goods or services, namely:—

- (a) falsely represent that goods or services are of a particular standard, quality or grade, or that goods are of a particular style or model;
- (b) falsely represent that goods are new;
- (c) represent that goods or services have sponsorship, approval, performance characteristics, accessories, uses or benefits they do not have;
- (d) represent that the individual or corpora-

- tion has a sponsorship, approval or affiliation [he, she or] it does not have;
- (e) make false or misleading statements concerning the existence of, or amounts of, price reductions;
- (f) make false or misleading statements concerning the need for any goods, services, replacements or repairs; or
- (g) make false or misleading statements concerning the existence or effect of any warranty or guarantee."

Apart from the criminal sanction for a breach of Section 53, an individual or corporation infringing Section 52 or 53 is liable to proceedings for injunction and for damages suffered by an injured party. In view of the obvious impossibility of our insuring that advertisement submitted for publication comply with the Act, advertisers, and advertising agents will appreciate the absolute need themselves to ensure that the provisions of the Act, including the sections specified above, are complied with strictly.

It is suggested that in cases of doubt advertisers and advertising agents seek legal advice.

## SUNGRAVURE PTY. LTD.



# 'Magic' table lamp uses low-cost Touch Switch.

A touch-controlled switch can be put to a variety of uses. In this article, we explain how to make such a device from economical parts, and then show how to incorporate this into an attractive table lamp.

by ROSS TESTER

When I was a boy, I made a table lamp. It was one of my first wood-work projects at school, and was my pride and joy. That was, until the teacher politely asked "How do you turn it off?" I had forgotten the switch—and it was almost impossible to fit one to it.

Just lately, I've made another lamp without a switch. At least, that's what it looks like—until you touch it. Surprise! It comes on. Touch it again, and it goes off.

All this has come about by means of a touch switch—one of those electronic toys which can be put to a large variety of uses, and not all of them trivial, either. You may have noticed many modern lifts have call buttons which do not need pressing—just touching. Some of the latest generation of colour television receivers similarly have channel selector buttons which are touched to call up the channel. Both these are examples of touch switches in action.

While the examples given are likely to be controlled by integrated circuits, it is

just as easy (and often cheaper) to do the job with discrete components. For example, our touch switch circuit uses garden-variety transistors—we happened to use BC108s, but any small signal NPN transistor would do the job. And considering BC108s have been selling for as low as 5c each, and regularly for less than 20c each, this helps keep costs down.

In fact, practically all components in our touch switch could come from a well-stocked junk box. Even if you buy all new components, the touch switch circuitry shouldn't cost more than about seven to ten dollars (depending mainly on the cost of the transformer).

Before we go any further, we had better explain just how our touch switch works, and variations possible on the original. Actually, while they are called touch switches, most devices of this type are really proximity switches—that is, they work by something coming close to the touch plate or pad, but not necessarily touching it.


They do this because the body of the

person attached to the hand or finger touching (or coming close to) the pad represents quite a large order of capacitance to ground—even though there is no physical connection between the body and ground. (No, Virginia, you don't have to stand in a flowerpot to make the thing work.)


Turning our attention to the circuit, the first transistor is connected as a Colpitts RF oscillator, with a frequency somewhere around 400-500kHz. Actual frequency of operation is unimportant, so long as the frequency doesn't happen to be either 455kHz or above 530kHz, which could tend to make radio reception in the near vicinity a little difficult!

Assume, for a second, the touch plate is not being touched, nor is anything close to it. The output of the oscillator is fed via a voltage doubling rectifier to a Schmitt trigger, which is actually a level detector whose output changes very quickly between two states—high and low—as the input voltage passes a certain threshold.

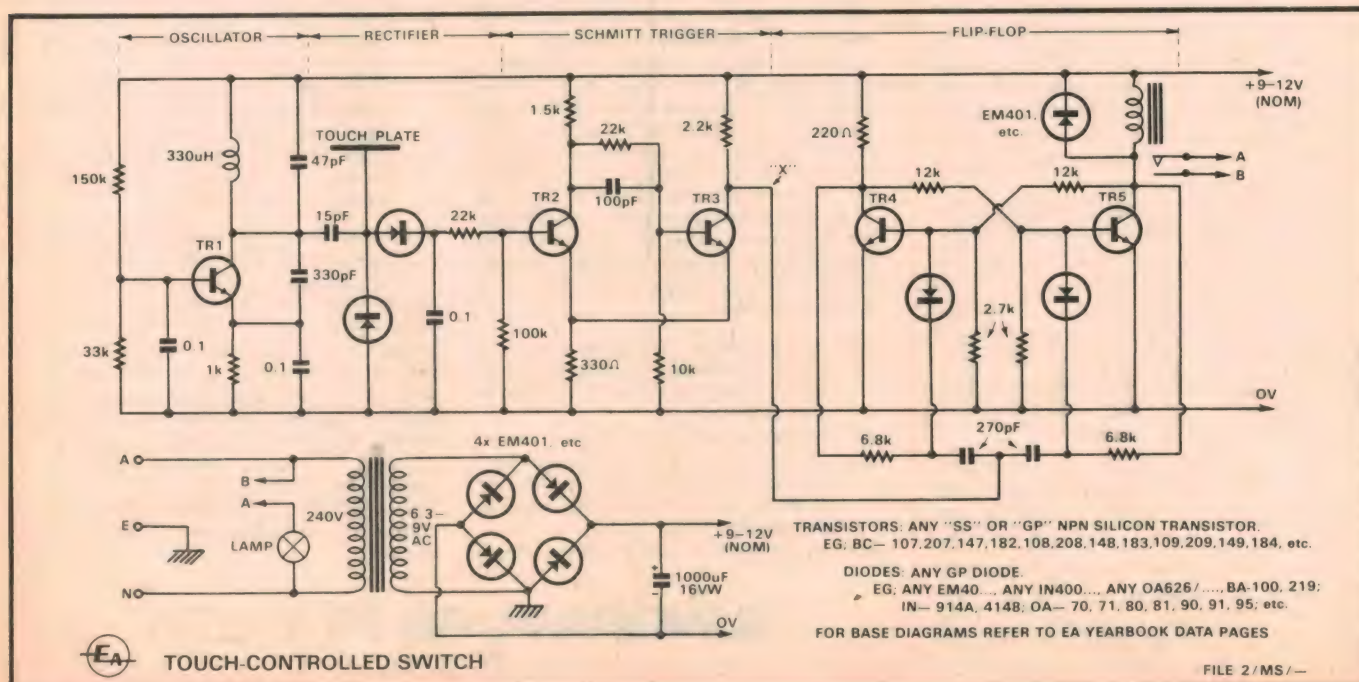Normally the Schmitt trigger sees a high input voltage, as this is the level at the output of the rectifier. However, when a hand touches, or comes close to, the touch plate, things begin to happen! The voltage doubler is fed via quite a low value of capacitance—in our case it was 15pF—which is easily swamped by the





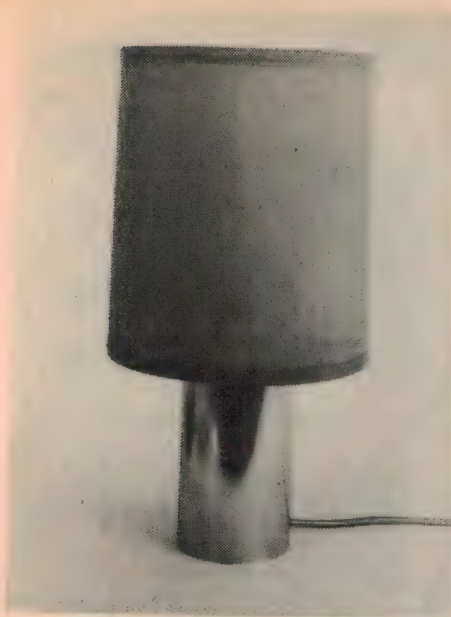

much larger capacity of the body.

In fact, the body and the input capacitor form a capacitive voltage divider—and in a capacitive voltage divider, where the capacitors are uneven in value, the greater voltage drop is across the smallest capacitor. It may be easier to visualise this by reference to Fig. 2. This shows two AC generators, one with a single C in series and one with a capacitive voltage divider across it.

In the first example, assuming negligible losses in the capacitor, the output voltage is the same as the generator voltage. In the second, the output voltage is less than the generator voltage, and if the top C is small with respect to the bottom C, the output is much less than the generator voltage.

So it is with the touch switch. The body represents the bottom C, and it is much larger than the top C. So the body robs the system of much of the energy which is being generated by the oscillator—so much, in fact, that the output of the voltage divider is negligible.

Take the hand away, and the system reverts to the conditions as in the first example. There is no longer a divider, only a series C, so the voltage doubler "sees" all of the output from the oscillator.

When the input to the Schmitt trigger is high, TR2 is forward biased, with its collector voltage quite low. It is too low, in fact, to enable TR3 to turn on, as its base is held at  $\frac{1}{3}$  the TR2 collector voltage by its base bias resistors. Therefore, TR3 is turned off and its collector voltage—and therefore the Schmitt trigger output—is high.

When the input goes low, TR2 is turned off, and its collector voltage goes high. This carries the base of TR3 high, and turns TR3 on. Its collector voltage then drops to a low voltage level, and so the output of the Schmitt trigger goes low.

Transition between the two states is very rapid as the Schmitt trigger passes the threshold in either direction, due to the large amount of feedback between the two transistors, assisted by the speedup capacitor across the 22k bias resistor.

So now we have a touch switch which has a very definite high and low output state—touch the plate and the output goes low instantly. Remove the hand and the output goes high instantly. Where do we go from here?

It depends on what you want the touch switch to do. If, for example, you want the touch switch to ring a bell when the plate is touched, a simple 1-transistor relay driver is all that is necessary. If you want the device to "latch up", this can

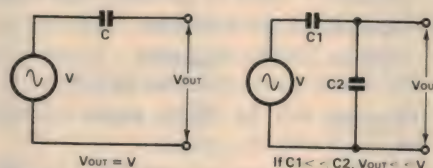


FIG. 2

be done quite simply with some of the relay contacts.

We have gone one better than both of these. By the addition of a flip-flop (bistable multivibrator), we can make the touch switch act as a true switch—touch it once and the switch turns on, touch it again and the switch turns off. An additional two transistors and a few minor components are all that are necessary to achieve this.

Referring back to the circuit diagram, transistors TR4 and TR5 are interconnected so that one's base is connected to the other's collector and vice versa. Therefore, only one of the two can turn on at any one time, as there will be no bias available for the one which is "off" because the collector of the one which is "on" will be low. However, if the "off"

transistor is biased on by some external means this will force the previously conducting transistor off, by robbing it of its bias.

In practice, it is easier to force the conducting transistor off. This is done by means of a diode gate, which supplies a negative-going pulse to the conducting transistor base. If this negative-going pulse takes the base to less than 0.6V above the emitter, the transistor turns off, thus supplying bias to its partner.

The diodes ensure that only the conducting transistor receives this turn-off pulse, thus allowing the partner to conduct without any hindrance. So it can be seen that each time a negative-going pulse arrives at the gate, the diode steers it to the correct transistor and toggles the flip-flop. By making one of the collector loads a relay, we can actuate or deactuate it by supplying a pulse to the gate—and this is just what we do.

The Schmitt trigger output is normally high, and when the touch plate is touched, it goes low—that is, it is a negative going pulse. This is fed into the gate and so toggles the flip-flop. If the relay was closed, it now opens—and vice versa. In the interests of reliable triggering, we have made the collector loads equal—a 220 ohm 1W resistor matches the resistance of the relay coil. While this might appear wasteful of power, it assists the flip-flop by making both sides as equal as possible, so one side is not harder to toggle.

One might ask why use a relay at all—why not some other form of power control device which does not use as much power itself? The answer is safety. The touch switch is quite suitable for controlling mains loads (and we will say more about this in a moment) but, because you can actually touch the plate which is connected into the circuit, isolation is needed. A relay provides this isolation.

So now we have an on-off touch switch—what will we do with it? One use which immediately sprang to my mind is a touch-control bedlamp. Have you ever woken in the middle of the night with a baby screaming and tried to find that teeny weeny switch to turn the lamp on? (You're not married and have no kids—oh well...). How about when you want to get up at 4 am and you knock the lamp over trying to turn it on to see the time.

To make construction of a lamp as easy as possible, we elected to use a single length of extruded aluminium tube as the base, plugged each end with a 25mm thick disc of softwood. The electronics are mounted on the bottom disc inside the tube, while a ceiling-type lighting fixture screws to the outside of the top disc thus allowing a lampshade to be fixed.

The aluminium tube should not be too hard to acquire—especially if you have a specialist aluminium centre nearby. Ours came from The Aluminium Centre in Sydney Road, Balgowlah, who cut the tube to the size required. They informed



ل.ن.ب.ط  
-539C



**At \$399\***  
**the only**  
**DUAL TRACE oscilloscope**  
**with DC to 20MHz bandwidth**



*The bwd539C stands at the forefront of oscilloscope design and manufacture. Be ready for tomorrow's measurements with an oscilloscope as new as today.*

**Negligible phase difference between channels over video pass band**

**and ALL these outstanding features:**

- \* DC to 20MHz — 3db bandwidth — 17n Sec Rise Time!
- \* 10mV to 50V/cm sensitivity — 12 step attenuators.
- \* 1mV/cm — 10Hz to 100kHz single channel — for very low level signals.
- \* 100nS to 1S/cm time base — 19 steps + 5—1 vernier.
- \* <5Hz to 30MHz triggering — bright AUTO base line.  
TV line & frame selection included.
- \* Identical X-Y to 2MHz, phase corrected to 2° from DC to 200kHz — for vector displays & amplifier testing.
- \* Precision 1V p-p cal waveform coincident with power line zero cross over — for probe alignment & an ideal trigger source for power line measurements.
- \* An 8x10 cm display, 3.3KV EHT — for bright crisp waveforms.
- \* Measures signals to beyond 40MHz — sensitivity chart included.
- \* 5% calibration including effects of a 10% power line variation — accuracy that doesn't change with the time of the day or from job to job!

FIS Australian Capital Cities  
plus sales tax if applicable.

MB7613  
B

**B.W.D. ELECTRONICS PTY. LTD.**

MILES STREET, MULGRAVE, VIC., 3170  
PHONE: (03) 561 2888  
CABLES: OSCILLOSCOPE, MELB.  
N.S.W. PHONE: (02) 929 7452  
DISTRIBUTORS: S.A.: (08) 269 1244  
W.A.: (092) 25 3144  
QLD.: (072) 52 7255  
TAS.: (002) 23 1843



Winner of  
Award for  
Outstanding  
Export Achievement

**1955/1976 21 YEARS OF AUSTRALIAN DESIGN INNOVATION**

B.W.D. Electronics Pty. Ltd.,  
P.O. Box 325, Springvale, Vic., 3171.

Please let me have full details  
on the bwd539C oscilloscope

Name .....

Company .....

Address .....



us that this is normal at most aluminium shops, as the aluminium is sold by the kilogram, so you pay for exactly what you get with no "fudge factor" for cutting from a longer length.


The tube diameter was as large as we could buy—100mm od, (approx. 93mm id) and approx. 200mm long. Length of the base is really a matter of personal preference, determined to a large extent by the type of lampshade to be fixed to it. If you have access to a lathe, the ends of the tube can be smoothed most easily. If not, a file will do the job, but it will take just a little longer.

The wooden disc "plugs" may cause a few problems for some readers. Ideally, they should be turned on a lathe for proper fit, but they can be cut using a coping saw and truing them with a rasp. They can also be turned on an electric drill. The bottom disc should be a tight fit—so tight, in fact, it needs to be belted in with a mallet. This is for appearance more than anything else—it saves having to put screw holes in the base of the tube where they can be seen.

The top plug can—and should—be a loose fit in the tube, as it is held in by screws which are normally hidden by the shade. If anything does go wrong with the touch switch, it is not too difficult a job to remove the top plug and hammer the bottom one out.

Incidentally, should you have a lathe at your disposal, don't be afraid to drill a hole through the centre of each plug—you will need to anyway. This can be up to about 12mm or so. It is easier to grip the wood from the centre using a bolt than to try to grip the outsides.

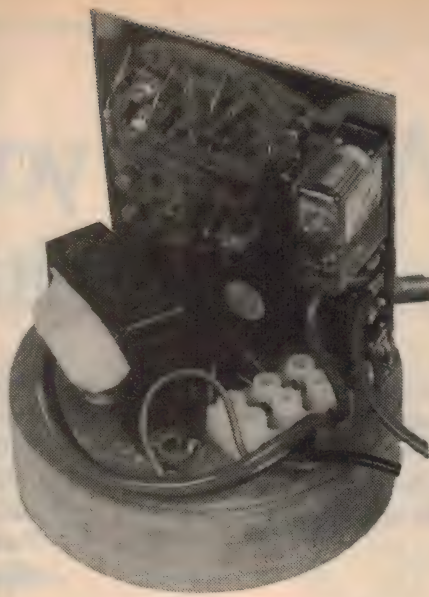Once the plugs have been cut to size, the electronics can be fitted. The printed circuit board is attached with two right-angle brackets so it is vertical. It is important to maintain at least 5mm spacing between the edge of the PCB and the



The PCB, transformer and mains wiring mounted on the bottom "plug", shown front and rear. Note particularly the method of fixing the tinplate contact strip to the plug and PCB; also the insulation tape covering strategic (mains voltage) locations.



Above: The batten lamp holder, mounted on the loose-fitting top "plug", which in turn is held in place by three countersunk head woodscrews. Below: The component layout, shown on the PCB pattern, which is reproduced actual size to facilitate tracing.

edge of the base plug—otherwise you risk a short to the metal cylinder. At best, this will stop the switch working; at worst, you will connect 240V to the cylinder. Need we say more?

(Just to be on the safe side, after assembling the PCB I covered all exposed mains connections and tracks with insulation tape before final assembly.)


The connection between the PCB and the metal cylinder is best shown by the photograph. A strip of thin tinplate is used, which should be bent to the correct shape before soldering into place. Also, a channel is cut into the base plug to take this extra thickness. It must be deep enough to allow the base to slide into the tube, but shallow enough to ensure reliable contact between the tinplate and aluminium.

The channel can be tapered a little—deepest at the top, to achieve this aim. The edge of a file can be used as it does not have to be deep. Then the tinplate can be cut slightly narrower than the file to fit in the channel.

A single panel pin holds the tinplate in place on the base plug—don't rely on a solder joint to hold it. With the tinplate held in place, solder the end to the correct point on the back of the PCB.

The next step is to drill a hole through the side of the base for the mains lead to pass through. This can be done from just about any position around the circle, as the associated keyway in the aluminium tube can be drilled later to match it. The hole is drilled on a radius, about 12 mm up from the underside of the base, and about 6 mm in diameter.

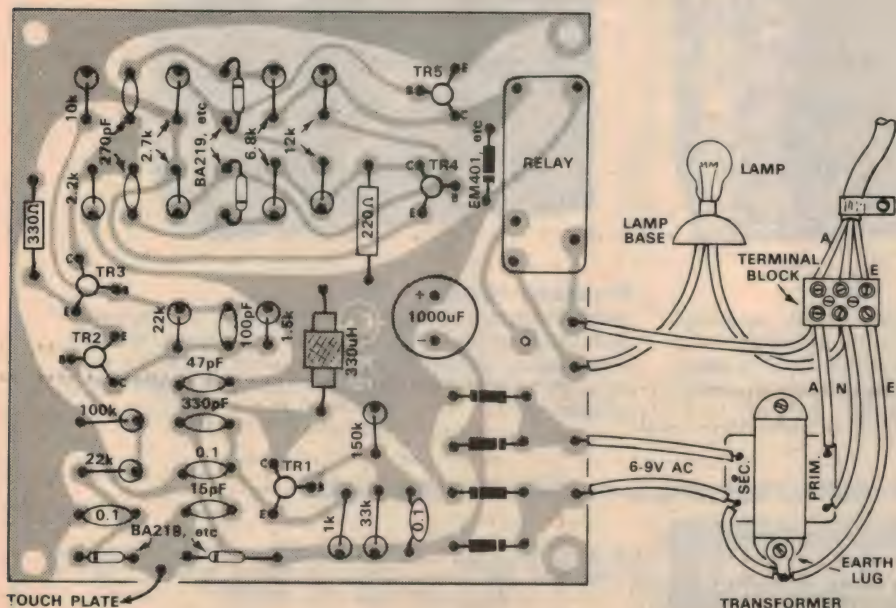This hole mates with the one mentioned previously, that drilled through the centre of the wooden cylinder to assist turning. The incoming mains cord passes through both these holes, first the horizontal and then up through the vertical one to the "works".






# What do you look for in a multimeter?

- ☐ 1M $\Omega$  (7pF) input impedance of AC voltmeter?
  - ☐ 2 $\mu$ A full-scale taut-band meter movement?
  - ☐ 30-position range selector switch?
  - ☐ Double protection against damage?
  - ☐ Wide application of current and resistance ranges?
  - ☐ Protective side boards?
- (N501)
- ☐ Negligible measurement loss?
  - ☐ Double protection of the movement?
  - ☐ Polarity conversion switch?
  - ☐ Current ranges of 1.2A and 12A?
  - ☐ Detachable indicator?
  - ☐ HF current blocked?
- (460-ED)

## sanwa has it all!

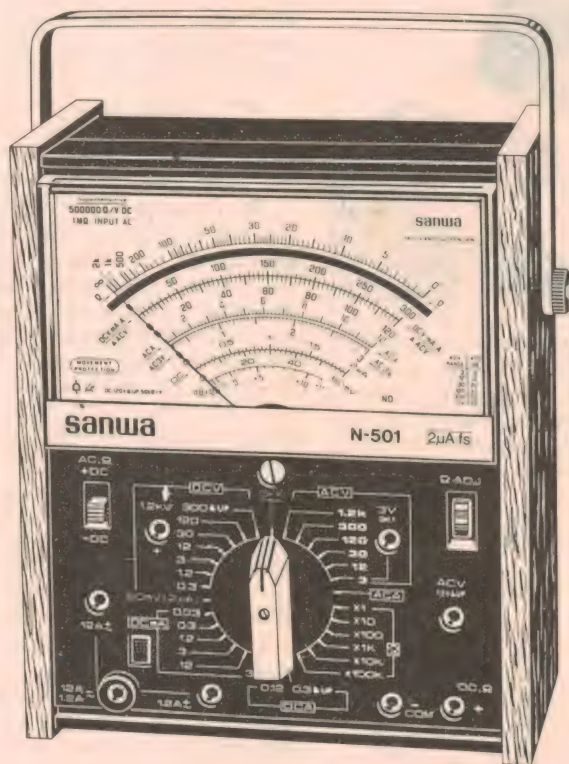

### Multimeter N-501

The N-501 is unprecedented for its ultrahigh sensitivity equivalent to a v.t.v.m. with no vacuum tube or FET used. It has been accomplished by the development of a meter movement of full-scale sensitivity of 2 $\mu$ A and thorough pursuit of the rectifying circuit of the instrument.



### Multimeter 460-ED

100,000 ohms per volt with  $\pm 2\%$  accuracy for DC ranges with only 10 microamperes loss at full scale. H.F. current blocking when making DC measurements. Polarity switch. 12 amps AC AND 12 amps DC ranges. Mirrored scale. 30KV probe available.

For further information please ring any of the following numbers:—



## WARBURTON FRANKI

ADELAIDE 356-7333 • BRISBANE 52-7255 • HOBART 23-1841  
MELBOURNE 69-0151 • PERTH 65-7000 • SYDNEY 648-1711  
• WELLINGTON N.Z. 698-272



The transformer and mains wiring can now be attended to. A 3 section mains terminal block holds the incoming mains wires and inter-connections to the transformer—refer to the wiring diagram for full details. A small mains cord clamp holds the lead itself.

The mains earth lead goes to the transformer case and also to one side of the transformer secondary. This is to try to cut down as much hum induction as possible.

Incidentally, some readers may wonder about the latitude allowed in the choice of transformer. On the circuit, we have specified a 6-9V secondary. The reason is that the circuit itself will happily work on supplies from around 6 to 18 or so. The relay, however, needs 8-12V DC to work correctly—and a transformer whose rectified voltage falls within these limits is quite satisfactory.

As it happens, the two transformers recommended are both centre tapped types. The 2851 is a 12.6V CT (in which case only half the secondary is used) while the 2840 is a 9V CT (ignore the CT on this one).

Remember when wiring the mains section that you are dealing with a device which people touch—your wiring must be exemplary. With correct wiring, this device is quite safe. But if you boo-boo...

The wiring of the light socket is best left until last—both for safety reasons and because the leads should be cut as short as possible for hum induction reasons—and this is not possible until both plugs are in position. The checking operations to be described can be carried out by listening to relay operation—either a single click for correct operation or “chatter” or no sound for incorrect operation.

Now comes the curly part—matching the switch to the cylinder! Perhaps a word of explanation is in order. Remember how the switch works—capacitor action dividing the voltage when the plate was touched. Unfortunately, this is exactly what the cylinder is—a “body” attached to the touch plate. In fact, this can cause the switch to lock on or off, as it sees a load on its touch plate at all times.

For this reason, a small amount of juggling of the coupling capacitor might be necessary. We found that the value shown, 15pF, was exactly right for our tube—but it may not be right for other lengths of tube. So it must be checked, and the easiest way to do this is to lower the tube onto the base just far enough to contact the tinplate strip, and see if it works when you touch it. If it doesn't work at all, or breaks into “chatter”, the value has to change. Go up if it chatters, down if it doesn't work at all.

As a guess, the outside limits would be about 10pF to 25pF. The lower you go, the more sensitive it becomes, but also is more sensitive to hum fields—hence the chatter. And vice-versa, of course. Even with the optimum value of capacitor in our version (chosen by trial and error) we were still able to make the thing chatter by cheating. If the whole flat of the hand was brought in close to the cylinder and held there, the relay would chatter—but this is not the correct way of using it, so we weren't too concerned. A single touch is all that is necessary.

By the way, if you are not planning on making the touch switch in the lamp-shade form but wish to use it for some other purpose, it may interest you to know that the lower you make the capacitor the more like a true “proximity

# Know Where You are Going

Choose a career in the field of Electronics — the Nation's most progressive and fastest expanding industry.

Advancement in this modern science demands technical ability, a sound knowledge of basic principles and applications. You can master the subject by training at the Marconi School, and be ready to grasp the opportunities that occur in the various branches of Radio Technology.

## BROADCASTING

A thorough grounding is available to students in the broadcasting field, leading up to the P.M.G. Broadcast Station Examination.

## COMMUNICATIONS (Marine)

An extension to the Broadcast Operators course and extending into the fields of Navigation Aids and Electronic Devices used in mobile communications as required by the P.M.G. Certificates of Proficiency.

## APPLIED SERVICING

Comprehensive training in the maintenance and repair of radio and television receivers offers substantial rewards to competent technicians. Marconi School training covers all aspects of radio and television receiver circuit applications, practical exercises in fault finding and alignment procedures.

The Marconi School Radio Servicing correspondence course is approved by the N.S.W. Apprenticeship Commission

Classes are conducted at:

67 Lords Road, Leichhardt.

Day: 9 a.m. to 4 p.m.

Evenings: 6 p.m. to 8.30 p.m. or by Home-Study Courses (except practical instruction on equipment).

## SEND FOR PROSPECTUS

There is no obligation

NAME.....

ADDRESS.....

**MARCONI SCHOOL OF WIRELESS**  
Box 218, P.O., Leichhardt 2040  
A service of  
Amalgamated Wireless (Australasia) Ltd.

## ALL THE PARTS YOU WILL NEED . . .

1 printed circuit board, 77 x 77mm, code 76/s3

5 small signal NPN transistors (BC108, BC548 or similar)

4 small signal diodes, (BA219 or similar)

5 1A power diodes (EM401, OA626 or similar)

RESISTORS (¼ or ½W 5% except where shown)

1 x 220ohm 1W, 1 x 330ohm, 1 x 1k, 1 x 1.5k, 1 x 2.2k, 2 x 2.7k, 2 x 6.8k, 1 x 10k, 2 x 12k, 2 x 22k, 1 x 33k, 1 x 100k, 1 x 150k

CAPACITORS (LV, Ceramic or poly)

1 x 15pF, 1 x 47pF, 1 x 100pF, 2 x 270pF, 1 x 330pF, 3 x 0.1uF, 1 x 1000uF 12VW PC electro.

1 x SP C/O relay, PCB mounting, coil approx. 250 ohms

1 x 330uH (approx.) RF choke

1 x power transformer, sec. 6-9V at 100mA (+), miniature type, PF2851, M2840, etc.

## ADDITIONAL PARTS REQUIRED FOR LAMP

1 x 100mm dia. aluminium tube, 200mm long

2 x wooden discs, approx. 25mm thick x 100mm dia. (see text)

1 x bc lamp batten holder, HPM 366P, Ring Grip BH1 or equivalent

1 x shade to suit base.

## MISCELLANEOUS

Mains cord (3-wire, ANE) and plug, mains cord clamp, figure 8 lead (for internal mains wiring) 3-way mains terminal block, solder lugs, tinplate scrap, wood screws (8 in all, 3 with csk heads), solder, etc.

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with higher ratings may generally be used, providing they are physically compatible. Components with lower ratings may also be used in some cases, providing the ratings are not exceeded.



# WOULD YOU SPEND AN HOUR A DAY TO EARN MORE MONEY?

A better job. A bigger pay packet. And the satisfaction of doing your job well. A big reward for only an hour a day. Because if you spend that hour studying with an ICS program, you will be making a big step towards achieving your ambitions.

**Learning with ICS is simple, satisfying and rewarding.** The ICS method of teaching, and the knowledge and skill you rapidly acquire, will give you greater confidence in your work, and your ability to progress.

**Keep your present job while you learn.**

You don't lose a day's pay while you learn. And because you decide when you study, and where you study, you



don't lose valuable time travelling to and from classrooms, and you can't miss any of the tuition program.

**Thousands have done it — you can too!**

Since it started, ICS has helped nearly nine million people in their study needs. Check through the list of programs on this page. Find the career that suits what you want for your future.

**International Correspondence Schools**  
400 Pacific Highway, Crows Nest, NSW 2065  
Telephone: 432121  
New Zealand: 182 Wakefield Street, Wellington

**Accountancy**  
Inst. Chartered Secretaries & Administrators — A.C.I.S. Degree  
Commercial Education Society of Australia — Diploma in Accounting  
Modern Bookkeeping  
Bookkeeping and Office Practice — C.E.S.  
Certificate  
Costing  
Elementary Bookkeeping

**Art**  
Commercial Art  
Recreational Art  
Water Colour and Oil Painting  
Cartooning  
Showcard and Sign Production  
Basic Art for Everyone  
Water Colour Painting  
Oil Painting  
Showcard and Ticketwriting  
Sign Painting and Designing  
Advertising Layout and Illustration

**Motor Mechanic**  
Motor Mechanic  
Institute of Automotive Mechanical Engineers — General Craftman & Associate Member  
Queensland "A" Grade Motor Mechanic  
Queensland "B" Grade Motor Mechanic  
Victorian Automobile Chamber of Commerce — Senior Motor Mechanic or "A" Grade Certificate  
Basic Motor Engineering  
Automatic Transmission Specialist  
Automobile Engine Tune-Up  
Automobile Electrician  
Driver's Maintenance  
Panel Beating and Spray Painting  
High Speed Diesel Engines

**Building and Architecture**  
Building Contractor  
Building Sciences  
Quantity Surveyor  
Building Supervisor  
Clerk of Works  
Architectural Assistant

**Carpentry and Joinery**  
Builders Draftsmen and Plan Drawing  
Basic Building  
Carpentry  
Bicklaying  
Plumbing

**Modern Management**  
Inst. of Business Administration — Associate Degree  
Commercial Education Soc. of Aust. — Diploma in Management  
Industrial Management  
Works Management  
Office Management  
Personnel Management  
Small Business Owners  
Modern Marketing Management  
Modern Supervision  
Stores Supervision  
Purchasing and Supply Management  
Club Management  
Modern Management

**Computer Programming**  
Complete Programming and Data Processing  
Electronics Computer Servicing Specialist  
General Computer Programming  
Cobol Programming  
Computer System Analysis

**Sales and Marketing**  
Institute of Sales and Marketing Associate Membership  
Advertising Institute of Australia — Complete Program  
Public Relations  
Modern Marketing Management  
Sales Management  
Retail Departmental Management  
Company Representative  
Copy Writing  
Advertising Layout and Illustration

**Secretarial**  
Typewriting  
Stenography  
Clerk-Typist  
Gregg Shorthand with Speed Building  
Gregg Speed Building  
Pitman's Shorthand

**Colour TV Service Technician**  
TV Service Technician  
Television Principles  
Television Engineering  
Television Servicing

**Writing**  
All Media Professional Writing  
Professional Writing  
Short Story Writing  
Freelance Journalism  
Script Writing  
Technical Writing  
Typewriting

**Drafting**  
Drafting  
Mechanical Drawing and Tool Design  
Electrical and Electronic Drafting  
Structural and Architectural Drafting  
Drafting for Air Conditioning  
Builders Draftsmen and Plan Drawing

**Electronics**  
Electronics Technician  
Communications  
Broadcasting Specialist  
Industrial Electronics Specialist  
Electronics Computer Servicing Specialist  
Audio, Radio, Hi-Fi, Sound Systems Specialist  
Basic Electronics  
Electronic Instrumentation and Control Systems  
Electronic Technology  
Electronic Maintenance  
Radio and Electronic Telemetry  
Electric Motor Repair and Servicing

**Mechanical Engineering**  
Mechanical Engineering Technology  
Works Management  
Hydraulic and Pneumatic Power  
Boiler Inspector  
Boiler Attendant

**Civil and Structural Engineering**  
Civil Engineering  
Surveying and Mapping  
Structural and Concrete Engineering  
Structural Engineering  
Overseer of Works


**Electrical Engineering**  
Electrical Engineering  
Electric Motor Repair and Servicing  
Industrial Electrician  
Electrical Mechanic

**Hotel/Motel Management**  
Hotel/Motel Management  
Club Management  
Financial Management for Hotels and Motels  
Hotel/Motel Owner

**Air Conditioning and Refrigeration**  
Heating, Ventilation, Air Conditioning, Refrigeration Technology  
Air Conditioning and Refrigeration Technology  
Commercial and Domestic Refrigeration and Air Conditioning  
Servicing  
Domestic Appliance and Refrigeration Servicing  
Air Conditioning Technology

*This list is correct at the time of submission for publication, and may vary.*

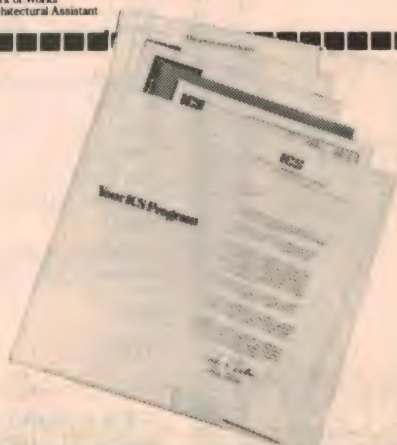**Mail the coupon today** and you will receive a career guidance kit, without cost or obligation, that will tell you how the ICS study method works, and what the particular course teaches you.



**International Correspondence Schools**  
400 Pacific Highway, Crows Nest, NSW 2065. Telephone: 432121  
New Zealand: 182 Wakefield Street, Wellington

Please provide me with Career information on

NAME

ADDRESS

POSTCODE

OCCUPATION

AGE

15/01/24/OA

**ICS**




detector" it becomes. In fact, with a value of 1pF and a small touch plate, it will actuate from at least 20 mm away and more. But this only holds where the mains hum field can be kept away.

Once you are sure the switch is working correctly, pull the base out of the tube and connect the "lamp" leads to the terminal block and PCB. Note the relay is in the active side of the line, following normal mains wiring practice.

Now we are almost ready for final assembly. First of all, a keyway has to be cut in the tube for the mains cord. This can be done with a 6 mm drill, drilled about 10 mm from the bottom of the tube. Open it out to a slot with a file, taking care not to mar the appearance.

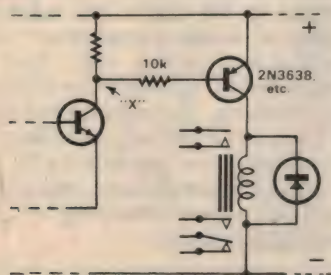The three holes to hold the top plug can also be drilled. Divide the circle into three (remember the "flower" pattern you used to draw at school with a compass—this accurately divides a circle into 6—and so 3), and drill the holes to suit the size of screw you are using. The best type is a countersunk head, nickel plated, around one inch long and a fairly small gauge.



This one transistor relay driver may be substituted for the flip-flop for "on when touched" operation. Extra relay contacts could be used to latch on. Point "X" corresponds to point "X" on the main circuit diagram, immediately after TR3.

The holes can be drilled about 10mm down from the top of the plug. While you're about it, drill a pilot hole to match the holes in the aluminium—this will assist in final assembly. Remember to use a smaller drill, though! Remove the plug, and countersink the holes as necessary.

Now is the time to place the bottom plug in position. Carefully line up the mains cord keyway and the mains cord emerging from the base, and push the base hard down into the tube. If it is a proper fit, you won't get very far before you have to use a hammer and block of wood to keep it going. Don't belt the base too hard, take it in small "bites" working around the circle. Stop when the base is just proud (1-2mm) of the aluminium. This allows the lamp to rest on wood, rather than on aluminium.

The light fixture can now be screwed to the plug top. If you examine the fixture itself, you will note that the socket can be removed from the base by pushing it out from the front. It can be replaced from the front by turning it so the catches on the socket can pass through the slots

in the base. A turn of a few degrees will then place the catches behind their counterpart on the base and the ring can then be screwed on to make it captive.

Separate the two halves of the socket, and screw the base into the middle of the top plug. Make sure you are exact here, as any error will appear amplified when you place a shade on. With the socket firmly on the wood, pull the lamp leads up through the tube and through the hole in the plug. Now push the plug down into the tube so it is 20mm or so down from the top.

Pull the lamp leads fairly tight, and cut them off so there is approx. 20mm protruding from the tube. Bare them back 5mm, and screw them into their positions on the socket. A normal socket has three holes—use the two outside ones. Now pull the top plug back up, and loosely fasten it in place with the woodscrews.

Push the socket into position on its base (as just described) noting how much slack there is in the leads. If there is too much, and the leads go too close to the tube, hum troubles may result, as we found. Ideally, the mains leads should pass directly up the centre of the tube. If there is too much slack, repeat the last couple of steps until there is as little slack as you can handle. Then screw the ring onto the socket to tighten it up.

If the ring keeps turning and the socket comes out of its base, you haven't turned the socket so the catches engage.

Release the ring and turn the socket around slightly—then re-tighten. Last of all, do up the screws on the side and the lamp is finished.

As a final check, place an ohm-meter (1) across the lamp socket terminals; (2) between each of the terminals and the barrel of the lamp; (3) between each of the mains plug pins and the barrel of the lamp. If there is a reading between any of these, something is wrong and should be checked before use.

The lampshade is left up to the individual. They may be bought quite readily, or may be made from parts obtained at specialist shops. Either way, choose one which is not too small—it will look odd because of the "chunkiness" of the base—nor one too large, which may promote instability even though the base is quite heavy.

Lamp wattage is as suited to the shade bought—the relay has a 5 amp (1200W) rating, so there are no problems there.

And that's about all there is to it. Remember the touch switch applications are limited only by your imagination and the relay rating!

By the way, if you want something to keep a toddler amused for hours, show them how to use the touch lamp—just once. My one year old thinks she's the ant's pants: on off on off on off ...

The only trouble is, the perplexed look when she touches a similar looking conventional lamp and it doesn't work! 2

## chronostop

lic. OMEGA

**H**IGHLY accurate electronic stopwatch designed for laboratory, industrial and sports timing.

**T**HE display of minutes, seconds, 1/10's and 1/100's of seconds is easy to read even in sunlight.

**F**OUR timing modes allow one button control, solves difficult timing problems and leaves one hand free for note taking. The instrument carries a 12 month guarantee.

**\$185** Plus Sales Tax.



**AUSTRALIAN TIME EQUIPMENT PTY LTD**  
192 Princes Highway, Arncliffe, N.S.W. 2205  
Phone: 59 0291



# Crystal-locked converter for the LF and VLF bands

Discover for yourself the mysteries of the normally inaccessible low and very-low frequency radio bands, with this easy to build solid state converter. Battery powered and low in cost, it will operate with almost any conventional short wave receiver.

by IAN POGSON

Have you ever wondered what signals there are in the frequency range below the broadcast band? Most of us have just a vague idea that there is a maritime distress frequency on 500kHz, together with the standard receiver intermediate frequency on 455kHz. Apart from that who knows?

The real old timers know that in the early days of radio, most of the activity was on the low frequencies, having wavelengths in thousands of metres. This is true, but what of the present time? The best way to find out is actually to have a listen for yourself. To this end, a converter is required and we have developed a fairly simple one which may be connected ahead of any suitable short wave receiver.

In developing a converter for low and very-low frequencies we adopted the philosophy that it should be as simple as possible, but capable of doing the job reasonably well. It should also be possible to feed it into a wide variety of receivers capable of tuning at least part of the short wave bands.

The basic converter consists essentially of an untuned RF amplifier with a ring mixer and a crystal oscillator. We chose a crystal on 7.5MHz and this is fed into the mixer. Signals below say 500kHz will be amplified and these are also fed into the mixer where they are mixed with the crystal frequency resulting in sum and difference frequencies. These will appear as "sidebands" on each side of 7.5MHz.

By feeding the output of the converter into a receiver capable of tuning to 7.5MHz and either 500kHz above or below, then a received signal on say 200kHz may be tuned in at either 7.3MHz or 7.7MHz, and so on.


From this it may be seen that it is possible for the converter to bring in signals down to very low frequencies indeed, limited only by the selectivity of the main receiver, which will be required to separate the wanted signal from the crystal signal which will appear right on 7.5MHz. For this reason we have used the double balanced ring mixer.

This mixer is theoretically balanced but

due to characteristics of components, this is not normally achieved in practice with the basic circuit. A much better balance can be achieved by adding an adjustable potentiometer and a capacitor, which we have done. By these means, it is possible to reduce very considerably the strength of the crystal as tuned in on the receiver, and this allows us to tune even lower frequencies.

As the input to the RF amplifier is not tuned and in order to avoid strong local broadcast stations from causing unwanted interference and worse, there is a low pass filter between the aerial input and the base of the RF amplifier. This filter substantially reduces the

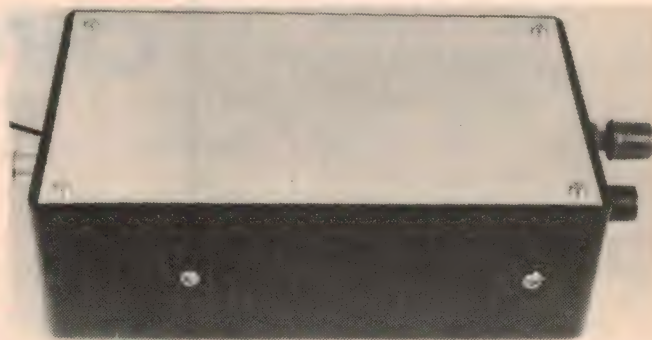*The completed prototype. Output is via a coax socket mounted on one end, with the aerial and earth terminals at the other end.*



ingress of any signals above 500kHz, and this also sets the upper limit to which the converter can be used.

At this point I should mention that although I have used a crystal on 7.5MHz, this is not mandatory and crystals over quite a wide range may be used. The oscillator circuit will accommodate crystals between about 2MHz and 12MHz or so. When selecting a crystal it is well to keep in mind that it is easier to use one which is on an integral number of MHz, with the next best one on a multiple of 100kHz. This makes it easier to determine from the main receiver dial calibrations as to the actual frequency of the signal being received. If you use a very "odd" crystal frequency, you will be involved in a mental calculation every time you want to work out the frequency of the LF signal.

A look at the circuit diagram will show how all this has been done. Immediately following the aerial terminal is a low pass filter consisting of a 2.5mH RF choke and a .0018uF capacitor. A link is shown immediately following and more will be said about this later on. A BC548 transistor is shown as a conventional amplifier with a multiple collector load consisting of a 2.5mH RF choke and a 4.7k resistor. This stage is followed by an emitter follower to transform from a relatively high impedance to a low impedance into the ring mixer which follows.


As the input of the mixer has to handle frequencies which are for all practical purposes in the audio and supersonic ranges, an audio transformer with a laminated iron core is used. Four germanium diodes, type OA91 or similar are used for mixing. The output transformer, which has to handle only high frequency components is one wound on a TV balun core. A 2.2k potentiometer and a 6-60pF trimmer are added to the mixer circuit for balancing purposes.

Another BC548 transistor is used in a simple Pierce crystal oscillator circuit. The oscillator output is fed into the centre tap of the mixer input transformer. The oscillator circuit should function satisfactorily over a wide frequency range without change in circuit constants.

Output from the converter is taken from the secondary of the output transformer of the mixer and this is fed into the aerial terminal of the short wave receiver.

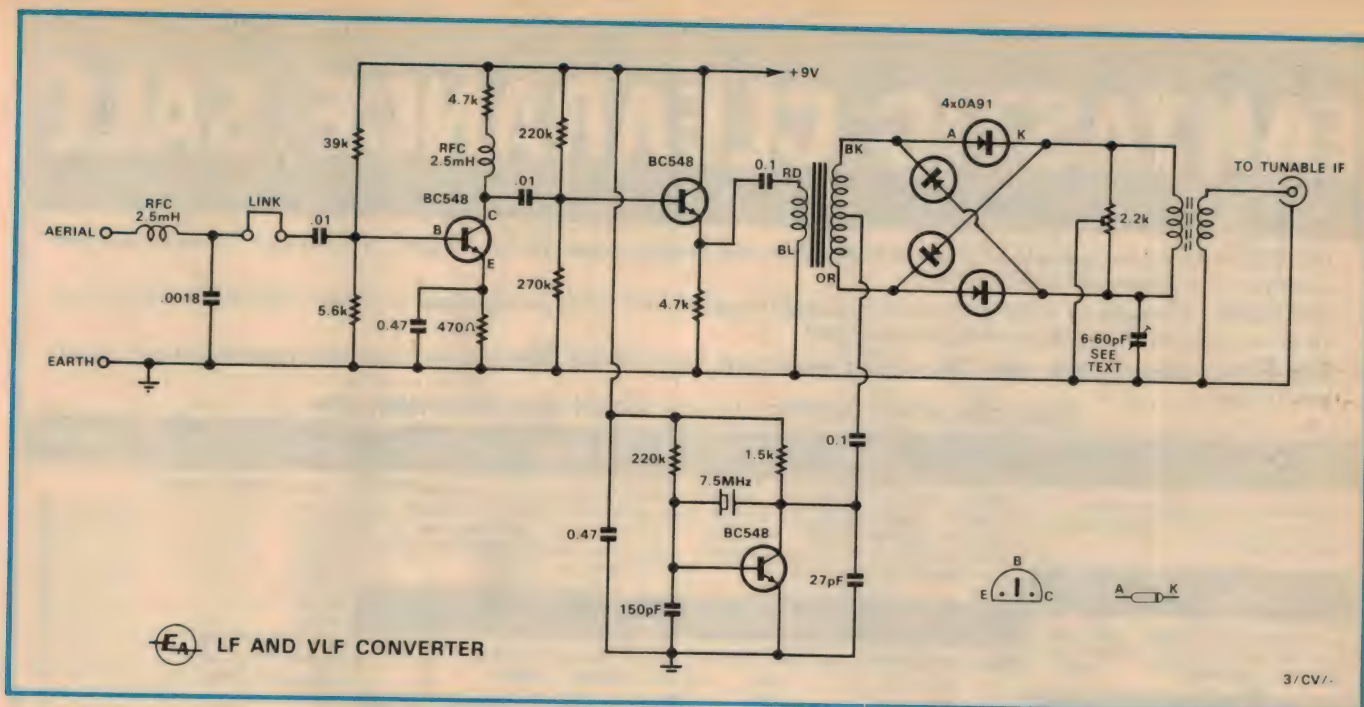Obtaining components for the converter should not present any problems but a few comments about some of the items may be helpful. The converter is built into a moulded plastic box with an aluminium lid. The box measures 150mm x 90mm x 50mm and is designated UB1, being available through Dick Smith Elec-





tronics Pty Ltd, either directly or through your local supplier. The iron cored transformer is type TRD223 and is made by Ferguson Transformers; it too should be obtainable through your local supplier.

The crystal is an item which is left very largely to the discretion of the builder. It may be possible to salvage one from your junk box or alternatively to get one from disposals sources. The old type in the FT234 holder is suitable provided that the frequency available meets your requirements. On the other hand, there are manufacturers such as Bright Star Crystals who will grind one to the frequency of your choice. We suggest that it be ordered by quoting the frequency required, HC-6/U, 30pF, ambient temperature and tolerance .003%.

The transistors may be the new BC548, or they may be the older BC108, or the cheaper "gold-top" package type BC208, or equivalents of these types. The diodes may be the type specified or almost any germanium type would be satisfactory. All of the other components should present no problems.

As mentioned before, we built our converter into a moulded box but this is not critical and if you have access to another box which will accommodate the components, then this could be used. Also, as the device is so simple and to keep costs down, we have not used a PCB. Most of the components have been mounted on miniature tag wiring board instead.

As may be seen from the photograph, we used two boards, each with 16 pairs of tags, to mount the components. One board was used for the RF amplifier, including the input low pass filter and emitter follower. The other board accommodates the crystal oscillator and ring mixer. It may be noted that we did

not use all of the tags available and if you wish, there is no reason why you should not use shorter boards.

We have provided wiring diagrams for the two boards and this should make the job of wiring quite easy. The general layout is not very critical and you may use your own layout and method of wiring, provided that you do it so as not to run

into any instability troubles. It will be necessary to wind the mixer output transformer before it can be fitted to its board. To wind the transformer, take two lengths of 28B&S enamel wire and twist them together to a pitch of about 6mm. Wind ten turns, each turn consisting of a pass through each hole in the transformer core. The finished transformer

## For fine detail work — a hands free magnifier



The **Magna-Sighter** is a precision 3-D binocular magnifier that leaves your hands completely free for work. It has hundreds of applications, and is invaluable for scientists, technicians, craftsmen, toolmakers, hobbyists, etc. Slips easily over the head—over glasses, too. Proved and used by many U.S. universities, space research bureaux, government departments and major industrial organisations. Available in 3 different magnifications. Price \$21.00

STC 846

## MAGNA-SIGHTER

For further information send this coupon today:

STOTT TECHNICAL SERVICES

(Division of Stott's)

Technical Correspondence College Pty. Ltd.)

159 Flinders Lane, Melbourne, Vic., 3000

Please send me full information on the 3-D Magna-Sighter. I understand that no Sales Representative will call.

Name.....

Address.....

Postcode.....



# FANTASTIC CLEARANCE SALE

**BC108**—metal can, gold plated, marked, guaranteed, new, no substitute—10 for \$1 (limit of 10 to each customer). Limited quantity at this price so get yours now!!!

**2N3055-1**—made by S.T.C. silicon N.P.N. power transistors TO3 metal package (marked, new)—10 for \$6.50 (limit of 10 to each customer). Get these now before they go!!!

**EM404**—silicon rectifier 400V, 1A, marked, guaranteed, new—10 for 90c (limit of 10 to each customer). Hurry, these won't last!!!

10% DISCOUNT FOR ORDERS OVER \$20. MONEY BACK IF NOT SATISFIED!

POLYESTER PACK	2N301	HA1322	TRANSISTORS AND DIODES
SUPER PACK OF POLYESTER CAPS ALL 10% INCL. 160V, 270V, 400V TYPES — 100 FOR \$3.50.	2N301 (NEW, GUARANTEED). AUDIO OUTPUT GEWRMANIUM TRANSISTOR ACTUALLY MARKED 2N301/2836 BUT SUPERIOR IN QUALITY. SUPER BARGAIN AT \$1.50 EA. OR 10 FOR \$12.	AUDIO POWER AMP. I.C. HA1322 (NEW, GUARANTEED) 5.5 WATTS PEAK. SUPPLY VOLT 13V, INPUT IMP. 36KOHM INCL. CIRCUIT DIAGRAM. FANTASTIC VALUE AT \$2.25 EA. OR 4 FOR \$8.	LOOK AT THESE PRICES!!! BC548..... 10 FOR \$1.80 BC328..... 10 FOR \$1.80 BC338..... 10 FOR \$1.80 AS148..... 10 FOR \$1.80 AS149..... 10 FOR \$1.80 AS320..... 10 FOR \$1.80 AS322..... 10 FOR \$1.80 BC557 (BC177, BC157) .. 10 FOR \$1.70 BC558 (BC178, BC158) .. 10 FOR \$1.70 BC559 (BC179, BC159) .. 10 FOR \$1.70 EM402..... 10 FOR \$1.00 1N5059 GLASS RECTIFIER 10 FOR \$1.00 1S188 (OA90)..... 10 FOR .80 2N1637..... 10 FOR \$2.00 2N1110 (OC45)..... 10 FOR \$2.00 XA101 (OC45)..... 10 FOR \$2.00
CERAMIC CAP. PACK	DIGITAL T.T.L. I.C.'s	PA234	
SUPER PACK OF CERAMIC CAPS INCL. LOW AND HIGH VOLT. TYPES. TOP QUALITY — 50 FOR \$1.	NEW, GUARANTEED. LOW, LOW PRICES! 7400.....35c 7401.....35c 7402.....35c 7404.....35c 7408.....35c 7410.....35c 7413.....80c 7420.....35c 7430.....35c 7440.....35c 7441.....\$1.20 7442.....\$1.00 7447.....\$1.50 7473.....90c 7474.....90c 7475.....\$1.00	PA234 1W R.M.S. AUDIO AMP. I.C. INCL. CCT DIAGRAM — 95c EA.	
ELECTROLYTIC PACK		ELECTROLYTICS	
SUPER PACK OF ELECTROLYTICS. TOP QUALITY PIGTAILS. LOW AND HIGH VOLT. — 25 FOR \$2.50.		TOP QUALITY PIGTAILS AT BARGAIN PRICES 2500uf/25v (ELNA)..... 5 FOR \$3.50 1000uf/25v..... 6 FOR \$2.50 1000uf/18v..... 10 FOR \$3.50 32uf/300v..... 6 FOR \$2.50 25uf/300v..... 10 FOR \$2.50 16uf/300v..... 10 FOR \$2.00 2uf/300v..... 10 FOR \$1.50 40uf/200v..... 6 FOR \$2.00 6.4uf/25v..... 10 FOR \$1.00	
RESISTOR PACK			COPPER CLAD BOARD
SUPER PACK OF RESISTORS. MOSTLY 1/2 WATT, 1 WATT. 5% AND 10% RESISTORS. NO SHORT LEAD RUBBISH — 100 FOR \$1.25.			REAL VALUE — 6" x 3"..... 4 FOR \$1. 9" x 12"..... \$1.75 EA.

## DISCOUNTS FOR VOLUME BUYERS

IDEAL FOR ALL RADIO CLUBS, SERVICEMEN AND GROUP BUYERS ETC., ETC.

STYROSEAL CAPACITORS	TRANSISORS & DIODES (BULK PRICES)	POLYESTER GREENCAPS (100V)
680pf/1000v..... 200 FOR \$14 100pf/125v..... 200 FOR \$ 6 680pf/630v..... 100 FOR \$ 4 680pf/125v..... 100 FOR \$ 3 270pf/125v..... 200 FOR \$ 6 220pf/125v..... 100 FOR \$ 3	BC338..... 100 FOR \$14 BC557..... 100 FOR \$14 BC558..... 100 FOR \$14 BC559..... 100 FOR \$14 AS148..... 200 FOR \$22 AS149..... 200 FOR \$22 AS320..... 200 FOR \$22 AS322..... 200 FOR \$22 IS188 (OA90)..... 200 FOR \$12 XA101 (OC45)..... 100 FOR \$10 2N1110 (OC45)..... 100 FOR \$10 PA234 1W R.M.S. AUDIO AMP I.C. INCL. CCT DIAGRAM..... 25 FOR \$20	001uf/100v..... 100 FOR \$3.50 01uf/100v..... 100 FOR \$3.80
ELECTROLYTICS	MINIATURE TUNING CONDENSERS	TANTALUMS (Miniature Type)
TOP QUALITY PIGTAILS 1000uf/25v..... 25 FOR \$10 OR 100 FOR \$30 2500uf/25v..... 25 FOR \$16 32uf/300v..... 25 FOR \$12 2uf/300v..... 100 FOR \$11	(INCLUDES INBUILT TRIMMERS) 25 FOR \$10.	4uf/6v..... 100 FOR \$4.00 5uf/3v..... 100 FOR \$3.50 5uf/10v..... 100 FOR \$4.50 7uf/3v..... 100 FOR \$3.50 4uf/10v..... 100 FOR \$4.50
		SUPER BARGAIN PACKS
		POLYESTERS (100 PER PACK)..... 10 PACKS FOR \$30 RESISTORS (100 PER PACK)..... 25 PACKS FOR \$25 CERAMICS (50 PER PACK)..... 25 PACKS FOR \$20

Discounts on all orders: over \$20 — 10%  
over \$100 — 12%  
over \$200 — 15%

Basic post and pack 60 cents. Please assist by including extra postage for heavier parcels. Take advantage of these rockbottom prices as supplies are already limited. STOCK UP NOW!!! DON'T DELAY!!! POST YOUR ORDER TODAY!!!

POST AND PACK 60c OR EXTRA FOR HEAVY PACKAGES

# MICRONICS

P.O. BOX 175, RANDWICK, N.S.W. 2031



## Crystal-locked converter



The input to the RF amplifier can be tuned by means of loopstick aerial and a variable capacitor. Details are given in the text.

may be glued to the board during the wiring process.

Having wired the boards, it may be a good idea to wire them and the iron cored transformer together temporarily to make sure that they do work before fixing them permanently into the box.


To do this, you will need a battery or other power supply capable of delivering 9V at a few milliamps, a suitable LF aerial, and a receiver capable of being tuned to the crystal frequency and up to 500kHz above or below it.

The aerial may be a random piece of wire about 15m long and preferably outside and elevated, but more will be said about possible aerials later on. When connecting the output of the converter to the receiver it should preferably be done via a short length of coaxial cable. For the time being, set the mixer balancing pot and capacitor to mid position. With all made ready, carefully tune the main receiver for signals. You will be most likely at this stage to be more successful by tuning between 200kHz and 400kHz away from the crystal frequency. Within the range between the frequencies just quoted there are a number of aircraft beacons which are usually identified by a Morse code signal.

Later on I will give a list of stations which I have logged on this converter in

the Sydney area. Meanwhile, assuming that you have received one or more of these signals, you are now in a position to fit the converter into its case and make final adjustments.

As may be seen from the photograph, we have fitted a board to each side of the box, with the iron cored transformer screwed to the bottom of the case and mounted close to the rest of the mixer. A coax socket is mounted at one end to take the output lead and two terminals are mounted at the other end, one each for the aerial and an earth if required. We ran an earth lead from a solder lug on the coax socket to each of the boards. Two leads for the 9V supply are connected to the board near the crystal

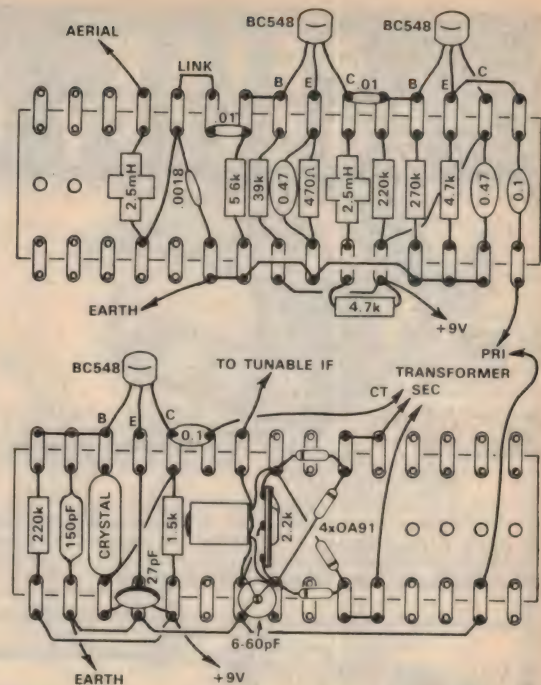

oscillator and are run through a hole drilled in the end of the box near the coax socket. These two leads are also extended from the board across to the other one and near to the input of the RF stage. From nearby an aerial and earth lead are each run to the respective terminals at the end of the case.

With all the wiring completed, the converter is again connected to the receiver and the receiver is tuned to the crystal frequency. If you have a signal strength meter on the receiver, it will no doubt be reading full scale and the meter will help considerably in balancing the mixer. If you do not have a meter, then you can try to adjust the balancing controls, or just leave them set as before.

The process of adjusting a ring mixer for balance is generally quite an exacting procedure and it must be undertaken with considerable care. Try rotating the pot first, either for a sign of a fall in the meter reading or a rise in noise from the loudspeaker. Set the pot precisely for either of these indications. Now try slowly adjusting the trimmer capacitor for a similar effect. If you can rotate the trimmer throughout its range without making much difference to the balance, then the trimmer is on the wrong side of the mixer. The best thing to do is to reverse the connections from each transformer, the secondary of the input transformer and the primary of the output transformer.

Now continue the process of adjusting the capacitor for minimum meter reading or maximum noise and then try the pot again. Repeat these adjustments until you have the minimum possible meter reading or maximum noise. You will find that the procedure is most exacting and it can drive you "up the wall" if you try to get the ultimate from it. Generally, all

### LIST OF COMPONENT PARTS


- |  |  |
|--|--|
| 1 Utility case, 150mm x 90mm x 50mm, type UB1 (Dick Smith)           | 2 .01uF low voltage greencap   |
| 1 Transformer, Ferguson type TRD223 or similar                       | 2 0.1uF low voltage greencap   |
| 1 Balun core, Neosid type 1050/1/F14                                 | 2 0.47uF low voltage greencap  |
| 1 Crystal, selected frequency, HC-6/U, 30pF, ambient temp, tol .003% | Resistors (½W or ¼W unless stated otherwise)   |
| 1 Socket for crystal   | 1 470 ohms   |
| 2 2.5mH RF chokes  | 1 5.6k   |
| 2 Terminals, 1-red 1-black   | 1 1.5k   |
| 1 Coaxial socket   | 1 2.2k trimpot   |
| 4 Diodes, OA91 or similar  | 2 220k   |
| 3 Transistors, BC548, BC108, BC208 or similar                        | 2 4.7k   |
| 2 Miniature tag boards with 16 prs tags                              |  |
| Capacitors   | Sundries   |
| 1 27pF NPO ceramic   | Screws, Nuts, hookup wire, solder lugs   |
| 1 6-60pF Philips trimmer   | Note: Resistor wattage ratings and capacitor voltage ratings are those used on the prototype. Components with higher ratings may generally be used, providing they are physically compatible. Components with lower ratings may also be used in some cases if available, providing ratings are not exceeded. |
| 1 150pF 630V polystyrene   |  |
| 1 .0018uF low voltage greencap                                       |  |



# PETER SHALLEY


554 PACIFIC HWY.  
KILLARA NSW 2071

TEL:  
498 2611

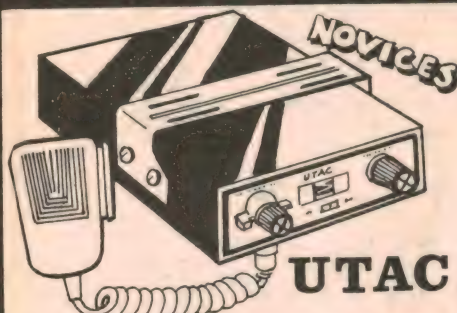

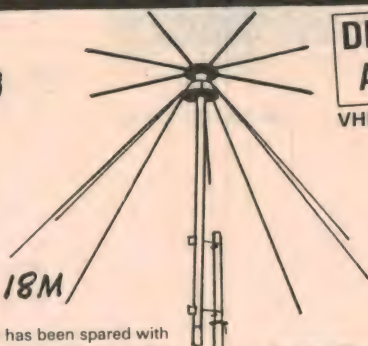**UTAC 18M**

This must be the best value around to-day. No expense has been spared with this 5 watt. It is built into a solid all metal case. Fully synthesized on the 23 U.S. C.B. channels. 19 transistors, 12 semiconductors. Squelch, P.A. illuminated channel selector. Heavy duty remote mike complete with all mounting hardware circuit. Cannot be repeated **\$99** \$3.00 p.p.



**DISCONE AERIAL**

VHF 80-480 MHz.

**\$69.95**




**mini 6 TOKAI 5 WATT 27MC (5041)**

Miniature transceiver takes up to 6 channels. Squelch, meter, remote mike. Designed for boating use. We think this beats them all. **\$119** P.P. \$2.00
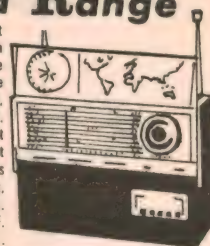
## World Range

This magnificent receiver is fitted with pushbutton and slide controls. 3 antennae tone control, squelch, dial scale, L.E.D. tuning light. 240 volt 2 battery. Inbuilt zone chart. Covers B/cast, 1.6-4.4 MHz, 4-12 MHz. F.M. 88-108 MHz. V.H.F. 108-175 MHz. There's little it won't tune in to. Others sell this radio for much more.




**\$59** \$2.00 p.p.

## Pint-Size Powerhouse!

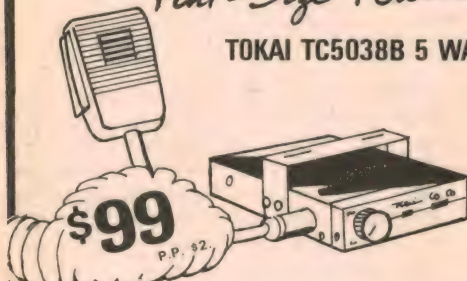**TOKAI TC5038B 5 WATT 27MC.**

We think this is the smallest 5 wattor avail. Only 1 1/4" thick, but what a performer. 3 channel facility, squelch, T/mit & stand by lite, remote mike & mounting h'ware supplied. State req. freq.



**\$99** P.P. \$2.

## Ground Plane Antennae

**FOR 27MC**

Vertical G.P. with 3.8db gain. Ideal for confined space. 212" high. Omni-directional.

**\$49.95**

P.P. \$5.

## Great Value Hand Phones

**TOKAI 1607 1 WATT**


27MC. 3 channel facility, tone call, meter, 13 trans. Guaranteed non plastic case. Vinyl carry case & strap. The best we think at

**\$97** POST FREE

**CONTACT CT 10 1 WATT**

This is our special bargain. 12 trans., 2 channel switch, tone call, robust metal case. Hard to beat at

**\$39.95** POST FREE

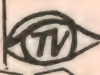


## MONITOR and DOOR PHONE

**SAVE OVER \$100 ON THIS C.C.T.V. MONITOR AND INTERCOM**

Complete outfit consisting of

- 1 Camera on flexible mount with F.1.6 lens and 30' flex.
- 2 5" T.V. monitor with intercom and 3 picture adjustments. Good for low light situations. Down to 20LUX monitor pool, shop or front door.
- 3 Intercom & alarm button for speech with picture. Used to be \$399

**\$249** P.P. \$7.00

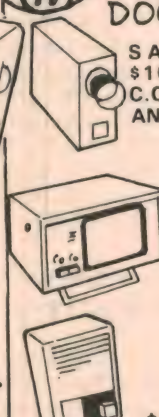

## CB CORNER X-TALS

CB-XTALS

For novices & experimenters. Supplied in pairs with 455 KC spacing. Available now on

27.085 27.240 27.340  
27.085 27.255 27.890  
27.125 27.275 27.890  
27.165 27.320 27.900  
27.910

**\$6.50 PR.** POST FREE




## CB TEST RIG INDISPENSABLE FOR THE NOVICE

Performs lots of functions


1. XTAL check.
2. Power out.
3. Modulation.
4. S.W.R.
5. Rel. field. str.
6. Oscillator etc.

**\$45.95** P.P. \$2

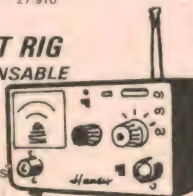


Packs a 5 watt wallop wherever you go. No installation for this one. 6 ch. fac. 17 tr. 3 Di. Squelch, tone, P.A., Bat. saver, meter. Guaranteed all metal case. Vinyl carry case. Power plus for

**\$119** P.P. \$2

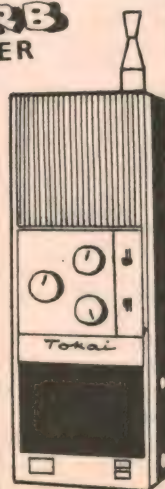

## Super Snoop

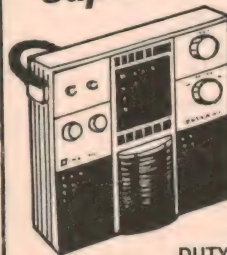

**DUTY-FREE**

Covers broadcast band and 56 to 210 MC in 3 bands: Tone control. A.F.C. . . . L.E.D. tuning light. Earphone. Runs off 240V or bats. Only

**\$49** P.P. FREE

Conventional G.P. 108" elements. Aluminium, highly efficient. Value at

**\$39.95**

P.P. \$5.

**A 27MC CENTRE LOADED AERIAL.** Short on size, but not on signal! Just 20 inches long. Includes centre loading coil, stainless steel spring and beautiful black phenolic base on the new "Quick Grip" mount. Solderless lead connection with a PL-259 connector at set end of coaxial cable. **\$19.50**

**B 27MC GUTTER GRIP.** The gutter clip CB mobile antenna designed to mount on rain gutter of any automobile. Features no hole installation. All antenna parts chrome plated brass or stainless steel. Gutter clamp zinc plated. Includes RG 58/U cable and PL-259 connector. (No Spring.) **HIGHLY EFFICIENT. \$19.50**

A

A

B


B

## 12 VOLT REGULATED POWER SUPPLY

Made to OUR specs to suit YOUR rig. Why limit the performance of your gear with an old style 12 volt supply? The PS3N gives min 12 volt under 3 amp load (surge to 5 amp). Built in electronic circuit breaker.

Solid construction. On/off switch bezel light. Smoothed. Ripple voltage 30 mV. Ready to wire into your system.

**\$29** P.P. \$2.00

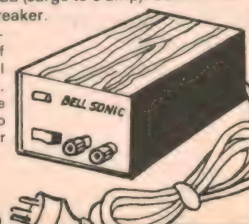



## Converter

one can do is to get the best possible null and then leave it at that. After all, it is not of vital importance. It simply allows you to tune closer to the crystal frequency, corresponding to a very low received frequency, possibly 10kHz or even lower.

At this stage, your low frequency converter is ready for use and it is up to you to explore this part of the spectrum as you see fit. There seems to me to be plenty of scope for experimenting with aerials, in particular.


After listening for some time, you may find that your interest may settle on one specific frequency or band of frequencies. Also, you may notice that the amount of noise heard on these frequencies is very high. To increase the efficiency with regard to being able to tune in some specific frequencies and to reduce the noise as well, it is possible to tune the input to the RF amplifier. You may recall that early in the description of the circuit there was reference to a link between the input low pass filter and the RF amplifier. The link may be removed and a tuned aerial circuit may be connected instead.

The tuned circuit consists of a ferrite rod loopstick, commonly used on present day broadcast receivers, and an ordinary 3-gang variable capacitor. We used a Roblan gang with each of the 415pF sections connected in parallel and the coil was wound on a ferrite rod which we happened to have about at the time. The rod is 200mm long and 12mm in diameter. If you can get one this size then well and good, but the more commonly available rods are more like 9mm in diameter and may be somewhat shorter. However, so long as it is not one of the very small ones, good results may be obtained.

It will depend very much upon the frequency range which you want to tune, as to the winding details for the coil. Each individual requirement will have to be treated accordingly but a few details of some windings may give some ideas as to where to start for any particular case. Here are some examples.

To tune from 100kHz to 300kHz, we wound a coil consisting of 100 turns of 30B&S enamel wire, tapped at 6 turns from the earthy end. Rather than count the turns, if you neatly close wind the coil and make it 2in or 51mm long, then that will be close enough. To tune from about 40kHz to 100kHz, a winding consisting of two 100 turn layers was required. A tap was made at 12 turns from the earthy end and a piece of paper was added in between the layers. A winding consisting of five 100 turn layers and tapped at 30 turns and with 560pF across it will resonate at about 22kHz.

Having made up your coil, the ques-

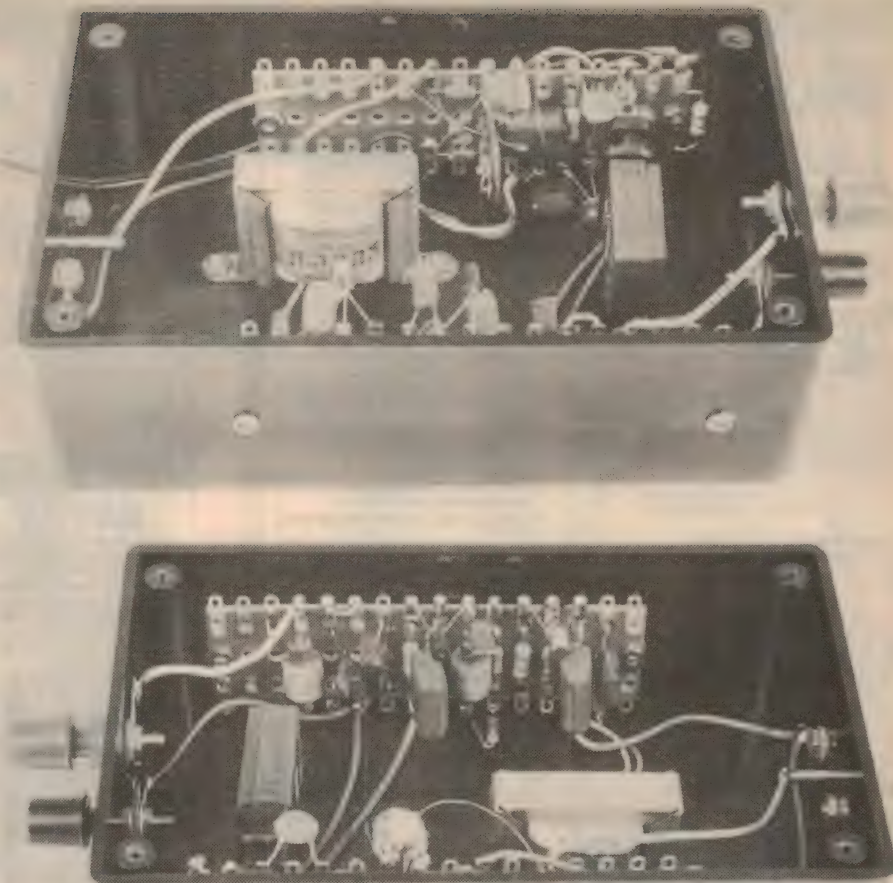

*These two views clearly show the layout inside the case. Battery leads are run through a hole drilled in the end of the box near the coax socket.*

tion arises as to how best to arrange the coil and gang mechanically. The loopstick coil is directional and should be rotatable, while the gang should best be fixed. The coil may be separated from the gang by say a piece of figure 8 twin flex up to about 1m long. This will allow the loopstick to be rotated conveniently. Another similar flex may then be run between the earthy end and the tap, to the earth connection on the converter and the .01uF capacitor before the base of the RF amplifier.

With the tuning arrangement completed, you will find that some skill is required to tune in the low frequency stations. In addition to tuning the short wave receiver as before, it will also be necessary to keep the front end tuned circuit manually in line with the main tuning. This is not quite as difficult as it may first appear because it is quite easy to peak up the front end tuned circuit on noise. Care is needed in the first instance but once a station is logged, it may be recorded on a suitable dial provided for the purpose. In addition to the above procedures, it is also necessary to rotate the loopstick and peak it on the station.

To give you some idea as to what to

look for at least in the Sydney area, here is a list of the stations and the approximate frequencies which I logged on this converter. In the VLF region I was able to tune the US navigation station located at North West Cape, in Western Australia and on 22.3kHz. On the higher frequencies I logged the following, being identified in Morse code. BK 213kHz, ETL 220kHz, SDM 235kHz, WOL 244kHz, WPB 255kHz, CN 282kHz, SY 319kHz, RI 350kHz, KAT 357kHz, WLM 369kHz, VIS 500kHz.

In addition to this list, there are many other stations on various frequencies and locations. There is a station in Canberra on somewhere about 40kHz. Then there are various Loran stations on 100kHz and other frequencies and although they are located well outside the Australian scene, it just may be possible to receive one or more of them.

This is not all by any means, although once again many are located at great distances from Australia. There are stations in operation down as low as about 10kHz. There may be a lot of fun in trying to log some of them, even though the information which is transmitted is of little if any entertainment value.



# Dick's New Kits for '76

## L.E.D. LADDER KIT


**\$16.75**

EA L.E.D. LADDER  
As in E.A. March 1976

Push the button - make the light climb up the ladder - but it gets harder near the top.

Easy to build uses one small P.C.B. uses sixteen red light emitting diodes. Special decorative front panel.

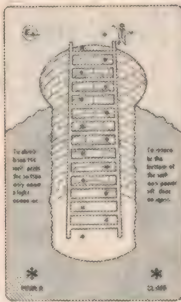All parts supplied.  
Cat. K3390 Complete Kit for only \$16.75



A GAME OF SKILL

## NOVICE TRANSVERTER KIT

DICK SMITH "NOVICE TRANSVERTER"

10 metres to 80 metres at up to 30W p.e.p.

\* Designed by Australia's top R.F. Engineer, exclusively for us.

\* The cheapest and best way for a novice to get going on 80 metres.

\* Put in any signal (AM/FM/SSB) on the 27MHz novice band and it is instantly "Transformed" down to 80 metres.

\* Inbuilt receiver converter "Transverts" 80 meter signals up to 10 meter novice bands.

\* Max power 10 watts and 30 watts p.e.p. SSB from as little as 100mw input (and suitable 100mw-3 Watts).

\* Easy to build (takes about 3 hours) fiberglass boards, fully reverse voltage protection.

\* Input and output 50ohm.

\* Free "Contest" forms with each unit - you may win a brand new Kenwood TS520.

\* 13.8 volt DC (max) operation - ideal for Mobile rigs.

\* Supplied with special 27 MHz Xtal which allows frequency to 81 transverters to 80 meter section of novice band.

Cat. K3134 .... Very Special Offer \$99.50

Dick's  
LOW  
Price

**\$99.50**

## MOSQUITO REPELLER KIT \$5.50

Ideal for picnics, barbecues or around the house. Even good when fishing.

WHY BUY ONLY ONE !!  
At this price they're a super special complete with instructions in our Deluxe UB3 Zipper Case.

Cat. K3380 ..... ONLY \$5.50

## AMP KIT \$27.50

NEW 45 WATT 2 METRE R.F. AMP KIT

Fantastic new 2 metre R.F. Amp kit, simple design (you'll make it in less than an hour). Uses the new 2N6084 45 watt transistor - 8-12 watts in - gives 35-45 watts out - at 13.8 ohms. Fully solid state switching, double sided fiberglass board, everything supplied including expert instruction.

There's even provision on the board for a VSWR meter!

Edystone Box to suit (if required)

Cat. K3132 ..... Really Good Price \$27.50

## ELECTRONIC ORGAN KIT

Kit including all electronic parts, high quality Mitsubishi Keyboard (as used in article) - everything other than the cabinet (you can easily build that yourself!).

See price in next issue of this magazine.

KEY BOARD ONLY ..... \$97.50  
FOR COMPLETE KIT PRICE SEE NEXT MONTHS ISSUE OF THIS MAGAZINE.

IDEAL BEGINNERS KIT!  
START YOUR OWN DENSHI WAY.



**ST100 DENSHI KIT**

Features a built in yourself radio. Comes with Morse key, earpiece, & components for building alarm circuits and electronic gun.

Cat. K 2120 ..... \$19.95

**NEAR COST!**

## AUDIOPHILES DELIGHT !!

AC320 \$36

Milliwatt meter:  
- 10 mV to 30V in 8 ranges  
- 52 dB to +32dB  
- Frequency response 20Hz to 100 KHz ± 1 dB  
- Input Impedance 1 Megohm  
- Accuracy ±3% F.S.D.

The unit runs for ages off a 9V transistor radio battery and weighs only 300 grams.

Yes, now you can check the level of PMG lines, signal sources etc. easily.

You must have one of these for only—\$36.00

DIMS: 92mm x 145mm x 42mm  
EXCELLENT PRICE \$36.00

## CRT HIGH VOLTAGE TEST PROBE

SK-9000

Built-in meter assures safe and easy measurements up to 30,000 volts DC.

600mA DC range enables to monitor the cathode current of the horizontal output tube of TV set.

Barriers are installed to protect the probe handle from high voltage.

The test probe is compact, light and easy to handle.

**\$30.50**

DC Voltage: 30,000 volts (internal resistance 600MΩ)

DC Current: 600mA (450mV drop)

Accuracy: ±3% (of full scale at 20° C)

Temperature coefficient: ±0.15 % per 10C

Size and weight: 374 X 48 X 45mm, 240g

Accessories: 1 pair Test leads

Cat. Q1440 ..... ONLY \$30.50

## NEW ELECTRONIC STOP WATCH KIT

NOVUS TIMER KIT (ET JAN 1976)

Special kit includes silk screened printed circuit and all components to build this handy timer. INCLUDING THE NOVUS 650 CALCULATOR.

Cat. K3340 ..... \$18.50



**\$18.50**

SEE E.T. JAN. '76

## PACK OF 300 RESISTORS

WHAT A SENSATION !!

Now we have improved our already famous computer resistor pack.

For example, in this pack you get 20 x 1 K ohm and only 2 x 560 K resistors - 300 useful values in all, as selected by a computer.

All resistors are 1/4 watt 5% tolerance carbon film high stability - not cheap composition types. They come in a compact neatly printed box. 60 different values 10 ohms to 1 meg.

Box measures 2 7/8" x 1 3/4" x 1 3/4"

There honestly isn't a hobbyist or serviceman who should not have a box.

Cat. R7010 FANTASTIC PRICE OF \$5.90

**\$5.90**

Less than 2¢ a part

## BELLSONIC CAR CONVERTOR

Converts 6V D.C. to 12V D.C.

Ideal for running 12V Car radios, car stereos etc. In any 6V vehicle.

Used to be \$29.90

Cat. M95922 ..... Only \$22.00

**\$22.00**

BELLSONIC

12V D.C. CONVERTER

INPUT: 6V D.C. OUTPUT: 12V D.C.

200mA

## SALE SPECIAL

see E.A. nov. '75

only

**\$27.50**

SAVE \$7 on regular price of \$34.50

PROFORDS FANTASTIC

ALARM CLOCK KIT

AN INCREDIBLE CLOCK, THE DC8 HAS EVERYTHING

\* HUGE 10mm FLUO READOUT

\* BRIGHT DISPLAY HOURS, MINUTES, AM, PM

\* ELECTRONIC ALARM TO THE MINUTE

\* 7 MINUTE SNOOZE CYCLE \* 240 Volt OPERATION

\* MODERN CASE AND FILTER PANEL \$3.00 EXTRA IF REQUIRED.

Cat. K3340 ..... X IT VERSION \$27.50

FULLY BUILT AND TESTED UNIT \$37.50

**\$27.50**

PROFORDS

FANTASTIC

ALARM CLOCK KIT

AN INCREDIBLE CLOCK, THE DC8 HAS EVERYTHING

\* HUGE 10mm FLUO READOUT

\* BRIGHT DISPLAY HOURS, MINUTES, AM, PM

\* ELECTRONIC ALARM TO THE MINUTE

\* 7 MINUTE SNOOZE CYCLE \* 240 Volt OPERATION

\* MODERN CASE AND FILTER PANEL \$3.00 EXTRA IF REQUIRED.

Cat. K3340 ..... X IT VERSION \$27.50

FULLY BUILT AND TESTED UNIT \$37.50

**\$27.50**

PROFORDS

FANTASTIC

ALARM CLOCK KIT

AN INCREDIBLE CLOCK, THE DC8 HAS EVERYTHING

## SOLID STATE INSULATION TESTER

MODEL SK-3000

\* Compact, lightweight versatile insulation tester measures up to 1,000 Meg ohms.

\* Low ohm measurements are convenient on two ranges, X1 and X1K.

\* Zero ohm adjustment can be made easily by Ohm ADJ. knob.

\* With 250V AC range.

**\$66.00**

SPECIAL

SPECIFICATIONS

Meg Ohm Rated voltage: 500 volts

Rated resistance: 0 - 1,000MΩ (center 20MΩ)

Low Ohm X1 range: 0 - 1,000Ω

X1K range: 0 - 1MΩ

AC Voltage: 0-250 volts

Accuracy: Meg Ohm: ±4% (of scale length)

Low Ohm: ±4% (of full scale)

Batteries: UMA3 X 4

Size and weight: 148 x 8 x 78 x 50mm, 540g

Accessories: 1 pair Test leads and Vinyl leather case.

Cat. Q1430 ..... ONLY \$66.00

**\$66.00**

SPECIAL

SPECIFICATIONS

DC Voltage: 30,000 volts (internal resistance 600MΩ)

DC Current: 600mA (450mV drop)

Accuracy: ±3% (of full scale at 20° C)

Temperature coefficient: ±0.15 % per 10C

Size and weight: 374 X 48 X 45mm, 240g

Accessories: 1 pair Test leads

Cat. Q1440 ..... ONLY \$30.50

**\$30.50**

SPECIAL

SPECIFICATIONS

## BOOKS

COLOUR TELEVISION THEORY by G. Hutson

326 pages of text, diagrams and illustrations (some in colour) in this handbook edition. A must for students, engineers and technicians who wish to have a thorough understanding of the PAL system. Describes the difference between PAL, NTSC and SECAM. Standard work on subject.

Cat. B3210 ..... \$12.50

## AUDIO CYCLOPEDIA

By Howard M. Trzmaine

The most comprehensive and authoritative reference volume on audio ever published. Its 25 sections cover every aspect of the audio art from the basic principles of sound to the latest in solid-state equipment. 1760 pages.

Cat. B1096 ..... Normally \$39. . NOW \$26.00

TTL C00KBOOK by Don Lancaster

TTL (transistor-transistor logic). The purpose of this book is to show you what TTL is, how it works and how to use it. The author suggests several TTL projects that the reader may wish to try, relying on his own resources. WAS \$10.75.

Cat. B1246 ..... SAVE \$2.00 . NOW \$8.75

## NOVICE RADIO GUIDE

This book is the perfect book for any beginner. Several chapters of theory help the reader to both prepare for his licence and also to better understand his station as he puts it together.

Cat. B2280 ..... Very reasonable price \$4.75

## Super Sensitive Metal Detector \$9.75

Just tell a builder or handyman about this fantastic gadget - locates any metal object - wires, pipes, reinforcing steel, even nails, inside walls and plaster etc.

\* Light comes on in presence of metals

\* Penetration/sensitivity control locates metal 6" away

\* Supersensitive electronic circuit pinpoints even small nails

\* Easy to operate from 9V transistor battery

Range depends on size of metal object. Ideal for electricians who once had to pay \$30 - \$40 for such a unit. (9 Volt battery 40¢ extra)

Cat. X 1060 ..... \$9.75

## SIGNAL INJECTOR \$4.75

This Signal Injector (TE-101) uses a circuit designed to make blocking modulation for high frequency at low frequency of 1 KHz.

Transistorised. Complete with battery.

Cat. Q 1270 ..... \$4.75

## FANTASTIC 8 DIGIT PANAPLEX READOUT

(Shown approx 30% actual size)

\* 8 LARGE Digits for less than 90¢ each.

INCLUDING GOLD PLATED SOCKET. 180 Volt OPERATED IDEAL FOR CLOCK AND CALCULATOR PROJECTS.

AVAILABLE SOON : Driver Transistors and Power Transformer to suit.

Cat. S 3890 ..... \$6.75

## MJ001 IC TEST CLIP

DON'T PAY \$1.40 EACH

**PAY ONLY \$1.00 for 2**

A MUST FOR ALL MULTIMETERS

Cat. W4580 BARGAIN AT ONLY \$1.00 For TWO

## JUMPER LEAD KIT

J5119 Jumper Lead Kit

Here's ten 15' leads with croc. clips. Two each in five colours. Worth over \$2.00.

Cat. W4570 ..... NOW ONLY \$1.50

**\$1.50**

SPECIAL

5 for \$1.

BAKELITE T03 TRANSISTOR SOCKETS.

High Quality. SPECIAL PRICE! Cat. P4023 30¢ ea.

Buy 5 for only \$1

## DICK SMITH ELECTRONICS CENTRE

Head Office & Mail Orders

162 Pacific Highway Gore Hill N.S.W. 2065 tel:439 5311

telex:AA20036

cables:DIKSMIT Sydney

Shop hours:

Mon-Fri 9.5.30 Sat 9-12

Also at CITY 125 York St tel:291126 (Nr Town Hall)

and BANKSTOWN 361 Hume Hwy tel:709 6600 (Nr Chapel Rd)

bankcard welcome here



BE SURE OF YOUR HUGE, ALL NEW, 1976 DICK SMITH CATALOGUE. ORDER APRIL 1976 E.A. TODAY!

# DICK SMITH AMP Model 6000


**30+30 WATTS RMS  
100 WATTS MUSIC POWER**

Frequency Response: 20-30000 Hz  $\pm 1$  dB  
(at normal listening level)  
Load Impedance: 8 ohm

DICK SMITH MODEL 6000 STEREO AMPLIFIER  
As reviewed in E.A. February 76.

Hum and Noise (1HF) Phono.....Better than 70 dB  
Aux.....Better than 75 dB

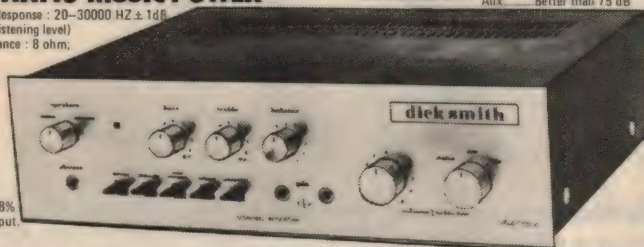Harmonic  
Distortion:  
Less than 0.8%  
at rated output.




A professional high fidelity amplifier that is value packed. Similar powered units sell for around \$189.00.  
Inputs for microphone, turntable, tuner etc.  
Smart brushed satin finish, weighs in at 12 lbs and measures  
36 x 9.5 x 25.5 cms. 240 volts AC. Cat. A 1262 ..... \$129.

**Dicks Price \$129**


## EXPO CPR 145A AC/DC CASSETTE with AM/FM RADIO

DICK'S  
PRICE  
**\$69.95**

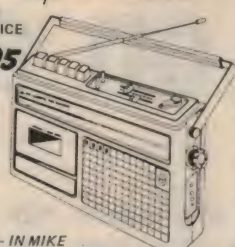

BUILT-IN MIKE  
PUSH BUTTON CONTROL  
VOLUME & TONE SLIDE CONTROLS  
Cat. A 4056 ..... \$69.95

## CRAZY!

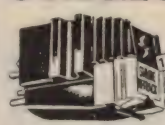

**SHURE**  
Made in U.S.A.

100 only  
M91ED  
**SAVE \$19**

A GENUINE SHURE M91ED STEREO  
CARTRIDGE WITH ELLIPTICAL DIAMOND  
STYLUS (THAT'S NEEDLE LADIES) THIS  
UNIT IS SO GOOD IT CAN EVEN BE USED  
WITH FOUR CHANNEL (MATRIX) RECORDS.  
NORMAL 1/2inch SPACE FIXING WILL FIT  
MOST TURNTABLES.  
FOR THE TECHNICS - OUTPUT IS:  
5.0mV per CH @ 1,000Hz @ 5cm/sec PV.

NORMALLY RETAILING FOR \$44.00

## DICK'S CRAZY PRICE

WHY NOT CHANGE  
YOUR CARTRIDGE NOW?  
Cat. C 5515 ..... \$25.

**\$25**

## SAVE

LAST YEAR WE WERE  
SELLING THIS  
REMARKABLE  
CALCULATOR  
FOR \$59.00

## FORDS SCIENTIFIC CALCULATOR

8 Digit FLURO Readout  
(more expensive than LED's)  
Memory + 4 Functions  
+ Trig, Log and most  
scientific functions.  
Floating decimal.  
Comes complete with  
case and batteries.


Cat. C 3010 ..... \$29.95  
Tax Free

**\$29.95**

TAX FREE  
\$32.20  
Inc. Tax

SAVE BY BUYING  
ONE OF THE  
FEW LEFT AT ONLY

## TAPE RECORDER SWITCH

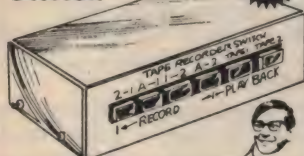

AUDIOPHILES & TAPE ENTHUSIASTS  
GRAB ONE OF THESE!!  
YES, THIS LITTLE UNIT IS THE ANSWER TO  
YOUR PRAYERS.

DIG THIS CUTE ITEM!  
Dub from one tape unit to another tape unit  
using this beaut tape switch. Yes - if your Amp  
does not have dub features then just add this  
switch unit and have a feature more expensive  
Amps boast of! No need for messy patch  
cords here. Now you can simply switch between  
your audio gear.

Cat. C 7220 ..... \$12.50

**BARGAIN \$12.50**

## FANTASTIC

OVER 1800 HAPPY  
CUSTOMERS CAN'T  
BE WRONG.

## AM/FM STEREO ~ MONO TUNER

"VERY GOOD VALUE INDEED." NEVILLE WILLIAMS  
IN FEB. 75 EDITION ELECTRONICS AUSTRALIA.

GUARANTEED FOR 12 MONTHS



The ECHOSOUND TUNER is incredible value for money  
with separate AM and FM front ends, 10 transistors and  
14 diodes. Covers FM 88 to 108MHz AFC. 60dB S/N.  
35 db separation. 600mV output AM 535 to 1605kHz  
ferrit rod antenna. Features multiplex adaptor complete  
with built in stereo indicator. 240V AC operation.  
Complete in walnut case.

Cat. A1410 ..... Now \$65.

P&P  
FREE

was  
**\$75**

now

**\$65**

DICK'S PRICES  
ARE LOWER

## ELEGA DR-196C

COMPLETELY NEW DESIGN  
SUPERHIGH VELOCITY  
TYPE HEADPHONES.

SPECIFICATIONS  
Sensitivity 100dB  
SPL/mW  
Frequency Range  
18-22,000Hz  
Matching Imp  
edance 4-150  
maximum input  
0.1W  
weight 130gr  
without cord.

\*Newly Designed  
\*Compact & Light Weight  
\*Velocity Type  
\*Super Compact  
Drive Unit  
\*Young Look Jeans type  
Headband



Cat. C4122 ..... \$29.50

**Dicks Price \$29.50**

## CASSETTE SPECIALS!

**BASF C90 \$2.99**

1500 ONLY - GENUINE BASF C90  
CHROMIUM DIOXIDE IN SNAP PACK.  
DON'T BE MISLED THIS IS  
THE GENUINE PRODUCT.

SAVE \$2 ON OUR SHOP LISTED  
PRICES FOR SINGLES. BUY  
ANY QUANTITY ONLY \$2.99 EACH

**BASF C60 \$1.50**

From  
WE NOW HAVE 5,000 ONLY BASF C60  
C90SM in "SNAP PACKS" STILL AT  
THE FANTASTIC PRICE OF \$1.75 each  
OR \$1.50 each ON LOTS OF 10 OR MORE  
HURRY WHILE STOCKS LAST!!!



## EXPO 1212 STEREO AMP

EXPO DX 1212 12+12 WRMS STEREO AMPLIFIER

Full control amplifier - smart design with switches for  
loudness - tape monitoring - stereo/mono and high  
filter. Will take your Goldring ES 705 through its  
magnetic phono input. Frequency response from  
20Hz to 25kHz - S/N ratio better than 60dB on phono  
Also accepts stereo Headphones 8-16 ohms.

SAVE \$20 at  
DICKS price of

**\$99**

Cat. A1004 ..... \$99.


## WSV8 EXTENSION SPEAKER

HUGE 8" Speaker in WALNUT  
Cabinet with black grill cloth.  
Has built in volume control so  
that sound can be adjusted  
independently.

Normal Price \$18.50  
Cat. A2450 ..... Now \$10.75  
ROAD FREIGHT ON



## SALE VINYL COVERED CUBE SPEAKER

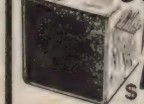


Ideal extension speaker.  
Handsome complete unit  
with 4" speaker. Buy now  
and SAVE well over \$2.00  
Cat. A2457 ..... \$4.50



**INCREDIBLE  
EXPO CR50  
NEAR  
COST!  
\$79.**

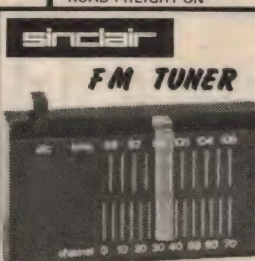A Tuner - Amplifier offering fantastic features:  
Full 6 watts RMS per channel. Two speaker system switch  
plus all usual controls. And greatest of all - Full MPX Stereo  
FM Radio incorporated plus AM Radio. Feature this unit in  
your rumpus room audio system for this ridiculous price.  
Cat. A1660 ..... Near Cost Give Away Price ..... \$79.



Provides a drift-free ultra sharp  
performance with strong  
automatic frequency control  
coupled with dual varicap  
electronic tuning, followed by  
a 4-pole ceramic filter IF  
section for extra selectivity.  
Greater adaptability results  
from the tuner & stereo decoder  
section being made available  
separately. Tuning Range 88 to  
108 MHz. AFC switchable,  
with thermistor control to  
prevent drift. One 26 transistor  
IC. Distortion 0.3% at 1kHz for  
75kHz deviation. 23-32 volt  
Power requirement.

Cat. F4315 ..... \$34.50



## PROJECT 80 STEREO DECODER

This unit gives a 30dB channel  
separation with an output of  
150mV per channel. Gallium  
arsenide light emitting diode  
automatically lights up to  
show when a stereo transmission  
is tuned in. One 19 transistor  
IC. Power requirements  
23-30 volts. Size 47x50x20mm.  
Cat. F4320 ..... \$21.

SAVE OVER \$7  
BUY BOTH FOR  
**\$48.50**

# DICK SMITH

**ELECTRONICS CENTRE**  
Head Office & Mail Orders

Shop hours:  
Mon-Fri 9-5.30 Sat 9-12

162 Pacific Highway Gore Hill  
N.S.W 2065 tel:439 5311  
telex:AA20036  
cables:DIKSMIT Sydney

Also at **CITY 125 York St**  
tel:291126  
(Nr Town Hall)  
and **BANKSTOWN**  
361 Hume Hwy  
tel:709 6600  
(Nr Chapel Rd)



NEW POSTAL CHARGING SYSTEM  
Our new system can save you money! The larger your order  
the cheaper the packing and postage! Minimum charge is now  
\$1.00. Remember it doesn't just cost us stamps to send out  
mail orders. If you want your order sent by Air mail, C.O.D.  
or Comet it will cost extra.

Order Value	Charge
\$5 - \$9.99	\$1.00
\$10 - \$24.99	\$1.50
\$25 - \$49.99	\$2.50
\$50 - \$99.99	\$3.50
\$100 or more	\$5.00

By Comet Freight. Minimum packing and handling charge \$1.00 - we dispatch 'freight on' and you pay when you receive the goods.  
To avoid damage, all bulky or fragile articles will be sent by 'Comet' freight on (i.e. freight paid by you on delivery).



# Simple function generator based on a single IC

What's cheap to construct, easy to build, has six spot frequencies, three waveshapes, an adjustable output level, and runs from a small 9V battery? It's the MINI-GEN, of course, so if you have a need for a small portable test oscillator, read on.

by DAVID EDWARDS

Mounted in a small plastic box, and powered from a tiny "216" type 9V battery, this little generator will supply sine waves, triangular waves and square waves with amplitudes in excess of 2V RMS at frequencies of 10Hz, 30Hz, 100Hz, 300Hz, 1000Hz and 3000Hz. We estimate that the total cost of all components will be about \$15.00.

The MINI-GEN, as we have christened it, is based on a single low cost integrated circuit. This IC, the LM3900, contains four differential input operational amplifiers in a single 14 pin DIL package. Designated "Norton Amps", these new op-amps have current differencing inputs rather than conventional voltage differencing inputs, and operate from a single supply rail.

Essentially, the output voltage of the op-amp is determined by the difference between the currents applied to the inputs, rather than by the voltage dif-

ference as is usually the case. Both input terminals are clamped at  $+1V_{BE}$  above ground, and input resistors are used to convert from input voltages to input currents.

Output biasing is obtained by providing a current path from the positive supply rail to the non-inverting input.

Referring now to the circuit diagram, we can see how the four op-amps have been combined to produce the required waveforms.

Amplifiers 1 and 2 function as a combined triangle and square wave generator. Initially, C1 is charged, and the output of amp 2 is low. C1 commences to discharge in a constant current mode, and the output of amp 1 decreases linearly with respect to time. No current flows through  $R2 = \frac{1}{2}R1$ , and the rate at which C1 is discharged is determined by R1 alone.


When the current supplied to the

inverting input of amp 2 via  $R_{in}$  falls below that supplied to the non-inverting input via  $R_b$ , the output of amp 2 goes high. This supplies current to the non-inverting input of amp 1 via  $R_2$ . Since  $R_2$  is exactly half of  $R_1$ , this current is twice that through  $R_1$ , and  $C_1$  commences to charge at the same rate at which it was discharging. This causes the output of amp 1 to ramp upwards.


The high output of amp 2 also supplies current to its own non-inverting input via  $R_f$ . This means that the output of amp 2 will not go low again until the voltage at the output of amp 1 is such that the current through  $R_{in}$  exceeds the sum of the currents through  $R_b$  and  $R_f$ . When this does happen,  $C_1$  commences to discharge again, and the output of amp 1 ramps down again.

Thus a triangle wave is produced at the output of amp 1, and a square wave at the output of amp 2. The latter has an amplitude only slightly less than the supply rails, while the amplitude of the former depends on  $R_{in}$ ,  $R_f$ , and the supply rail.  $R_b$  determines the quiescent output voltage of amp 2.

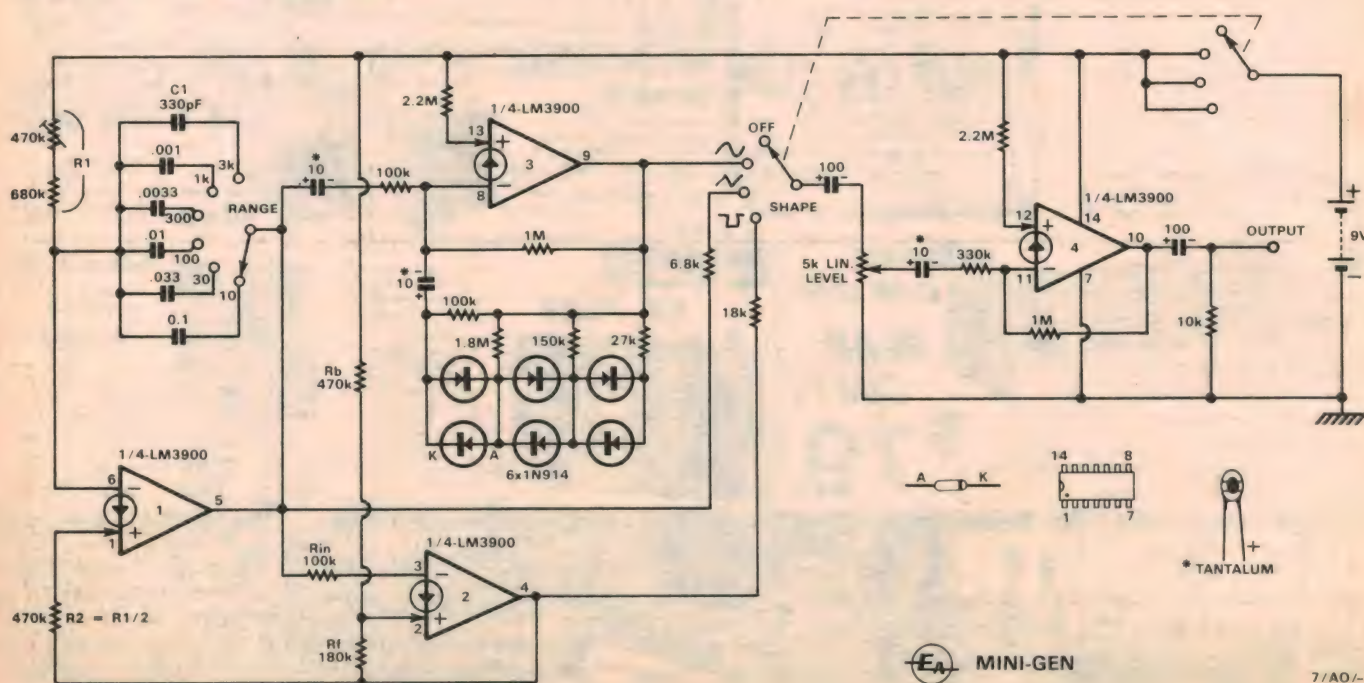Frequency of operation is determined by R1, R2 and C1, and is substantially independent of supply voltage variations. If R1 is made twice R2, the





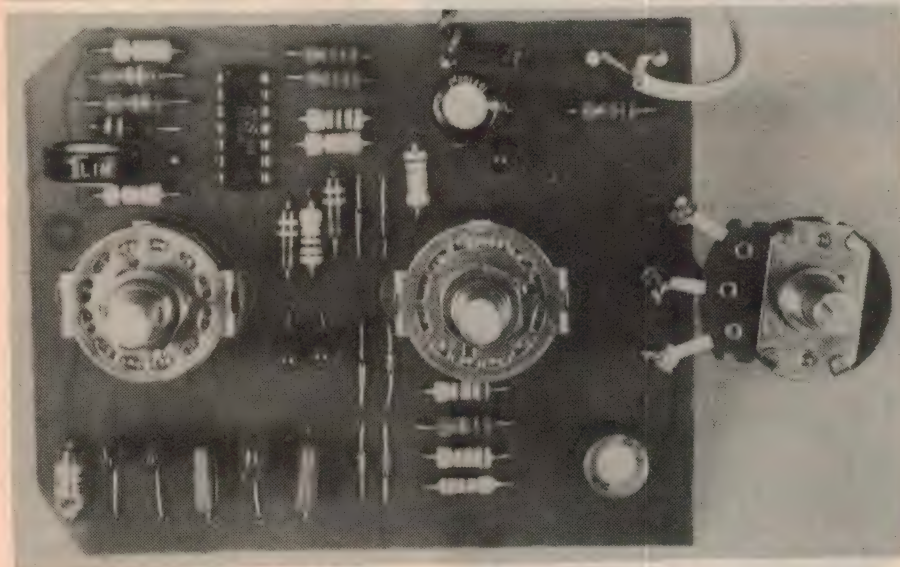

Details of the front panel layout are shown in the photograph at top. Directly above is a view of the assembled PC board.

waveform from amp 1 is triangular rather than sawtooth, and the square wave from amp 2 has a mark/space ratio of unity.

The circuit diagram shows R1 composed of a fixed resistor in series with a variable one. If you do not have access to test equipment, simply make R1 and R2 from three 470k high tolerance resistors. If you do have access to test equipment, the values shown in the diagram can be used. The trimpot can then be adjusted so that the mark/space ratio of the square wave is unity. This will then minimise the second harmonic distortion present in the sinewave output.

A six position single pole switch is used to select different values of C1, to give a range of frequencies. The maximum useable frequency is about 3kHz; with frequencies higher than this slew rate limiting occurs inside the op-amps, and the output waveforms deteriorate markedly.

Low frequency operation is limited

only by the input bias currents, and operation at frequencies of the order 0.1Hz is quite feasible. At these frequencies, large capacitors may have to be used, and leakage may become important.

With the values shown on the diagram, the nominal operating frequencies are 10Hz, 30Hz, 100Hz, 300Hz, 1000Hz and 3000Hz. With standard value components, actual operating frequencies should be quite close to these figures.

Amp 3 is connected as an AC coupled sinewave shaping amplifier. Diodes in the feedback network are used to convert from the triangular wave input to an approximate sinusoid, by selectively changing the slope. The output sinewave has a distortion of about five per cent, and is reduced in level with respect to the input.

The SHAPE switch, which also functions as a power switch, selects one of the three waveforms and feeds it to the

## PARTS LIST

### SEMICONDUCTORS

- 1 LM3900 quad op-amp.
- 6 1N914 silicon diodes.

### CAPACITORS

- 2 100uF 16VW PCB mounting electrolytics.
- 3 10uF tantalum.
- 1 0.1uF plastic.
- 1 0.033uF plastic.
- 1 0.01uF plastic.
- 1 0.0033uF plastic.
- 1 1000 pF plastic.
- 1 330pF plastic.

### RESISTORS (all 1/2W)

- 2 2.2M, 1 1.8M, 2 1M, 1 680k, 2 470k, 1 330k, 1 180k, 1 150k, 3 100k, 1 27k, 1 18k, 1 10k, 1 6.8k, 1 680k linear trimpot, 1 4.7 linear pot.

### MISCELLANEOUS

- 1 2 pole 6 position rotary switch, SRM162 (S2302) or equivalent.
- 1 3 pole 4 position rotary switch, SRM143 (S2303) or equivalent.
- 1 plastic utility box, type UB1, 150 x 90 x 50mm or similar.
- 1 RCA socket and jack.
- 3 knobs.
- 1 printed circuit board, 99 x 82mm, coded 76ao3.
- 1 miniature 9V battery and clip to suit.

Scrap aluminium, solder, hook-up wire, machine screws and nuts, circuit board pins, tinned copper wire.

Note: resistor wattage ratings and capacitor voltage ratings are those used in our prototype. Components with higher ratings may generally be used provided they are physically compatible. Components with lower ratings may be used in some cases, providing ratings are not exceeded.

LEVEL control. The resistors in series with the triangle and square wave inputs, have been chosen to equalise the three waveforms in terms of peak-to-peak level at the LEVEL control wiper.

The output from the LEVEL control is amplified by amp 4, which has an AC gain of about 3 and acts as an output buffer. The output is AC coupled via a 100uF electrolytic capacitor. This size capacitor is necessary to prevent noticeable degradation of the square wave at very low frequencies. The 10k resistor across the output provides a charging path for the capacitor on initial turn-on.

Construction of the MINI-GEN is very simple. We have designed a small printed circuit board, coded 76ao3, on which nearly all components mount. This board has been designed for use with the type of switches mentioned in the parts list. These are available from Dick Smith Electronics at a very reasonable price.


As you can see in the photographs, the





Test and  
Measuring  
Instruments

# PHILIPS

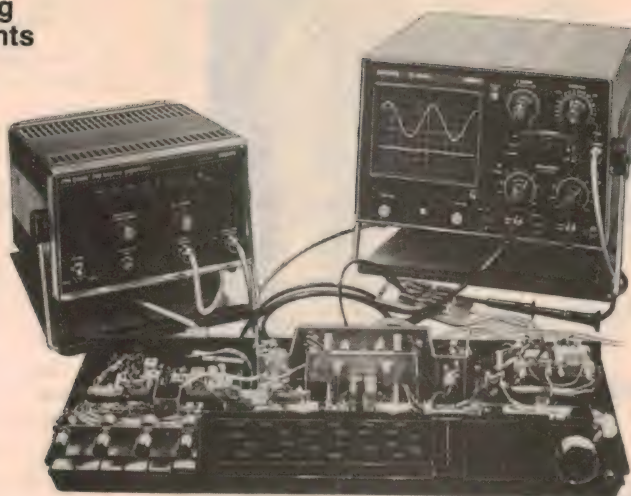

## Aligning F.M. stereo receivers?



### Save time with this stereo generator.

Most stereo faults are a result of component drift, an effect that can be fairly simply corrected by re-aligning the receiver.

A transmitted stereo signal is difficult to quantify and is not suitable for receiver alignment. The Philips FM6456 produces a standardised stereo multiplex signal from which the various signal components can be selected by push buttons. These signals are reproducible and easy to use for adjustments. The stereo signal is fully adjustable.

The test signals provided include a crystal controlled 19 kHz Pilot, internal one and five kHz Modulation, provision for external modulation, right channel only, left channel only, both channels in anti-phase ( $R = L$ ). The generator produces, when switched, a 100 MHz signal which can be frequency modulated by the multiplex signal.

The test signals provided by the PM 6456 facilitates the tracing of such faults as phase error between the pilot signals and the regenerated

carrier, demodulation phase error and probably the most common fault, crosstalk between channels.

External modulation of the RF output with a stereo record player or tape recorder allows a final audio check to be made and is a useful feature for demonstrating F.M. Stereo receivers to your customers. For further information phone our nearest office or send this coupon.

To: Philips Electronic Systems  
Scientific & Industrial Equipment Division  
G.P.O. Box 2703, Sydney, N.S.W. 2001  
Phone Sydney 8888222

Please send me information on the Philips  
FM Stereo Generator


Name .....

Address .....

Postcode .....



### Simple function generator

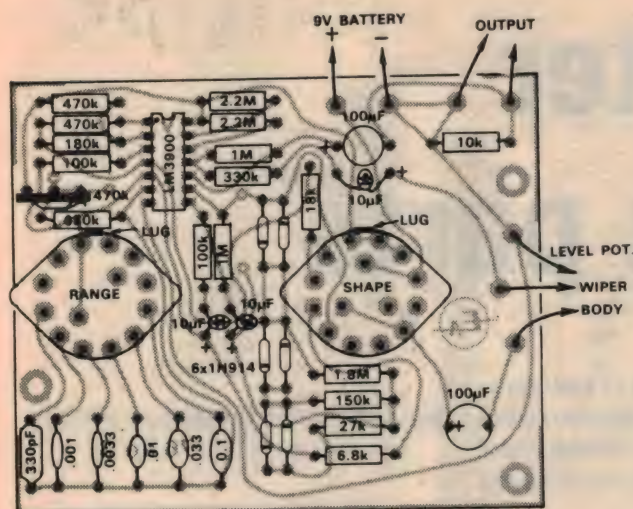

Layout of components on the PC board. Pay attention to polarity conscious components.

PCB is simply soldered directly to the switches. This provides ample mechanical support, and eliminates the need for spacers and the like. The LEVEL pot is also mounted directly on to the PCB, using short wires as standoffs.


If, for any reason, you are unable to obtain suitable switches, other types can be pressed into service by simply wiring them to the board, using short lengths of hook-up wire. In this case, it will be necessary to support the PCB, so we have provided space on the pattern for three mounting holes. Comparison of the PCB pattern with the circuit diagram will enable the appropriate connection points to be determined.

Construction is best started by drilling the PCB to take the switches. Use a drill


which is only slightly larger in diameter than the lugs of the switches, and then, if necessary, bend the switch lugs to suit. Do not solder the switches in place at this stage.

Next, using the PCB overlay as a guide, fit and solder all the remaining components to the PCB. The IC may be carefully soldered directly to the board. Check carefully that all polarity conscious components are fitted correctly. The battery connector is soldered directly to the relevant terminals, using PCB stakes if desired. The leads to the output socket can be either twisted hookup wire or shielded cable.

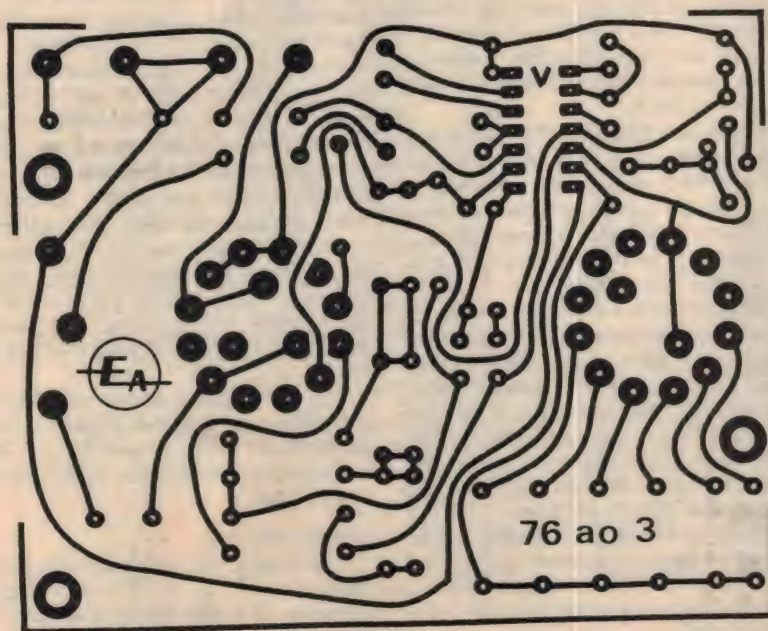Drill the required three holes in the front panel next. These should be located on the centre line, with the centre one



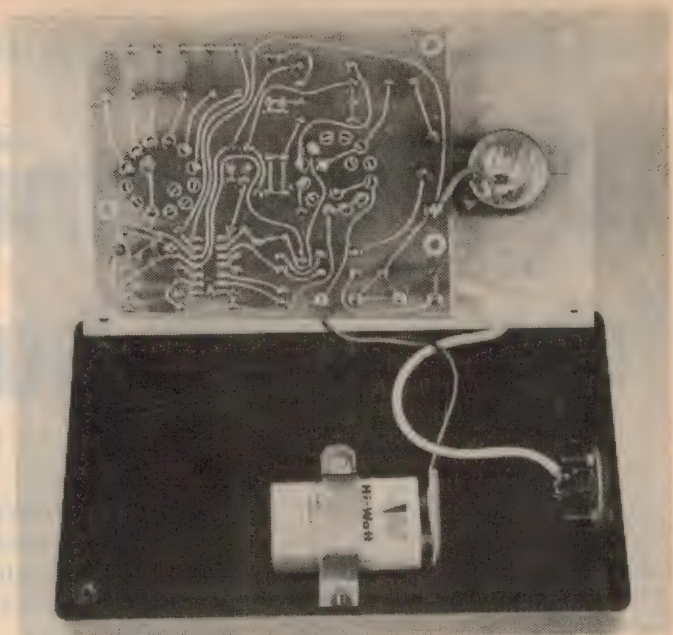The PC pattern, reproduced actual size to facilitate tracing.



The PC board is mechanically supported by the two switches soldered directly to it. Note battery clamping details.


in the exact centre of the panel, and the other two spaced 51mm away on either side. Stick-on lettering can now be applied directly to the panel, and protected by spraying with a clear lacquer.

The switches can now be fitted to the PCB. The locating lug on the body of the switch should be placed on the side of the board near the IC. Only the lugs required need be soldered to the pattern. This will make later removal, if required, a lot easier.

Now loosely crimp three short lengths of tinned copper wire to the lugs of the LEVEL pot, and fit it to the front panel, using nuts on both sides. It must be fitted with the minimum amount of bush above the panel. If extra nuts are not available, the pot can be packed out with washers.

Then fit the switches and PCB assembly to the panel, and feed the copper wire through the correct holes. The switches must also be mounted with nuts on either side of the panel, to provide sufficient clearance for the components. After all the nuts have been tightened, solder the wires both to the pot lugs and to the PCB. This will locate the pot, and the front panel can now be removed if necessary.

The body of the LEVEL pot should be connected to the negative supply rail by a short length of hook-up wire. This will connect the front panel and knobs to the negative supply rail also, and provide a partial shielding effect for the circuit.

Complete the construction by clamping the battery to the bottom of the case, and fit the output connector to the end next to the level control. If you have fitted a trimpot as part of R1 monitor the output and adjust it for best waveform symmetry or minimum second harmonic component, as detailed earlier. 



For the experienced amateur:

# DSB transmitter from junk-box parts

There must be many radio amateurs who have a collection of old components lying idle in the junk box. This article should provide some incentive to turn those components into something useful. It describes a DSB transmitter that is simple to build and uses a minimum of costly components.

by **JIM WALLICH (VK2BNQ)**

36 Darnley St., Gordon, NSW 2072.

Many ideas have come about by chance. The subject of this article is just such a case.

I had intended to build a compact SSB transmitter suitable for both fixed station and mobile use and covering 160, 80 and 40 metres. However, early in the drafting stages I found that my expensive little mechanical filter was missing since moving house from Melbourne to Sydney. I was not prepared to indulge in the extravagance of buying a new one, but what was I to do with this burst of pent-up energy to build something?

It was then that I conceived the idea of making a similar transmitter, but using DSB and with a minimum of costly components. Perhaps some of those forgotten bits and pieces in the junk box could be persuaded to talk.

I first satisfied myself that the reception of DSB would present no problems to anyone with an SSB receiver. However I later found that unless I told anyone I was on DSB, they assumed I was on SSB.

DSB is less efficient than SSB. But for a true comparison of talk-power one should relate AM, DSB and SSB to each other. The two side band signals are superior in every respect, and the performance of this DSB transmitter gives no cause for dissatisfaction.

The design criteria were to be economy, simplicity, reliability and mobility. The result has been an outstanding success and I felt compelled to pass it on in this article to those whose pockets may not be too deep, to those wanting a low-priced compact rig, to the young amateur, and to the maniac like me who just likes to build.

## CIRCUIT DESCRIPTION:

In most respects the circuit follows standard well proven lines, so individual stages will no doubt appear familiar. Two tubes are used in the audio stage, the

second feeding directly into the balanced modulator at low impedance from the cathode. Consequently, there is more than sufficient gain.

The crystal oscillator, V4, uses a crystal on 2465kHz. Any crystal which is within plus or minus 200kHz could be used without affecting coil dimensions or capacitor values elsewhere in the circuit. Beyond this limit I am not prepared to comment. Certainly this and the VFO frequency selections should not be departed from too much, otherwise spurious frequency products will become a problem.

The balanced modulator is straightforward. Although I could not get a matched pair of germanium diodes, the carrier suppression is excellent. In point of fact I have used two quite different types of diodes, though their reverse DC resistance is similar. Output from the balanced modulator is DSB. This is amplified by V3 and fed into a double balanced mixer, V6, where it heterodynes with the output of the VFO.

It is important that the VFO be clearly understood, as it is the heart of the design. The VFO coil can be switched to three separate bands of frequencies which, when mixed additively or subtractively with the crystal frequency, will give output on the required band.

Construction must be rigid to ensure freedom from mechanical movement and frequency shift, particularly as the switches are part of the frequency sensitive circuits. For this reason, it is recommended that heavy gauge aluminium be used for both screening and the chassis.

The plate circuit of the VFO is tuned by L2 to ensure plenty of output. The 330 ohm resistor connected from one side of the 470pF coupling capacitor to ground provides sufficient damping to achieve a flat frequency response over the 1900kHz band.

The VFO is required to cover from

4265kHz to 6125kHz and this is done by arranging a tap so that we can select 4535-4685kHz on one switch position (for 40 metres), and 5965-6165kHz on another position (for 80 metres). The 160 metre band is covered by using the third position of the switch, to bring in additional capacitance such that the VFO covers 4265-4325kHz.

The output of V6 is to a band switch to feed three separate coils, one for each band. The primary winding of each of these coils is bifilar wound.

The driver stage is straightforward, as is the power amplifier. However, the 150pF coupling capacitor from SW1E to V7 should be located in the same compartment as V6, away from the V7 plate circuitry associated with SW1F. The lead to the grid of V7 should be screened right up to pin 2. It would even be worth extending the screening over the pin. Earth both ends of the shielding.

Power supply requirements have been met by a 350-0-350V mains transformer with a 150mA rating. Diode bridge rectification was used, giving an off-load voltage of 800V and an on-load voltage of 660V (HT1). The centre tap provides 340V off-load and 300V on-load (HT2).

The transmitter has been designed for either 6V or 12V heater supply, depending upon your mains transformer. The appropriate wiring details are shown in the circuit diagram. Relays may be 6V or 12V.

Bias is obtained in my case by using a small speaker output transformer connected back-to-front and using a 3V tap in the mains transformer. In this way I get -250V bias.

## COMPONENTS:


The choice of components such as resistors and capacitors was dictated largely by size. No special thoughts were given otherwise. Resistors were ½W, capacitors can be disc ceramic or plastic






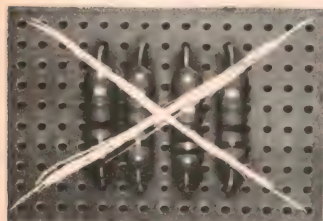
# How to cut costs on your valuable P.C. board real estate...



## use type GLP miniature resistor.

IRH Components introduces the Metal Glaze type GLP resistor, a miniature  $\frac{1}{2}$  watt, with a maximum surface temperature rise of  $50^{\circ}\text{C}$ , the physical dimensions of many other  $\frac{1}{8}$  or  $\frac{1}{4}$  watt resistors but a full  $\frac{1}{2}$  watt rating at  $70^{\circ}\text{C}$  ambient.

The smaller size allows .4" (10 mm) lead spacing as standard for horizontal printed circuit board mounting — reduces demand on expensive PC board real estate. Even greater packaging density can be achieved by vertical mounting.

Another IRH "FIRST," the Australian made GLP is a result of extensive research, development & testing for Australian conditions.

STOCK THE GLP resistor and you automatically stock  $\frac{1}{8}$  watt,  $\frac{1}{4}$  watt and  $\frac{1}{2}$  watt and significantly reduce your resistor inventory. USE IT with confidence.

**irh**  
**COMPONENTS**

DIVISION OF NATRONICS PTY. LIMITED  
The Crescent, Kingsgrove, N.S.W. 2208. Tel. 50 0111  
74 Reglan Street, Preston, Vic. 3072. Tel. 44 5021



### GLP FEATURES INCLUDE:

- Low cost.
- Small size. Length 5.5 mm  
Diameter 2.0 mm.
- $\frac{1}{8}$ ,  $\frac{1}{4}$ ,  $\frac{1}{2}$  watt rating.
- Thick film reliability.
- 60/40 plated leads for excellent solderability.
- Solvent resistant coating and colour bands.

To: IRH components, The Crescent, Kingsgrove, N.S.W. 2208

Please forward your engineering bulletin featuring the GLP resistor.



NAME.....

ADDRESS.....

.....POSTCODE.....

GLP/76



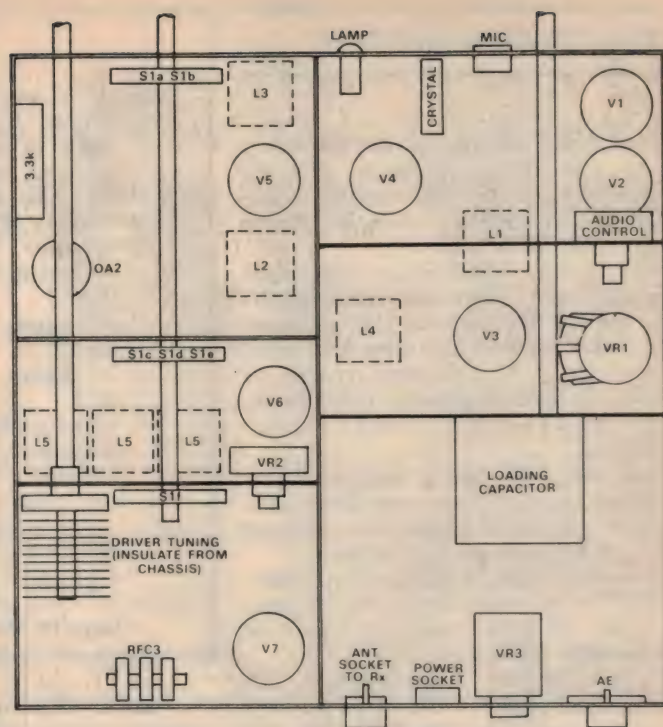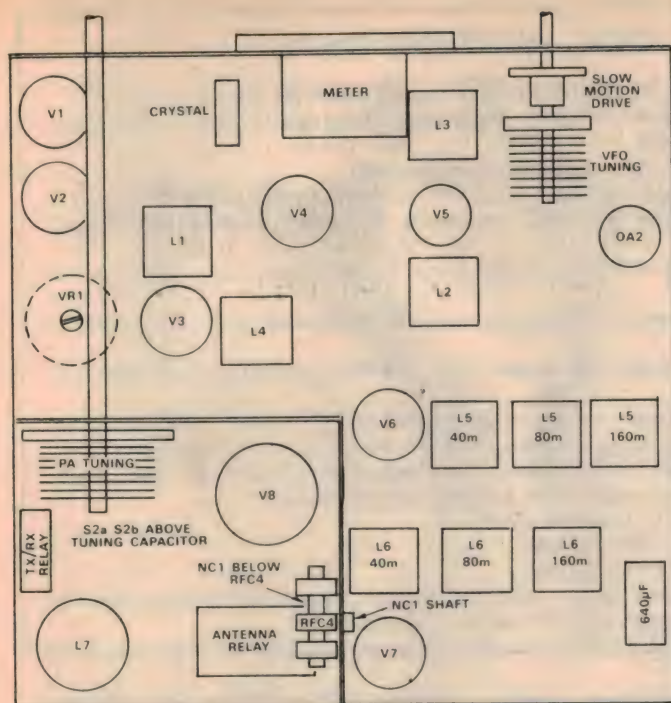

The above-chassis and below chassis component layouts are shown at left and right respectively.

encapsulated. Where this generalisation is departed from, a note is shown on the circuit diagram.

Coil formers are 0.3" Alladin, except in the case of L7. The 160 metre coil L5 is a 2 1/4" type whereas all the rest are 1 1/4" long. All RF chokes are standard receiver type, the only considerations being that where applicable they can carry the current involved (RFC4), and that the same type should not be used in both the plate circuit and the grid circuit of the same valve.

Switches are obviously a vital part of this design. Following is a run down of the various switches used:

- SW1A and SW1B is a double pole triple throw switch on the same wafer, and is contained in the VFO compartment;
- SW1C, SW1D and SW1E are contained in the balanced mixer section. If possible get a single wafer triple pole triple throw, otherwise you may have to use 2 wafers as I did.
- SW1F is contained in the driver compartment. This and all the previously listed switches are ganged.
- SW2A and SW2B are contained within

the PA section, above the chassis. They should be single wafer double pole triple throw and should be capable of handling the strong RF circulating.

#### VARIABLE CAPACITORS:

The 50pF VFO tuning capacitor should obviously be a mechanically sound component, free of backlash. The 100pF PA tuning capacitor used was an old receiver type. The spacing therefore cannot be described as wide, but it is not as close in as for normal ganged tuning capacitors. The object is to find a compromise between maximum capacitance, minimum acceptable spacing and overall physical size.

The loading capacitor used was a twin ganged 350/350pF. Use a 500/500pF if you have one of small enough size or, better still, a 500/500/50pF.

#### LAYOUT AND CONSTRUCTION:

This article would be too lengthy if I were to go into detail on the subject of layout. I will therefore confine my remarks to the most important points.

The accompanying diagrams show the chassis layout. Not illustrated are SW2A and SW2B which are placed directly

above the PA tuning capacitor. Likewise for NC1 which is secured to the PA compartment screen below RFC4, with the spindle passing through towards V7. The loading capacitor is placed underneath the chassis.

The underside of the chassis is divided into screened compartments by a grid or honeycomb which was pre-cut, drilled (for switches, feedthroughs, etc.), and then assembled and fixed into the chassis.


Various controls are fixed onto this grid of screens. For example, the audio gain control passes through one screen such that the potentiometer is on the audio side while the spindle extends into the balanced modulator side. Similarly, VR2 is mounted under the chassis, and the bias control VR3 is mounted on the back skirt of the chassis with its spindle protruding to the rear.

I spent considerable time planning the layout of each stage to avoid a bird's nest. I recommend the trouble as time well spent.
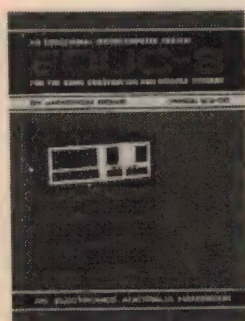
#### VFO CONSTRUCTION AND ALIGNMENT:

The VFO must be sturdy to avoid frequency shift. The slightest movement of a wire or a screen will shift the frequency. All screens should thus be of heavy gauge aluminium and all interconnecting wires in this section free from movement.

The selection of components such as TR1 and its associated padder, TR2, and the negative coefficient capacitor C1 will have to be made by trial and error as these are dependent upon layout, the coil, and stray capacitance. The values given below are a basis from which to start, and are those finally used by myself.



### EDUC-8 COMPUTER SYSTEM

The latest addition to our handbook series brings the published articles on our EDUC-8 do-it-yourself computer system together inside a single cover. It also provides additional information, including how to expand the memory, arithmetic and input-output facilities. If you haven't started building the system, it would make an ideal guide; if you are well advanced, you'll find it makes an attractive and convenient operating manual.

\$3.00 plus 60c p & p

Electronics Australia, PO Box 163, Beaconsfield 2014



## DSB TRANSMITTER

In winding the coil note that the ferrite core enters from the earthy end. As adjustment to the coil must be made from the top of the chassis, the earthy end of the coil is at the top.

To align the VFO, power is switched on at HT2 only. Remember that you cannot remove any valves as this will upset the heater balance. Disconnect the 6146 screen supply. A calibrated receiver or other accurate frequency determining device covering the VFO range is required.

Set the VFO tuning capacitor to 5 degrees open (i.e., at nearly full capacitance). Alignment should now proceed on a step-by-step basis as follows:

(1) Switch to the 7MHz position. Solder a 47pF N750 capacitor into the C1 position and adjust the core to get the circuit to oscillate at 4535kHz.

(2) Switch to the 1.8MHz position. Solder a 220pF capacitor into the C2 position and adjust TR1 so that the circuit will oscillate at 4265kHz.

(3) Switch to the 3.5MHz position and adjust TR2 for oscillation on 5965kHz. It may prove necessary to add extra capacitance across TR2.

As the aim is to get all bands to commence at the same point on the dial, it will be appreciated that failure to achieve this by the above steps will entail further experimentation with the values of C1, C2 and the padder across TR2.

### TRANSMITTER ADJUSTMENT:

Unlike the more general method of lining up, I prefer to start at the initial stages, i.e., the oscillators, and work forward. You will require a VTVM with an RF probe, and a meter capable of reading 1500V. Proceed with alignment as follows:

(1) Disconnect HT1 supply and 6146 screen supply.

(2) Turn audio gain to minimum.

(3) Switch to 7MHz.

(4) Check V4 for oscillation and adjust L1 for maximum RF output.

(5) Place RF probe at junction of D1 and

## COIL WINDING DATA

Coils L1, L2, L3, L4, L5 and L6 are wound on 0.3-inch Alladin formers.

L1 — Primary 70 turns 36 SWG; secondary 25 turns 36 SWG wound over centre of primary.

L2 — 56 turns 36 SWG, enamelled, close wound.

L3 — 28 turns 29 B&S, tapped 11 turns from earthy end of winding.

L4 — Primary 70 turns 36 SWG; secondary 70 turns 36 SWG wound over primary.

L5 — 160 metres: primary 85 double turns 32 B&S; secondary 40 turns 32 B&S.

80 metres: primary 40 double turns 32 B&S; secondary 20 turns 32 B&S.

40 metres: primary 25 double turns 29 B&S; secondary 25 turns 29 B&S.

Primaries are bifilar wound, meaning that two wires are wound on at the same time next to each other. Thus 85 double turns = 170 turns total. The start of one wire is joined to the finish of the other to form the centre tap. Insulate secondary from primary with thin paper.

L6 — 160 metres: 140 turns 40 SWG.

80 metres: 95 turns 32 B&S.

40 metres: 50 turns 29 B&S.

L7 — 49 turns 20 SWG on a 1-inch coil former, tapped at 25 turns and 15 turns for 80 metres and 40 metres respectively.

D2. Adjust VR1 for minimum reading (should be about mid-way position).

(6) Turn audio gain up  $\frac{1}{2}$  to  $\frac{1}{2}$ ; place RF probe at pin 8 of V2. Check for increase on modulating with voice.

(7) Check V5 is oscillating.

(8) Place RF probe on V6 side of 470pF capacitor from V5. Adjust core of L2 for maximum.

(9) Short out L3. Turn VR1 fully one way to upset balance. Place RF probe on pin 7 of V3, adjust L4 for maximum, open short on L3.

(10) Place RF probe on secondary of 40 metre band coil, L5. Adjust core of L5 for maximum. (I recommend that at this stage coil cans be omitted so that coils can be dipped to the right frequency in circuit, and actual output frequencies readily checked.)

(11) Place RF probe on same point as for step 10. Adjust VR1 for minimum reading. TR3 is not at this time connected into circuit. Touch each side of VR1 with an insulated screwdriver and connect TR3 to the side which causes a further drop in the reading. Proceed to adjust TR3 and VR1 in conjunction to obtain minimum

reading. (TR3 = Philips 30pF concentric + extra capacitance if required.)

(12) RF probe as for step 11. Adjust VR2 for minimum reading.

(13) Detune L2 and observe if reading for step 12 is reduced further. (A sensitive receiver with an S meter can be more revealing at this point than a VTVM.) Detuning L2 reduces the injection voltage into V6. An optimum point will be reached where the residual carrier cannot be reduced further without substantially reducing the output on modulation. At this point, measure the RF voltage at the V6 side of the 470pF coupling capacitor from V5. Select R1 to give this voltage when L2 is peaked at maximum.

(14) Place RF probe on pin 5 of V8. Adjust 40 metre coil of L6 for maximum on modulation (or unbalance VR1 again instead of modulating). The driver tuning capacitor should be half open. Readjust L4 and L5 for maximum reading.

(15) The HT1 supply and the 6146 screen supply should now be reconnected. Plug in a suitable 75 ohm dummy load. Switch on and adjust VR3 for standing current of 12½mA (VR1 at maximum carrier suppression).

(16) Retune L6 40 metre coil for maximum whilst modulating.

(17) By careful layout, neutralising has been found unnecessary. If required, the process of neutralising can be carried out in the normal manner.

(18) Tune PA tuning capacitor for dip, and increase loading capacitor to give a peak current of 112mA.

The set is now operational on 40 metres. An abridged version of the above process is used to tune the transmitter to 160 metres and 80 metres.

Finally, the accompanying tables give a complete list of coil details and a range of helpful voltage measurements. This should complete the information necessary to enable the experienced amateur to duplicate the design.

## TABLE OF VOLTAGE MEASUREMENTS

	With Push To Talk OFF	With Push To Talk ON	PTT on and with Modulation*
High HT	800V	660V	580V
Low HT	340V	300V	250V

\*This indicates over-running of mains transformer, but is acceptable

RF probe on V4 anode: 1V

RF probe on junction D1/D2: negligible no modulation; with modulation 0.2V

RF probe on V5 anode: 160 metres 1.2V; 80 metres 0.8V; 40 metres 1.1V


RF probe on V3 anode: no modulation 0.1V; with modulation 1.7V

RF probe on L5 secondary: no modulation 0V; with modulation 1.6V

RF probe at tap of L6: no modulation 0.2V, depending upon degree of carrier balance

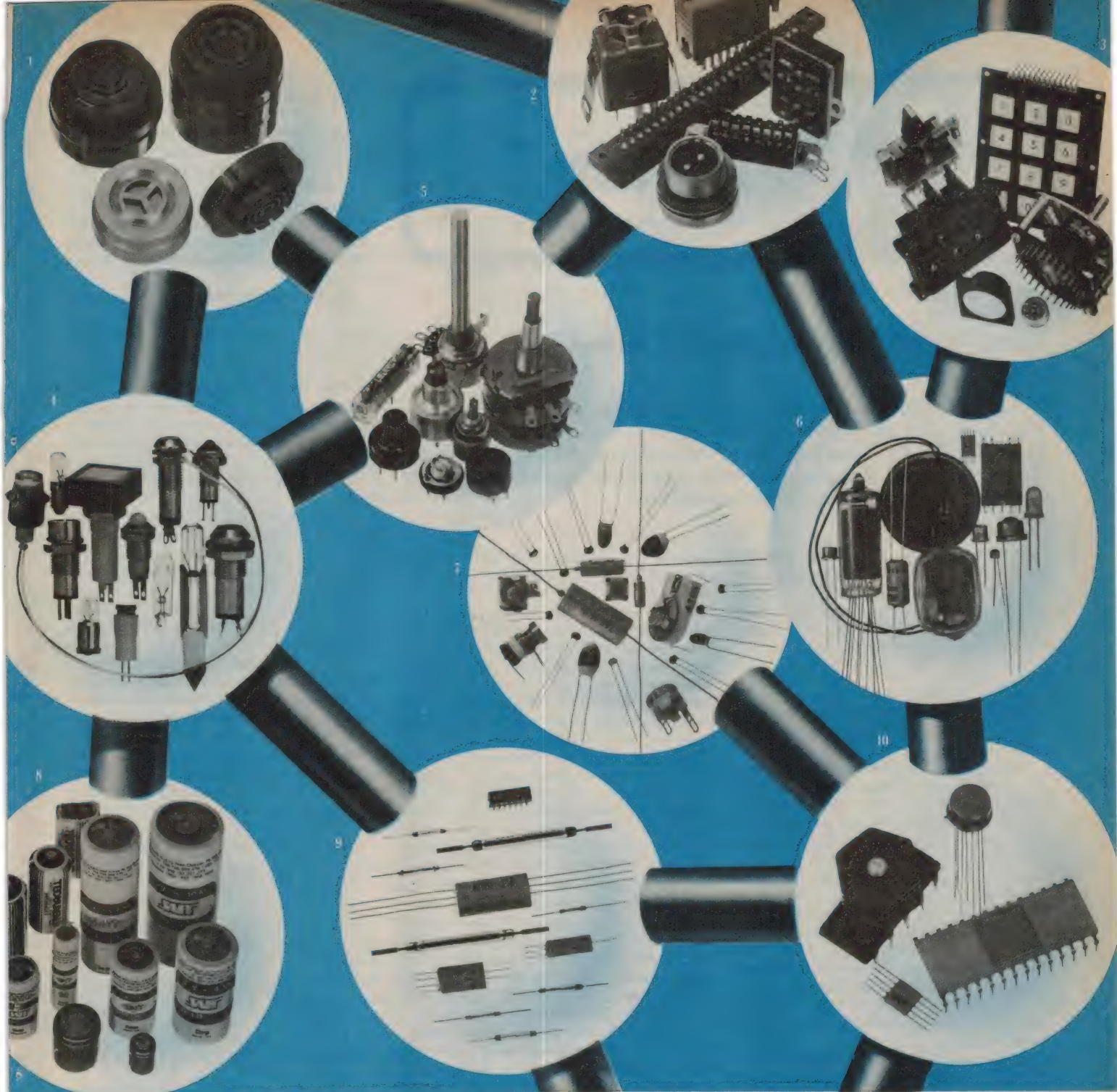Bias: on "Receive" -250V; on "Transmit" -55V





# An integrated nuclei of quality.

Plessey brings you today's most advanced, professional components from leading international manufacturers. JFD, Mallory, EECo (USA), OKI, Okaya-Rodan, NEC, Kokusai (Japan), SAFT, Sloan (Europe) and Painton, Hivac (UK) are just a few of the many renowned names represented by the Plessey Professional Components Division.

A basic cross section of the wide range available through Plessey and its agents is depicted above and includes: —

- 1/ Sonalerts electronic audible signals
- 2/ Connectors P.C. edge, multi-circuit, heavy duty, BPO and DEF approved
- 3/ Switches rotary, lever key, thumbwheel, touch-activated (incl. illuminated)
- 4/ Lamps & indicators filamentary, neon and LED styles
- 5/ Potentiometers moulded carbon track and wire-wound of both commercial and professional standard
- 6/ Optoelectronic devices LDR's, LED's, photodiodes, phototransistors, photocouplers and 7 segment, alphanumeric and cold cathode displays
- 7/ Capacitors tantalum, electrolytic, chip ceramic, variable ceramic, precision piston trimmers
- 8/ Batteries nickel cadmium (rechargeable) and lithium (primary)

- 9/ Dry reed inserts and relays
- 10/ Microelectronic I.C.'s communication, audio and power control styles, MOS devices,

high speed dividers, microwave devices (X-band etc.)

**PLESSEY**   
Plessey Australia Pty Limited  
Components Division  
Box 2 PO Villawood NSW 2163  
Telephone 720133 Telex 20384

Melbourne Plessey Australia Pty Ltd 42 3921  
Adelaide K.D. Fisher & Co. 223 6294  
Brisbane L.E. Boughen & Co. 370 8097  
Perth H.J. McQuillan Pty Ltd 68 7111  
N.Z. Henderson (N.Z.) 6 4189

Please send me more information on items ticked

1 ☐ 2 ☐ 3 ☐ 4 ☐ 5 ☐ 6 ☐ 7 ☐ 8 ☐ 9 ☐ 10 ☐

Name \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_  
Post Code \_\_\_\_\_

**COUPON**





## Time is running out for BC band DX

In terms of topicality, the letter reproduced below is about two months out of date, because it refers to material published in our 1975/6 Year Book. However, it raises a matter which is overdue for discussion—the changing attitude of the administering authorities, and of Government to the role of radio stations in the community.

Before getting on to this matter, however, it may be as well to reproduce, and comment upon, that part of the letter which refers to the Year Book, published in mid-December. The letter, by the way, comes from P.D. of Melbourne:

Dear Mr. Williams,

I am writing to you to comment on several articles which appear in the E.A. Yearbook.

Firstly, congratulations on the Book. It is so good to see that you have kept the high standard of your magazine and produced original articles, rather than a selection of reprints from the past year, as some overseas journals seem to do.

I am also glad that the Yearbook continues a list of Broadcasting Services. As a correction, the frequency of the ABC FM station in Melbourne will almost certainly be 105.7MHz, as tests on the previous frequency showed interference with a channel 5 repeater. There may also be frequency changes in other cities, as I believe that problems have arisen elsewhere.

As indicated in your listing, 3MBS-FM started transmitting on a frequency of 92.5MHz, but the power has since been increased considerably and is now 4kW ERP. When the power was increased, there was a considerable amount of TVI to both channel 0 and channel 7, made worse by the fact that the FM station is not co-sited with the TV stations and there is a large difference in signal strength in the residential area of Kew near the FM station. As a consequence 3MBS-FM has changed frequency to 93.7MHz with significant reduction in the TVI. In retrospect, 92.1MHz was not a good choice. The second harmonic falls within channel 7, and it is the second harmonic of channel 0. Even with the best possible suppression of spurious signals, non-linear tuners still regenerate interfering signals if the FM signal is strong

enough. In addition, there were reports of interference by channel 0 to the FM station.

I notice that you reprint, apparently without credit, the article from the Telecom Australia house journal on the test transmissions for the ABC station here in Melbourne. A pity, I think, because I believe that full credit was not given to all the people involved within Telecom Australia. Also, from a partisan viewpoint, I didn't really like the implication in the heading that said "... music of quite unaccustomed depth, purity and strength" as 3MBS-FM since the increase in power in September to 4kW could fairly be said to provide a strong, pure and deep signal! And despite the remark later in the article 3MBS (not 2MBS, you copied their mistake) has a range considerably greater than 15 miles. It is received well in Geelong. Also, in addition to the test periods indicated which actually seem to be on the weekend as well as weekdays, the ABC station has music tests each afternoon.

The article is, I'm afraid, a good example of what happens when a journalist with no apparent technical background attempts to cover a technical subject, and I'm a little surprised you printed it unchanged.

In central Melbourne and the Camden-Campbelltown areas the BCB has awarded non-commercial licences for stations which are commercial within the terms of the Broadcasting and Television Act but which will not have regular commercials. I believe 3CR, run by the Community Radio Federation, will start broadcasting early in the new year on 840kHz.

I'm intrigued by your reference to "open hostility flaring in Melbourne" because of deep seated differences? Do you refer to the differences over the suitability of the ABC as a body to take the reins of an access station like 3ZZ, or

perhaps the reported suggestions that 3ZZ might be replaced by a station with a 2JJ type format?

The points you raise about commercial viability are of course valid, but I think that there are strong counter arguments. In North America, in what I believe would be called "markets" of equal size to our major cities, there are many more radio stations than we have, suggesting that at least there is a capacity for some increase here.

Special interest stations, be they for an ethnic audience, serious music lovers or lovers of jazz, would not necessarily attract listeners from existing stations but might provide a service for people who do not listen to radio now as their favourite form of listening is not available. Special interest stations could be funded by commercials, by business sponsorship or by listener subscription, and need not be a drain on government funds.

As you point out, for a long time the question of broadcasting was put in the "too hard" category. The Minister for the Media, Dr Cass, received a report of an investigation into public broadcasting he commissioned shortly before the recent upheavals. I hope that this will be given due attention.

As a final comment on your article, I think that the pattern of broadcasting on 3ZZ Access Radio since it started in Melbourne do not support your remarks. As I have heard it, access radio has been at times unprofessional, at times boring but also at times illuminating. It certainly in no way has become a facility providing a rostrum for "irrational or obscene" individuals.

Thanks for your attention to my comments, and an interesting magazine.

P.D. (Melbourne)

First off, we are glad that P.D. (and others) appreciated our efforts with the Year Book and, in particular, the emphasis given to radio and television broadcasting. If there are errors and omissions in the station list, we can only apologise and will hopefully seek to eliminate them when the list is up-dated next time around.

It sounds like a very simple assignment to compile a list of stations, locations and frequencies and perhaps it would be if it were not just one of a multitude of tasks to which our staff have to address themselves. The problem is that official lists are usually many months out of date and it isn't easy to keep track of changes particularly, as at the end of last year, when they were being promoted by other than the usual authority!

The interference problems between FM and TV, mentioned by our correspondent, generate yet another hazard to published lists and the saga is likely to continue as new FM stations come progressively into service. The Broadcasting Control Board warned that problems would arise, but they now have



to find ways around them. Unfortunately, potential solutions have to be tested by trial and error because so much depends on how interference-prone the receivers are that are being used by Mr Everyman on Everystreet!

And the story on Melbourne's unexpected FM broadcaster? Yes, it did come from the Telecom house journal, from which we also obtained the pictures. Omission of the credit line was perhaps a minor oversight, but the article did carry its own credit to the organisation. We reprinted the item because of its potential interest and the fact that it fitted neatly into the context of the Year Book. Perhaps a few phrases were somewhat "journalistic" and perhaps the credit was not spread as widely as our correspondent thinks appropriate but we judged it to be interesting, nevertheless.

And that brings us to the second part of the letter which calls for more lengthy comment:

*I hope you will not mind if I mention a few points suggested by your accompanying article "Radio will change in '76". In addition to the factors mentioned in your article, I think that there was one other very important influence in broadcasting in the past year. This is the opening of the MF band to many more stations.*

As you will recall, the Broadcasting Control Board in a surprise announcement towards the end of the independent inquiry into FM said that it would be possible to double the number of AM stations in Australia: interesting as, for many years, it had been said that there was little room, especially in south-eastern Australia, for more stations.

I have not seen any journal articles or papers outlining the basis for the new policy, but from various public talks it would seem that this is made possible by advances in technology and a changed policy.

The new policy talks in terms of a defined service area. The station (national, commercial and especially community) is given a defined area to serve and the signal is tailored to serve this area alone, generally by the use of multi-array directional antennae. Thus the existing clear channels, until recently enjoyed by the majority of capital city stations, will give way to re-use of the same frequency several times, with directional arrays protecting the stations sharing a common frequency within their defined service areas.

This new policy is closer to the U.S. FCC policy for AM, which classifies frequencies into usage categories, ranging from "clear" channels serving large areas by sky-wave to local channels with over a hundred stations sharing a single frequency, with low power and very limited service areas.

I believe that the licensing of new commercial stations in and around Sydney and Melbourne and the new experimental stations you mention are part of the

opening of the MF band. In addition to the ethnic stations you mention, and 2JJ, there are several other new stations that perhaps, political events willing, indicate possible changes in broadcasting. The university station 5UV in Adelaide has come in out of the cold, and though not shown on your list is now on the main AM band. It is broadcasting access, music and student programming and perhaps will be typical of the University and college stations recently given experimental licences (such as 4ZZZ-FM in Brisbane).

While all this is being turned over again in March, what appeared in the Year Book was actually written some time in October last (in between other jobs) and when a change in Government was being viewed merely as a possible complication. The article reflected the uncertainty, the apprehension and the undercurrents that characterised the broadcasting scene at the time. Details aside, the broad comment still stands, as also does the main thrust of the article and the end of the editorial in the front of the book: the need to "sort out what has happened and to evolve workable—if compromise—plans which will give a sense of direction to everyone involved".

(As we go to press, a new factor is entering the scene—an economy drive by the Government which is likely to slow up the process of change in any direction!)

The announcement by the Broadcasting Control Board suggesting the availability of more channels in the medium-wave broadcast band was interpreted by many as a clumsy about-face occasioned (1) by political pressure and/or (2) by technical pressure from the then-current FM inquiry.

Pressures there were, and it may have seemed like an about-face, but it did not herald the discovery of any new technical capacity for more stations. It was essentially a formal acknowledgement of a gradually changing attitude to band usage.

The early objective of medium-wave planning in Australia was to give as many stations as possible a unique frequency, so that their audience could be as wide as possible. Listeners took pride in the number of broadcast stations they could tune in successfully and station engineers derived their own special pleasure from long-distance reception reports. There had to be something rather special about a transmitter which could be picked up thousands of miles away!

Gradually, however, provincial listeners began to tire of their battle with daytime static and night-time fading and to agitate for their own regional and local stations—even if they had to share frequencies with stations in other states. So the process began: an audience shift away from distant big-city transmitters to local stations.

Paralleling this were two other impor-

## FREQUENCY RESPONSE EXPLAINED

Frequency response is the range of frequency in the audio spectrum that a unit will reproduce accurately. Frequency response is just one of the many such terms explained in "The New, Improved, Updated, More Detailed Hi-Fi Explained in Simple Language by Kenwood Booklet". It will make hi-fi specifications and terms much clearer. Because when you know more about good hi-fi, you'll be better able to appreciate Kenwood hi-fi.

## WHAT GOOD HI-FI IS ALL ABOUT.



## KENWOOD

We want you to know what good hi-fi is all about, so we are giving you our booklet absolutely free. This is a complete dictionary of hi-fi terms and explanations and is available at your nearest hi-fi specialist, displaying the Kenwood sign.

Distributed and serviced in Australia by Jacoby Mitchell Company.

Head Office: 215 North Rocks Road, North Rocks, N.S.W. 2151. Telephone: 630-7400


JM 250





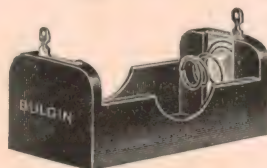**EDDYSTONE RECEIVERS**

The word Eddystone is synonymous with quality communications receivers used throughout the world. 10 KHz to 870 MHz. (Send for a short form catalogue).




**BULGIN BATTERY HOLDERS**

In this day of battery operated equipment some device to hold batteries is essential from 1 to 3 cells in popular sizes.



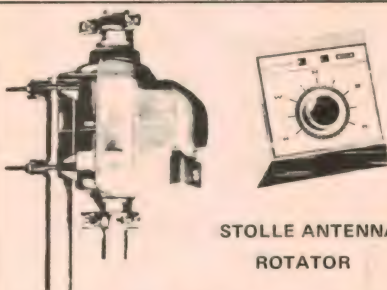**EDDYSTONE DIE CAST BOXES**

Made of diecast aluminium. Ideal for screened boxes or instrument cases. 6 sizes to choose from.




**STOLLE ANTENNA ROTATOR**

An antenna rotating device where the motor and support bearing are mounted on the antenna mast and the control unit on the equipment operating table.



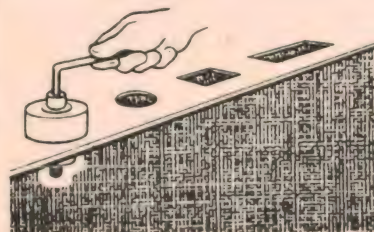
**SENNHEISER HEADPHONES**

The Sennheiser "Open-aire" stereo headphone range needs no introduction to Hi-Fi or professional users. These headphones not only have exceptional reproduction (20-20,000 Hz) but weighing only 5 oz they can be worn for long periods without fatigue.



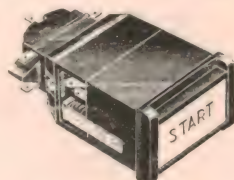**Q MAX CHASSIS CUTTERS**

This cutter is made from tool steel and will give exceptional life. Sizes 3/8" diam. to 3" diam., plus 1" and 1 1/16" square, and 21/32" x 15/16" rectangular.



**BULGIN SWITCHES**

There is one for nearly every application, from instruments to control units. Fully illustrated in the Bulgin catalogue available on request.




**PASO AMPLIFIERS**

A complete range of PA equipment from the mike to the speaker through amplifiers, mixers, etc. is available.



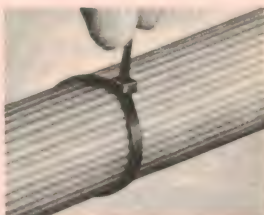**BULGIN FUSE HOLDERS**

There is a Bulgin fuse holder for practically every type of installation including open, screw-in fuse cap, line cord, etc.



**PANDUIT WIRING COMPONENTS**

Cable harnesses must be tied, hung, mounted, identified and ducted. A full line catalogue is available upon request.



**SONNENSCHN BATTERIES**


Lead-acid, sealed, rechargeable batteries from 2 to 12 volts and up to 36 Amp-hour capacity.



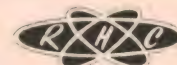**SENNHEISER CONDENSER MICROPHONES**

Transistorised microphones of the Sennheiser type are capable of coping with the most difficult problems. A microphone of wide frequency range, exceptional directivity, and more than adequate output.

Cunningham Components are available through Wholesale Houses or direct from any of the following branch offices:



Ring or Write for Cunningham Illustrated Catalogue.

**R.H. Cunningham**  
Pty. Ltd.

VIC.: 493-499 Victoria St., West Melbourne, 3003. Tel.: 329 9633  
N.S.W.: 4-8 Waters Rd., Neutral Bay, 2098. Tel.: 909 2388  
W.A.: 65 Balcombe Way, Balga, 6061. Tel.: 49 4919  
QLD.: L.E. Boughen & Co., 30 Grimes St., Auchenflower, 4066. Tel.: 70 8097

Telex: Melbourne 31447, Sydney 21707, Brisbane 41500



## FORUM

tant factors. The management of commercial stations began to realise that, from the viewpoint of an advertiser, the audience that really mattered was the one within commuting distance of the station—not scattered individuals and DX-ers out in the sticks! They had their own local station and their own local suppliers.

And, on the technical front, engineers had to concede that an aerial system which produced strong sky-waves and DX reports, did so by diverting that energy from the local ground wave. In this respect it was a liability.

As a result of all this, over many years, we have seen a gradual increase in frequency sharing, a gradual increase in the number of broadcast stations, and increasing use of aerial systems emphasising local coverage.

What the Control Board did, a few months ago, was simply to spell out what would be possible if this already established trend was to be carried to some kind of a conclusion. By confining each station's "rights" to a more rigidly defined area, many more transmitters could be accommodated in the same spectrum space.

However the Board's statement may have been misinterpreted by some at an emotional level, the broadcasting industry was under no illusions: one way or another, the "cake" was likely to be cut into smaller pieces!

Two propositions emerged from the debate, both with the potential to increase band occupancy: (1) more extensive sharing of existing channels and (2) sharing, plus a reallocation of frequencies on the basis of 9kHz separation.

That was all before the change in Government. How the present administration will react is anybody's guess but my tip is that it will (1) confirm the status of the Broadcasting Control Board and (2) have the Board inquire into the need for more local stations and the implica-

tions of that recommendation on band usage.

We would expect that the desirability or otherwise of more medium-wave stations will be decided primarily on social, commercial and economic grounds, with band occupancy a largely consequential result. We doubt that much thought will be given to the DX enthusiast who likes to log and listen to stations outside his own area.

We do wonder, however, whether the position could also become hopeless for the genuinely isolated listener and for tourists with car radios who tend to rely on a few, powerful, interference-free signals. After all, one doesn't want to spend the whole of one's life listening to cassettes!

## THE NOISE PROBLEM

A rather grim corollary to all this is typified in the letter from a reader in Earlwood, NSW: the problem of interference from TV receivers. He mentions switched-mode colour sets in particular but the problem is much older than that, going back to the line deflection circuits of quite ordinary monochrome receivers. Maybe TV sets don't radiate far but, when there's one in every house in every street, they don't have to, to make their presence felt!

Add to TV receivers the ever-increasing use of thyristor type speed controls and light dimmers, plus an array of other electrical and electronic gadgetry, and we have a seemingly irresistible, rising tide of man-made RF interference.

Administrations can legislate against flagrant abuse of our electromagnetic environment but the tide still continues to rise. More transmitters, more powerful transmitters, improved technology will certainly maintain our local communications but we can only look back wistfully to the days when the main hazard to radio reception was the gently undulating ionosphere and the occasional thunderstorm.

Maybe those days have gone forever, along with many other aspects of a less technological age.

## INTERFERENCE FROM TV SETS

Dear Sir,

I would like to raise the question of side effects associated with the switched mode type of power supply coming into increasing use in large screen colour television receivers.

The problem with this type of supply is the interference generated by the switching action. Although the manufacturers take considerable trouble to screen the supply and use of a considerable number of suppression components, my own experience suggests that the interference problem is still significant.

In the city of Wollongong it is difficult to use a broadcast band receiver, tuned to a Sydney station (50 odd miles away) when the household TV receiver is in use. Even in my own home in a Sydney suburb, I notice objectionable interference on the weaker stations from my own switched-mode TV receiver. I feel that the situation is moving rapidly towards what you mentioned in the August "Forum", with A's TV receiver affecting the radios of B and C, as well as his own.

L.H. (Earlwood, NSW)

## printed circuits

- Accurately machine printed/etched.
- Phenolic & fibreglass-gold/tin plated.
- Special manufacturers' packs of 10.
- EA, R & H, ET, Philips. Mullard available.
- Specials to your drawing
- Plus post 50c Imm despatch.

76E02	2.50	75SW11A	2.80	DRS-RC1	4.00
75PC12	2.50	EA76F1	2.80	ET1534	2.00
ET144	2.00	ET1129	2.50	ET28	2.50
ET1439	3.00	ET14206	2.20	ET123B	2.20
ET123A	2.20	ET1119	2.60	75F2	2.50
75L11	2.50	ET1438	2.50	75V12	2.50
75F12	2.80	ET11124	2.50	ET1122	3.00
75CL9	2.00	75PC12	2.50	ET121	2.00
ET1120	2.00	ET1118	2.50	ET1117A-B	2.80
ET1704	2.50	ET1500	2.00	75T19	2.00
75R7	3.00	75CD7	2.50	75FM5	2.50
75T10	3.50	75FE5	2.00	75T16	5.00
75T09	3.50	ET1533A-B	2.50	ET1440	4.50
ET1400	2.00	75W3	2.00	ET1532	2.20
ET1529B	3.30	ET1529A	4.50	ET1702	2.50
ET601R	2.80	ET601P	2.50	EB5RT	3.00
75E6	2.50	75SD4	2.50	75A01	2.50
ET14AE	2.50	ET41402	3.20	ET430	2.00
ET314	2.00	ET116	2.50	EB8	3.00
EBK1	3.00	ET528	2.00	ET312	3.00
75D1	2.50	74MX12D	3.50	74MX12C	2.80
74MX12B	3.20	74MX12A	2.60	ET701	2.50
ET527	2.00	ET428	2.80	ET313	2.50
ET530	2.00	ET427	2.50	ET426	2.00
74MX8	2.00	74EM9	2.50	74T08	2.50
ET429	2.20	EBX	5.00	EB10T	5.00
EBP	5.00	EBM	5.00	EBD	5.00
EBA	5.00	EBT	5.00	EBF	6.00
EBG	6.00	74C5	4.20	74D8	4.00
ET424	2.50	ET311	2.50	ET528	2.50
ET114	2.50	74SA5	4.00	ET601M	2.50
ET601L	2.50	ET422	3.30	74S3	2.50
ET601J	3.00	ET423	2.20	ET420F	3.30
ET521B	2.00	ET601H	2.50	ET601G	2.80
74A1	2.20	74HPL	2.00	7312T	2.80
ET601D	2.20	ET601C	2.80	ET420C	2.40
ET420D	2.40	ET420B	2.80	ET420A	2.20
ET524	2.80	ET601B	3.30	ET601N	3.30
ET601F	2.80	ET601E	3.90	ET601A	3.30
73T11	2.80	73P11	2.80	ET520A-B	4.40
73C12	4.90	73BA9	2.80	ET113	3.10
ET419	2.20	ET218	3.50	ET137	1.70
ET309	2.80	ET414D	1.30	73T07	2.80
73S6	1.30	ET521	3.90	ET213	1.10
ET418	3.30	73D1	1.70	ET518	2.20
733C	2.80	73T1	2.80	ET414C	2.80
ET414B	2.80	ET414A	2.80	72M12	2.80
72SASB	2.80	ET413	2.80	ET034A	3.10
72S11	2.80	72G7	2.80	7210	1.30
7211T	3.30	ET037-40	6.00	72SA10	3.10
72C8	2.80	ET029	2.20	72S10	2.80
72R9	2.80	72SA9	2.80	ET033	3.30
72MX8	3.10	72T3	3.30	ET026	2.80
721F6	2.20	71A8	2.80	72P3	2.20
72R2	2.80	72T2D	2.20	ET023	2.80
ET021	2.80	72T2A-B-C	4.40	73V1B	3.30
73V1A	6.60	72SA1	3.30	71C12	4.40
ET019	2.80	ET018	2.80	ET017	2.80
ET014	2.80	ET007	2.50	71T12	3.30
ET011	2.00	71P8	2.80	72C2	3.90
ET012	2.20	72A6	2.50	72T5B	2.20
ET034	2.90	71SA4C	3.30	71SA4B	2.80
71SA4A	2.80	ET025	2.80	71W7B	2.20
71W7A	2.20	ET003	2.80	71R1	2.50
71D3	2.20	ET005A	2.50	71T02	2.20
70SL1	4.00	70PA1	4.00	70R01	4.00
70TX2	4.00	70F10	2.20	70A2	4.00
ET004	4.00	70CD1	2.20	70G7	2.00
70P6	4.00	71A8	2.50	70K6	4.00
70BF08	2.20	70TX1	6.00	70C4	6.00
70C1	4.00	70P1	2.50	69C11	6.00

## ALL SILICON 30/60w PA PORTABLE AMPLIFIER



6 1/2" w x 3 1/4" h x 8 1/2" d.  
12-16v; two inputs; 5 & 100mV.  
No. 763D: 15 ohm output.  
No. 763A: 125, 250, 500 ohm output. All \$70 each. For 240v operation \$103. Plus freight \$2.

COILS and IF's All \$2.50 ea. plus post 50c

RF CHOKES Plus post 50c

381 AIR: 2.5mh 50ma—Pye 70c.

381 IRON: 10uh to 1,000uh 25ma 70c.

FILTERS

27: Line filter 2 amp \$14.

29: Line filter 10/20 amp \$37.50.

Plus Post \$1.50.

30: Pulse filter 2 amp \$12.

MAIL cheque or money order  
(add postage) direct to:—

**RCS radio pty ltd**  
651 FOREST RD BEXLEY  
NSW 2207 587 3491





# The Serviceman

## Batteries — and international standards

One of every serviceman's regular jobs is replacing batteries in a wide range of battery operated appliances—from pocket radios to movie cameras. While this should be a simple task, batteries and battery holders are not without their problems, as a recent incident emphasised.

While it may seem surprising that so many people cannot perform this simple job themselves, the fact remains that womenfolk, elderly people, and even some "with it" types become confused when faced with the task of fitting several cells in a typical battery holder.

Another point which becomes obvious to anyone refitting batteries regularly is that many holders designed to hold groups of cells leave much to be desired. A common problem is that they are moulded from plastic which tends to flow under stress, particularly the stress due to spring type negative contacts intended to ensure reliable contact at both ends. This can so distort the case that the spring pressure is substantially reduced.

Another problem concerns the eyelet style contacts usually used for the positive terminal. Again it seems to be a plastic problem, whereby these eyelets, while tight enough when new, gradually work loose. Since the electrical connection is normally via a lug secured under the eyelet noisy and intermittent behaviour results.

All of which is by way of being general background. What started me on the subject was a most unusual fault in the battery system of a 27MHz hand-held transceiver. It is powered by eight "AA" size cells to provide a nominal 12 volts. The cells are held in a fairly standard plastic holder, in two layers of four, with spring contacts at the negative end and eyelets at the positive end.

I thought I had encountered most battery faults, but this owner's complaint rather rocked me. According to him the batteries were overheating. In greater detail he explained that he had fitted a new set of batteries, only to find that the unit performed poorly while its own built-in battery meter indicated that the voltage was dropping fast. When he removed the cover in an effort to determine why, he realised that some of the cells were quite hot. Without stopping to enquire further he quickly removed the cells, packed the whole lot up, and

sought my help at the first opportunity.

The first thing I did was to check each cell by measuring its voltage across a suitable load. The owner had in fact given me both sets of cells; the ones he was discarding and the new ones intended as replacement. It appeared that the unit was a new one, the discarded cells being

*Australian batteries and cells are made to standards set down by the Standards Association of Australia (SAA), the specific standard being C387-1967. Shown here is portion of an engineering drawing from Union Carbide Aust. Ltd, makers of "Eveready" batteries, of the popular 1.5V "AA" size cell. These dimensions conform in all respects to the SAA specifications. These are based, in turn, on the International Electrotechnical Commission (IEC) standards.*

of Asian make, as supplied with it, while the replacement ones were local "Eveready" types. At least this prevented them from getting mixed up.

The discarded cells read about 1V or a bit less, which was more or less what I expected. Most of the new cells read around 1.4V—again what one might expect—but two of them read only a little over 1 volt, which was rather puzzling.

Next I connected a milliammeter between one terminal on the battery box and the mating terminal on the lead connector, switched the unit on, and then pushed each cell into place. When the last one went in the needle moved up

scale to what I felt was a reasonable "no-signal" reading. But then I realised that the current was falling and I glanced quickly at the set's own meter. It was falling too and, at the same time I realised that the cells were getting hot.

More precisely, it was two cells only, as I realised when I quickly pulled each cell from the holder. This seemed to suggest that the fault was in the holder rather than the set itself. I examined the holder carefully but could find nothing which would cause such behaviour.


So I took a single cell and fitted it into each position in the holder in turn. It wasn't long before I found a position in which the single cell started to overheat; a situation which left no doubt that the holder was at fault.

But what kind of a fault? I could see nothing obvious and the situation was reaching the silly stage. Then I took another look at the cells. The "Eveready" cells had a metal disc on top with a central hole through which protruded the positive terminal. I assumed (correctly) that this disc was part of the leakage protection assembly. The Asian cells had no such fitting, only a red insulating disc.

### "EVEREADY" No. 915

type — Leclanche  
S.A.A. Designation — R6

### DIMENSIONS

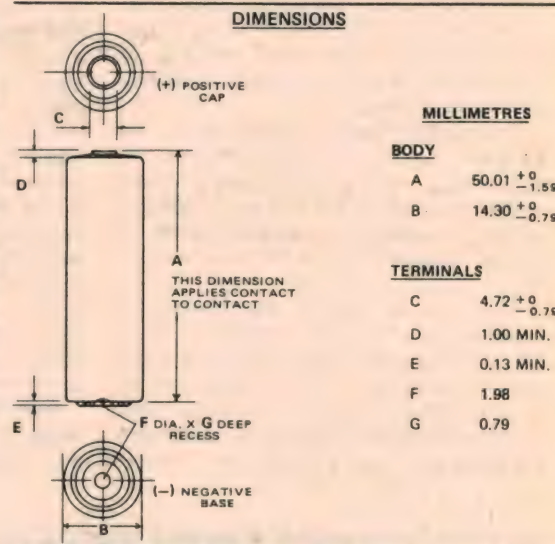

On an impulse I reached for the multimeter and measured the voltage between the positive terminal and the metal disc. It showed 1.5V, clearly indicating that the metal disc was in contact with the outer zinc container of the cell.

That much established I took another look at the positive terminal on the battery holder, then slipped the cell into place again. As I suspected, that was where the trouble was. The opening in the eyelet was large enough to allow both the positive terminal and the metal disc to touch it.

I'm afraid this discovery came as rather a shock, as well as posing a lot of ques-



tions. Did it mean that this equipment could be used only with imported cells, not featuring leak resistant techniques? Did it mean that standards—international standards which are supposed to prevent this kind of thing—had fallen down somewhere? And if so, which was wrong, the battery holder or the local battery manufacturer?

There was also the more immediate question of how to solve my customer's problem—other than by telling him to use only a certain type of battery. I took another look at the eyelets and decided that the margin by which the combination failed was quite fine, which was probably why only two cell positions were faulty.

The eyelets had a marked curvature and it seemed to me that if I could flatten them slightly it would have a twofold effect; the hole into which the positive terminal fitted would be reduced slightly, thus preventing the terminal from penetrating so far, and the flattened eyelet would be further away from the metal disc as well.

In fact, the idea worked, and I was able to send the customer on his way with the reassurance that he should be able to use any cells that he was able to buy anywhere.

But what of my original questions? How had this happened and what had gone wrong? I was so intrigued that I rang someone I knew at Union Carbide, who make the "Eveready" cells, told them what I had found, and asked them could they help.

The result was a very interesting discussion. They were well aware of the problem I had encountered and had already taken steps to prevent it. In fact, in all Australian made cells the metal disc is coated with an insulating material on the underside to prevent it making electrical contact with the zinc case. Under these conditions, of course, no problem could exist.

My friend went on to suggest that the cells I had were probably made in New Zealand. (Sure enough, a quick check on the label confirmed this.) Apparently the local factory had run into production problems, due to industrial disputes, and in order to keep faith with customers, the company had imported a quantity of cells from the New Zealand company. And, for some reason, this factory had not yet adopted the practice of insulating the discs. As soon as this was realised the New Zealand company was advised that all future supplies should conform to this requirement. In the meantime, the first batch was released on the basis that they would still be satisfactory in all but extremely rare cases.

On the broader questions, my friend confirmed that there were international standards, known as the IEC Standards, designed to ensure compatibility between cells and equipment anywhere in the world. These standards were the basis of the SAA (Standards Association

of Australia) standards, and that all Australian cells were made to these standards.

Unfortunately, some Asian manufacturers have tended to ignore these standards, at least in regard to some of the finer points. This applies to both the battery manufacturers and, presumably as a result, a lot of the appliance manufacturers. Thus it is not unusual to find appliances which will not accept the local cells.

(I can confirm this. A colleague has an Asian made multimeter in which the battery holder is just too small to take the local cells, whereas Asian cells are a neat fit.)

According to the Union Carbide spokesman, this has caused a lot of embarrassment, and not only to the local battery manufacturers. Battery companies in Europe and America, who also adhere to the international standards, are just as upset at the situation. Like the Australian manufacturers, they are frequently accused of making incorrect size cells, whereas it is the appliance which is non-standard.

I gather that this situation has developed into something of a battle of wills. The Asian manufacturers have the advantage that they make a very large proportion of appliances now in use. On the other hand, European and American appliance manufacturers are not slow to exploit any suggestion that Asian appliances are non-standard and might create a problem for the buyer.

My friend went on to say that it now appears that the Asian manufacturers are beginning to realise that this situation, while perhaps to their advantage in the short term, could work against them in the long term. Hopefully, this will mean greater design care on their part in the future.

To change the subject, here is a story from a friend who is also in the electronics industry—in fact he has been part of it for longer than I can remember.

He bought a colour set, one of the top locally made brands. While well versed in matters electronic, he did not feel competent to take on this new fangled device and bought a service contract to cover it.

This particular set uses a dial lamp to illuminate the channel selector and, after a few months, this lamp failed. My friend probably could have replaced it, but hesitated to plough through a mass of cables he didn't understand in order to get to it. So he called the makers and had them send a serviceman out.

After the lamp had been replaced the serviceman asked, "Do you have a service contract?" When my friend replied that he did the serviceman commented, "Just as well. Otherwise I would have had to charge you \$25."

"You're kidding!" said my friend.

"No I'm not," was the reply. "That's the charge. What's more, these lamps are crook. I've changed hundreds of 'em.

They come from overseas and the set manufacturers have complained that they don't last, but the makers claim they are the only ones who have had trouble. And while they're squabbling about it, I'm replacing globes left, right and centre."

And finally, a brief summary of two more Rank Arena service bulletins. Their previous bulletins were summarised in the January 1976 issue.

## RANK ARENA TECHNICAL SERVICE BULLETINS

### ISSUE No. 5

Chroma Board PWC 411

Factory changes on run No. 415-5. (Not required on receivers in the field.) PAL IDENT alignment instructions for runs 415-1-2-3. PAL IDENT alignment instructions for run 415-5.

Models C2601/2

Errata for service manuals and circuit diagrams. Damped wave effect produced by vertical/horizontal line junction of cross-hatch pattern.

### ISSUE No. 6

Model C1454

Excessive green due to 4.43MHz radiation. (Sets with green sticker on carton or underside of receiver do not require modification.)

Model C2601

Modification to minimise failure of IC 753. Factory modification only.

All Models

DC power supply modification. Improved horizontal centring.

Models C2204, C2603, C2604, C2605

Counter measure for horizontal ringing.

All Models

Elimination of low channel regeneration.

Model 2603

Improvement to channel 0 tuning range.

Model C1454

Correction to resistor reference numbers. Corrections to service manual parts list. Change of deflection output board.

Models 2603 & 2604


Increased fuse rating.
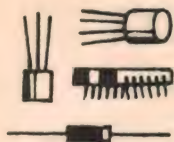
## BASIC ELECTRONICS 5th edition now on sale

Begins with the electron, introduces and explains components and circuit concepts, details the construction of simple receivers. Separate chapters on test instruments, servicing, amateur radio, audio techniques, stereo sound reproduction.

Price: \$3.00 plus 60c pack and post. (From "Electronics Australia", PO Box 163, Beaconsfield 2014.)





## What's new in Solid State

### More on opto-coupler uses

Following on from the introductory discussion given last month on opto-couplers, here is some further information on these handy devices. Extracted from applications material given in a recent issue of Philips' "Elcoma Brief", it gives a good idea of how to use the devices in typical circuit coupling situations. We reproduce the material by kind permission of Philips Industries.

One of the more important applications of photocouplers is in coupling digital sub-systems, because the high insulation resistance and low coupling capacitance given eliminates problems caused by earth loops and noise spikes.

#### TTL-to-photocoupler interface

The photocoupler can be driven from 7400 series TTL using one of the circuits shown in Fig. 1. Ideally, the operating speed of the photocoupler should be as high as that of the logic. Unfortunately, however, photocouplers operate at an appreciably lower speed, mainly because of the desaturation time of the phototransistor receiver. The phototransistor circuit should therefore be designed to have a low impedance, giving the highest possible switching speed and the most favourable noise margin.

The current transfer ratio is relatively low and fixed. The IR emitter diode current must be as high as possible to ensure saturation of the phototransistor in spite of the low impedance output circuit. However, as the diode current can be up to 30mA, the main restriction is set by the maximum permissible output current of the driving TTL gate. For active level LOW and active level HIGH, this is:

##### Active LOW

- 16mA with noise margin.
- 40mA without noise margin.

##### Active HIGH

8mA without noise margin.

The values of R (nearest preferred value) given in Figs. 1a and 1b are for gate currents of 16mA and 8mA respectively.

#### Receiver-to-TTL interface

The simplest circuit is shown in Fig. 2. The required value of R1 depends on the current in the IR diode, the current transfer ratio of the photocoupler, and the input requirements of the TTL gate. The value given (3.3k) allows the maximum speed for a photocoupler with  $I_f = 16\text{mA}$  and  $I_c/I_f = 20\%$ . The data rate is typically 100kbits/s.

#### Relay replacement

Fig. 3 shows how a photocoupler can

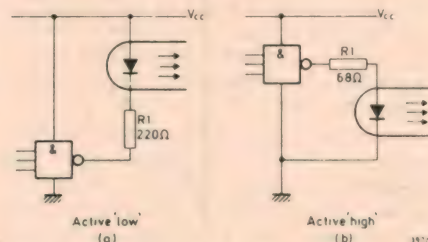


Fig. 1: TTL-to-opto-coupler interface circuits, (a) active low (b) active high.

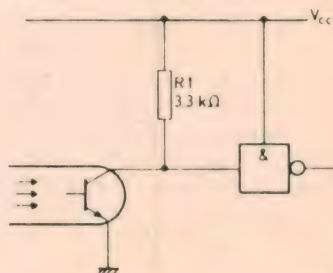


Fig. 2: Interfacing from opto-coupler receiver to TTL input.

be used as a direct replacement for a relay. The advantages of such a substitution are: faster operation, no contact bounce, longer life, and high insulation resistance. The main disadvantages are the limited output current and on-resistance.

#### Relay driver

Fig. 4 shows how a photocoupler can be used to protect low-power switching logic from transients occurring in an inductive load carrying high current. Using a photocoupler with a current transfer ratio of 20% and  $I_f \approx 12\text{mA}$ , a load current  $I_L$  of 1.5A can be switched with  $V_{CE(sat)} < 2.5\text{V}$ .

Switching speed at full load (1.5A) is:

$$t_{on} = 10\mu\text{s},$$

$$t_{off} = 2.5\text{ms}.$$

#### Analog transmission

There is a wide range of industrial and consumer applications where photocouplers can be used to transmit analog signals between equipments at unequal earth potentials, or where it is necessary for several analog signals to be added in series to supply a common amplifier input.

Fig. 5 shows a practical analog isolator circuit. The circuit has 3dB roll-off points at 6Hz and 80kHz. Total harmonic distortion at 8V pk-to-pk output is less than 1.5% between 100Hz and 20kHz.

This circuit can be used in applications where the photocoupler replaces a transformer for isolating equipments with and

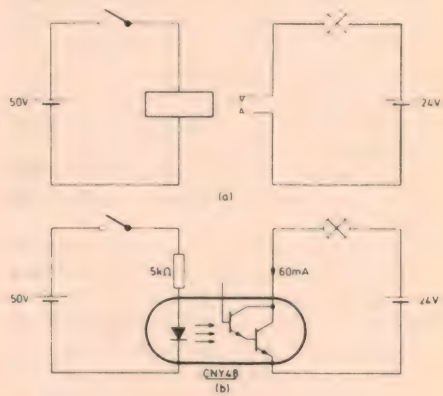


Fig. 3: Direct replacement of relay by an opto-coupler.

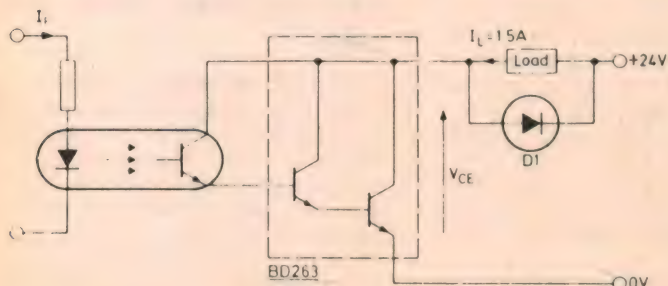


Fig. 4: Protection of low power logic circuitry from relay switching transients using an opto-coupler.

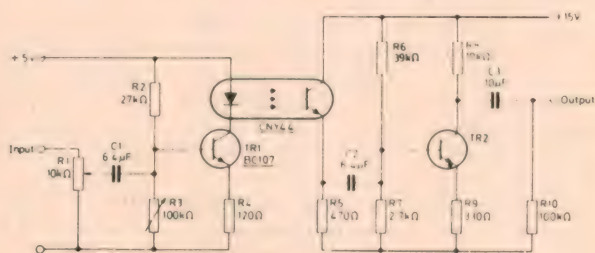


Fig. 5: A practical isolator circuit for coupling audio and other analog signals below 80kHz.



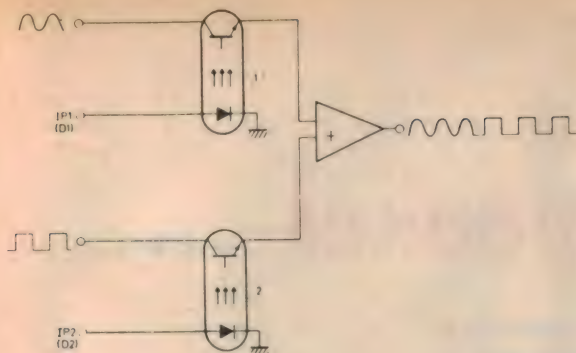


Fig. 6: Two opto-couplers used with an operational amplifier to function as an analog multiplexer. The switching signals remain referenced to ground, while the actual switches "float".

without earthed chassis.

Fig. 6 shows a schematic arrangement where photocouplers are used in an analog multiplexer. The advantages of using photocouplers are that the phototransistors float in the analog signal lines but the gating IR diodes operate with respect to fixed potentials. In Fig. 6, when the IR diode of photocoupler 1 is turned on at  $IP_1$ , and the IR diode of photocoupler 2 is turned off at  $IP_2$ , the sinewave appears at the output of the amplifier. Alternatively, with the diode of photocoupler 1 off and that of photocoupler 2 on, the squarewave appears at the output. With both diodes on, the resulting signal at the amplifier output is the sum (or difference) of the two transistor input signals.

#### Overcurrent sensor

A photocoupler can be used as a simple, fast overcurrent sensor in a power supply circuit. The basic circuit is shown in Fig. 7. The IR diode of the photocoupler does not conduct until the voltage across the shunt reaches the knee of the IR diode forward characteristic ( $\approx 1.5V$ ), when the diode current increases rapidly. Diodes D1 to D3 with resistor R1 form an overcurrent bypass

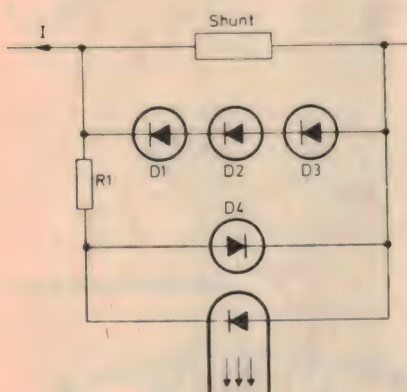


Fig. 7: An opto-coupler may be used as an overcurrent sensor for power supplies and similar circuits, as shown.

network. These diodes should be silicon types with  $V_f \approx 0.7V$  and sufficient current rating for the application. Diode D4 protects the IR diode from possible reverse voltages.

Series resistor R1 should be chosen so that the IR diode passes sufficient current

before the combination of the IR diode forward voltage ( $\approx 2.1V$ ) and the drop across R1 causes diodes D1 to D3 to conduct. The circuit will also operate well on AC but then D1 to D3 should be replaced by two similar networks connected in inverse-parallel.

I think you'll agree that this information from Philips gives a good idea of the many applications of opto-couplers.

To conclude this month, there is news of a new bucket-brigade analog delay line device. It is also from Philips, so that this firm is now able to offer two such devices—the MN3001 which they released a few months ago (see our article in the December, 1975 issue), and the new one.

The new bucket brigade delay line is designated type TDA1022. A monolithic dynamic shift register in MOS technology, the TDA1022 is intended for analog signal processing and can provide a delay from 51.2ms to 0.512ms as the clock frequency is varied from 5kHz to 500kHz.


A special feature of the new device is the low attenuation of only 2.5dB at 25°C. This enables a number of devices to be connected in cascade to obtain long delays without undue losses. The input voltage range is typically 2.5V, when the total harmonic distortion is only 0.6%. The signal-to-noise ratio of a typical device is 70dB.

The TDA1022 is intended for both consumer and professional applications. Reverberation effects, variable compression and expansion of speech in tape recorders, and vibrato and tremolo effects in electronic organs and musical instruments are a few examples of consumer applications. In the professional sector, equalizing speech delays in public address systems, speech scramblers, and timescale conversion multiplex systems in telephony, including linked compander and expander systems, are typical applications of the TDA1022.

The TDA1022 is designed for operation at ambient temperatures from -20°C to +55°C, and is supplied in a 16-pin plastic DIL encapsulation. (J.R.)

For further data on devices mentioned above, write on company letterhead to the firms or agents quoted. But devices should be obtained or ordered through your usual parts stockist.

## INTRODUCING E-Z-MACRO-HOOK

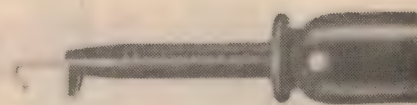


PART NO. XH



The Heavy-Duty Test Hook. Ideal for connections to large leads, terminals and lugs. Conductor and Hook are equivalent in current carrying capacity to 14 AWG wire (.064" Dia.—1.65mm Dia.). Spring-loaded and heavily insulated to a single contact point to assure true readings.

**Construction:** One-Piece Nickel Silver Conductor and Hook. Made for test connections over diameters up to .125" (3.175mm). Durable Heat and Chemical Resistant Nylon Body and Plunger. Stainless Steel Compression Coil Spring provides approximately 40 ounces (1244 Grams) contact pressure.

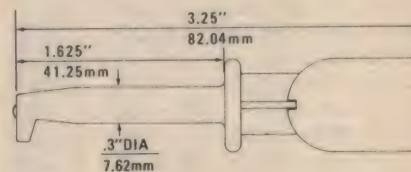**Colors:** Red, Black. Specify color when ordering.



#### Available from:

**SYDNEY:** Dick Smith, Radio Despatch, Pre-Pak  
**MELBOURNE:** J. Magrath, Radio Parts  
**ADELAIDE:** Graphic Electronic Industries Pty Ltd  
**PERTH:** W. J. Moncrieff Pty Ltd  
**BRISBANE:** Fred Hoe & Sons Pty Ltd  
**CANBERRA:** The Electronic Shop  
**NEWCASTLE:** Digitronics Pty Ltd

or direct from:



99 Alexander Street, Crows Nest, NSW  
Telephone: 439 2488  
36 Park Street, South Melbourne, Victoria  
Telephone: 69 7782



# Build your own electrostatic loudspeaker — PART 2

Following the constructional details of electrostatic speaker units, in the previous article, this article discusses the number of units required, the method of mounting and interconnection and, finally describes an amplifier system with an active crossover network to feed both bass and electrostatic speakers.

by A. A. RENDLE\*

Having mastered the construction of individual units, it remains to make the best use of them in a complete system. The three main questions are: (a) how many units are needed? (b) how should they be arranged? and (c) how do we drive them?

The polar response (directivity) of a sound source is determined by its shape and size in relation to the frequency of the signal it is radiating. Fig. 9 shows the polar response of a line source, as a function of length and wavelength. The effective length of our electrostatic unit is about 75mm which, at 10kHz, is about three wave lengths and this gives a very narrow polar response. All the sound, at this frequency, would be radiated in a narrow beam.

A good way to overcome this problem, is to arrange a number of units in an arc, as in Fig. 10. This will give a polar response, at different frequencies, of the general pattern shown in Fig. 11. The ripple pattern is caused by interference between the units, and does not matter if the amplitude of the ripple is kept reasonably small. For the best overall polar response, over a range of frequencies, the arc should be as wide and shallow as possible, implying a large number of units.

The prototype system (Fig. 10) uses 8 units, with a radius of 500mm which gives an arc of just over 90 degrees. As can be seen from Fig. 11, this gives good dispersion over an angle of 60 degrees, from about 1kHz up. Below 1kHz, the polar response is filled out by the bass speaker.

Another possible arrangement would be to stack the elements vertically, with each element pointing in a slightly different direction. An angle of 15° between elements would be about right. This has not yet been verified in practice. Yet another method uses a combination of horizontal and vertical stacking: an arrangement apparently favoured by Janszen.

The elements are combined into an

array by taping them on to a strip of 25mm thick soft polyurethane foam; the sort used for chair cushions. Use plastic insulating or masking tape. When installing the array, the foam faces inside. The foam does two important jobs: as well as supporting the elements, it provides an acoustically resistive load, to control the main diaphragm resonance.

All the elements are simply wired in parallel, i.e. each of the three terminals on an element are wired to the same terminals on the other elements. The best way of doing this is to make up a wiring harness with solder lugs at the appropriate points for attaching to the terminals. Don't put the lugs on the terminals and then solder the wire, as the heat may damage the plastic. When fit-

Right: Fig. 10. How eight units are arranged in an arc to give maximum spread with minimum mutual interference.

Below: Fig. 11. Typical polar diagrams produced by multiple units mounted on a 90° arc. The diagram on the left represents the case where arc radius is twice the wavelength, and that on the right a radius of eight times the wavelength. ("Elements of Acoustical Engineering" by Olsen.)

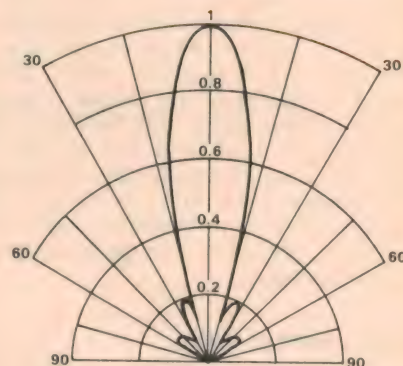


FIG. 9 LENGTH = 3

Fig. 9. Polar diagram when speaker is 3 wavelengths long. ("Elements of Acoustical Engineering" by Olsen.)

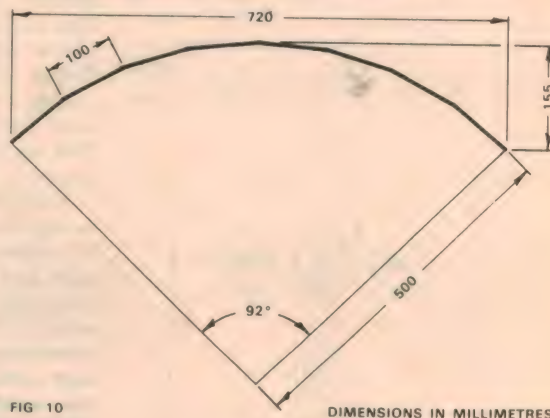


FIG. 10

DIMENSIONS IN MILLIMETRES


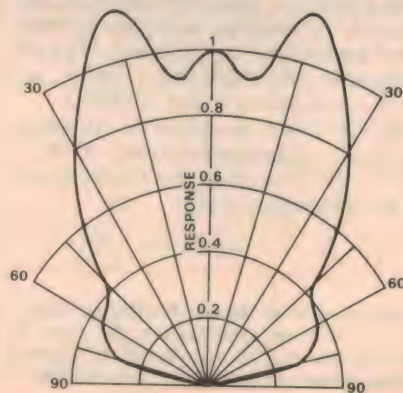


FIG. 11

RADIUS = 2λ

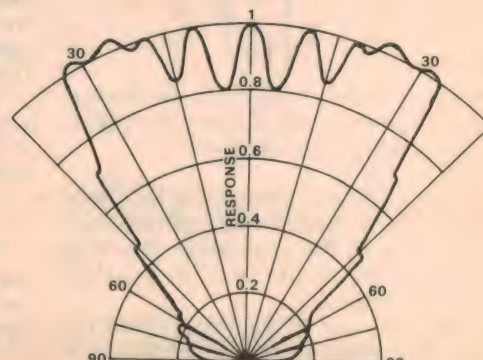

RADIUS = 8λ

\* 82 Bible St., Eltham, Victoria 3095



The electrostatic array can either be free standing above the bass enclosure, radiating back and front, as in the Bowers and Wilkins Model DM 70, or it can be mounted in a closed absorbent cavity. Both were tried in the prototype system and, in the end, the closed arrangement was preferred. This avoids reflections, off the walls, from the rear radiation, which tends to confuse the stereo image. If the speaker was standing in front of hanging curtains, or some other absorbent material, this would not be a problem.

If you follow the closed approach, the sealed cavity would just be a section of the bass enclosure. The depth should be at least 200mm, and it should be fitted with a wedge of absorbent wadding, such as glass fibre. The dimensions of the prototype enclosure are shown in Fig. 13.

Any good moving coil system may be used with the electrostatic speaker. The main thing is to choose an arrangement which will do full justice to the potential quality of the electrostatic speaker. The actual choice of a unit and enclosure will depend on the level needed for the particular room, and how low you want to make the low frequency cut off. For a large room, 300mm or 380mm speakers are recommended. Another very interesting possibility would be to combine a low frequency horn with the electrostatic array; this could give superb results.


In the prototype system, 300mm Goodmans Audiom 61s were used, in large vented brick enclosures, but any similar bass speakers, such as the Philips 12100/W8, would serve well. The Philips speakers have a free air resonance of 15Hz, and will work well in a sealed enclosure of 50 to 100 litres.

With the variety of excellent integrated and hybrid circuits around these days, life is made very easy for people building their own amplifiers. The system used here is merely an assemblage of several well known and popular circuits. Separate power amplifiers are used to drive the electrostatic and bass speakers via active crossover filters: the so called electronic crossover arrangement. Using hybrid power amplifiers, the extra cost is not very great, and the problems of designing and building LC crossover filters between the power amplifier and the speakers are avoided.

The preamplifier (Fig. 14) uses the still unsurpassed National LM 381, followed by a passive tone control circuit and an LM 301A operational amplifier, arranged to give a gain of 10. The gain is determined by the ratio of  $R_b$  to  $R_a$ . If you



Fig. 13. Details of the closed absorbent cavity used for the electrostatic units. Note the fibreglass wedge in the rear of the enclosure.

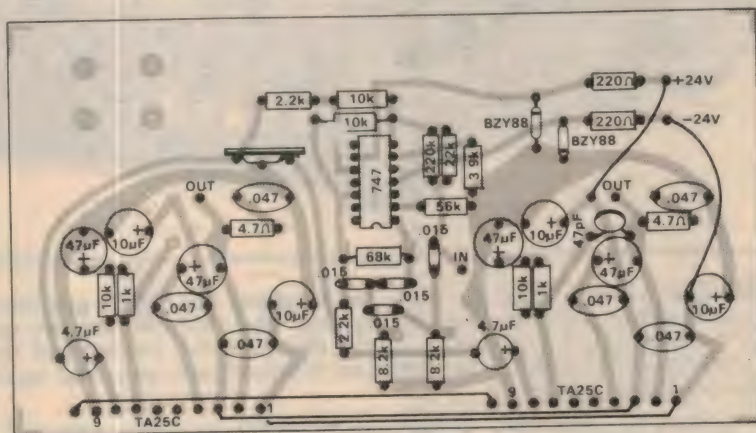

Component layout of the printed board, shown from the component side. The high frequency amplifier is on the right and the low frequency on the left.

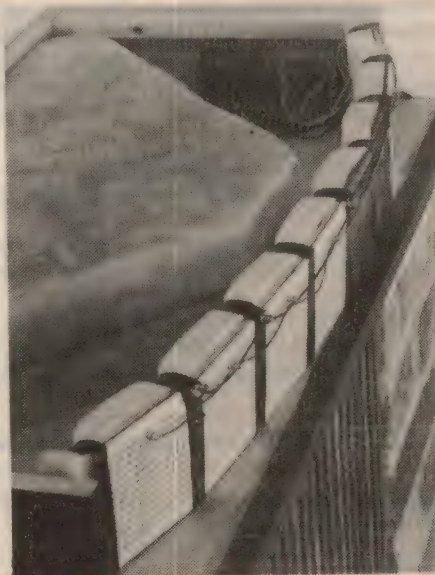


Fig. 12. Electrostatic speaker cavity, with cover removed, fitted to the top of the brick bass vented enclosure.

need more, or less, gain, the value of  $R_a$  or  $R_b$  may be altered to give the required ratio.

The active crossover filters (Fig. 15) were described in the April, 1972, issue of *Audio*, by Michael W. King. The arrangement is particularly neat and economical. A high pass filter is used to feed the electrostatic speaker power amplifier, while the complementary low pass filter is derived by taking the sum of the input and output of the high pass filter. This gives, in effect, the low pass filter. With the component values shown, the crossover frequency is about 530Hz. Alternative values of  $C_0$  are given in Table 1, for different crossover frequencies.

STC Type TA 25C (also sold as Sanyo Type STK 032) thick film hybrid circuits were selected for the power amplifiers (Fig. 15). A small capacitor is added to the feedback path on the amplifier driving the electrostatic speaker, to control slight ringing, due to the capacitive load. A full array of 8 elements reflects a load of about 2 microfarads, and requires a





## Arlunya Series 7500 Data Acquisition Equipment



**SERIES 7500** is designed for durability and reliability and fills the gap between expensive monitoring systems and chart or manual recording methods of gathering data. The 7500 data loggers are instruments in the strict sense of the word. Connect the analogue input signals, select the operating modes and recording can commence immediately. If you measure temperature, strain, flow, pressure, displacement, electrical quantities etc. etc. then Arlunya data loggers will save your time and money.

- Basic System expands from 10 channels to 1000 channels by adding 10 channel plug in switching modules.
- Choice of switching modules, type L (low thermal reed relay, residual thermal noise  $<2\mu\text{V}$ ,  $5-45^\circ\text{C}$ ), type F FET switch modules for high speed applications, etc.
- First and last channel scan selection with skip facilities using function programmer.
- Choice internal or external digitiser, compatible with most TTL BCD output DVMs, Digital Multimeters, Counters, etc.
- Real and elapsed time digital clock has 99 days, 23 hours, 59 minutes and 59 seconds capability with Automatic Battery Take Over and Stable Crystal Timebase. Wide range of switch selectable clock controlled sample rates.
- Three modes of initiating channel scans and measurement under clock control including "pre determined", "dual scan" and "slot Scan".
- Monitor Mode allows display of any one selected channel with display updated each time channel is scanned or display of each channel measurement as scanned. Time can be displayed instead of data when desired. Separate channel identity display.
- Ability to drive wide variety of output recording devices such as printers, teletypewriters, paper tape punches, incremental reel or cassette digital recorders etc. Simultaneous recording on more than one output device possible in some cases.
- Selection of number of output words per line and inter record gap size.
- Switches enable output word formats to be changed with character deletion, choice between ASCII or EBCDIC etc.
- Mains (115/240V 50/60 Hz) or external battery 12V operation (when using Arlunya internal digitiser and printer or digital cassette magnetic tape recorder output device).

Designed and manufactured in Australia by

**ARLUNYA PTY. LTD.**

P.O. Box 113, Balwyn, Victoria, 3103, Australia.  
Telephone (03) 836 6533.

Telegrams or cables: Arlunya Melbourne, Australia.

Surprise me with data showing the high quality and modest cost of Arlunya Data Loggers.

Name .....

Address .....

Post Code .....









## NEW Trio CS-1560

### The 15MHz dual trace with a 10MHz price tag

Who else gives you:

- ☐ DC to 15 MHz
- ☐ 10mV/cm
- ☐ 0.5 $\mu$ S to 0.5 S/cm
- ☐ X-Y + Intensity mod
- ☐ Dual trace
- ☐ Free probes

at this price ?

The CS-1560 is a highly reliable and stable dual trace triggered sweep oscilloscope with all solid state circuits and a 130mm screen. With its high vertical sensitivity of 10mV/cm, bandwidth of DC to 15MHz, and sweep time of 0.5 $\mu$ sec/cm to 0.5sec/cm, it is ideal for a wide range of applications from analyzing and adjusting television sets to various research, development and production processes, and also for educational purposes.

#### Check these features:

- Extremely wide bandwidth of DC to 15MHz with its high vertical sensitivity of 10mV/cm.
- Sweep time extends from 0.5 $\mu$ sec/cm to 0.5sec/cm in 19 ranges. Further, as TV-V and TV-H Syncs are available for measuring video signals and x5 magnified sweep, its range of application is extremely wide.
- Very easy X-Y operation with high input sensitivity for Lissajous measurements.
- For dual trace operation, either CHOP or ALT is automatically selected by the sweep time.
- With "AUTO FREE RUN" function, a sweep is generated even without an input signal.



# \$399

Complete with 2 probes worth \$70.00!!

- Thanks to newly developed blanking circuitry, starting of wave-form display is clear and sharp.
  - Stabilized accelerating high voltage DC power supply (with DC-DC converter) makes the sensitivity and intensity free from effects of line voltage fluctuations.
- You get all this plus FREE x10 probes for \$399.00 (plus Sales Tax).


## O.3% accuracy D.M.M for only \$120!

**STOP PRESS:** Prices subject to change due to new Customs Duty. Please check before ordering.

The New high accuracy DL703 multimeter is the ideal replacement for conventional moving coil instruments. Accuracy is better than  $\pm 0.3\%$  of reading  $\pm 0.15\%$  of full scale on D.C.

**Ranges:** DC volts 2 to 1000V D.C. current 0 to 200mA  
AC volts 2 to 350V Ohms 200 $\Omega$  to 20M $\Omega$

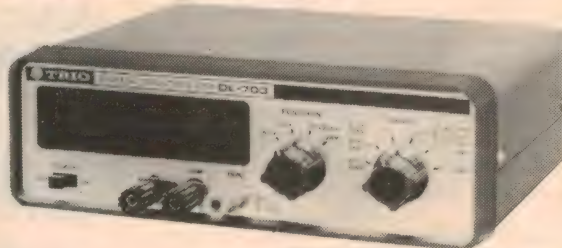Housed in tough metal case, the DL703 operates from 240V a.c. mains. Display is bright 3 $\frac{1}{2}$  digit LED. Maximum sensitivity is 1mV. Auto zero. Auto polarity. Dual slope. All this for only \$120.



## Use the coupon NOW

Simply mail coupon or call in — Sydney: 68 Alexander Street, Crows Nest 2065. Tel: 439 3288. Melbourne: 53 Governor Road, Mordialloc 3195. Tel: 90 7444. Take advantage of your Bankcard.



9PM20

Please supply me with ..... Trio CS1560 oscilloscopes.

- ☐ at \$399 excluding sales tax. I enclose an official order or exemption certificate.
- ☐ at \$459 tax paid.

If ordering by mail please add \$5.00 for insured delivery.

If you are not delighted with these instruments, return them within 7 days for a refund less delivery costs.

Please supply me with ..... Trio DL 703 digital multimeters

- ☐ at \$120 excluding sales tax. I enclose an official order or exemption certificate.
- ☐ at \$138 tax paid.

If ordering by mail please add \$2.50 for insured delivery.

I enclose cheque/money order to value \$.....

Name: .....

Address: .....

# PARAMETERS<sup>PTY</sup>LTD



But if too high a voltage is used, the system is likely to break down, and spark across, somewhere. In practice 2kV seems to be about the limit.

In the prototype system, an old valve type mains transformer, with a 350-0-350 volt secondary, was used. With a voltage doubler (see Fig. 15), the output is about 1.8kV. A commercial transformer, the A&R 60029 is also available. The polarizing supply must be be connected via a high resistance (at least 10M), for safety.

The  $\pm 24$  volt supply for the power amplifiers is straightforward, using an 18V-0-18V transformer, such as the A&R PT5526. Zener diodes are used to provide  $\pm 15$  volt for the earlier stages.

The relative sensitivities of the bass and electrostatic speaker/amplifier combinations are adjusted with the balance control on the inputs of the power amplifiers. Ideally, this would be done using a signal generator and sound level meter, but it seems possible to get a good balance by ear. Using a variety of records, or other program source, adjust the balance control, for left and right channels in turn,


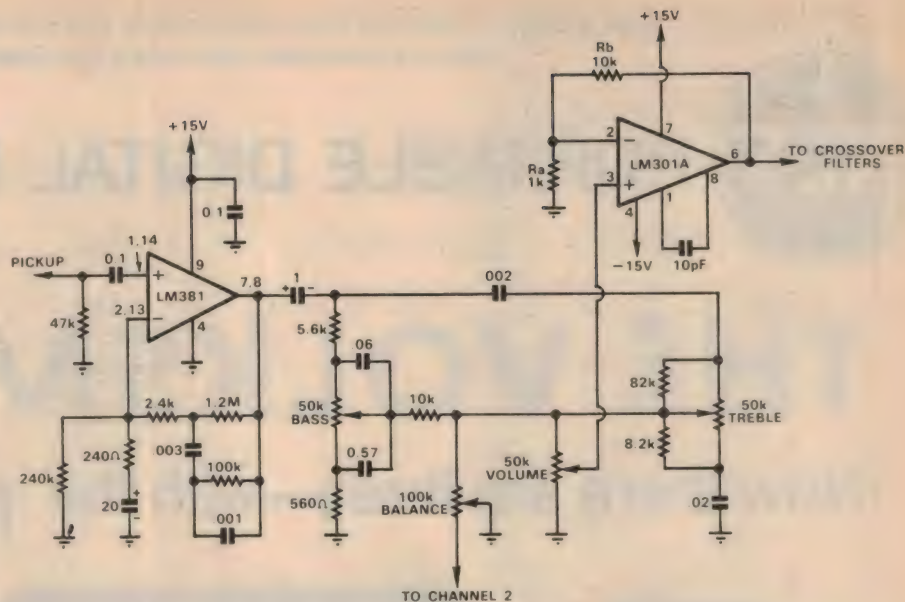



FIG. 14 PREAMPLIFIER (FINAL VERSION)

Fig. 14. Circuit of the preamplifier. The gain can be varied by varying the feedback resistors,  $R_a$ ,  $R_b$ , associated with LM301A. Values shown give a gain of 10.

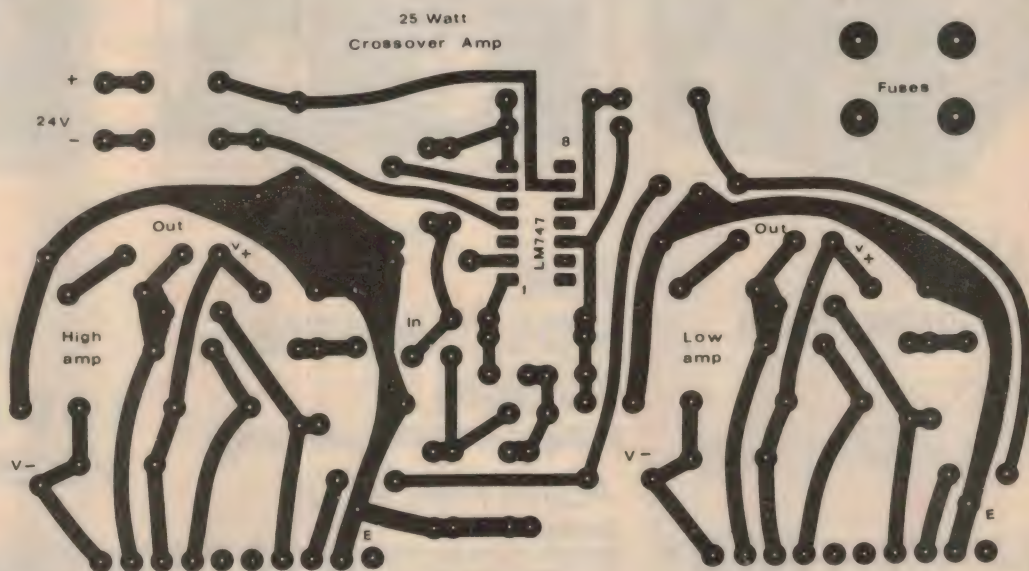Right: The printed board pattern, shown actual size. Ready made boards should be available from suppliers when this article appears.



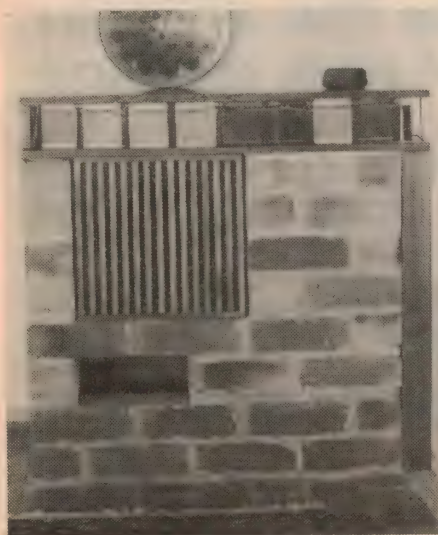Below: The author's brick enclosure with electrostatic system above it. "... gives a lot of satisfaction on everything from Suzi Quatro to Bartok!"



until the balance seems right.

The author's own system, as described above, has evolved over a number of years, as the design of the electrostatic elements developed. The rest of the system consists of a Shure V-15 Type III pick-up cartridge, in a Lustre arm, modified to get rid of excess mass, and a JH turntable. With this combination, the whole system gives a lot of satisfaction on everything from Suzi Quatro to Bartok! The clarity of detail on orchestral music is very good, and string tone is smooth and silky.

The system has plenty of power in reserve, so that a high listening level can be used, without overloading on peaks—this is essential in any really good system. In conclusion, the author hopes that anyone having a go at making their own electrostatic speakers, as a result of these

articles, will get as much fun and satisfaction out of the project as he has had!

#### FURTHER READING:

1. "Electroacoustics", by F. V. Hunt, Harvard University Press, and J. Wiley and Sons, 1954, pp. 167-212, 202, 205.
2. "Wide Range Electrostatic Loudspeakers", P. J. Walker, Wireless World, May, June, August, 1955.
3. "Horn-Load Electrostatic Loudspeaker", Josef Merhaut, Journal of the Audio Engineering Society, November, 1971.
4. "Full-Range Electrostatic Loudspeakers", H. J. Leak and A. B. Sarkar, Wireless World, October, 1956.
5. "An Electrostatic Loudspeaker Development", Arthur A. Janszen, Journal of the Audio Engineering Society, April, 1955.



High quality at low cost from the company that has led the Digital Revolution since 1952 when we developed the world's first Precision Digital Voltmeter.



## PORTABLE DIGITAL MULTIMETERS

# THE VOLKSMETERS


Now there are three—with the **NEW!! LM-3.5**



**LM-3**  
Full three digits.

**THE  
VOLKSMETER**

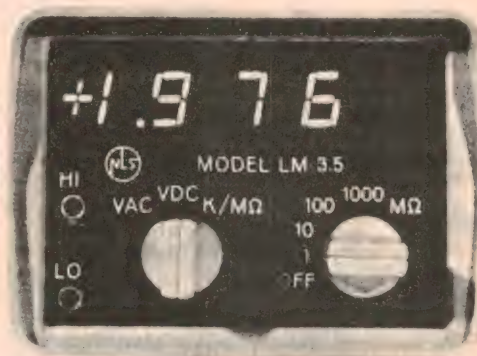With Rechargeable  
Batteries & Charger Unit **\$99\***



*Actual Size*

**THE  
VOLKSMETER +**  
3½ digits  
3 digits + 100% over-range  
Active Filter Input!

With Rechargeable  
Batteries & Charger Unit  
and Three Current Shunts. **\$127\***



**LM-4**  
Full four digits.

**LAB ACCURACY  
VOLKSMETER**

With Rechargeable  
Batteries & Charger Unit **\$180\***

**THERE'S A PLACE IN YOUR TOOL BOX FOR A TOUGH  
LITTLE VOLKSMETER, ASK ANYBODY WHO ALREADY  
HAS ONE**

*Volksmeters are available throughout Australia at the following local distributors, radio shops, hobbies & electrical stores:*

**Melbourne:** Radio Parts (all stores), Lawrence & Hanson, I.E.T. Pty Ltd, Magrath's.  
**Sydney:** Dick Smith (all stores), Lawrence & Hanson, Radio Despatch Service, I.E.I. Pty Ltd.

**Adelaide:** Compar Distributors Pty Ltd.  
**Brisbane:** Lawrence & Hanson  
**Perth:** Lawrence & Hanson  
**Newcastle:** Digitronics, Division of Edmonds, Moir & Co.

**Geelong:** Teleparts (also new store at Morwell).  
**Hobart:** Lawrence & Hanson.  
**New Zealand:** Pye Ltd., Systems Division.

Other products include panel meters, digital voltmeters, data acquisition systems Mil Spec DVMs, comparators, serializers, digital clocks, word generators, signal conditioners, scanners, digital printers, special-purpose digital instruments, and MOS/LSI array testers. For more information on these NLS instruments/systems, contact:



**Non-Linear Systems, (Australia) Pty. Ltd.**

P.O. Box 122, Glen Waverley, Victoria, 3150, Australia.  
Telephone: (03) 232 4506/232 7535. Telex 34082.

\*All prices plus  
15% sales tax  
if applicable.



# Circuit & Design Ideas

Conducted by Ian Pogson

Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.


## Application for 74C14 CMOS Schmitt trigger

National Semiconductor has just recently added a new CMOS IC to its range. The package consists of six Schmitt triggers and is designated the 74C14. It offers the advantages of low supply current and infinitesimal input loading, available only from complementary MOS.

The circuit for CMOS Schmitt trigger oscillator is remarkably simple, as may be seen from the diagram. The diagram shows an application how the output power from a Schmitt oscillator running at about 400kHz, is fed to five touch switches. Note that the metalwork of the touch switch is isolated from the circuitry by the dielectric of the ceramic capacitors. This is an important safety point. A reasonable ground plane is essential for efficient dipole action by the body, to the finger that is touching the touch plate.

With no finger applied to touch pads T1-T5, sufficient energy is transferred to the input capacitance of the CMOS Schmitt triggers to keep them well above the switching voltage  $V_{TL}$ . However, application of a finger absorbs sufficient energy to allow the 10M bleed resistor to pull an input below  $V_{TL}$ . In the demonstration model, we have the output driving a LED directly as a visual indication. In a system application, logic 'one' level indicates an active switch. Remove the finger and the lamp is extinguished—the logic level goes to zero.

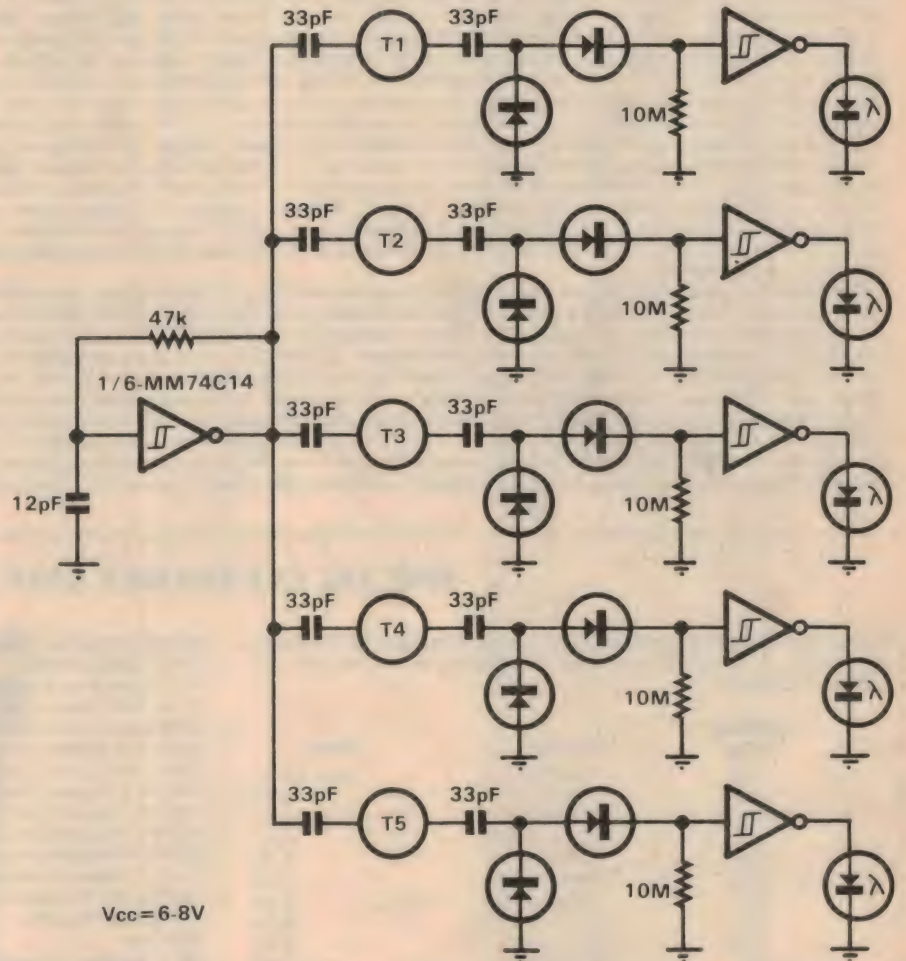Variations of the circuit which come to mind are feedback matrices to cause latching and/or exclusivity. Such approaches are useful in touch-button




tuning for FM station preselectors or TV tuners.

(By Richard Percival, National Semiconductor.)
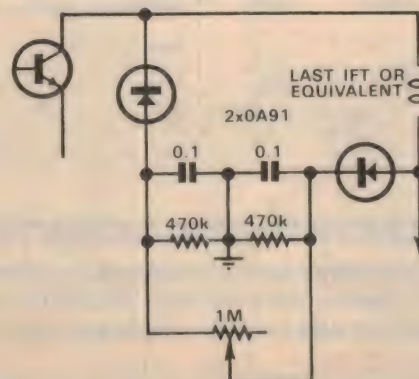
## Try this IF noise limiter

During development work on a VLF receiver the need arose for some sort of noise combating device. The usual search for and trial of various circuits was undertaken and finally I came across this one which met the need for a simple yet effective noise limiter.

The circuit is not unlike the "Bishop" IF noise limiter and it is possible that the circuit which I have used may have stemmed from the Bishop. It appears to have been first described many years ago by VK3ZCN and so it is not new or original as far as I am concerned. Sometimes a good circuit lies hidden and little used by



a majority of people who may be able to use it to advantage and it is for this reason that I am including it in these columns.

In its original form, the noise limiter used a 6AL5 twin thermionic diode and I have replaced it with two OA91 diodes. Germanium appears to be superior to silicon in that clipping is more effective. The amount of clipping is minimum with all of the 1M potentiometer in circuit, with maximum clipping when shorted.

(By Ian Pogson, "Electronics Australia".)



# A COMPUTER CONCEPT BECOMES AN EXCITING REALITY

In January of 1975, MITS (Micro Instrumentation & Telemetry Systems) stunned the Computer world with the announcement of the Altair 8800 Computer that sells for under \$500 in kit form. The Altair 8800 is a superbly engineered, variable word length computer. Its byte orientation structure was designed to give the Altair the most efficient utilization possible—an efficiency only found in the most advanced computers. It has a cycle speed of 2 microseconds; it can directly address 65k bytes of memory and 256 input/output devices; and it has 78 basic machine instructions with variations over 200 instructions. The Altair 8800 has been designed with buss orientation to be easily expanded and easily adapted to thousands of applications. It is ideal for the hobbyist who wants to get involved with computers. Yet, it has the power and versatility for the most advanced data processing requirements. Its basic memory of 256 words of static RAM memory can be expanded to 65,000 words of directly addressable memory, static or dynamic memory, PROM or ROM memory, or a floppy disc system which can store over 300,000 bytes of information on a flexible disc with a data transfer rate of 250K bits/sec. Using standard MITS interface cards the Altair 8800 can be connected to MITS peripherals (computer terminals, line-printers, audio-cassette interface, character alpha numeric display, teletype, etc.). **TODAY MITS IS ANNOUNCING THE ALTAIR 680 COMPUTER** for under \$350 in kit form, plus freight. The Altair 680, built around the revolutionary new 6800 microprocessor chip, it is the lowest priced computer on the market. The Altair 680 comes with power supply, front panel control board, and CPU board inclosed in a case. In addition to the 6800 processor, the CPU board contains the following; 1) 1024 words of memory. 2) Built-in Interface that can be configured for RS232 or 20mA Teletype loop or 60mA Teletype. 3) Provision for 1024 words of ROM or PROM. The Altair 680 can be programmed from the front panel switches or it can be connected to a computer terminal or Teletype. With a cycle time of 4 microseconds, 16-bit addressing, and the capability of directly addressing 65,000 words of memory and a virtually unlimited number of I/O devices. It can be expanded to an advanced custom intrusion system, programmable scientific calculator, automatic IC tester, complete accounting system, sound and light controller, or it can be all of these things at the same time. The list of applications is literally endless. See WHK Catalogue for details on both computers, also listed in the same catalogue price reductions on modules for the Altair 8800, 4K memory boards under \$220, etc. All units come with complete documentation. Manuals with circuit diagrams can be purchased separately.

Also listed in our catalogue:—7-decade counter-latch-decoder-driver CMOS IC, will count up to 9,999,999 ideal for frequency meters, time interval counters, etc; 8-digit stopwatch IC needs only a crystal, switches and display, can also be used as 24 hour clock; 4-decade presettable up-down counter-decoder-driver IC, ideal for batch counters; crystal time bases for clocks and frequency meters; 12V battery operated chronometer kits ideal for boats and cars; digital clock kits with large Liquid Crystal Display or extra large LED displays; digital clock IC's with alarm, date & month display; TTL, CMOS, ECL & Linear IC's; Memories, Character Generator IC's; very low cost analog to digital converter IC's; Function Generator IC with sine, square and triangle wave outputs; low cost red, yellow, green and orange LED's; Alpha numeric displays; solid state linear temperature transducers; solid state pressure transducers; dual tracking voltage regulators; Hall Effect devices for magnetic field measurements; Magneto Resistors; Printed Circuit Boards; Anti-Reflective Filters for Displays; Drafting Templates with electronic symbols; Dual Stereo Preamplifier IC's; CBS SQ Decoder IC's; Four Channel SQ Decoder IC's; Electronic Attenuator IC 0-90dB; Power Amplifiers, new infra-red Transmitter/Receiver kits for Headphones use on your TV set; TV games; Construction plans for Laser Pistols, FM BUG Transmitter, Wind Generators and many others; Infra-red Viewers; Diffraction Gratings; Polarization Filters; Fresnel Lenses; Fiber Optics; Heatpipes; Scientific Calculators; etc, etc.

## SPECIAL CLEARANCE SALE

We have a large quantity of brand new, German made, CRADLE RELAYS in stock which we sell at a fraction of original cost. All relays are for DC operation and supplied with dust cover.

Type	Operating Voltage	Contacts	Price
A	4-12	1 set N.O.	each \$0.70
B	12-24	1 set N.O.	0.70
C	0.5-1.5	1 set N.C.	0.40
D	1-3	1 change over	0.70
E	4-8	1 change over	0.70
F	18-30	1 change over	0.60
G	4-8	1 change over	0.70
H	4-8	1 N.C. 1 N.O.	0.80
I	6-12	6 sets N.C.	0.40
J	4-8	6 sets N.C.	0.40
K	18-24	6 sets N.C.	0.40
L	4-8	6 sets N.C.	0.40
M	15-30	6 sets N.C.	0.40
N	15-30	3 sets N.O., 2 change over	0.80
O	15-30	4 sets N.O., 1 change over	0.70
P	12-24	2 sets change over	0.80
Q	18-24	2 sets N.C., 4 sets N.O.	0.60
R	18-24	4 sets change over	0.70
S	6-12	7 sets N.O., 1 change over	0.85

Please give 2nd choice, 10 or more less 10%.

240V Transformers, 60V CT, 100V 5 watt type	\$2.20
6A, 400V Triac, TO-48 Case	1.60
309K 5V, 1A Voltage Regulator	2.25
1N 914 Signal Diodes	per 10 0.60
400V, 1A Diodes	per 10 1.00

2N 3055 Metal Can Transistor	\$0.95
AA117 Signal Diodes	0.04
7401 Quad 2 Input NAND Gate	0.12
74141 BCD Decimal decoder	0.48
4929 dual 2-Input NAND & INV.	0.23
74191 UP/DOWN Counter	1.02
7454 4-wide, 2-Input AND OR INV	0.13
TAA141 3 stage AF Amplifier	0.90
TAA420 5 stage AF Amplifier	1.53
TAA521 Operational Amplifier	0.45
TAA721 Differential Amplifier	0.45
TAA722 Differential Amplifier	1.20
TAA981 AM/FM Amplifier	0.51
723 Voltage Regulator	0.90
555 Timer	0.85
741 Operational Amplifier	0.45
301 Operational Amplifier	0.60
556 Dual Timer	1.60

Post and pack \$1.00 per order.

WHK No 7 catalogue \$2.00 plus 0.50 p/p with the catalogue you receive two \$1.00 vouchers which can be used towards the purchase of goods. Catalogue free to INDUSTRY & EDUCATION DEPARTMENTS.

Please forward WHK No 7 Catalogue.	Please Print
Name .....	
Street .....	
Town .....	Postcode .....
	EA3.76



## W.H.K. ELECTRONIC & SCIENTIFIC INSTRUMENTATION


MANUFACTURING, IMPORT, EXPORT, WHOLESALE & RETAIL

2 GUM ROAD, ST. ALBANS, 3021. VICTORIA. AUSTRALIA. PHONE: 396-3742 (STD area code 03)

POSTAL ADDRESS: P.O. BOX 147, ST. ALBANS, VICTORIA. AUSTRALIA. 3021.


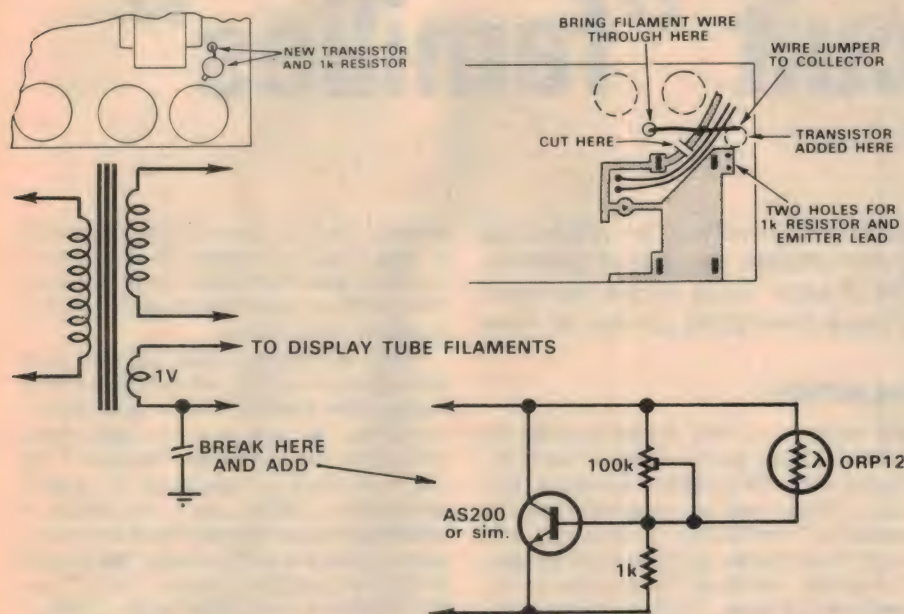
## Automatic brightness for digital clock



Having built the LSI Digital Clock as described in April, 1975, the follow-up article describing a Quartz Crystal Drive for it in September, 1975, prompted me


to suggest a very simple modification which I have incorporated into my clock and may be of interest to other readers.

I built my clock for use in the bedroom but I found it much too bright at night. After trying a number of ideas, I arrived at the following variable intensity circuit which has been very successful. The circuit was added between the display tube filament connections and the main board earth. The hardest part was to find somewhere to fit the parts.


The CdS cell was fitted through a hole in the back panel, just behind the power transformer, facing backwards and receiving only ambient light. The preset potentiometer is mounted across the LDR terminals and held in place with a dab of epoxy resin. The earth for the tube filaments is cut to the right of the transformer fixing point as shown in the diagram. The filament wire is lifted carefully from its earth pad, extended, and by drilling a small hole in the board it is then soldered to the filament line next to the cut copper track. The AS200 transistor and the 1k resistor are mounted next to the power transformer as shown and connected to the LDR by a short twisted pair. After assembly the 100k potentiometer is adjusted to give a satisfactory minimum brightness in a dark room.

(By Mr A. G. Briggs, 580 Lowe Street, Hastings, N.Z.)
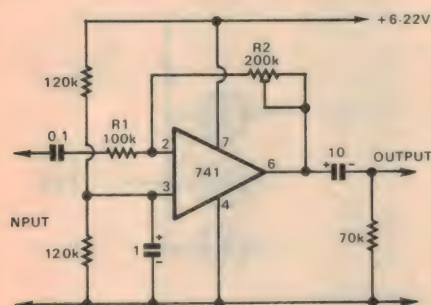
## General purpose amplifier uses uA741c IC



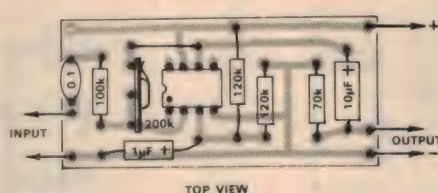Here is the circuit and PCB layout of a general purpose interstage amplifier using the uA741c integrated circuit. The unit may appeal to readers looking for a small interstage amplifier to be fitted into limited space. I used the unit to boost preamplifier output (nominally



250mV) to drive fully hybrid amplifier units calling for 500mV input.

The circuit is not particularly original but the advantage of this version lies in its small size, minimum number of components, negligible distortion, simply adjusted levels of amplification and may be operated over a wide range of supply voltages.


(By Mr W. Hansen, C/o University of Canterbury, Christchurch, NZ.)

## Different brake light warning indicator

In "Electronics Australia" for March, 1972 (p80) and May, 1972 (p82) a very useful brake light warning indicator was described.

After some experimenting this is the circuit which I settled for. A LED is connected in series with 1.2k and the LED is shorted out under normal conditions. This appears to work satisfactorily and it gave an indication when one lamp was removed and the brake pedal was operated. I prefer this mode of operation to that described in the original articles.

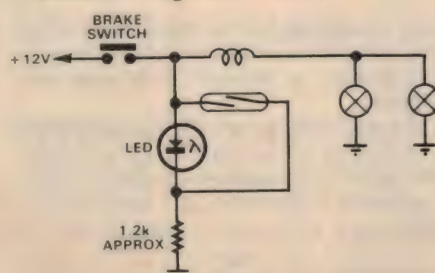(By R. Blackwell, 22 Glenwood Drive, Bellevue Heights, SA 5050.)



## RADIO DESPATCH SERVICE

869 GEORGE STREET  
SYDNEY

CNR GEORGE & HARRIS STS  
RAILWAY SQUARE  
TEL 211-0816, 211-0191

## SPECIALS LIMITED QUANTITIES

	each
2N3055 TO3 case .....	\$1.00
5082/4850 1/4" Red LEDs .....	10 for \$2.00
BC109C .....	10 for \$2.50
BC108C .....	10 for \$2.50
BC107 .....	10 for \$2.50
5 BC107 + 5 BC108C + 5 BC109C for	\$3.50
I.R.C. W.W. 3W pots	
1K-2K-2.5K-3K-7.5K-10K .....	\$1.20
RCA plug to RCA plug curly patchcord	\$0.50
6W fluorescent hand lantern with cord attachment and connection to cigarette lighter of car .....	\$15.00

OPEN SATURDAY MORNINGS



# Logic circuit "families"

A number of different technologies have been evolved for producing circuit modules, and "families" of circuit modules, capable of performing often required logic functions. This chapter looks at the common logic families, and explains how they were developed as well as how they work.

by JAMIESON ROWE

In this chapter we are going to digress for a while to look at some of the types of practical circuitry which are commonly used nowadays to perform logic functions. Hopefully this will let you put basic digital theory and practice into perspective, before we go further into the subject.

As we saw in the preceding chapter, the basic logic functions can be performed simply using mechanical switches. The very earliest digital logic circuits in fact used this approach, dubbed for convenience "switch logic".

While adequate for simple circuits and systems, switch logic proved to have quite serious drawbacks. In particular, it called for very complex switches whenever the logic "input" from a switch was required to be effective in a number of different parts of the circuit.

A way around this was to supplement switches with relays, which could be used to effectively multiply the number of switch poles available. Thus was born "relay logic".

While relays can provide the required number of poles, they share with switches the problem of unreliability and mechanical contact "bounce". This together with the relatively long time taken for a relay to operate has tended to restrict switch and relay logic to those applications where only a very low speed is required. Examples are the control of traffic lights and building elevators (lifts).

When the limitations of switches and relays became apparent, logic circuit designers tried other approaches. One was to use small lamps and light-sensitive resistors, giving "opto-electronic logic" (Fig. 1(b)). This avoided the unreliability and contact bounce of relays and switches, but didn't offer much else. The speed of operation was still quite low, due to the thermal lag of the lamps and the resistive lag of the photoresistors.

The first real breakthrough came with the development of diode logic. This used semiconductor diodes, in conjunction with pull-up and pull-down resistors. Using suitable combinations of diodes

and resistors, it was found possible to produce simple gates capable of performing the AND, OR and other functions (Fig. 1(c)). These had no moving parts to produce unreliability or bounce, and could thus operate at quite high speeds. The diodes introduced losses due to forward voltage drop, but these could easily be compensated using transistor amplifiers. Simple transistor inverters could also be used to perform the NOT function where required.

Not long after diode logic came resistor-transistor logic, or "RTL" for short. This

devices. Each of the modules performed a useful and commonly required logic function, and all modules were designed to be electrically compatible with the other members of its family.

Many worthwhile logic systems were designed around RTL, which offered quite respectable performance coupled with reliability, low cost and uncritical signal and circuit requirements. However it did not lend itself to operation at speeds above about 4MHz, due to the effects of transistor charge storage and stray capacitance across the load resistors. As a result designers gradually turned away from RTL to other forms of logic as the demand grew for logic circuits capable of operating at higher speeds.

The next logic family to come into prominence was transistor-transistor logic, or TTL for short. This has been an extremely popular family of logic

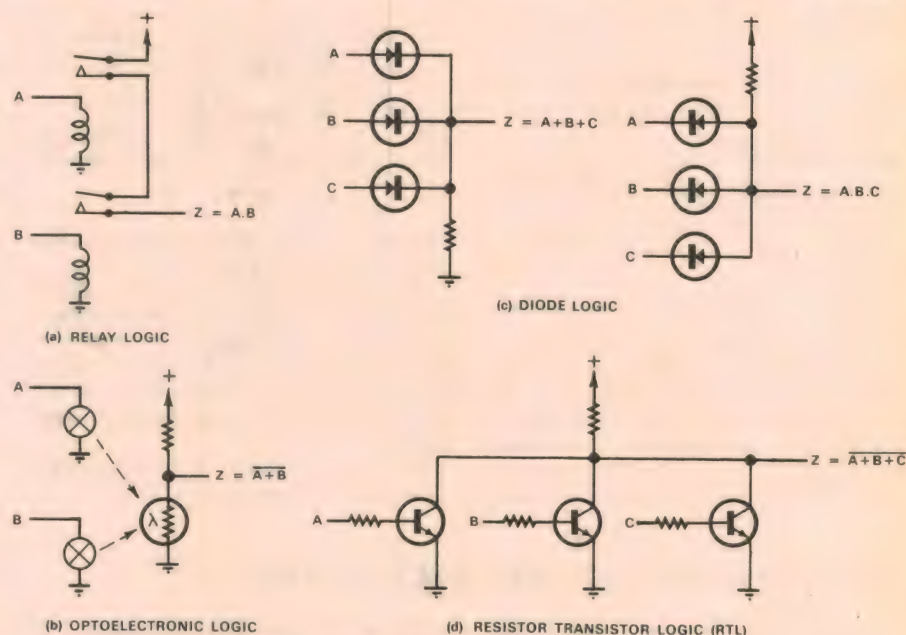


FIG. 1: EARLY TYPES OF LOGIC

used combinations of transistors (Fig. 1(d)), with resistors as loads and input current limiters, to perform both logic and inversion.

RTL was the first type of logic to be used in integrated circuit logic modules, which first appeared on the commercial market at about the beginning of 1966. At first there were only three modules, but as time passed other useful modules were added to form a complete "family" of RTL

modules, and grew from a relatively small number of "basic gate" devices to encompass hundreds of different devices, including medium-scale integration or "MSI" types containing functional subsystems and large-scale integration or "LSI" types containing complete systems.

The basic TTL gate is shown in Fig. 2(a). It is virtually a further development of the second diode logic gate shown in Fig.



1(b), with a multi-emitter transistor replacing the diodes. A second transistor is used as an output buffer and inverter. If all of the input emitters are held at the "high" voltage state, the current flowing into the input transistor's base flows out the collector, and biases the output transistor into conduction so that its collector goes low. But if any of the input emitters is taken low, this provides a "sink" for the base current, and the output transistor is turned off. Its collector voltage thus rises to the "high" state.

If we choose to regard the "high" voltage state as logic true (1), and the "low" state as logic false (0), the gate thus performs the NAND logic function, with the output false only when all inputs are true.

Practical TTL gates are a little more complicated than this, with additional transistors and other components to increase operating speed and give improved reliability. The first practical TTL devices to appear were the well-known "54/74" series, originated by Texas Instruments. The basic circuit for a 7400 series gate is shown in Fig. 2(b). If you compare it with the basic gate, you will see that the main difference is the addition of a pair of "totem-pole" output transistors to increase the operating speed and the output current capability. Clamp diodes are also added to the inputs, to prevent damage to the multi-emitter transistor from negative-going transients.

A great many 7400-series devices based on this circuit have been produced, and used in vast numbers of highly successful digital systems. However as time progressed, circuit designers began to demand devices with either lower current consumption, faster speed, or both.

In an effort to satisfy the demands for lower current consumption the IC makers produced a family of devices known as

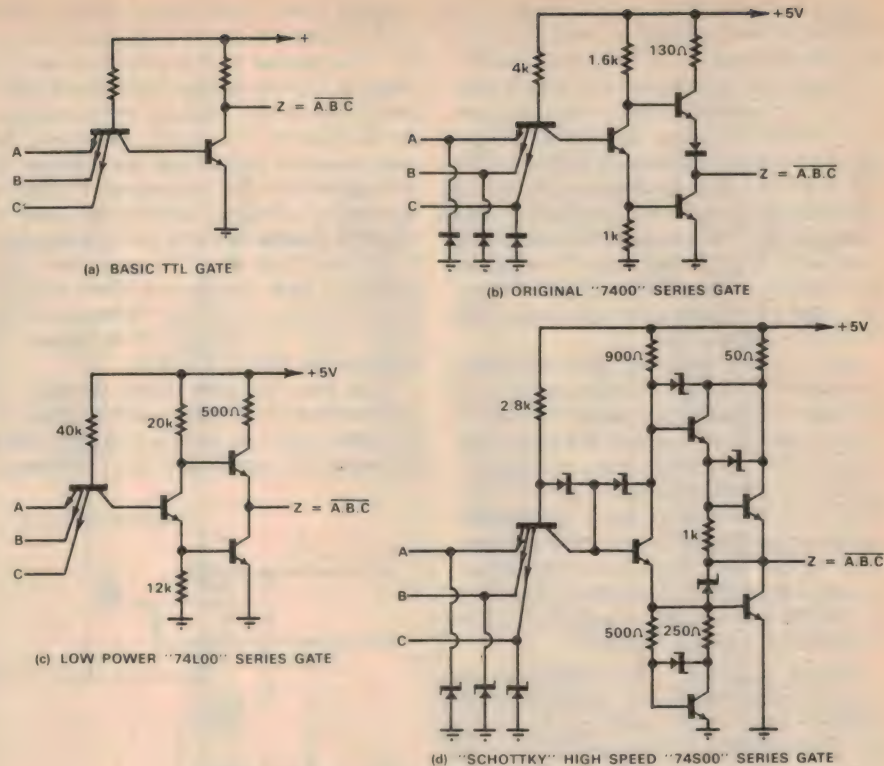


FIG. 2: VARIETIES OF TRANSISTOR-TRANSISTOR LOGIC (TTL)

named 74S00. Like the low-power series these were still based on the original TTL circuit, but here the various resistor values were made smaller to increase speed—at the expense of higher current. With 74S00 devices the transistors were also shunted with metal-semiconductor or "Schottky barrier" diodes as shown in Fig. 2(d), to prevent them from saturating. This obviated charge storage effects, and gave a further marked increase in speed.

The most recent variant of TTL to evolve is a series of devices known as "low-power Schottky TTL", and designated 74LS00. These combine the higher resis-

future.

Until the IC makers developed Schottky-clamped TTL, engineers designing very high speed digital systems often found that 74H00 devices were just not fast enough. As a result of their demands for extremely high speed gates and other logic elements, the makers came up with an alternative form of logic called "emitter-coupled logic" or ECL. This used a technique known as current steering, with transistors deliberately kept out of saturation to avoid the slowing-down effects of saturation.

The circuit of a basic ECL gate is shown in Fig. 3. At its heart are a number of input transistors with their collectors and emitters connected together, and with their common emitter line also connected to the emitter of a further transistor  $T_s$ . The base of this transistor is tied to a reference voltage, supplied by a temperature-compensated voltage divider and an emitter follower transistor, and its collector is connected to another emitter follower used as an output buffer.

The gate works in the following way. Due to the fixed bias voltage at its base, transistor  $T_s$  tends to conduct. This has two effects, one being that the collector current causes a voltage drop across its collector load resistor, and also at the output of the gate. The output of the gate thus goes to its "low" logic level. The second effect of  $T_s$  conducting is that it tends to act like an emitter follower, passing sufficient current into the 650ohm emitter resistor to produce a voltage drop about 0.7V less than the base voltage.

This tends to reverse bias the multiple input transistors, so that if the input bases are held at the low logic level, these transistors are cut off. However if any one or

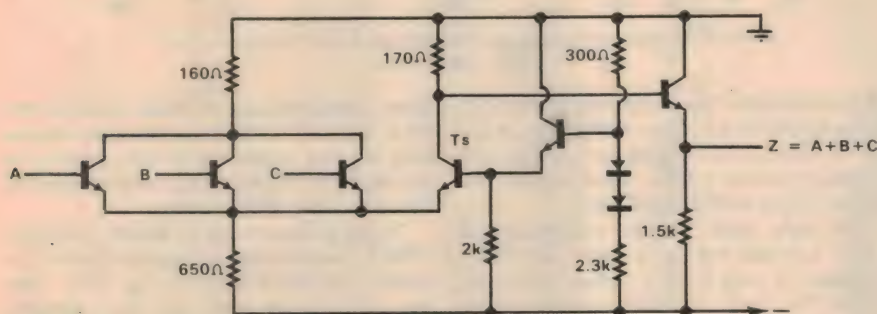


FIG. 3: EMITTER-COUPLED LOGIC (ECL)

"low-power TTL", or LPTTL, with the series designation 74L00. These were based on the same circuit configuration as standard TTL, but with the resistor values increased to reduce the current levels as shown in Fig. 2(c). This also reduced speed, but in many low power applications this was not important.

In order to satisfy those who demanded higher speed, they produced a "high-speed TTL" series, designated 74H00, and also a "Schottky TTL" series, desig-

tor values of low-power TTL with the speed improvement of Schottky barrier clamp diodes across the transistors. As you might guess, they have been evolved to satisfy the demands of those wanting high speed as well as low power dissipation. The 74LS00 series offer roughly the same speed as the original 7400 series, but with the reduced dissipation of the 74L00 series. If not eclipsed by other technologies, this series seems likely to become the "standard" TTL family of the



more of the input bases are taken to the high logic level, which exceeds the fixed bias on the base of  $T_s$ , then the transistor or transistors concerned are able to conduct. This passes current into the common emitter resistor, tending to raise it above the voltage produced by the emitter current of  $T_s$ , and so reverse biasing  $T_s$ . Accordingly  $T_s$  cuts off, and its collector voltage rises. The gate output voltage also rises to the "high" logic level. If we regard the "high" voltage level as logic "true" (1), this particular gate obviously performs the OR function.

As you can see, the gate effectively works by "steering" the current from the 650ohm emitter resistor either through  $T_s$  or through one or more of the input transistors. The operation does not depend upon any of the transistors being saturated, and in fact the gate is deliberately designed so that saturation cannot occur. This allows very high speed operation, and ECL devices are capable of operating at speeds greater than virtually any other technology: beyond 500MHz.

Circuit designers had pressures on them to reduce the power consumption of medium speed logic systems long before the development of low-power Schottky TTL, and as a result many turned away from TTL in an effort to find a technology capable of offering reasonable speed coupled with low power dissipation.

The technology they turned to was MOS technology, based on metal-oxide-semiconductor field effect transistors (FETs) rather than bipolar transistors. There are a number of types of logic circuit based on MOS technology, the three most widely used being NMOS, which uses predominantly N-channel MOSFETs; PMOS, which uses P-channel MOSFETs, and complementary or CMOS, which uses complementary pairs of both.

All three are currently in use at the time of writing, although NMOS and PMOS are used mainly in LSI devices incorporating complete digital systems. The technology mainly used for general-purpose small scale integration (SSI) logic modules is CMOS, which many people have described as the most elegant type of logic circuit to appear to date. It certainly offers many attractive features, including medium speed, very low current drain and low cost.

A basic CMOS gate is shown in Fig. 4(a). This is a two-input gate, and as you can see it uses only four transistors: two P-channel types in parallel at the top, and two N-channel types in series below. There are no resistors or other circuit elements.

The inputs of the transistors are tied together in complementary pairs, and shown, so that with either logic level applied to the inputs, only one transistor of each complementary pair can be conducting at any one time. If an input goes high, its N-channel transistor turns on while its P-channel transistor cuts off, and vice-versa.

If both inputs are high, both of the N-

channel lower transistors conduct, while both P-channel upper transistors are cut off. The output of the gate is thus held down at the low voltage level. But if either input is taken low, this cuts off its associated N-channel transistor, breaking the path between output and low voltage. At the same time the associated P-channel transistor conducts, closing the path to the high voltage rail, and taking the output to the high logic level. This condition also applies if both inputs are taken low, so that if we regard the high voltage level as logic "true" (1), the gate may be seen to perform the NAND function.

Note that the gate draws virtually no current from the supply in either of its static states, since no conducting path exists between the two supply rails. Whenever

however, being only about 800uW at 1MHz and 5V supply compared with about 10mW.

A basic CMOS gate which performs the NOR function if the high voltage level is regarded as logic true (1) is shown in Fig. 2(b), for you to compare with the gate just described. As you might expect from logic, it is basically a mirror image of the first gate, with the series and parallel pairing reversed.

While they perform the required logic functions, the basic CMOS gates shown in Figs. 4(a) and (b) have two main practical disadvantages. One is that the switching characteristic tends to be somewhat poor, giving indecisive switching when input logic levels do not differ by almost the full supply voltage. The

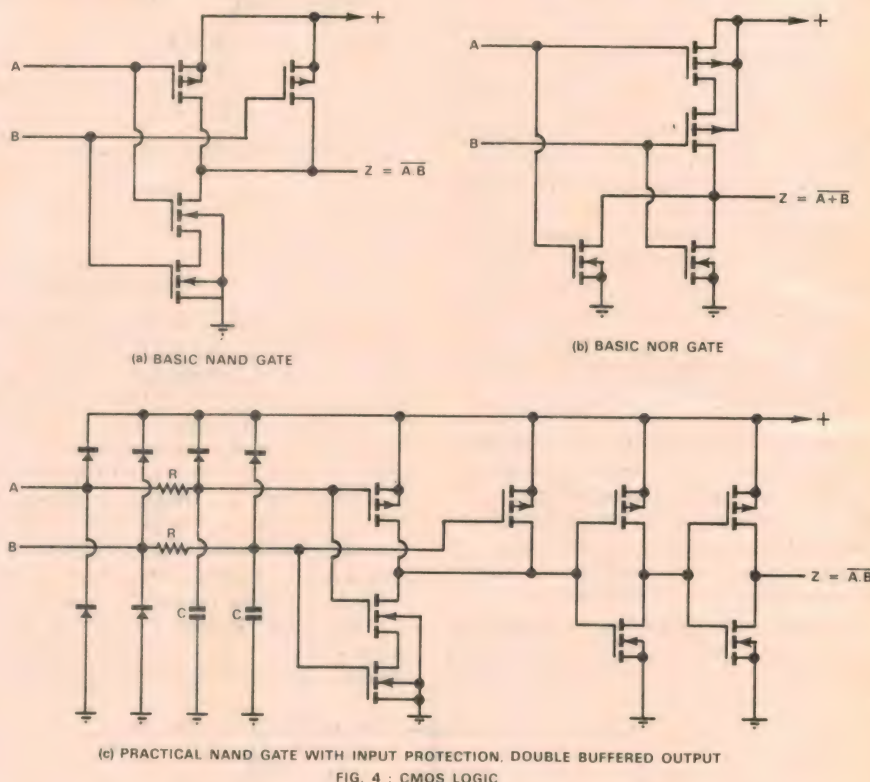


FIG. 4 : CMOS LOGIC

one of the upper transistors is conducting, at least one of the lower transistors is cut off. So that a CMOS gate has almost zero quiescent current drain, being an almost perfect static switching circuit.

The only time the two transistors of each complementary pair conduct together is very briefly, when changing states. This is due to differing control voltage thresholds, so that the transistor going into conduction "comes on" faster than the other transistor turns off. This means that each time the gate changes state, it momentarily becomes a low impedance path across the supply, and draws a short pulse or "spike" of current.

Because of this the average current drain and power dissipation of a CMOS gate under dynamic conditions rise from their very low quiescent levels, in a linear fashion. The power dissipation is still very modest compared with a TTL gate,

other disadvantage is that without any form of input protection, the gate insulation of the transistors can easily be damaged by static charges and transients, like any other MOS devices.

To get around these problems, practical CMOS devices tend to have additional circuitry like that shown in Fig. 4(c). Here the output is provided with two cascaded complementary MOS inverter stages, which give a very much sharper switching characteristic. This is known as "double buffering". The inputs are also protected from damage by means of a series R/parallel C transient filter, together with diodes which ensure that the transistor gates cannot be taken more positive than the positive rail nor more negative than the negative rail.

One of the important practical advantages of CMOS, apart from its very low power consumption, is that it can operate over a wide range in supply voltage—



typically from 5 to 15V, but some devices will operate from voltages as low as 1V.

The final type of logic to evolve to date is integrated injection logic (I<sup>2</sup>L) or merged transistor logic (MTL), developed independently by IBM and Philips, and announced by both in early 1972. This is a type of logic which reverts back to bipolar transistor technology, but with a difference: like CMOS, there are no passive circuit elements, only transistors.

MTL was designed primarily for large-scale integration (LSI), and it is based on a multi-output inverter rather than a free-standing gate. The basic circuit of an MTL inverter is shown in Fig. 5(a).

As you can see, it has no "pull-up" resistors or transistors provided for any of the outputs, which are simply the multiple collectors of a single NPN inverter transistor. Instead, the input of each inverter is provided with a pull-up transistor, as shown. It consists of a PNP transistor connected as a current source, whose current biases its associated inverter transistor into conduction unless otherwise diverted out of the input terminal.

The reasoning behind the transfer of the pull-up element from outputs to input is that this saves the power which would otherwise be wasted in pulling up unused outputs. By having the pull-up element at all inverter inputs, bias current is only drawn where it is actually needed; unused outputs are simply left unconnected, and draw no current.

The actual logic is performed with MTL inverters by connecting together outputs from a number of inverters to the input of another, using the technique known as "wired logic" or "dot logic". This was developed with earlier types of logic, as designers found that in certain situations they could achieve logic functions such as AND and OR merely by connecting the outputs of gates together.

The idea is simpler than it may sound, as Fig. 5(b) shows. If outputs from each of the two MTL inverters are connected together, the junction will be taken down to the low voltage level if either of the inverter inputs goes high. In other words, the simple connection of the two outputs produces a potential "NOR gate", if we

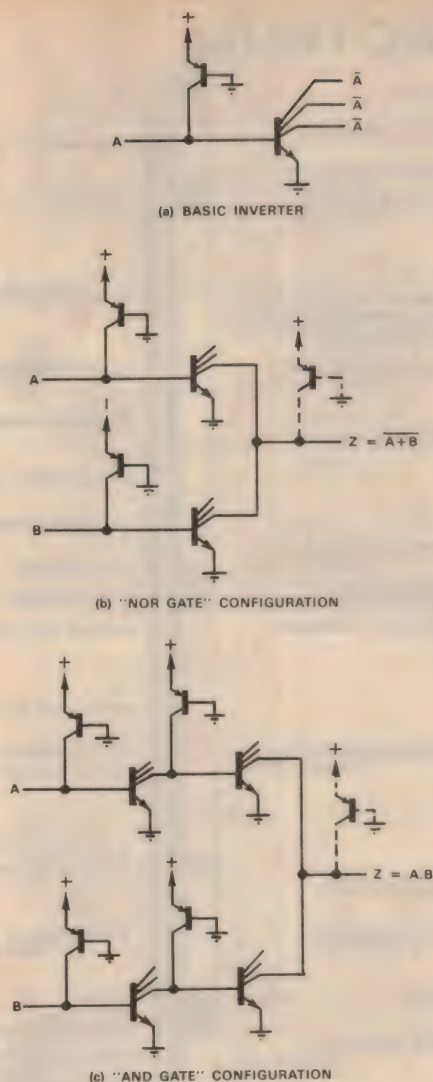


FIG. 5: INTEGRATED INJECTION LOGIC (I<sup>2</sup>L) OR MERGED-TRANSISTOR LOGIC (MTL)

think in terms of the high voltage level corresponding to logic true (1). All that is needed to achieve the NOR function is the pull-up action, which will be provided as soon as we connect the junction to the input of another inverter.

Fig. 5(c) shows how a 2-input AND function may be realised using MTL

elements. Here outputs from two inverters are fed to two further inverters, and outputs from each of these are again tied together. This time a "wired-AND" function is produced, however, because it will be potentially able to rise to the high voltage level only when both of the original inputs are also at high level. This corresponds to the AND function if the high voltage level is regarded as logic true (1).

Note that with this configuration, there would be nothing to stop us from using the inverted inputs available at the outputs of the first inverters, as well as the AND output. It is this "multiple function" capability of MTL which makes it particularly well suited for large-scale integration of complete logic systems.

Another feature which makes MTL ideal for LSI devices is that it involves very few IC fabrication steps — even fewer than for CMOS. This is because the PNP transistor current sources are actually "lateral" transistors, formed in the silicon IC chip simply by placing the base diffusion "island" of the NPN inverter transistor near a common P-type region "busline" connected to the positive supply. An MTL inverter is thus little more than a single NPN transistor structure, and is inherently both small and self-isolating.

A further significant feature of MTL is that its power dissipation for a given speed is even lower than CMOS. In fact MTL has been shown to have the lowest theoretical speed-power product of any logic technology yet developed, with a figure of .001 picojoules compared with about 0.1pJ for CMOS and about 100pJ for standard TTL. Like CMOS, MTL will also work at low voltages — down to about 1V.

In this chapter we have looked at the various "families" of logic devices which have evolved to date, and the technology on which they are based. I hope this helps you visualise the direct electronic implementation of the basic logic functions introduced in chapter 2, and thus gives you a solid foundation on which to build as we go further into logic system design.

IDEAL GIFT FOR MUSIC LOVERS...

**DECCA** record brush

1,000,000 CONDUCTIVE BRISTLES  
no anti-static fluids needed

The new DECCA Record Brush consists of a million tiny fibre 'bristles'. As you brush the record surface, upward of a thousand 'bristles' enter each groove and remove more dust and grit than any other product available. In addition, each 'bristle' is *electrically conductive*. Static on the record is removed as you clean, without the aid of special fluids.

\*\$12.50 at leading Hi-Fi stores & record bars.


Australian Agent: British Merchandising Pty. Ltd., 49-51 York St., Sydney.  
Ph. 29-1571.

\*Recommended retail price.





# FREQUENCY SPECTRUM

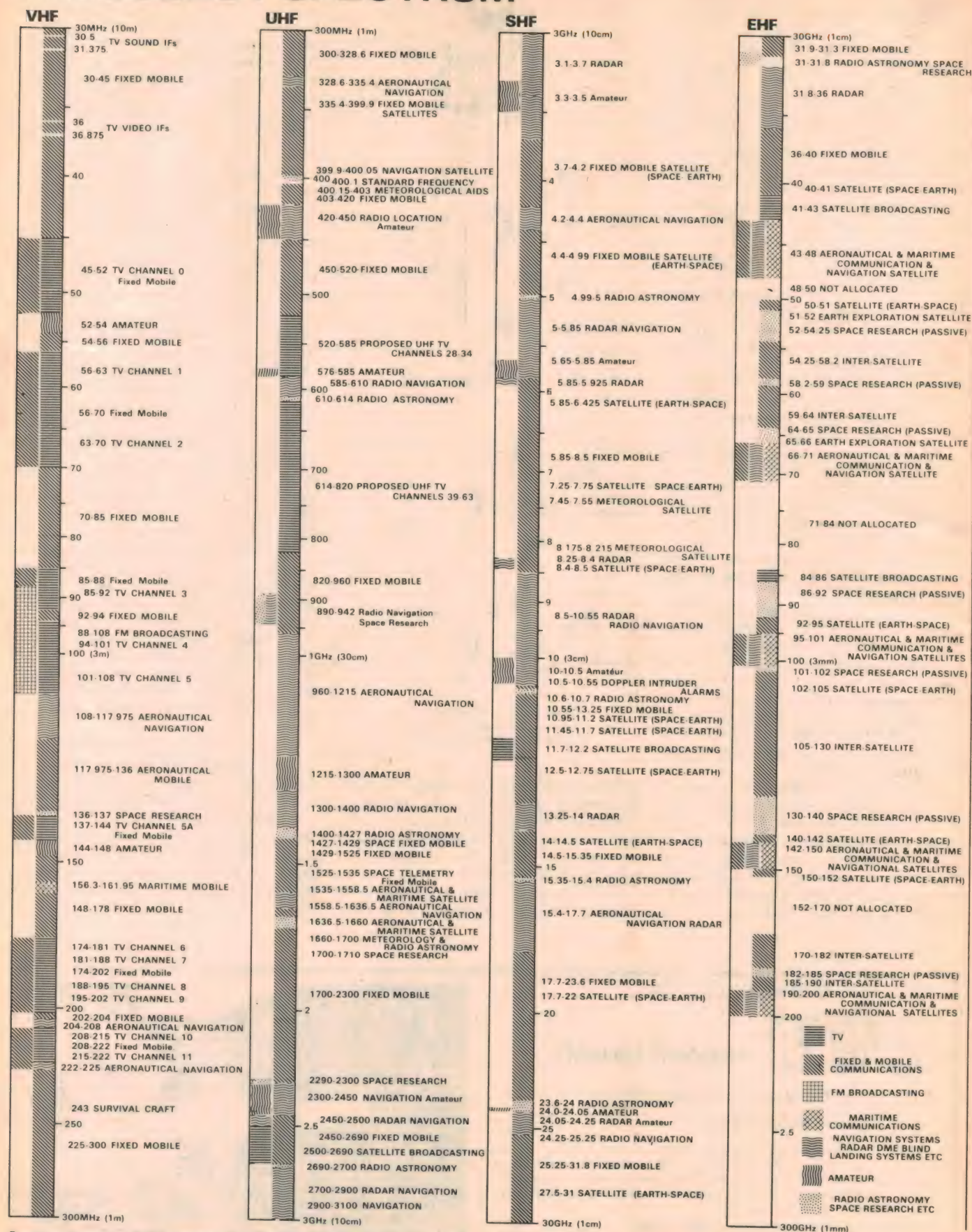


Services shown in small letters are secondary services. They must not cause interference to the primary service, and must tolerate any inter-

ference from the primary service. "Passive" segments: All emissions prohibited. Passive (receiving) devices only allowed.



# DISC RECORDS—NEW & OLD

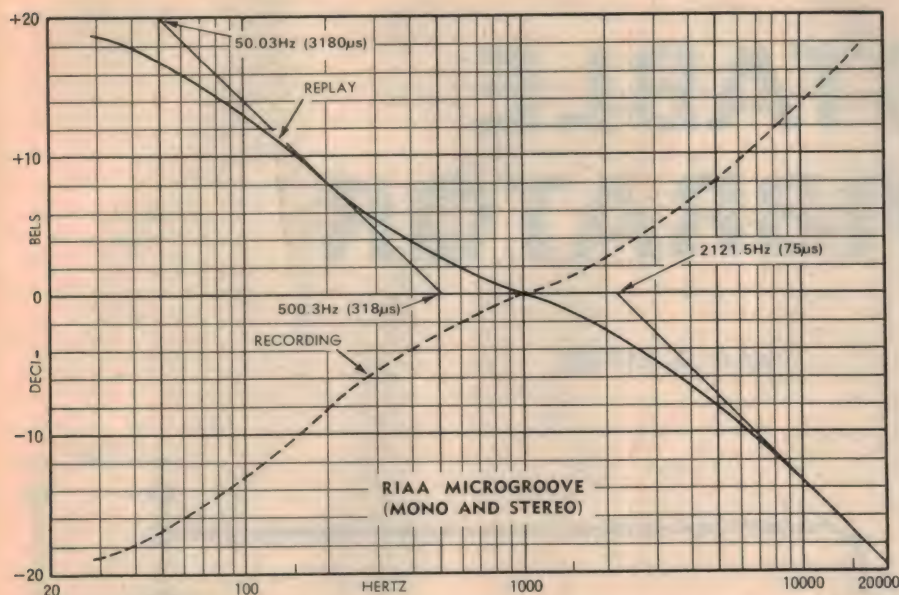

Inner recording diam (in) 3.75  
Centre hole diam (in) 1.5 or 0.285  
Other details as for mono or stereo above.

## COARSE GROOVE MONO

Nominal speed (rpm) \*78  
Nominal diam (in) 12 or 10  
Outer record diam (in) 11.52 or 9.52  
Inner record diam (in) 3.75  
Centre hole diam (in) 0.285  
Average pitch (grooves/in) 110  
Normal stylus tip radius (in) \*0.0025  
\*Actual figure for some older discs varied from this by up to 2 rpm.

Some older discs played better with a styli up to 0.0035 in radius. Many late 78 rpm discs could be used to advantage with 0.002 stylus.



Steel and thorn needles wore to fit the groove. Radiused, jewelled styli (right) on the walls. Angle of stylus taper is 40-50 degrees; groove angle about 90 degrees.

## MODERN MONO / STEREO / QUAD


Nominal speed (rpm) 33 1/3  
Nominal diameter (in) 12  
Outer recording diam (in) 11.52  
Inner recording diam (in) 4.75  
Centre hole diam (in) 0.285  
Average pitch (grooves/in) 300  
Stylus tip radius, normal (in) 0.0007  
Stylus tip radius, min (in) 0.0005  
Stylus, bi-radial, average .0008 x .0003

Other details as for stereo or mono above.

Now virtually an obsolete format.
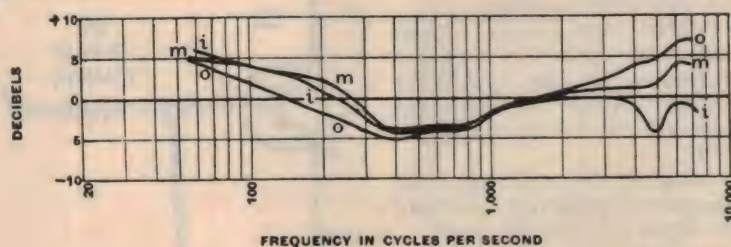
## 45rpm MICROGROOVE

Nominal speed (rpm) 45  
Nominal diameter (in) 7  
Outer recording diam (in) 6.625





Curves by Buchmann and Meyer (1931) indicate the frequency distribution of noise in 78rpm discs of the era, for outer, middle and inner grooves. It tended to interact with available pickups to produce a prominent noise peak at the natural resonance of the system—usually around 3 to 4kHz.

## MONO MICROGROOVE

As for 12 in stereo records above, except for stylus details. Most can be played with normal conical or bi-radial stylus, as for stereo but older pressings may give cleaner sound with a stylus of 0.001 in (1.0 mil) radius.
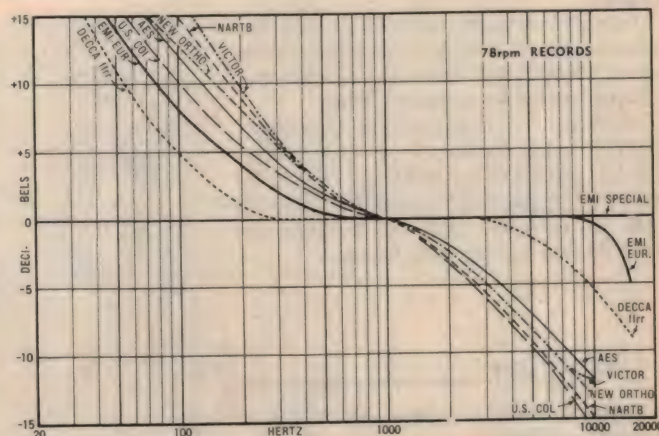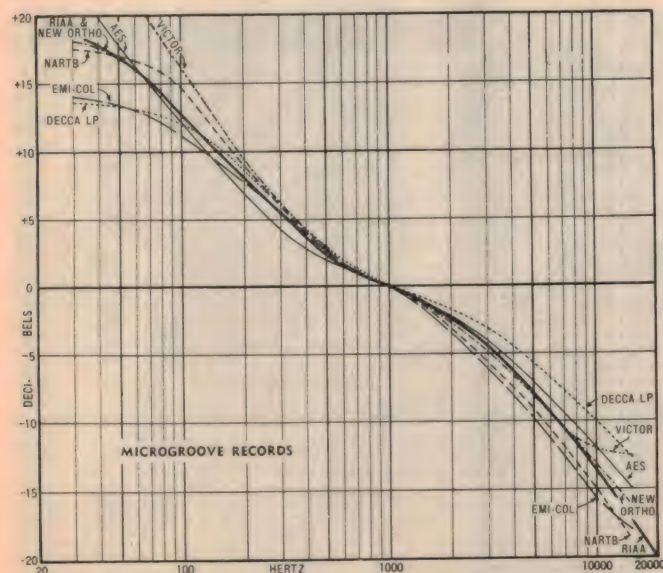
## 10 in MICROGROOVE

Nominal diameter (in) 10  
Outer recording diam (in) 9.52



At the top left are the standard RIAA record and playback curves used for modern stereo discs. The same playback curve is repeated at left (solid) and compared with curves for early mono microgroove discs. For vintage record enthusiasts, playback characteristics of various 78rpm discs is shown above.



# THE BISTABLE MULTIVIBRATOR

by A. J. LOWE

One of the commonest circuits in electronics is the bistable multivibrator—and that's what this month's Teach Yourself Board aims to demonstrate. The layout of the board and the circuit are as shown in the photograph and the diagram.

Construction is straightforward, but care must be taken to prevent the crossed wires in the centre of the model from touching one another. As in earlier models the switches are simply strips of springy brass soldered to a nail at one end and set to close a circuit when pressed on to a nail at the free end.

Resistors in the base circuits, R1 and R2, should be selected on test to ensure that the transistors saturate. The higher the gain of the transistor the higher the base resistor can be for any particular load current.

After completing the exercise on the opposite page, try connecting this board to the "Transistor as a Switch" board.



Connect both boards to the same battery. Connect the Q1 collector on the bistable board to the left hand end of the resistor R on the "Transistor as a Switch" board. (Do NOT press the switch on this board.)

Press the bistable switches. Note that when lamp 1 is alight the light on the other board is off. The output of the bistable controls the separate lamp.

Next try the "Unijunction Transistor" board. Simply connect the + terminal on the UJT board to the collector of Q1 and join the negative rails together. You can now control the UJT by pressing the switches on the bistable board.
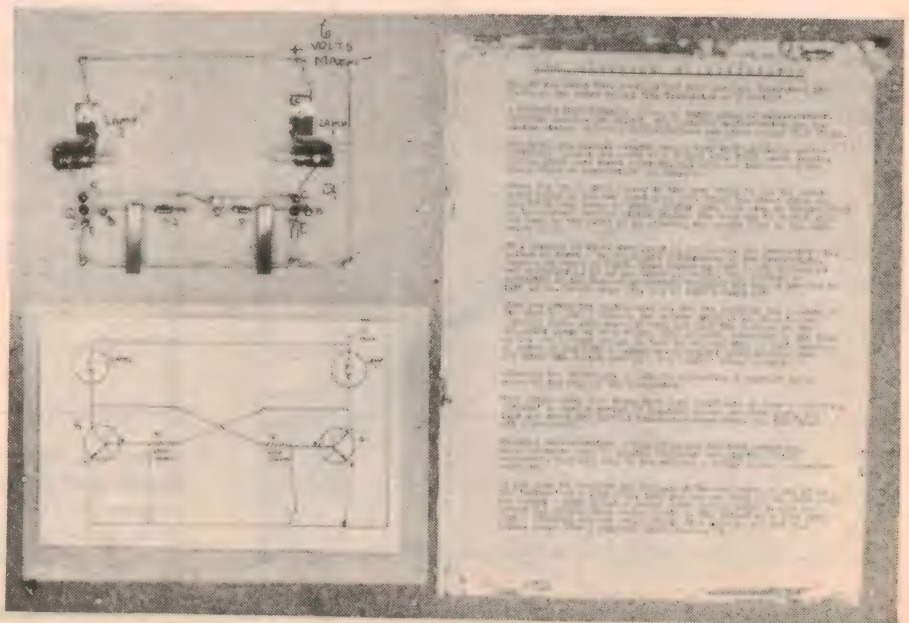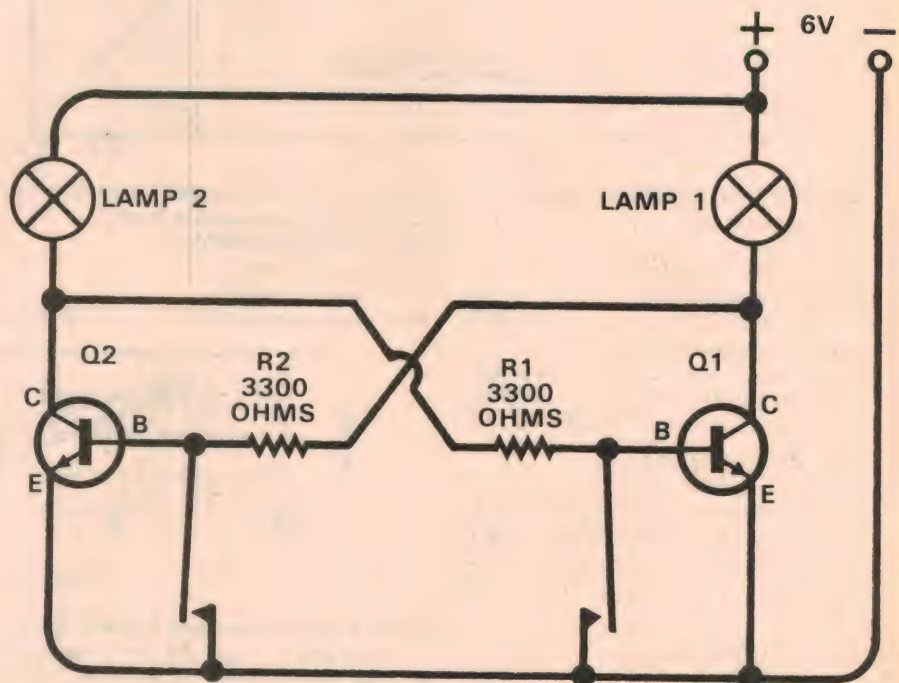
## PARTS LIST

- 2 resistors 3300 ohms or as selected
- 2 lamp holders
- 2 lamps 6 volts 0.1 amp (bicycle tail lamp type)
- 2 transistors BC 209 (National) or similar npn type
- 1 6 volt battery
- Nails, wire, brass.





## HOW THE BISTABLE WORKS

Before you study this board please make sure you understand the facts on the board called "The Transistor As A Switch".

A BISTABLE MULTIVIBRATOR is one of the three types of multivibrator. Bistable means—TWO STABLE. The bistable multivibrator has two stable states. Bistable multivibrators are sometimes called FLIP FLOPS.

The model and circuit diagram show a very basic bistable multivibrator. Connect the model to a 6 volt (NOT MORE) power supply, taking great care about polarity. You will see that one of the lamps comes on immediately and stays on.

Press the brass strip nearer to the lamp which is on. The other lamp comes on and the first lamp goes off. Press the other strip and the first lamp comes on again. Either lamp will stay on indefinitely, so the circuit has two stable states. The only way to switch from one lamp to the other is by pressing the switch near to the lamp which is on.

What happens is this: When power is connected, one transistor will switch on first—due to slight differences in the transistors. Suppose Q1 comes on first. This lights up LAMP1. The voltage at the collector of Q1 is now about 0.2 volt. This voltage is connected to the base of Q2 through resistor R2, and is too low to turn Q2 on. So Q2 stays off, and so LAMP 2 stays off.

When you press the switch near Q1, you are reducing the voltage on its base to zero—because the switch connects the base to the negative rail. This turns Q1 off, and then the voltage at its collector jumps to 6 volts. This is still connected to the base of Q2, and is high enough to turn Q2 on. And this is what happens. Q2 comes on and LAMP 2 lights up. A similar thing happens when you press the switch near Q2—and LAMP 1 comes on again. Pressing the switch is, in effect, connecting a negative going pulse to the base of the transistor.

More complicated flip flops have more components to make a "steering circuit" so that a series of negative pulses can come along one line and reach the correct transistor every time, and turn them off alternately.

Bistable multivibrators—flip flops—are one of the most common and basic elements used in digital computers and digital control equipment. They are used by the million—mostly inside integrated circuits.

If you like to consider the voltage at the collector of say Q1 as the "output" of a flip flop, then you can see that it can have only two values—high (about 6 volts) often called LOGIC 1, and low (about 0.2 volts) often called LOGIC 0. The output of a flip flop with a steering circuit would change from high to low and vice versa, every time a negative pulse reached it.

**NOW**

is the time to order  
**YOUR**

**76**

**callbook**


Don't wait until 1976 is half over. Get your new **Callbooks** now and have a full year of the most up-to-date QSL information available anywhere.

The new 1976 U. S. **Callbook** has over 300,000 W & K listings. It has calls, license classes, names and addresses plus the many valuable back-up charts and references you have come to expect from the **Callbook**.

Specialize in DX? Then you're looking for the new, larger than ever 1976 **Foreign Callbook** with over 225,000 calls, names and addresses of amateurs outside of the USA.

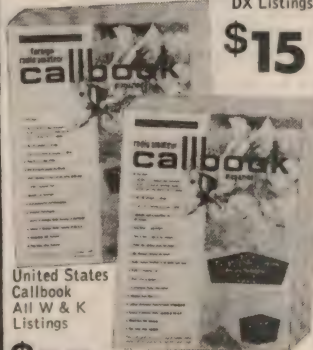**At Dick's Three Famous Electronics Stores NOW !**

Foreign Radio  
Amateur Callbook  
DX Listings



**\$15**

Send \$1.50 per Order  
for Packing & Postage

**DICK SMITH**  
**ELECTRONICS CENTRE**

Head Office & Mail Orders  
162 Pacific Highway Gore Hill  
N.S.W. 2065 tel: 439 5311  
telex: AA20036  
cables: DIKSMIT Sydney

Shop hours:  
Mon-Fri 9-5.30 Sat 9-12

Also at **CITY 125 York St**  
tel: 291126  
(N. Eam Hill)

and **BANKSTOWN**  
361 Hume Hwy  
tel: 709 6600  
(N. Creek Rd)



**bankcard**  
welcome here



# INDEX TO VOLUME 37—April 1975 to

## General Features

From a hi-fi ideal to a sonic earthquake .....	Apr	14
How safe are computers from sabotage? .....	Apr	28
Electromagnetic radiation in frequency measurements .....	Apr	31
Power FETs usher in a new breed of hi-fi amplifier .....	May	14
Solar cells: the promise of sunshine electricity .....	May	28
Frequency calibration using a colour TV set .....	May	33
Does loud music make you deaf? .....	Jun	14
The role of electronics in closed cycle living .....	Jun	26
Electronic technology and modern art .....	Jun	31
Motional feedback: a different approach to loudspeaker design .....	Jul	16
Sound-on-Slide: a new audio visual concept .....	Jul	30
Arcoibo: world's largest radio telescope .....	Jul	32
Confused about speakers? .....	Aug	12
Observatory aims for the stars with Cosmos .....	Aug	28
Robot technology—now and in the future .....	Aug	30
Automatic distortion reduction: the Akai A.D.R. system .....	Sep	15
Workshop computers for tomorrow's executives .....	Sep	28
Impressive advances in ultrasonic technology .....	Sep	34
New kit teaches digital concepts to tyros .....	Sep	60
Binaural microphones and headphones .....	Oct	12
The colour TV set as a daily newspaper .....	Oct	30
Electrically guided driverless vehicle system .....	Oct	35
Einstein's theory and the detection of gravity waves .....	Oct	36
Advanced radio communications for firefighting and rescue .....	Oct	41
Computerised modelling and laser techniques aid loudspeaker design .....	Nov	12
Nouveau, Neu, New! Cassettes and tapes from BASF .....	Nov	15
Educational TV via a satellite .....	Nov	26
New machine for the blind—for reading, writing and arithmetic .....	Nov	31
Computer system monitors racing car performance .....	Nov	32
Andrew Kay—inventor of the digital voltmeter .....	Dec	22
The Lightwriter—a new "voice" for the mute .....	Dec	24
The hunt is on for Spacelab scientists .....	Dec	26
Remote controlled vehicle for undersea exploration .....	Dec	30
Computers will automate shopping .....	Dec	31
A look into the electronic crystal ball: LSI technology and where it's taking us .....	Yearbook	
Some observers predict a floppy future for the video disc .....	Yearbook	
Ernst Alexanderson: GE's most prolific inventor ..	Yearbook	
New directions for the global electronics industry .....	Yearbook	

Two way radio for small boats .....	Yearbook	
The current state of the soldering art .....	Yearbook	
Amateur radio — background to this fascinating hobby .....	Yearbook	
Arthur Cushman talks about shortwave listening ..	Yearbook	
Melbourne's FM station beats the gun .....	Yearbook	
Hifi-stereo question box — the problems that puzzle enthusiasts .....	Yearbook	
The Quad current dumping power amplifier—a new approach .....	Jan	10
Wave power: energy for Britain's future .....	Jan	22
The world's first integrated circuit—in 1926! .....	Jan	24
Infra-red astronomy: a fresh look at the stars ..	Jan	26
How close to reality is artificial vision? .....	Jan	28
TV sound in the red—infra-red! .....	Feb	13
You, computers and society in the next two decades .....	Feb	34
Time diversity techniques for reliable HF teletype .....	Feb	38
NBS brightens the way for highway safety .....	Feb	40
Line output "jungle" ICs for colour and b/w TV sets .....	Feb	70
Developing a new recording tape .....	Mar	12
The impact of radio on the maritime services ..	Mar	28
Optical fibre techniques in avionics data transmission .....	Mar	32
When considering loudspeaker enclosures, how tight is airtight? .....	Mar	46

Introduction to digital electronics: Logic circuit "families" .....	Mar	92
Practical electronics demonstration: The bistable multivibrator .....	Mar	98

## Circuit and Design Ideas

Timer IC and photocell vary LED brightness .....	Apr	85
555 chip impulses pendulum .....	Apr	85
Note on audio oscillator .....	Apr	85
A low range ohmmeter .....	Apr	87
A LED synchroscope .....	Apr	87
LEDs monitor supply voltage .....	May	81
Motor reversing using silicon diodes .....	May	81
100-hour timer uses plating cell .....	May	81
Brake light pulser uses 555 chip .....	Jun	83
Simple combination lock for cars .....	Jun	83
Analog-computer-type active filter .....	Jul	77
Simple magnetiser or demagnetiser .....	Jul	77
Precision mV source from op amp .....	Jul	79
Crystal-derived 50Hz for clocks .....	Jul	79
Adding Ge-Si ident to TX-FET checker .....	Jul	79
Very low frequency converter .....	Aug	75
Alternative to high wattage zener diodes .....	Aug	75
Capacitance measuring adaptor for digital counter .....	Aug	75
Wobulator .....	Aug	77
Logic gates and LED indicate phase lock .....	Aug	77
A novel metronome .....	Sep	78
Cross modulators—a novel circuit .....	Sep	78
Accurate current generator .....	Sep	79
Simple volume expander .....	Sep	79
Economical crystal oven .....	Oct	77
Preamplifier for magnetic pickup .....	Oct	77
Sawtooth oscillator .....	Oct	79
Adjustable bipolar level with one reference ..	Oct	79
An unusual regulated power supply .....	Nov	77
Wow and flutter tests .....	Nov	77
Method of measuring amplifier distortion .....	Nov	77
Additional dividers for VNG reference .....	Nov	79
Simple educational device .....	Dec	65
Improvements to pathfinder unit .....	Dec	65
Front end protection technique .....	Dec	65
Metronome or code practice oscillator .....	Dec	67
An alternative to the Wheatstone bridge .....	Dec	67
Longer life for circuit board etchant .....	Dec	67
4-channel network for 2-channel amplifiers ..	Yearbook	
Transistor RF power amplifier hints .....	Yearbook	
FM tuning indicator .....	Yearbook	
Testing transformer temperature .....	Yearbook	
Solid state hang AGC .....	Jan	69
A 2.304GHz signal source .....	Jan	69

## Theory

Multiplexing LED digital display circuitry .....	Apr	50
Resistors — how to combine preferred values ..	Jun	55
Suppressing RF interference from model railways	Jun	59
Practical electronics demonstration: diodes .....	Aug	46
Practical electronics demonstration: transistors ..	Sep	66
LF quartz crystals in TO-5 case .....	Oct	53
Practical electronics demonstration: Ohm's law ..	Oct	82
Using the LM3900 quad op-amp IC .....	Oct	46
Practical electronics demonstration: silicon controlled rectifiers .....	Nov	80
Practical electronics demonstration: the unijunction transistor .....	Dec	80
Designing a speaker crossover network .....	Jan	58
Practical electronics demonstration: the field effect transistor .....	Jan	62
A new, updated Digital Electronics Course .....	Jan	72
Practical electronics demonstration: using the transistor .....	Feb	94
Introduction to digital electronics: Basic logic elements .....	Feb	96

## Constructional Articles

Swing over to stereo with an add-on decoder .....	Apr	34
Frequency reference derived from VNG .....	Apr	42
The 3-45L speaker system .....	Apr	54
Interfacing EDUC-8 with a Philips 60SR printer unit ..	Apr	66
Playmaster 145: 8 input stereo/mono mixer Pt 3 .....	Apr	74
Fluorescent readout LSI digital clock .....	Apr	88
A control unit for intermittent wiper action .....	May	34
Novel tapered column for "super bass" response .....	May	40
Building your own digital calculator — a guide .....	May	44
Light trigger for slave flashguns .....	May	48
Design for a PAL-S colour TV receiver Pt 2 .....	May	54
Using the Philips 10GHz Doppler module .....	May	64
A full ASCII-type input keyboard for EDUC-8 .....	May	72
The incredible Optomin .....	Jun	32
A direct conversion receiver for 3.5MHz .....	Jun	40
Design for a PAL-S colour TV receiver Pt 3 .....	Jun	42
Using one TV aerial for several sets .....	Jun	50
A high quality AM synchrodyne receiver .....	Jun	66
Teaching unit EDUC-8 to play a melody .....	Jun	77
Plug into the Sun with a solar cell array .....	Jul	34
IF strip with decoder for an FM stereo tuner .....	Jul	38
A simple ultrasonic movement detector .....	Jul	44
An upgraded capacitor discharge ignition system .....	Jul	46
LED flasher based on inexpensive IC .....	Jul	52
A general purpose record player .....	Jul	54
Interfacing EDUC-8 to teleprinters & magnetic tape ..	Jul	69
Direct conversion receiver — an addendum .....	Jul	97
RF front end for FM stereo receivers .....	Aug	34
Transistor-assisted ignition system .....	Aug	41
High quality speaker system uses KEF drivers .....	Aug	48
A frequency shifter for public address systems .....	Aug	54
Turn and brake lights for a trailer .....	Aug	61
Interfacing a Burroughs Self-Scan display panel to your EDUC-8 .....	Aug	71
Experimental 10GHz link using PWM & a Gunn diode ..	Sep	36
Playmaster 146 AM-FM tuner .....	Sep	48
Sustain unit for guitar amplifiers .....	Sep	58
Pathfinder and visitor alert unit .....	Sep	70
Quartz crystal drive for fluorescent readout clock .....	Sep	74
A simple gain tester for silicon transistors .....	Oct	42
Simple tachometer for auto tune-ups .....	Oct	47
Mains supply for car cassette players .....	Oct	50
Commercial front ends for PM 146 AM-FM tuner .....	Oct	54

1/MS/12		
7/RO/53		
1/SE/38		
2/CC/9		
1/MX/10		
2/CL/17		
3/MS/53		
1/SE/39		
2/CC/10		
3/EF/12		
6/COTV/2		
3/MS/54		
2/CC/11		
1/EM/35		
2/SW/64		
6/COTV/3		
6/ATV/11		
2/TU/41		
2/CC/12		
3/MS/55		
2/TU/42		
3/MS/56		
2/TI/12		
3/MS/57		
1/SA/54		
2/CC/13		
2/SW/64		
2/TU/43		
3/TI/13		
1/SE/40		
1/PA/31		
3/MS/58		
2/CC/14		
3/TI/13		
2/TU/44		
1/EM/36		
2/MS/35		
7/CL/18		
7/VT/12		
3/TM/11		
2/PS/36		
2/TU/45		
Solid-state "vibrator" circuit .....	Oct	58
Optical/magnetic preamplifier improves sound from 9.5 & 16mm projectors .....	Oct	66
Upgrading the Tucker Tm Mk II SSB transmitter .....	Oct	72
Loudspeaker protector prevents speaker damage .....	Nov	34
Fluorescent readout LSI digital alarm clock .....	Nov	38
Sharp-cut low pass filter for 9.5 & 16mm projectors ..	Nov	42
RF dummy load for testing transmitters .....	Nov	49
The measurement of "Q" and an economy Q-meter .....	Nov	70
Modified wiper pulser for variable speed systems .....	Nov	74
A dynamic noise filter for 9.5 & 16mm projectors .....	Dec	32
Voice-operated relay for tape recorders and transmitters ..	Dec	38
Water Warbler checks pot-plant soil moisture .....	Dec	42
Novus 650 calculator converts to a stopwatch .....	Dec	44
Bucket brigade device for audio time delays .....	Dec	60
Low-cost electronic dice .....	Dec	71
Additions to the automatic telephone exchange .....	Dec	72
Improving the Mk II PAL-S colour TV decoder .....	Dec	93
Electronic capture game for six or more players .....	Yearbook	6/COTV/4
Audio noise generator uses new digital IC .....	Yearbook	2/MS/36
Make your HP-45 calculator double as clock/timer .....	Yearbook	7/N/7
A sound and light experiment — how to build integrated speaker and light boxes .....	Yearbook	7/CL/21
Digital tachometer has switchable mph and kph readout ..	Yearbook	2/PC/20
Full size hifi speaker system .....	Yearbook	3/TM/12
Automatic lamp dimmer for creative moodlighting .....	Jan	1/SE/41
Stereo dynamic noise filter reduces tape hiss .....	Jan	2/PC/21
Simple noise transmitter for the 3.5MHz amateur band .....	Jan	1/F/10
A simple electronic mosquito repeller .....	Jan	2/TR/56
An electronic roulette wheel .....	Feb	3/MS/61
Save money on tune-ups with a power timing light .....	Feb	2/MS/38
Modulator and power supply for the novice transmitter ..	Feb	7/SC/5
Low cost alarm sensor is easy to install .....	Feb	2/TR/57
Build your own electrostatic loudspeaker Pt 1 .....	Feb	3/MS/62
A 30W 3-way vented loudspeaker system .....	Feb	1/SE/42
Electronic organ that's easy to build .....	Mar	1/SE/43
Novel 'LEDs & ladders' game .....	Mar	1/EM/37
Magic table lamp uses low-cost touch switch .....	Mar	3/MS/63
Crystal-locked converter for the LF and VLF bands .....	Mar	2/MS/39
Simple function generator based on a single IC .....	Mar	2/CV/21
DSB transmitter from junk-box parts .....	Mar	7/AO/23
Build your own electrostatic loudspeaker .....	Mar	2/TR/58
		1/SE/44



# March 1976

Unique continuity tester .....	Jan	71
Low-cost quality power supply .....	Jan	71
Reducing old valve receiver oscillator drift .....	Jan	71
Model railway signalling sensor .....	Feb	91
Battery condition indicator .....	Feb	91
Code practice oscillator .....	Feb	93
Discriminator displays 1st or 4 responses .....	Feb	93
Application for 74C14 CMOS Schmitt trigger .....	Mar	89
Try this IF noise limiter .....	Mar	89
Automatic brightness for digital clock .....	Mar	91
General purpose amplifier uses uA741c IC .....	Mar	91
Brake light warning indicator .....	Mar	91

## Forum

Electronics is a serious business! .....	Apr	60
Should Australia have a full-scale Citizens Band? .....	May	62
Snap reaction to "instant democracy" .....	Jun	64
AM sidebands: a mathematical fiction? .....	Jul	60
Why the ban on some colour TV sets? .....	Aug	64
Radio problem for small private boats .....	Sep	68
Who said the centimetre was dead? .....	Oct	62
Sidebands: as per a Fourier analyser .....	Nov	62
The colour balance in your TV set may be all wrong! .....	Dec	52
Forum looks at colour TV .....	Yearbook	
More about transformerless TV sets .....	Jan	54
Community aerials can be a headache .....	Feb	72
Time is running out for BC band DX .....	Mar	74

## Hi-Fi Reviews

Alpha HPE-777 Electret headphones .....	Apr	21
Sinclair Project 80 FM tuner & decoder .....	Apr	23
Technics RS-676-US stereo cassette deck .....	May	21
Kenwood KP-1022 player system .....	May	23
High performance belt-driven turntable: Micro Solid-5 .....	Jun	19
Audiosound Motet 2 "improved" loudspeaker system .....	Jun	21
Apan BFU-121 series 4000 automatic turntable .....	Jul	21
JVC 5515 FM-AM stereo receiver .....	Jul	22
Audiosound 75 ohm FM aerial .....	Jul	23
Sansui AU-2200 stereo receiver .....	Aug	17
New microphones from Primo .....	Aug	19
An economy FM-AM tuner .....	Aug	21
Sony STR-7035 FM-AM stereo receiver .....	Sep	19
Sound Technology's 100A measures THD down to 0.002pc .....	Sep	21
Yamaha CR-200 FM-AM stereo receiver .....	Oct	17
Sound Technology 1000A/1100A FM stereo multiplex test set .....	Oct	21
Quad FM3 tuner .....	Nov	17
Yamaha YP-450 turntable .....	Nov	21
Rotel RA-812 stereo amplifier .....	Dec	13
Yamaha YP-701 turntable .....	Dec	17
Yamaha CT-600 FM stereo tuner .....	Yearbook	
Peerless 20-3 loudspeaker system .....	Jan	13
Audiosound Motet 750 stereo system .....	Jan	15
dbx 119 Dynamic Range Enhancer .....	Feb	19
20W per channel amplifier from Dick Smith .....	Feb	23
Harman Kardon HK2000 stereo cassette deck .....	Feb	25
Yamaha TC-800GL stereo cassette deck .....	Mar	17
Sony ST-4950 FM tuner .....	Mar	21

## Regular Features

Editorial
HiFi news
News highlights
Record reviews — classical
Record reviews — devotional, popular, jazz & rock
The Serviceman
What's new in solid state
Letters to the Editor
Book reviews
New product reviews
The amateur bands
Shortwave scene
Information centre
Marketplace
Index to advertisers
Notes and errata

## Reference Data

Reference data: audio DIN standard; capacitor markings RIAA equalisation curve; noise weighing curve; equal loudness curves .....	Yearbook
Transistor data .....	Yearbook
Australian, NZ, PNG broadcasting services .....	Yearbook
How to use colour TV test patterns .....	Yearbook
Reactance-frequency chart .....	Jan
FM standards .....	Jan
The frequency spectrum—1 .....	Feb
Listing of common diode types and parameters .....	Feb
Disc Records—old and new .....	Mar
The frequency spectrum—2 .....	Mar

## NEW C800 STEREO AMPLIFIER

### SPECIFICATIONS

**POWER OUTPUT:**  
25 watts per channel R.M.S. Total output 50 watts R.M.S. 8 Ohms.

**FREQUENCY RESPONSE:**  
20 cycles to 40,000  $\pm$  1dB

**HUM & NOISE:**  
AUX. 70dB. Mag. 60dB.

**INPUT SENSITIVITY:**  
Mag. 2mv. Aux. 250mv.

**EQUALISED:**  
Mag. RIAA.

**TONE CONTROLS**  
Bass 50cs  $\pm$  13dB. Treble 10kcs 15dB.

**HARMONIC DISTORTION:**  
Less than 0.1 per cent.

**LOUDNESS CONTROL:**  
50cs 10dB.

**SCRATCH FILTER:**  
(high filter) at 10kcs 5dB.

**RUMBLE FILTER:**  
(low filter) at 50cs 5dB.

**PROVISION FOR TAPE RECORDER:**  
Record or playback with din plug connector.

**SPEAKER SWITCHING:**  
Two sets of speakers can be connected and selected by switch on front panel; they can also be drawn together.

**HEADPHONES:**  
Headphone jack is situated on front panel.

**DIMENSIONS:**  
16½in. x 11in. deep x 5in. high. Weight 16lbs.

**POWER SUPPLY:**  
Regulated power supply with switching protection for output transistors.

**SEMICONDUCTORS:**  
33 Silicon transistors plus 7 diodes.



### BY CLASSIC

- \* Elegant and functional design
- \* Push-button controls
- \* Microphone input with separate control
- \* Provision for simulated 4 channel stereo
- \* Cabinet in teak or walnut oiled finish with matching metal trim

**\$169** (FREIGHT EXTRA)  
WITHOUT CABINET  
\$157.00

## NEW MAGNAVOX—MV50— 50 WATT SPEAKER SYSTEMS

AS FEATURED IN FEB. 1976 ISSUE OF ELECTRONICS TODAY

Complete kit of parts (less cabinet) comprising magnavox 10-40 10" bass unit. 625 mid range 6" two XJ3 dome tweeters, crossover network, innabond, speaker silk & plans of cabinet.

**\$68.00**

Freight extra  
per rail  
or air freight.

CABINETS AVAILABLE

## MAGNAVOX 8-30 SPEAKER SYSTEM (4 WAY)

**DRIVE UNITS:** Magnavox 8-30 high performance 8" bass unit. Magnavox 6J 6" mid range speaker. Magnavox new high fidelity dome tweeters (two supplied).

**SPEAKER KIT:** (less cabinet) comprises above speakers, 1mh inductance, 1 8mfd. & 1 4mfd. polyester capacitor, 1-3" & 1-6" tube, innabond, speaker silk & plans of cabinet.

**\$48.00**  
per kit

Post & pack  
(Reg. post) \$2.50

CABINETS AVAILABLE

## SPECIAL FOR MARCH:

## PLAYMASTER 143 AMPLIFIER KIT



**\$62.50**

De Luxe version.

Reduced from  
\$80.00

Complete kit of parts including all transistors for this high fidelity 25 watt amplifier, silver anodised panel with black lettering and matching silver anodised knobs & special transformer with electrostatic shield. Reg. post & packing \$3.00 extra.

De Luxe version of the 143 amp. with high & low filters as used in the 140 playmaster plus loudness control \$7.80 extra.

Freight & packing extra. N.S.W. \$5.00. Vic., Qld. \$7.00. W.A., Tas. \$8.50 (Reg. Post)

**CLASSIC RADIO** 245 PARRAMATTA RD, HABERFIELD  
2045 PHONES 798 7145, 798 6507



# Classical Recordings

Reviewed by Julian Russell



## Wagner—The Mastersingers of Nuremburg

**WAGNER — The Mastersingers of Nuremburg. Complete Opera.** Karl Riddersbusch (Sachs); Hans Sotin (Pogner); Klaus Hirte (Beckmesser); Jean Cox (Walther); Frieder Stricker (David); Hannelore Bode (Eva) and others with the Chorus and Orchestra of the Bayreuth Festival conducted by Silvio Varviso. Recorded live at Bayreuth. Philips Stereo 6747 167. (5 Discs).

The Mastersingers means different things to many different people. To some it is a comic opera, originally designed to bring in some much needed cash to keep Wagner in funds while he was working on mightier projects. Wagner had intended it to be a send up of both the Minnesingers he used in Tannhauser and the historical Mastersingers of some hundreds of years later. But Wagner didn't start on the work for some 20 years after its conception and during that time he had so matured musically and dramatically, that he felt it necessary to expand the work to its present proportions.

Others see it — as did Hitler — simply as a glorification of "our holy German art" and the noble sentiments of the German people, with emphasis on the bourgeoisie. But not many, even those who revere it, see it in the subtleties pointed out by Gottfried Wagner (the composer's great grandson?) in his brief but illuminating notes that accompany the distinguished set under review. For, despite some very minor shortcomings, this is a very distinguished recording indeed. Gottfried point out that no character is always quite so simple as he or she seems at first acquaintance; that a character might be singing one thing while thinking something quite different. And if you are unaware of these complexities you will be vastly entertained in confirming them when you play the work.

Wagner, a master dissembler himself, was no slouch when it came to painting people with similar characteristics. He gives us a city full of people unsure of themselves and the outcome of their thoughts and actions, or even in the spirit of the times in which they lived.

There is one thing I must make clear

right at the start. Despite his name—Silvio Varviso—here is no Italian trained in the traditions of Italian opera conducting a work as echt-German as The Mastersingers. Quite the contrary. Varviso was born in Zurich—a German speaking province of Switzerland, though it is true that the German spoken there differs essentially from that used in Germany—where he did his musical studies. All his life he has been associated with German music, in particular opera, which he has conducted in the chief music centres of the world. So you can set your mind at rest that you are not going to hear an Italianised version of the opera. His is a superb reading of this massive work, constructed on a treasure chest of exquisite details in its observations of the strength and weaknesses of human nature. His control of orchestra, vocal soloists and chorus is as firm as it is sensitive.

Another important recommendation. This recording was made live at a Bayreuth performance but produces very little distracting noises which intrude from stage movements. Techniques in this form of recording have improved out of all comparison since the first recording—Parsifal—made in this manner some years ago. Of course some extraneous noises are inevitable in recording a live performance. Thus you can hear furniture being moved on the stage by the apprentices during Act 1, and again their clod-hopping dancing in Act 3. But the audience are absolutely silent until they break into enthusiastic applause at the end of every act. There is no coughing, for to cough during a performance at Bayreuth is to invite strangulation at the hands of your neighbour. I have been there, so that I am speaking from experience.

As to the performance recorded here, it starts with an overture that is always solid but never ponderous. And there is no perceptible change of acoustic when the curtain rises without a break onto the church scene with the congregation singing a hymn. All through the opera the balance between chorus and orchestra and other singers is faultless and offers a true reproduction of the marvellous acoustics of the Festspielhaus that Wagner designed himself at Bayreuth. Many

record buyers might find the names of many of the cast unfamiliar but all are good. Perhaps the best known will be Karl Riddersbusch who gives a noble performance of the cobbler-poet Hans Sachs. The part of course was written by the composer as he saw himself, leaving out all his warts and weaknesses that those who met him finally became aware of, usually to their discomfort and often pecuniary loss.

Riddersbusch's Sachs has his noble moments, and sees far into the musical future. But that doesn't prevent him having human shortcomings in the way of cunning and mischief.

Another superb portrait is Hans Sotin's Pogner, the rich goldsmith, bourgeois and proud of it, the kindly but stern father of Eva, the young heroine of the opera. Her lover, Walther (Jean Cox), has a fine tenor voice after some initial uncertainty at the beginning, and is above all, a youthful sounding swain without the Bayreuth "bark". He is alternatively ardent in his wooing, irritated beyond endurance by his treatment at the hands of his judges, the Mastersingers, and rhapsodic in his singing of the Prize Song.

Eva (Hannelore Bode) also has a refreshingly youthful sounding voice used expressively to characterise a girl, who despite her gentle obedient exterior knows just what she wants and how to set about getting it. Frieder Stricker's apprentice David enlivens his part so that his first act instructions of Walther in the Mastersingers' rules never become the bore they sometimes do. Stricker constantly entertains as well as instructs. Beckmesser (Klauss Hirte), too, is not the grotesque idiot he is sometimes made to appear but instead a man convinced of his own rectitude, however mistaken his ideas. He makes a splendid contrast to Pogner's Rembrandt-like portrait of a rich, fur-clad burgher and Sach's leather-aproned shoemaker.

Not a point is missed by Varviso in his interpretation of the ever changing score whether it is the pomp of the Mastersingers, the swooning beauty of the Midsummer Night's music, the malice of Beckmesser, the lovely lyric passage between Pogner and Eva and the true magnificence of the chorale "Wach Auf."

There have been other good recordings of The Mastersingers but for my book this is the best that has so far appeared. True it is not absolutely perfect. But then a really perfect performance of this grand work is well nigh impossible to achieve, even with all the resources of a studio performance, where unsatisfactory bars can be cut out and others substituted. And don't forget that this is a live performance and therefore an invitation for things to go wrong. But there are here so few, even in the great fugue at the end of Act 2, that to have seen and heard it must have been a wonderful experience.



**RACHMANINOV—Piano Concerto No. 2 in C Minor. Variations on a Theme by Paganini. World Record Club Stereo C 00361 (0663-2).**

Although this is not Dolbyised it was recorded in stereo. The sound is reasonably good with some almost negligible background noise. The balance between soloist and orchestra is mostly good but I would like to have heard a little more of the orchestra in the fortissimo tutti in the second movement of the piano concerto. This composition is one of the most popular concertos in the current concert repertoire and much of it has been used for other purposes—the background music for the Noel Coward film *Brief Encounter*, for instance.

There are a few moments of discomfort in the engineering. In the second movement of the concerto the flute loses some of its characteristic timbre and the general tone coarsens. This I corrected for a while by switching on the Dolby control but soon reverted back to non-Dolby when the piano part became altogether too assertive at the expense of the orchestra. The playing of both soloist and orchestra is fine.

Both use very fast tempos in the Paganini Variations but the music is always under firm control by both. In this work and the concerto conductor and pianist use some very robust romantic treatment which, to my mind, is essential to a successful performance of either work. I also thought the balance between piano and orchestra consistently better than in the concerto though not up to the highest standards. Let's hope a Dolbyised version of the whole production might be issued some time in the future. The performances will warrant it. By the way, when Shostakovich Jnr. was out here last year, he told me that the correct Russian pronunciation of Rachmaninov's name is "Rachmaneenov" and that he, Shostakovich, pronounced his name with the accent on the second syllable.

★ ★ ★

**LAURIS ELMS (contralto) with GEOFFREY PARSONS (piano) in a recital of songs by Schubert, Liszt and Duparc. World Record Club Dolbyised cassette C 02224.**

Here is an Australian recording of world class, engineered by the Australian Broadcasting Commission for release to the members of the World Record Club in Australia. I have only one fault to find with the whole production—no texts accompany the songs, though admittedly some are well enough known by the average record buyer or concert-goer to need none. Ms Elms voice is a rich contralto, always expressive, always smoothly produced throughout its extremely wide range.

The makers of this cassette have no reason to feel timid about its release in any of the recognised music centres abroad. When necessary, Ms Elms can

## Mozart—Complete Wind Music: recommended

**MOZART—Complete Wind Music. Divertimentos, Serenades and so on played by the London Wind Soloists conducted by Jack Brymer. World Record Club Stereo Nos. 4771-2-3-4-5. (Five boxed Discs.)**

Although this set was first recorded some 13 years ago it is still very worth while acquiring, especially at its club price. It was hailed as an example of a very high standard of engineering in its day and it remains excellent, even by the highest of modern standards. Nowadays there are several competing wind groups but none that I have heard excel this English combination. There is no showing off, no spotlighting of soloists. All, under Jack Brymer, just play the music for what it's worth. All five discs are distinguished by the same highly faithful recording of the sound. And the players' skill is never in doubt during a single item. When one remembers that most of these works were written for performance in the open air and that wind instruments can have an ear-piercing quality, much ingenuity was displayed by the recording engineer in the matter of

restricting the dynamic range to within range of comfortable listening in an average sized music room.

As to style, this is the kind of Mozart I was brought up on and find it flawless here. And I must make special mention of the way the timbres of the various instruments are superbly blended. To my ear Brymer chooses just the right tempo for each item. Many of these pieces are masterpieces, others perhaps not quite so exalted. But to have them all in the one set to play at will—I cannot imagine anyone settling down to listen to all at one sitting—is an unqualified blessing. Although the title "complete wind music" is a little misleading when one remembers divertimenti of doubtful origin which have been omitted, a couple of cavalry band items also omitted, and a few other negligible pot-pourris, you will find in this collection all the music of importance that Mozart wrote for wind instruments alone. And among them you will find much to enchant you, including some that the most enthusiastic of Mozartians will be hearing for the first time. Highly recommended.

hold a tranquil sounding note for a surprising length of time. The Lorelei included in the recital is not the familiar Schumann setting of Heine's poem but another, less familiar one by Liszt. The accompanist is Geoffrey Parsons, one of the world's best and, as a rule, I admire vastly everything he does. I in no way subscribe to the theory that an accompanist should be self-effacing and Parsons is never guilty of this practice. But in the Lorelei I do think that for once he overplays the dramatic piano part here and there. But this is the only slight blemish on an otherwise perfect combination of singer and pianist.

Ms Elms' diction is always exemplary even when one concedes that her French accent is not always that of the 16th arrondissement. And it is unusual to find non-French singers able to cope as she does with the sometimes cruelly long French legatos. Importantly Ms Elms, despite the unquestionable beauty of her lower register—and all the others for that matter—never indulges in the contralto hoot so popular, alas, with so many English oratorio singers. Some listeners might object to an occasional portamento up to a high note though others will maintain just as vigorously that it is quite permissible wherever she uses it. I find it incredible that Ms Elms should be represented in the English Gramophone Catalogue only by a smallish part in Britten's *Pete Grimes*. I think this is depriving a large record buying public of a most enjoyable experience. Here is singing to delight connoisseurs and ordinary music lovers alike and Australia may well feel proud of the two artists on

this cassette. By the way I also have discs recorded by Ms Elms that I shall be reviewing in later issues.

**FERGUSON**

*Manufacturers of:  
Electrical / electronic  
equipment, wound  
components and  
lighting control  
equipment.*

**BRANCHES  
IN  
ALL STATES**

**Ferguson Transformers  
Pty Ltd.**

Head Office  
331 High Street, Chatswood  
NSW 2067

PO Box 301 Chatswood,  
NSW, Australia 2067

**Phone: 02-407-0261**





## Lighter Side

Reviews of other recordings

### Devotional Records

**THE NEW COVENANT** by John Fisher. Stereo, Light LS-5658-LP. (From Sacred Productions Aust., 181 Clarence St, Sydney and other capitals).

Christian musicals seem to be making their appearance as regularly as their non-devotional prototypes and there is no doubt that they are providing church musical groups with an incentive to sharpen their talents and to present the Gospel message in a new way.

This one is endorsed "A Teaching Musical" and, as such, contains a fair amount of spoken commentary between the numbers. In a sense, it might be regarded as a sermon in music, with the theme based on the need to live a genuine Christian life rather than merely to act the role.

The track titles are as follow: Let It Be Free—What Has Gone Wrong—Evangelical Veil Productions—Ways and Means—Alleluia—The Way Of Peace—I'm A Vessel—We All Get Hurt—We Have Died—Rest In Him—Alleluia (Reprise).

"Evangelical Veil Productions" is a bright, humorous number that is nevertheless the cornerstone of the musical. On the recording, at least, interest tends to sag a little after this number until things get going again on side 2, but this would not necessarily be the case with stage production. It's well worth a hearing, if you are on the look out for a new production or merely interested in Christian musicals. I gather that guitar and vocal scores would be available. (W.N.W.)

★ ★ ★

**GENTLE AS MORNING.** The Anita Kerr Singers. Stereo, Word WST-8646-LP. (From Sacred Productions Aust, 181 Clarence St, Sydney and other capitals).

Over many years, one has grown to accept the Anita Kerr Singers as an essential part of the Nashville scene, providing skilled backing for many featured artists. It comes as a surprise therefore, to learn that, for a considerable time, they operated from west coast USA; further, that

Anita Kerr now lives with her husband and two daughters in Switzerland, with London as her prime recording base.

In this album, the first of a new series, she has teamed up with the Word organisation to produce records and choral books. Her multi-role in this one includes arranger, conductor, soloist and mix-down controller.

With a generous rhythm orchestra and chorus, this talented and attractive artist presents ten tuneful modern style devotional songs: Sunday Morning—I Believe Now—Gentle As The Morning—Sonshiny Day—Gentle Like You—Don't Play The Game—Walk His Way—Live Love—That's For Me—And I Believe Him.

Fully imported from USA, the sound is very smooth and pleasant with just one slight technical blemish: a tendency for the sibilants on solo voice to blast

### Instrumental, Vocal and Humour

**THE FLIGHT OF THE BUMBLE BEE.** Attack On Limit. W&G QX quadraphonic WG-35/Q/5628.

The "Attack On Limit" part of the title is somewhat obscure but the jacket notes refer to the special "Master Sonic" cutting method used for this regular matrix recording, and to the use of electronically contrived sound to supplement the normal orchestral instruments. Either could account for the title.

But details aside, the album recorded in Tokyo by the Nippon Columbia Co Ltd has a very clean sound, easy on the ear, and featuring six well known neo-classical excerpts: The Flight Of The Bumble Bee (Rimsky-Korsakoff)—Zigeunerweisen (Pablo de Sarasate)—Fantasie Impromptu (Chopin)—Turkish March (Mozart)—Hora Staccato (Dinicu)—Carnival Of Venice (Benedict).

Some may be turned off by the admixture of synthesiser type sounds but, here anyway, they are merged into the orchestra, rather than being highlighted in any particular way. And, while a quadraphonic system can spread the

occasionally. But don't let that deter you if you would like to hear Anita Kerr and her singers "doing their own thing". (W.N.W.)

★ ★ ★

**THIS COULD BE THE DAY.** Mickey Holiday. Stereo. Singcord ZLP-897S. (From S. John Bacon Publishing Co, 12-13 Windsor Av, Mt Waverley, Vic 3149. \$6.95)

Mickey Holiday is a new name to this reviewer but he is pictured on the jacket of this American pressing as a youngish vocalist who would have obvious appeal on the Gospel rally platform. His voice is a pleasant baritone and one's first impression is that this is to be a recording of popular Gospel songs with a faint C&W flavour. But the style, and particularly the backing arrangements become more obviously orchestral, with even a trumpet chorus for "King of Kings and Lord of Lords", reminiscent of the "Hallelujah Chorus". Other titles are: Praise The Lord—This Could Be The Day—Thank You Jesus—Believe It Like It Is—My Prayer—Wise Men Should Still Seek Him—All I Need—Heaven—Come, Come.

In typing the list I noted that eight of the ten titles are endorsed "Holiday/Singspiration"—apparently his own compositions, with Singspiration as the publishers. The technical quality is good and you can buy with confidence if the titles appeal. (W.N.W.)

★ ★ ★

**SPECTACULAR CHORUSES.** The Philadelphia Orchestra under Eugene Ormandy with the Philadelphia Chorus, directed by Robert Page RCA Red Seal ARL 1-0580.

"Spectacular" is indeed the word for these high-powered performances of ten best known choruses with titles like: Land Of Hope And Glory—The Exodus Song—La Marseillaise—Battle Hymn Of The Republic—On Great Lone Hills (from Finlandia)—Meadow Lands—Hatikvah—Rule Britannia—Glory, Glory—The Star Spangled Banner.

Rule Britannia almost gets the 'Mesiah' treatment but all in all, it is a record of excellent quality, ideal to stir one out of any lethargy. It shows what musical professionalism is all about when you hear a record like this. I would highly recommend it as a demo disc. (N.J.M.)



**DONALD McINTYRE SINGS WAGNER.** The New Zealand Symphony Orchestra, conducted by John Matheson. Stereo, Kiwi SLD-39. (From local record shops or direct from Crest Record Co, 122 Chapel St, St Kilda, Vic 3812.)

By chance, two snippets of conversation preceded my listening to this recording: "I thoroughly dislike operatic excerpts; the whole work or nothing"; and "I like Wagnerian opera in small helpings . . . a full opera is a bit too heavy!"

If you happen to share the second view, read on. This is an all New Zealand record, recorded in Wellington Town Hall with the N.Z. Symphony Orchestra; conductor for the occasion was John Matheson, born in Dunedin, but with a considerable background as an operatic conductor at Covent Garden and elsewhere. Soloist Donald McIntyre was born in Auckland and is described in the jacket notes as the World's leading Wagnerian bass baritone, with an impressive record in the musical centres of Europe. Recorded under the auspices of the Arts Council of New Zealand, the album itself won the country's award as the best cultural merit album, with a similar tribute to the special double-fold cover. One can well understand why.

The excerpt titles are: Der Fliegende Hollander: Dit Frist Is Um. Die Meistersinger: Was Duffet Dock Der Flieder (Act II) and Wahn! Wahn! Uberall Wahn (Act III). Lohengrin: Du Furchterliches Weib (Act II). Die Walkure: Leb Wohl, Du Kuhnes (Act III).

To by hypercritical, the recording may lack somewhat in sparkle at the treble end, but it is smooth and quiet. In summary, if your interest lies in this direction, you should find this recording from across the Tasman a very satisfying purchase. (W.N.W.)

★ ★ ★

**THE MAGIC OF VIENNA.** June Bronhill, Peter Jeffs Eric Shilling; With the Gaiety Orchestra conducted by George Barker. Stereo, Astor SPLP-1450.

An unusual album, this; a program of Viennese style operetta, capably presented by the artists and orchestra listed above. It may be appropriate initially to list the excerpts and composers for your guidance: Werner March (Ziehrer)—I Must Behold Her ("The Conspirators", Schubert)—The Alligator and the Brahmin's Daughter ("The Beggar Student", Millocker)—I Gave My Heart ("Du Barry", Millocker)—Fragrance of May ("Count of Luxembourg", Lehar)—Pig Breeder's Song ("Gipsy Baron", J. Strauss Jr)—Polka Dance ("Count of Luxembourg")—Chambre Separee ("Opera Ball", Heuberger)—Fleet of Foot (J. Strauss Jr)—A Slap In The Face ("Beggar Student")—Roses In Tyrol ("Der Vogelhandler", Zeller)—Schonbrunner Waltz (Lanner)—Love Live For Ever ("Paganini", Lehar)

— Rector and Director ("Der Vogelhandler")—Love And Age ("Count of Luxembourg").

As will be evident it is a generous program and the presentation is equally generous, with detailed notes on the music and the artists, together with pictures, inside a handsome double-fold jacket.

The sound from the smallish Viennese style orchestra is intimate rather than expansive but it is completely clean. If the program appeals, you'll enjoy the album. (W.N.W.)

★ ★ ★

**THE JOLSON REVIEW, featuring Dai Francis.** United Artists L 35562 Festival Release.

Any one who remembers the 'Black And White Minstrel Show' on TV a few years back will recognise the format and quite a few of the voices, particularly Dai Francis.

Including the medleys, there are at least two dozen titles to enjoy, some of these are: Shaking The Blues Away—Alabama Jubilee—Rock A Bye Your Baby—Sonny Boy—Anniversary Song—He's Got The Whole World In His Hands—When The Saints Go Marching In.

The whole record has a bright and bouncy sound to clear away the blues. (N.J.M.)

★ ★ ★

**DES O'CONNOR, WITH FEELINGS.** Astor Release SPLP 1453

I must admit to being a Des O'Connor fan, particularly for his TV shows, and this record only reinforces my enthusiasm

The twelve titles are: Feelings—The Way We Were—Twelfth Of Never—I Won't Last A Day Without You—Misty—Spanish Eyes—Empty Chairs—Make It With You—Love Me Tender—Welcome To My World—You Were Meant For Me—So Close.

The musical backing was organised by Colin Keyes and the record would make an excellent addition to your ballad collection. (N.J.M.)

★ ★ ★

**JAMIE REDFERN'S GOLDEN HITS.** Jamie Redfern. Festival L 35724.

Jamie Redfern is a product of "Young Talent Time", and a protege of Liberace. With credentials like these, he shouldn't need much introduction, especially since this year he was crowned "King Of Pop". It should be sufficient merely to list the songs included on the record: When You Wish Upon A Star—I Thank You—Over The Rainbow—I Believe—Little White Cloud That Cried—Rainbow On The River—Once Every Year—Venus—Jenny—You'll Never Walk Alone—Tie A Yellow Ribbon—Hitch A Ride On A Smile—We'll Meet Again.


Technical quality is quite good, so if you're a fan, go ahead and purchase. (D.W.E.)

# LAFAYETTE
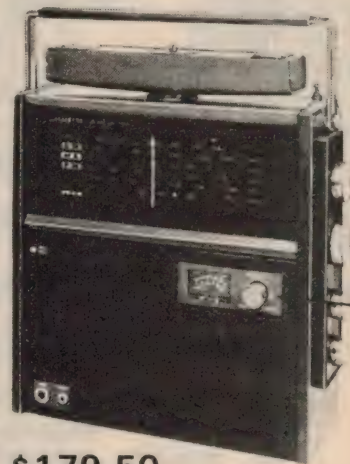
## "GUARDIAN 6600"

Direction Finder 6 Band Radio

Beacon—Broadcast—Marine  
FM—Aircraft—VHF



\$179.50

### 6 BANDS

(1) 160-390KHz Beacon (2) 550-1600KHz Broadcast (3) 1.6-4.6MHz Marine (4) 88-108MHz FM (5) 108-136MHz Aircraft (6) 147-174MHz FM VHF

BATTERY OR 240V AC OPERATION  
(With External Adaptor—Optional Extra)

### Features

- Rotatable Antenna for Direction Finding & Reception on Beacon, Broadcast & Marine Bands.
- Telescopic Whip Antenna plus External Antenna Jack for Reception on FM, Aircraft & VHF Bands.
- Signal Strength, Tuning/Battery Meter.
- Adjustable Squelch Control.

The "Guardian 6600" is Lafayette's most advanced Portable Radio for top reception plus Direction Finding. 19 Transistors, 15 Diodes and 2 Thermistors. Individually tuned circuits for best performance on each band. Adjustable RF gain control varies sensitivity and tuning meter for direction finding purposes. Supplied complete with comprehensive Operating Manual.

SIZE: 11½" W. x 10½" H. x 3¾" D. Shipping Weight 6 lbs.

## LAFAYETTE ELECTRONICS

d/v. of Electron Tube Distributors P/L  
94 ST. KILDA RD. ST. KILDA  
VIC., 3182 Phone 94 6036

Also available from  
RADIO HOUSE PTY. LTD., 306 Pitt Street and 760 George Street, Sydney, N.S.W.  
DICK SMITH ELECTRONICS CENTRE, 160 Pacific Hwy., Gore Hill, N.S.W.



# IMPORTED DUTCH PHILIPS speaker kits . . .

**POPULAR (7B)  
KIT OPTIMISES  
AMPLIFIERS FROM  
15-40 WATTS R.M.S.  
FOR NON-COLORED  
30-20,000 HZ RESPONSE. KIT - \$129 PR.**

Kit includes plans, all hardware and features the Philips 12B5 W8 woofers, sealed back midranges AD5060, ADO160/T8 tweeters and the exclusive G.H.E. crossover.



## 16 KITS . . . . . \$28-\$398 PR.

	Power W.	Frequency Range	Kit Price Pr.
7A1	15-50	25,20,000 Hz	\$229.00
7A	15-60	25-20,000 Hz	\$198.00
7B1	15-40	28-20,000 Hz	\$153.00
7B	12-38	28-20,000 Hz	\$129.00
7C	8-28	25-20,000 Hz	\$122.40
7D	6-25	25-20,000 Hz	\$89.96
6A	15-50	40-20,000 Hz	\$193.30
6C	4-18	25-20,000 Hz	\$69.00
5A	6-30	30-20,000 Hz	\$140.00
4A	8-30	40-20,000 Hz	\$140.00
3A	8-20	50-20,000 Hz	\$84.14
AD 8K40	15-40	55-20,000 Hz	\$87.84
ET1 400	15-40	30-20,000 Hz	\$87.98
3B	6-15	45-17,000 Hz	\$28.00
21	20-60	40-20,000 Hz	\$263.50
22	20-60	38-20,000 Hz	\$398.00

- ALL KITS COMPLETE ALL HARDWARE
- UNCONDITIONAL GUARANTEE 1 YEAR
- ENCLOSURE DESIGN SERVICE

TIMBER NOT INCLUDED

## HITACHI UDC 90 TAPE 12 PACK PRICE OF \$29

Voted by HI-FI review June 1975 as best performance/value for money tape available. 36 pack \$78.00, 60 pack \$125.00. UDC60/120 available at special savings too!



**USE OUR RAPID MAIL ORDER  
SERVICE—Despatch same day!**

**G.H.E.**  
GEORGE HAWTHORN ELECTRONICS PTY

ADD 5% FOR P&P  
966 HIGH STREET,  
ARMADALE VIC.  
TELEPHONE  
509 0374, 509 9725

## LIGHTER SIDE—continued

**LOWREY SHOWCASE.** Ray Thornley. Stereo, Troubadour TSE-041. (From local record shops or direct from Unison Productions, 118 Terry St, Rozelle)

I gather that this album has been around for some time but it has proved to be a consistent seller, because people who happen to hear it insist on buying a copy of their own. The reason is clear enough: the sound is gentle, rhythmic, varied and always very easy on the ear—ideal for relaxation or a candle-light dinner, particularly the latter.

Ray Thornley is a young Sydney organist who first took up the instrument as a diversion from University studies. Here, in true professional style, he plays a program of thirteen numbers:

Rhythm Of Life — Fiddler On The Roof — Misty — Serenata — Spanish Harlem — Scarlet Ribbons — El Cumbanchero — And I Love You So — Michelle — The Twelfth Of Never — Under The Double Eagle — My Cup Runneth Over — Yakkety Sax.

The recording is clean and quiet and the range of voices sufficient to quicken the interest of any popular organ enthusiast. (W.N.W.)

★ ★ ★

**THANK YOU BABY.** The Stylistics. Avco stereo L 35551.

The Stylistics are pleasant a pleasant hybrid of the Temptations and the Four Tops. Their strong point is harmony while their weak point is lack of the services of a good songwriter. Most of the songs on this album are innocuous and forgettable. They deserve better. Record quality ranges from good to fair.

Ten tracks are featured: Thank You Baby — Can't Give You Anything (But My Love) — What Goes Around Comes Around — I'd Rather Be Hurt By You (Than Be Loved By Somebody Else) — Disco Baby — Tears And Souvenirs — A Honky Tonk Cafe — I'm Gonna Win — Stay — Sing Baby Sing. (L.D.S.)

## CLASSICAL ORGAN: "Pride of place" . . .

**ORGELMUSIK IN DER WIESKIRCHE.** Franz Lorch. Pelca, stereo PSR 40 588. (From local record shops or direct from Crest Record Co, 122 Chapel St, St Kilda Vic 3182.)

I might have been able to pass on a great deal more information about this fully imported German album, had I been able to read the language. For those who can do so, the jacket contains detailed notes about the music, the church, the organ, and the player. I gather, however, that the church is in "Sound Of Music" country in Bavaria, dating back to about 1730. Outside the design is conservative but, inside, it is the most ornate and highly decorated church I have ever seen.

The organ presumably dates back to the same era, though presumably reconditioned and modified much more recently. Whatever the details, it is an outstanding example of the European organ builder's art, with pipes at every possible footage from 16' to ½', and tone colours from round flute to near-percussive, from chiff-rich to Krummhorn. It is one of the brightest, cleanest organ sounds you are ever likely to hear and the recording quality merits the same description. In fact, when I played it in our laboratory listening room, at least two other members of the staff decided on the spot to buy a copy for themselves.

The music, dating back also to the eighteenth century includes: J. S. Bach: Fantasie G-Dur BWV 572; Triosonate Nr C-Dur BWV 529. D. Buxtehude: Praludium und Fuge F-Dur; J. Pachelbel Partita, Christus, der ist mein Leben. V. Lubeck: Praludium und Fuge E-Dur.

The organist Franz Lorch is a musician of high repute and gives a performance which is virtually flawless, even if slightly clinical.

But one thing is certain: if you are interested in the classical organ sound, this album is likely to take pride of place in your record collection. Recommended. (W.N.W.)



**THE BEST OF DUKE ELLINGTON.** Jazz of World War II. Joker mono SM 3134.

This album is one of a complete series entitled "History of Jazz" produced on the Joker label and originating from Milan, Italy. The particular album would appear to have been remastered from original 78 rpm masters. As such, the quality is reasonably clean, even if greatly limited in bandwidth.

Any keen collector would consider this album of Duke Ellington performances worthwhile. In many ways I find it much more satisfying than his later performances, particularly those in his latter years.

Tracks featured are: Creole Love Call – It Don't Mean A Thing – Harlem Air-Shaft – The Kissing Bug – Prelude To A Kiss – Ring Them Bells – Diminuendo in Blue & Crescendo In Blue – In The Shade Of The Old Apple Tree – Frankie & Johnny. (L.D.S.)

Joker records are distributed by the Crest Record Company, 122 Chapel St, St Kilda, Victoria. Postal enquiries should be directed to P.O. Box 270, St Kilda, 3182.

★ ★ ★

**SONGS FOR LIVIN' & LOVIN'.** Heather McKean. Festival stereo L 35565.

Heather McKean sounds like Australia's answer to Loretta Lynn. I think it is a pity that so many C & W artists are content to mimic their peers rather than try to develop a style of their own. Heather McKean certainly has personality but would do better not to exaggerate her assumed nasal twang. Instrumental arrangements are typical of C & W and recording quality is good.

Track titles are: I Can Feel Love – Afraid To Live And Afraid Of Dying – Crack Of Dawn – I'll Always Be Your Woman – Just A Little Place To Cry – The Best Years Of My Life – Right Or Wrong – Hello Out There – Put It Off Until Tomorrow – All I Need Is You – Portable Blackmail – I'd Do As Much For You. (L.D.S.)


★ ★ ★

**HARPS ON MY MIND.** Hank Meadows. RCA Victor stereo VPL1-4014.

I must admit to being rather partial to harps and so it was with pleasant anticipation that I put this disc on to play. And I must concede that the instrumental work is very good and easy on the ear. But four tracks are spoilt when Hank Meadows is moved to sing. He moves me too but in a different way. He has a range of all of half an octave, sings mostly flat and often horribly off key.

If you don't mind skipping those tracks which have been spoilt, it is still very pleasant listening. Sound quality of the album which was recorded in Australia is excellent.

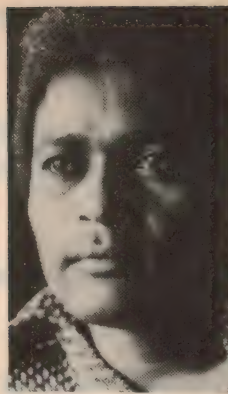Eleven tracks are featured: Venus – Dirty Old Man – Donna's Samba –



**CHARLEY.**  
Charley Pride.  
RCA Victor  
APL1-1038.

Charley Pride has eleven Gold Records, as well as numerous awards and this, his twenty-third album, certainly has the professionalism that one would expect. His deep, country voice wends its way through ten ballads in a very pleasant way.

While none of the tracks had any immediate and overwhelming appeal, I did enjoy listening to them. I have a feeling that this album will be a "grower"; its appeal will build up with playing.

As is usual with this label, record quality is quite good. As a bonus, a large colour poster is included with the record. (D.W.E.)

Amazing Grace – Blue To Green – Rain – Children's Games – Killing Me Softly With His Song – Rainy Days And Mondays – Morning Has Broken – Venezuela. (L.D.S.)

★ ★ ★

**THIS IS ME.** Caterina Valente. Astor stereo SPLP 1446.

Even when sleeve notes are brief they can over-praise. On this album they state that Caterina Valente's talent is vast and phenomenal. Most people are aware that Valente can sing in many languages. Well, my first thought on hearing this album was that mediocrity knows no language bounds.

Recorded live, the album indicates that, at best, Caterina Valente is a

**STEAM TRAINS: Kiwi style**

**A POWER OF STEAM.** Historic sounds of locomotives in the North Island of N.Z. Mono, Kiwi LC-48. (From Crest Record Co, 122 Chapel St, St Kilda. Vic 3182.)

Travelling just north of Wellington, a year or so back, I suddenly spotted on the tracks nearby a compact but impressive looking steam loco, surrounded by a crowd of enthusiasts—typical of steam enthusiasts the world over.

And just as typical is this recording, which I would infer from the notes to be the fourth such recording in the Kiwi catalog. Side 1 is devoted to the Ka 945 and 955 express locos, recorded passing

reasonably talented club singer; at worst, a vastly over-rated performer. Two tracks represent the nadir of her performance: "Dominique" which she lah-lahs through with a drunken Italian named Silvio Francesco and "Mother Gooseova" which is every bit as intellectually insulting as can be imagined. Other points of irritation are Valente's woefully overdrawn phrases and the brassiest of club orchestras.

Those still interested because of their misplaced jingoism will no doubt be unfazed by the comment that recording quality is poor on some tracks and run-of-the-mill elsewhere. My lack of enthusiasm prevents me from listing the track titles. (L.D.S.)

★ ★ ★

**REMEMBER DIANA.** Paul Anka. RCA Gold Seal ANL1-0896.

A listen to this re-issued album of Paul Anka has confirmed what I remembered of him and his songs: A mediocre singer with the most trivial of songs. Still, it was innocuous I suppose. But why revive it? It sounds even more trite now than it did fifteen or so years ago.

The ten forgettable tracks are: Diana – Love Me Warm And Tender – Put Your Head On My Shoulder – Puppy Love – Eso Beso – Remember Diana – You Are My Destiny – In The Still Of The Night – Love Makes The World Go 'Round – A Steel Guitar And A Glass Of Wine. (L.D.S.)

★ ★ ★

**A HOLIDAY IN GREECE.** Manos Tacticos & his Bouzoukis Astor Golden Hour GH 591.

If you have a liking for music in the Greek style, this record would surely be your bag. With twenty-one titles to pick from (the only ones I can recognise are 'Never On A Sunday' and 'Zorba', the rest being in Greek) and one hour's playing time, you certainly get your money's worth. The quality is good but the level is lower than usual, to avoid problems with the extended playing time. (N.J.M.)

the microphone, from a pacing vehicle, and from within the train itself. On side 2 is featured Bb 144, banking engine Ka 943 assisted by a Da 1461 diesel (treason surely!) and another Ka class (943).

From this side of the Tasman, one can only rely on the jacket notes for some idea of the locos and the locale but the sound will still be music to the ears of steam enthusiasts—even though rather sad music recorded in the 1965/6 era as the steam locos were being phased out of everyday service.

Technically the sound is a trifle lacking in top-end "bite" but it is quite clean, well up to the average enthusiast mono recording. (W.N.W.)



# New Products

## CL8963/H Doppler Alarm from ED & S

Doppler burglar alarms (sometimes called "radar") are a novel way of protecting property. An alarm of this type, specifically intended for use in the home, was recently submitted to us by Electronic Developments & Service Pty Ltd.

This alarm, designated type CL8963/H, is based on the Philips doppler module which we featured in the May 1975 issue. Actually, we presented the type CL8960, which only differs from the CL8963 in operating frequency.

The CL8963 is pre-set to 10.525GHz, the frequency approved by the Postal and Telecommunications Dept for doppler alarms. No licence is required for alarms operating on the approved frequency.


As sold, the alarm consists of a single die-cast box containing the doppler module, power supply, audio oscillator and wobulator on three fibreglass PCB's. A horn speaker and power supply completes the set-up.

The doppler module is mounted rigidly on one side of the box, with a cut-out for the microwave beam. The opening is covered by a thin piece of plastic. This, together with the plastic coating on the box itself, makes the unit impervious to moisture. The plastic coating is available in 16 colours.

Immediately above the cut-out is mounted a single LED, which glows whenever movement is detected. Apparently this is included so adjustments to sensitivity, etc, can be made

with the speaker turned off (via a switch).

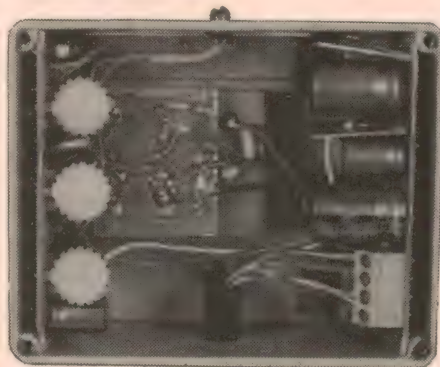There are three preset pots mounted just inside the lid. These control, in turn, sensitivity, alarm "on-time" and alarm delay. The first two are quite straightforward—the sensitivity is variable from 2 to 30 metres (more about this in a moment) while the alarm "on-time" increases the time the alarm sounds after movement stops.



The three PCB's, doppler module and controls are shown in this internal shot. The diecast box in which they are mounted measures 120 x 95 x 57mm.

This is quite useful. The alarm can be made to sound only while movement is actually occurring, or it can be extended up to fifty seconds. This we confirmed. A longer alarm means that a thief will not be able to risk short, quick bursts of sound as he moves and stops.

What the alarm delay is for in this module is a bit of a mystery. It delays the alarm sound by up to half a second—but the LED lights instantly. As it was, we found most satisfactory operation with the alarm delay turned right off.

Such a delay would be useful in a more involved system where, for example, the motion was analysed before turning on the alarm. This facility is provided in some alarm systems to avoid false triggering caused by small animals, birds, paper, etc. However, it appears quite out of place in this simple alarm.

In the brief test conducted in our laboratory, we judged sensitivity quite adequate. It was relatively easy to set the sensitivity control to protect certain areas while leaving others "free". For example, a corridor could be protected while leaving an office behind it out of range.

A small problem, we found was that the initial switch-on delay was not as long as expected. The specifications state the unit is completely inactive for the minute after switch-on. This was not so with the sample we had. It gave a small "burst" at switch-on, followed by just twenty seconds of silence. After that, the alarm sounded. Hopefully, this was just a fault confined to our unit.

Although we can understand the alarm being supplied without a transformer, we cannot see a reason for not supplying the horn speaker as an integral part of the alarm. Not that there is any problem regarding supply (both items are listed on the parts list) but it would seem more sensible to supply the alarm system complete with speaker, not as a non-optional extra.

The reason for not supplying a transformer is clear: the alarm is suitable for a range of power sources, AC or DC—and many installers would like their options left open regarding mains power. It is often a good idea to have the alarm independent of the mains, so batteries or a transformer/rechargeable cell setup would be desirable. If required, ED & S have rechargeable batteries available.

Despite the minor points raised, we found the CL8963H Home Alarm performs well, and is suitable for guarding quite large areas. It would be well suited to the average home environment or, as is becoming more and more necessary, guarding a pool area.

Construction is neat and straightforward, and servicing should not be too difficult. If a unit does fail, ED & S will be able to service it. The CL8963/H carries a recommended price of \$90.00 plus sales tax (15%) while the horn speakers are priced at \$13.00 (+ ST). For further information contact ED & S at 27 Buckley St, Marrickville, NSW 2204. (R.P.T.)

## DIGGERMAN ELECTRONICS

P.O. Box 33, Coramba, N.S.W. 2466

We offer a new realm in prices for hobbyists. Compare our prices. Return mail service.

### QUALITY ELECTROLYTIC CAPACITORS:

Cap.	UPRIGHT		AXIAL LEAD	
	16V	25V	16V	25V
1 uF	7c	7c	8c	9c
4.7 uF	7c	7c	8c	9c
10 uF	7c	7c	9c	10c
22 uF	8c	8c	9c	11c
33 uF	8c	9c	10c	13c
47 uF	9c	11c	11c	14c
100 uF	11c	12c	13c	17c
220 uF	13c	17c	15c	20c
470 uF	18c	23c	21c	32c
1000 uF	24c	37c	31c	40c

### POLYESTER FILM CAPACITORS: 100V 10% tolerance:

.001 — 7c	.01 — 7c	.1 — 10c
.0015 — 7c	.015 — 8c	.15 — 13c
.0022 — 7c	.022 — 8c	.22 — 15c
.0033 — 7c	.033 — 8c	.33 — 16c
.0047 — 7c	.047 — 9c	.47 — 19c
.0056 — 7c	.056 — 9c	
.0068 — 7c	.068 — 9c	

RESISTORS: 1/4W carb. film 5% E12 values 2.2 Ohm-1M. Record price of 2c each on single quantities.  
ZENER DIODES: 400mW 5% tolerance BZY88 values: 3V to 33V—15c each. 20 for \$2.60. May be mixed.

All goods top quality—satisfaction guaranteed or money back. No minimum order. One P & P charge of 40c regardless of quantity. Prices current for 3 months for benefit of late readers.  
N.Z. orders welcome by money order or draft—N.Z. surface mail 60c one charge.



# Elega DR-196C headphones

Most stereo headphones are styled along conventional lines which may not appeal to the young and trendy. So here is the Elega DR-196C which has a blue and yellow denim headband.

Apart from the unconventional styling, the outstanding feature of the Elega DR-196C stereo headphones is their comfort. Because of their very light weight of only 170 grams and "open-aire" construction they can be worn for long periods. In fact they are so light it is possible to forget you are wearing them.

An adequate range of vertical adjustment is provided for the earpieces but they lack the ability to rotate horizontally, which is necessary if they are to conform closely to the user's ears. A two-metre connecting cord is provided and it is fitted with the conventional stereo jack plug. The earpieces are labelled Left and Right but the labelling should be a little larger for easy recognition.

Impedance of the phones is 100 ohms approximately and this combined with relatively high efficiency means that these Elega phones are well-matched to virtually any amplifier or tape deck. Maximum loudness level is also more than adequate although distortion rises rapidly at high levels.

There is little acoustic isolation from outside noises as a consequence of the "open-aire" construction and the same disadvantage applies in the opposite direction. Other people in the same room may be irritated by a tinny rendition of the program.

We assume that the transducers are dynamic but we did not have access to any manufacturer's data at the time of writing this review. The sound is beamed through an open-pore plastic foam to the listener's ears. This foam is black while the rest of the earpiece is padded with grey plastic foam. The foam padding is not removable for cleaning which we regard as a disadvantage as far as hygiene is concerned.

Nor is the denim headband material removable when it inevitably becomes soiled. This problem does not occur with conventional headphones.


Sound quality is quite pleasant though clearly not as extended in bandwidth as more expensive dynamic or electrostatic headphones. We also noted some mid-range colouration which would tend to cause listener fatigue during prolonged listening sessions.

For those who regard comfort as all-important then the Elega DR-196C should certainly be considered, to determine if its performance satisfies your requirements. They can be obtained from all branches of Dick Smith Electronics.
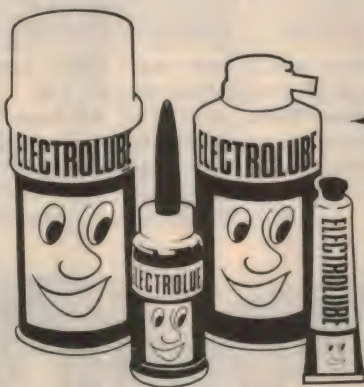
## NEW SUPPLIER FOR TRANSFORMERS & METALWORK

Star Delta Company Pty in conjunction with their subsidiary, Cowper Sheetmetal & Engineering Company announce that they can supply transformers, chokes and metalwork for projects described in "Electronics Australia".

Trade enquiries should be directed to Star Delta Company Pty Ltd, 8 East Street, Granville, NSW 2142.



Information on ALL Electrolube Products is available from Australian Agents:



**RICHARD FOOT (AUSTRALIA) PTY. LTD.**

63 HUME STREET, CROWS NEST,  
N.S.W. 2065. Telephone: 43-0326.

## ELECTROLUBE<sup>REGD.</sup>

- Electrical Contact Treatments
- Maintenance Chemicals
- Specialised Lubricants
- Contact Lubricants
- Contact Cleaning Strips
- Preclene
- Freezer Spray
- Printed Circuit Lacquer.

RF.1984



# DON'T KEEP YOUR CUSTOMERS DANGLING



**install a DORO answering system  
from any telephone in the world  
for less than \$1 per day**

At your command, Doro 320 Remote Telephone Answering System gives and receives messages, reviews them, saves all or part, starts tape fresh. It takes dictation for an hour, permits review or change at will. It records and confirms new outgoing announcements at any time. All by remote control.

A marvel of electronic technology! Fantastic performance! The only compact cassette machine engineered to respond faithfully to both dialing and hand-held transmitter. Check the price. You can't beat it anywhere.

Doro 320 is all quality. Built to last. See it to believe it. Fantastic.

*Doro 311 Automatic Telephone Answering System* meets the need of the busy executive on the go. Faithfully gives and records messages 24 hours a day. Precision engineered. Fully warranted. Reasonably priced.

Both Doro 320 and 311 are excellent for general office or central communication systems. Nationwide servicing.



APO PERMIT NO. C75-16-48

For more details and your nearest Doro dealer call or write:


Modern Dictating Systems Pty. Ltd.,  
75 Vulture Street, West End, Brisbane Qld. 4101; 5 Brunswick Street, Fitzroy,  
Melbourne Vic; 22 Pirie Street, Fyshwick, A.C.T.  
Telephone: 44 1591 Brisbane, 449 8110 Sydney,  
41 6068 Melbourne, 7 3262 Auckland. N.Z.  
95 7721 Canberra, Distribution enquiries welcome.

**doro**®  
COMPATIBLE SYSTEMS →



## NEW PRODUCTS

### Function / sweep generator

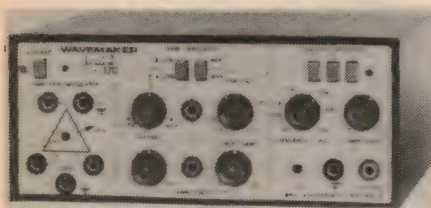


The model bwd 170 'Wavemaker' can operate as a self-contained function/sweep generator covering the 20Hz-50kHz range, or as a companion unit to almost any function generator. It provides a log or linear ramp to sweep VCOs, and amplitude modulation facilities.

Sine, square or triangle waves are switch selected and available at 5V p-p into 600 ohms or 10V p-p O/C. As a frequency doubler, input signal range is 0-5MHz. The unit will operate as a multiplier from DC to 1MHz with better than 10% linearity from DC to 100kHz.

Full details from BWD Electronics Pty Ltd, Miles St, Mulgrave, Vic 3170.
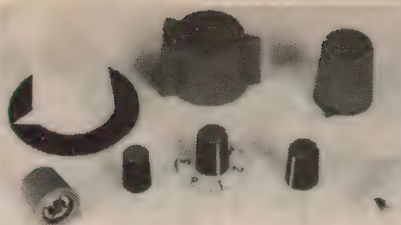
### Collet knobs

Pictured is a selection of collet knobs now available from Swan Electronics Pty Ltd (formerly McMurdo), Cnr Forster and




Hardner Rds, Mt Waverly, Vic 3149.

The knobs come in sizes of 10, 11, 15, 21 and 29mm, the last three all designed to fit standard 1/4-inch shafts. There are three basic knob colours (red, black and grey) and six pointer and cap colours.

Concentric fittings are available, as are figure dials and stators. Nut covers can be supplied for the smaller sizes.

### Miniature relays

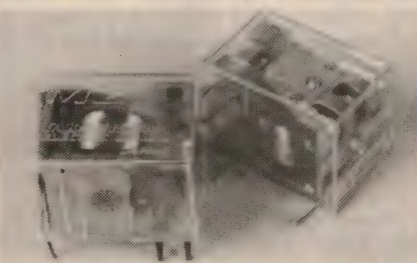

Available from Dick Smith Electronics, these two miniature relays are ideal for instruments, model control and applications where space is at a premium.

Designated types MZ5H and MZ12M,

both units feature single pole double throw contacts rated at 24V DC 1A or 100V AC 0.5A. Operating voltages are 5V and 12V respectively, and coil resistances are 56 ohms and 320 ohms.

Case dimensions are a compact 15 x 11 x 10mm (L x W x H) and weight is just 3.5g. The units can be interfaced to TTL via a suitable buffer, and fit 0.1-inch matrix board.

### E-Z-Hook range



Recently released in the E-Z range are the E-Z Mini-Hook and Mini-Hook XL combined with an easy-to-use pistol grip, and the E-Z range of Nailclips and Nailclip cable clamps (see Dec., 1975 EA).

All products in the E-Z range are now illustrated in a comprehensive 48-page catalog.

Further information from General Electronic Services Pty Ltd, 99 Alexander St, Crows Nest, NSW 2065.

# APOLLO HI-FI CENTRE



283 Victoria Rd, Marrickville. Ph 560 9019.

Open Thursday till 9PM, all day Saturday.



#### SANSUI AU4400

**POWER OUTPUT:** 23+23 watts into 8 ohms (both channels driven; at 1kHz).  
**THD:** less than 0.3% at rated power.  
**IMD:** less than 0.5% at rated power.  
**LOAD IMPEDANCE:** 4 to 16 ohms.  
**FREQUENCY RESPONSE:** 20Hz-30kHz, +1-2dB (at 1 watt).  
**DAMPING FACTOR:** approx. 50.  
**CHANNEL SEP.:** better than 45dB.



#### SANSUI SR525

**TYPE:** Manual single play transcription turntable.  
**MOTOR:** 20 pole DC brushless.  
**DRIVE:** Direct spindle, electronically servo controlled.  
**PLATTER:** 310mm aluminium diecast, 1.4kg.  
**WOW & FLUTTER:** less than 0.03% (WRMS).  
**S/N RATIO:** better than 64dB (IEC-B).  
**SPEED:** 33 1/3, 45RPM (±3.5% adjustable).



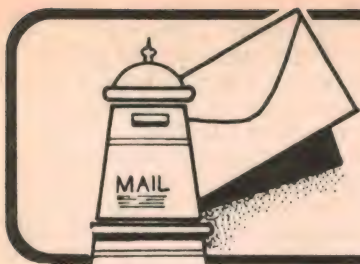
#### SANSUI TU3900

**FM SECTION**  
**TUNING RANGE:** 88-108MHz.  
**SENSITIVITY:** 2.0uV.  
**THD:** Mono less than 0.3%. Stereo less than 0.4%.  
**S/N RATIO:** better than 70dB.  
**SELECTIVITY:** better than 60dB.  
**AM SECTION**  
**TUNING RANGE:** 535-1605kHz.  
**SENSITIVITY:** 53dB/m at 1MHz.  
**SELECTIVITY:** better than 30dB at 1MHz (±10kHz).

ALSO AGENTS FOR: J.V.C., AKAI, A. & R., BOSE, VIDEOTON, PIONEER, SANSUI, KENWOOD, TEAC, J.B.L., HARMAN-KARDON, SONY AND MANY OTHERS.





## Letters to the editor

### Novice power limit

I refer to the article "Simple novice transmitter for the 3.5MHz amateur band" which appears on pages 44 to 49 of the January 1976 edition of your magazine.

In this article it is indicated that Novice Station licensees will be required to limit the direct current input power to the final stage of their transmitters to 10 watts. This is incorrect.

The power restrictions which apply to stations operated by Novice licensees are:

(a) All authorised emissions, except types A3A and A3J: 10 watts transmitter mean power output; and

(b) Type A3A or A3J emission: 30 watts transmitter peak envelope power output.

I hope this clarifies the situation.

W. McDonald,  
for the Superintendent, NSW,  
Regulatory & Licensing Section  
Postal and Telecommunications Dept.

### Limit Z-call tenure?

I was interested in your editorial comment in a recent issue of the magazine, on the matter of the issuing of a Novice Licence in the amateur radio service in Australia. As I see it, it is a matter of regret that whereas the Service already supports both a Full Licence (morse code at 12 WPM) and a Restricted Licence (no morse code), it would appear that there exists some special reason, of which I am unaware, why the Novice Licence (morse code at 5 WPM) should be reduced in tenure to 2 years. If the argument for reducing the tenure to 2 years is based on morse code, then surely the Restricted Licence or "Z-call" should likewise be of limited tenure? However if it is based on technical ability or lack thereof, then surely the Novice so desiring, could proceed to the Full Licence as he gains experience with simple equipment and of course one wonders why the Restricted Licence is required at all? Possibly it could be argued that all persons interested in amateur radio must be "encouraged" to acknowledge the Good Life and to become an amateur with a full licence, but then why penalise only the Novice? One suspects that each of these 3 licencees is a quite different type of person and that each could make a distinct contribution to Amateur radio within his own

right and without penalty. If the reason for the Novice limitation is none of the foregoing then I am at a loss to understand the decision.

My final thought on the amateur licence intrigues me greatly—the person aspiring to become a "real" amateur will, if successful, in due course probably ignore morse code transmission and the development of technical skills (surely the essential part of being an amateur) to become the proud owner of an XYZ5000 little grey or black box which has not even been manufactured in Australia.

T. F. Pyke  
Chatswood, NSW

**COMMENT: I agree, the justification for the 2-year limit on tenure seems very obscure and illogical. Perhaps in view of the pace of technological progress, ALL amateur licences should have limited tenure, with renewal at any level by examination!**

### Examinations

I would draw your attention to past A.O.C.P. examination papers, which I have been reviewing in anticipation of the forthcoming(?) examinations. I have been preparing myself for this event over the past two years and have devoted an enormous amount of leisure time in devouring A.R.R.L., W.I.A. and similar recognised texts for an average of sixteen hours per week.

I am a professional man and I am no stranger to examinations, nor would I consider myself dull or retarded in any way. Can you imagine my horror when attempting past papers, not at the subject matter but in the time required to satisfactorily answer? Following recognised examination techniques, a prudent candidate would budget his time in accordance with the allocation of marks. As all questions carry equal marks the seven questions should require twenty minutes to answer.

The paper for February, 1974, contains the following twenty minute gem:

"1(a) Draw the circuit diagram of an amateur station transmitter suitable for operation in the 144-148MHz band. Explain briefly the theory of operation of each stage of the transmitter.

(b) Describe how you would tune the transmitter described in (a)."

Could anyone answer this satisfactorily in the allotted time?

I contacted the examination clerk at the Radio Branch for clarification—sure enough circuit means literally circuit, including all values. Why?—"We must maintain a very high standard." How many candidates are successful?—"On average about ten percent of candidates manage to pass!"

What is the purpose of the examination? To ascertain if a prospective amateur has a satisfactory knowledge of the subject matter thereby earning the right to be licenced, or is its purpose to restrict the number of users on the amateur bands?

Sir, I believe this matter and the matter of the two year tenure for novices can, collectively, only place the long term interest of Amateur Radio in jeopardy.

Ian Purdie  
Toongabbie, NSW

### Kits & servicing

May I offer a word of caution to readers intending to build electronic equipment from kits imported privately from the United Kingdom. Unless you are a competent electronics serviceman—don't! If things go wrong you may be left holding the sticky end.

Last year I ordered a kit for a stereo FM tuner from a supplier who advertises regularly in Wireless World.

It is now my misfortune that, after a period of working reasonably well, distortion became increasingly apparent and no amount of adjustment would put it right. The decoder no longer functions and my electronics experience does not enable me to fault-find on a board containing 3 IC's, 14 transistors and 63 resistors.

I am therefore left with about \$95 worth of duty paid junk in the form of a Nelson-Jones FM tuner with varicap diode tuning and a Portus-Haywood phase-locked loop stereo decoder in non-working order, together with instructions and all relevant Wireless World reprints.

Perhaps an enterprising reader would care to make me an offer, since I intend to go and buy a cheap, inferior, but working Japanese tuner.

Ian R. Juniper  
French's Forest, NSW

**COMMENT: While modern integrated circuits and printed circuit boards make it possible for people with a very modest background in electronics to build up quite complex circuits, there is unfortunately no way at present of obviating the need for servicing skill if things go wrong!**

The views expressed by correspondents are their own and are not necessarily endorsed by the editorial staff of "Electronics Australia". The Editor reserves the right to select letters on the basis of their potential interest to readers and to abbreviate their contents where this appears to be appropriate.



# E.D.&E. (SALES) PTY. LTD.

## EDUC-8 COMPUTER—COMPLETE KIT

(OCT-NOV-DEC 1974)

**\$368.75 (Plus Tax)**

OR INDIVIDUAL COMPONENTS  
AS REQUIRED

K  
I  
T  
S

K  
I  
T  
S

### MAJOR STOCKISTS OF ALL GENERAL RADIO & ELECTRONIC COMPONENT PARTS — YOU NAME IT — WE WILL QUOTE

Valves — Transistors — Zener & Power Diodes — Semi-Conductors — Diacs — Triacs — S.C.R.'s — I/C's. Speakers — Microphones — Coils — IFT's. Transformers — Inst Cases — Metalwork. Players & Changers — Meters — Relays — Condensers — Resistors — Bezels — Styli — Cartridges — Recording Tape — Probes — Instruments — Potentiometers — Crystals — Ferrite Beads — Cores — Baluns — Terminals — Co-Axial Plugs & Sockets — Multi Connectors — Printed Circuit Boards — Copper Winding — Wire — Etc. — Etc.

### POPULAR KITS — TOP QUALITY — LOWEST PRICES

#### AUDIO

- 1 Direct Reading A.F. Gen.
- 2 SQ Wave Gen-10Hz-1MHz.
- 3 Solid State A.F. Gen.
- 4 Additive Freq Meter.
- 5 A.F. Tone Burst Gen.
- 6 Laboratory Solid State A.F. Gen.
- 7 Scaler/Divider Unit.
- 8 Crystal Freq Calibrator.
- 9 Direct Reading A.F. Meter. (0-200KHz — 10MV-2V).
- 10 High Performance A.F. Gen.
- 11 White Noise Gen.
- 12 —
- 13 —
- 14 —

#### AUTOMOTIVE UNITS

- 15 Tacho & Dwell Angle for Service Stations.
- 16 Dwell Extender Unit.
- 17 Solid State — CDI.
- 18 All Electronic Ignition System.
- 19 Windscreen Wiper.
- 20 Tacho & Dwell Unit.
- 21 Brake Light Warning.
- 22 Emergency Flasher.
- 23 High Efficiency Flasher.
- 24 Solid State Volt Reg.
- 25 Car Theft Alarm System.
- 26 Ignition Analyser & Tachometer Unit.
- 27 Strobe Adaptor for Ignition Analyser.
- 28 Car Burglar Alarm.
- 29 1975. C.D.I Unit.

#### BATTERY CHARGERS

- 30 6 Volt — 1 Amp.
- 31 12 Volt — 1 Amp.
- 32 Automatic H/Duty.
- 33 1-14 Volt — 4 Amp.
- 34 1973 Automatic Unit.
- 35 Constant Current Unit.
- 36 —
- 37 —

#### CONVERTERS — INVERTERS

- 38 12 VDC 300/600V 100W.
- 39 12 VDC 240 VAC 20W.
- 40 12 VDC 240 VAC 50W.
- 41 24 VDC 300 VDC 140W.
- 42 24 VDC 800 VDC 160W.
- 43 —
- 44 —

#### C.R.O. UNITS

- 45 1963 3" Calibrated.
- 46 1966 3" C.R.O.
- 47 1968 3" Audio C.R.O.
- 48 C.R.O. Electronic Switch.
- 49 C.R.O. Wideband P/Amp.
- 50 C.R.O. Calibrator.
- 51 —
- 52 —

#### INTRUDER WARNING SYSTEM

- 53 Electronic Thief Trap.
- 54 Infrared Alarm System.
- 55 Simple Burglar Alarm.
- 56 Light Beam Relay.
- 57 Car Burglar Alarm.

#### MULTIMETERS & V.O.M.

- 58 Protected D.C. Multimeter.
- 59 Meterless Voltmeter.
- 60 Wide Range Voltmeter.
- 61 F.E.T. D.C.
- 62 1966 V.T.V.M.
- 63 1968 Solid State V.O.M.
- 64 1973 Digital V.O.M. (1).
- 65 1973 Digital V.O.M. (2).
- 66 High Linearity A.C. Millivoltmeter.
- 67 —
- 68 —

#### PHOTOGRAPHIC UNITS

- 69 50 Day Delay Timer.
- 70 Regulated Enlarger Line.
- 71 Slave Flash Unit.
- 72 Sound Triggered Flash.
- 73 Solid State Timer.
- 74 Auto Trigger For Time Lapse Movies.
- 75 —
- 76 —

#### REGULATED POWER SUPPLIES

- 77 Laboratory Type 30/1 Unit.
- 78 Laboratory Type Dual Power Supply.
- 79 Serviceman's Power Supply.
- 80 Solid State H.V. Unit.
- 81 IC Variable Supply Unit.
- 82 1972IC Unit (E/T).
- 83 Simple 5V 1A Unit.
- 84 Simple 3-6V 3.5A Unit.
- 85 S/C Proof 0.30 VDC at 1A.
- 86 Reg 0-30VDC at 3A O/L Protected.
- 87 Variable Reg 12V-05A.
- 88 Reg O/L Load & S/C Protection 60 VDC at 2A (1973) — EA.
- 89 —
- 90 —

#### R.F. INSTRUMENTS

- 91 Solid State Test Osc.
- 92 Signal Injector & R/C Bridge.
- 93 Solid State Dip Osc.
- 94 "Q" Meter.
- 95 Laser Unit.
- 96 Digital Freq Meter 200KHz.
- 97 Digital Freq Meter 70MHz.
- 98 IF Alignment Osc.
- 99 27MHz Field Strength Meter.
- 100 100KHz Crystal Cal.
- 101 1MHz Crystal Cal.
- 102 Solid State Dip Osc.
- 103 V.H.F. Dip Osc.
- 104 V.H.F. Powermatch.

- 105 V.H.F. F/S Detector.
- 106 S.W.R. Reflectometer.
- 107 R.F. Impedance Bridge.
- 108 Signal Injector.
- 109 1972 FET Dipper.
- 110 Digital Freq Meter.
- 111 Simple Logic Probe.
- 112 Frequency Counter & DVM Adaptor.
- 113 Improved Logic Probe.
- 114 Digital Logic Trainer.
- 115 Digital Scaler/Preamp.
- 116 Digital Pulser Probe.
- 117 Antenna Noise Bridge.
- 118 Solid State Signal Tracer.
- 119 1973 Signal Injector.
- 120 Silicon Diode Sweep Gen.

#### TRAIN CONTROL UNITS

- 124 Model Control 1967.
- 125 Model Control with Simulated Inertia.
- 126 Hi-Power unit 1968.
- 127 Power Supply Unit.
- 128 SCR-PUT Unit 1971.
- 129 SCR-PUT Unit with Simulated Inertia 1971.
- 130 Electronic Steam Whistle.
- 131 Electronic Chuffer.

#### TV INSTRUMENTS

- 134 Silicon Diode Sweep Gen.
- 135 Silicon Diode Noise Gen.
- 136 Transistor Pattern Gen.
- 137 TV Sync & Pattern Gen.
- 138 Cross Hatch & Bar-Gen.

#### VOLTAGE CURRENT CONTROL UNITS

- 142 Auto Light Control.
- 143 Bright/Dim Unit 1971.
- 144 S.C.R. Speed Controller.
- 145 Fluorescent Light Dimmer.
- 146 Autodim-Triac 6 Amp.
- 147 Vari-Light 1973.
- 148 Stage etc. Autodimmer 2KW.
- 149 Auto Dimmer 4 & 6KW.

#### RECEIVERS—TRANSMITTERS—CONVERTERS

- 153 3 Band 2 Valve.
- 154 3 Band 3 Valve.
- 155 1967 All Wave 2.
- 156 1967 All Wave 3.
- 157 1967 All Wave 4.
- 158 1967 All Wave 5.
- 159 1967 All Wave 6.
- 160 1967 All Wave 7.
- 161 Solid State FET 3 B/C.
- 162 Solid State FET 3 S/W.
- 163 240 Communications RX.
- 164 27 MHz Radio Control RX.
- 165 All Wave IC2.
- 166 Fremodyne 4-1970.
- 167 Fremodyne 4-1970.
- R.F. Section Only.
- 168 110 Communications RX.
- 169 160 Communications RX.

- 170 3 Band Preselector.
- 171 Radio Control Line RX.
- 172 Deltahet MK2 Solid State Communications RX.
- 173 Interstate 1 Transistor Receiver.
- 174 Crystal Locked H.F. RX.
- 175 E/A 130 Receiver.
- 176 E.A. 138 Tuner/Receiver.
- 177 Ferranti IC Receiver.
- 178 Ferranti IC Rec/Amp.
- 179 7 Transistor Rec.
- 180 —
- 181 —

#### TRANSMITTERS

- 182 52MHz AM.
- 183 52MHz Handset.
- 184 144MHz Handset.

#### CONVERTERS

- 187 MOSFET 52MHz.
- 188 2-6MHz.
- 189 6-19 MHz.
- 190 V.H.F.
- 191 Crystal Locked HF & VHF.

#### AMPLIFIERS PREAMPS & CONTROL UNITS MONAURAL.

- 194 Mullard 3-3.
- 195 Modular 5-10 & 25 Watt.

#### STEREO

- 196 1972 PM 129 3 Watt.
- 197 Philips Twin 10-10W.
- 198 PM 10 + 10W.
- 199 PM 128-1970.
- 200 PM 132-1971.
- 201 ETI-425 Amp & Preamp.
- 202 ETI-425 Complete System.
- 203 ETI-416 Amp.
- 204 PM 136 Amp 1972.
- 205 PM 137 Amp 1973.
- 205A PM 143.

#### GUITAR UNITS

- 209 P/M 125 50W.
- 210 E/T 100 100W.
- 211 P/M 134 21W.
- 212 P/M 138 20W.
- 213 Modular 200W.
- 214 Reverb Unit.
- 215 Waa-Waa Unit.
- 216 Fuzz Box.
- 217 Sustain Unit.

#### PUBLIC ADDRESS UNITS

- 219 Loud Hailer Unit.
- 220 P.A. Amp & Mixer.
- 221 P/M 135 12W.
- 222 Modular 25W.
- 223 Modular 50W.

#### CONTROL UNITS

- 225 P/M 112.
- 226 P/M 120.
- 227 P/M 127.

#### MIXER UNITS

- 229 FET 4 Channel.
- 230 ETI Master Mixer.
- 231 Simple 3 Channel.

#### TUNER UNITS

- 232 P/M 122.
- 233 P/M 123.
- 234 P/M 138.
- 235 Simple B/C.
- 236 PM 146 AM-FM.

#### PREAMPLIFIERS

- 237 Silicon Mono.
- 238 Silicon Stereo.
- 239 FET Mono.
- 240 Dynamic Mic Mono.
- 241 Dynamic Mic Stereo.
- 242 P/M 115 Stereo.
- 243 —

#### MISCELLANEOUS KITS

- 244 Geiger Counter.
- 245 Direct Reading Impedance Meter.
- 246 —
- 247 Electronic Anemometer.
- 248 Simple Proximity Alarm.
- 249 Pipe & Wiring Locator.
- 250 Resonance Meter.
- 251 Electric Fence.
- 252 Metronome Ace Beat.
- 253 Transistor Test Set.
- 254 Electronic Thermometer.
- 255 Flasher Unit.
- 256 Lie Detector.
- 257 Metal Locator.
- 258 Stroboscope Unit.
- 259 Electronic Canary.
- 260 240V Lamp Flasher.
- 261 Electronic Siren.
- 262 Probe Capacitance Meter.
- 263 Moisture Alarm.
- 264 AC Line Filter.
- 265 Proximity Switch.
- 266 Silicon Probe Electronic Thermometer.
- 267 Transistor/FET Tester.
- 268 Touch Alarm.
- 269 Intercom Unit.
- 270 Light Operated Switch.
- 271 Audio/Visual Metronome.
- 272 Capacitance Leakage.
- 273 Audio Continuity Checker.
- 274 Bongo Drums.
- 275 Simple Metal Locator.
- 276 Keyless Organ.
- 277 Musicolour.
- 278 Stereo H/Phone Adaptor.
- 279 Attack Decay Unit.
- 280 Tape Recorder Vox Relay.
- 281 Tape Slide Synchroniser.
- 282 Tape Actuated Relay.
- 283 Auto Drums.
- 284 IC Vol Compressor.
- 285 Audio Attenuator.
- 286 Thermocouple Meter.
- 287 Door Monitor.
- 288 Earth "R" Meter.
- 289 Shorted Turns Tester.
- 290 Zenor Diode Tester.
- 291 Morse Code Osc.
- 292 Simple Electronic Organ.
- 293 Pollution & Gas Analyser.
- 294 Universal H/Phone Adaptor.
- 295 Super Stereo ETR 410.
- 296 "Q" Multiplier.
- 297 Optomin.

PHONE  
662-3506

**E. D. & E. (SALES) PTY. LTD.**  
118 LONSDALE STREET, MELBOURNE — 3000 — VIC.

PHONE  
662-3506



## LANTHUR ELECTRONICS

69 Buchanan Avenue, North Balwyn,  
Vic. 3104 P.O. Box 162. Ph. 85 4061

### ELECTRIC MOTOR SPEED CONTROLLER BASIC KITS

For controlling speed down to stop of any ac/dc brush type motors, especially hand tools of all kinds. Consists of triac, resistor, diodes, potentiometer, knob, 3 pin base & plug and circuit.

5 amp. size (1200 watt)      \$8.50  
10 amp. size (2400 watt)      \$9.50  
Price includes postage.

### LAMP DIMMER BASIC KITS

For controlling incandescent lamps from full to out at up to 1200 watts. Consists of triac, diac, capacitors, resistors, potentiometer, knob, ferrite rod, enamel wire & circuit.

Price including postage      \$6.95

### PLASTIC CABINETS

Suitable to contain above speed controller or lamp dimmer. Approx. size—117 x 62 x 35 mm. \$1.45

Post free if purchased with dimmer or speed controller kit. Otherwise plus postage 0.40.

### BATTERY SAVER BASIC KIT

Replaces batteries in radios, tape recorders, record players, toys, instruments etc. Consists of tapped transformer, bridge rectifier, filter capacitor & circuit. Will supply dc voltages from 6 to 15.

One amp. size \$7.75

Two amp. size \$14.50

Plus postage \$2.50. Excess postage will be refunded.

### BATTERY CHARGER BASIC KIT

For charging wet batteries 12 volt at 2 amps. Consists of transformer, bridge rectifier, ballast resistor & circuit. \$8.75

Plus postage \$2.50. Excess postage will be refunded.

### METERS

Moving iron type ac/dc. 10 amp. F.S.D. Clear plastic case approx. 55 x 55mm.

\$4.95 Inc. postage.

### NEW-LITE PROBE

A torch with a fibre optic probe attached. See around corners and hard-to-get-at places. Useful to everyone. Complete in carton with batteries and post free.

Price \$4.95



## Books & Literature

### Not recommended

**UNDERSTANDING ELECTRONIC COMPONENTS** by Ian R. Sinclair. Published 1972 by Fountain Press, London. Hard covers, 218 pages, 215mm x 130mm, illustrated by drawings and half-tones. Price in Australia \$10.50.

This is a companion book to "Understanding Electronic Circuits" by the same author, who is currently associated with the Braintree College of Further Education. Like the companion volume, this one is intended for students or readers who have a knowledge of electronics but who are seeking a deeper understanding of the subject.

The chapter headings are as follow: Introduction — Resistors — Capacitors — Inductors — Networks I — Networks II — Valves — Electronic Displays — Semiconductors I — Semiconductors II — Electromechanical Components.

Having just recently reviewed Ian Sinclair's "Electronic Circuits" more or less favourably, I was fully expecting a similar reaction to this one but it didn't turn out that way.

In sample reading, I came across an explanation (p 41) of why capacitors should not dissipate power; to my mind, it was not adequate. On page 51, the reader is likely to be left with the impression that a non-polarised electrolytic is essentially one using tantalum foil. On page 61 the author makes an exaggerated point that a centre-tapped transformer does not shift phase... it inverts the signal. On page 66 the reader is told that a gap is always provided in the core of large inductors. I had similar misgivings about series and parallel resonance (p 91), tuned lines (p 97), valve bias (p 109)

and a statement on p 114 that Miller effect causes oscillation "instead of amplification".

In all these cases, and others which I could mention, the informed reader could see what the author was getting at, but it was compromised by ambiguities arising from brevity, ill-chosen phrases, inappropriate sentence construction and a suspicion on part of this reviewer that Ian Sinclair is more at home with the generalities of circuits than the particulars of components.

What he says in the preface is quite true, of course: there is a limit to how much one can say about components in a book of a given size. But I am firmly of the opinion that a critical, independent reading of the manuscript prior to publication could have pin-pointed its weaknesses. As it now stands, I would not be happy to recommend it.

The review copy came from Thomas C. Lothian Pty Ltd, 4-12 Tattersall's Lane, Melbourne 3000. (W.N.W.)

### Children & TV

**TELEVISION'S CHILDREN**, by Kevin Tindall and David Reid. Published by the Audio-Visual Centre, Sydney Teachers College, 1975. Soft covers, 175 x 250mm, 72pp, with line drawings and diagrams. Price \$2.20 including postage.

This is the first of a planned series of research reports to be published by the Audio-Visual Research Centre of the Sydney Teachers College. Subsequent titles will report on TV and violence, educational TV, children's TV, TV and social change, parents and TV, and TV and achievement.

The authors of the present report are Kevin Tindall, the Director of the

# DECCA

## Record Cleaner WORKS AS YOU PLAY...

This new DECCA Record Cleaner removes dust and grit as your record spins on the turntable. It consists of an arm carrying a brush made from a newly-developed man-made fibre. Its "bristles" are incredibly fine, incredibly soft yet strong, and are also electrically conductive to remove static as well as dust. The result — Improved sound quality, reduced record wear.

\*\$13.95 at hi-fi stores and record bars.

Australian agent:  
49-51 York Street, Sydney.

British Merchandising Pty. Ltd.,  
Telephone 29 1571.

\*Recommended retail price.





Research Centre, and Lecturer David Reid.

They appear to have planned this first work as a preliminary introduction to the broad field of research into the complex relationship between TV and children. In this sense it perhaps sets the stage for the later titles, or at least maps out the areas which are planned for further investigation.

The book is divided into two main parts. In the first section, the authors give some basic facts about children's viewing habits, and discuss the various implications of these facts. They also draw attention to those aspects of the child-TV relationship about which parents, authorities and others have expressed concern.

The second section presents data and analysis of two TV viewing surveys conducted in the Sydney viewing area, in September 1974 and May 1975.

This subject is one which I find of special interest, as readers are probably aware. Not merely because I am a parent of young children, but also because I have a reasonable background in both the theory and practice (I was tempted to type "mal practice") of both electronic communication and education. But even if I did not have this prior interest, I believe I would still have found the book absorbing reading.

Did you realise, for example, that by the time the average young child of today leaves school at age 16, they will have been exposed to about 17,500 hours of TV compared with only about 15,000 hours in the classroom? It makes you think...

All in all the book presents a good deal of very interesting and thought-provoking material like this, and I believe it will be of value to anyone who is interested in the influence of TV upon child development.

If you're a concerned parent, it should be almost compulsive reading. The more so because it is written in quite readable prose, not weighty ivory-tower stuff.

Copies are available at the price given above from the Sydney Teachers College, PO Box 63, Camperdown NSW 2050. (J.R.)

## Standards history

**THE INTERNATIONAL BUREAU OF WEIGHTS AND MEASURES, 1875-1975.** Published by the US Department of Commerce National Bureau of Standards, 1975. Soft covers, 145 x 230mm, 248pp, many illustrations. Price in US \$3.00

Those who are interested in the development of our present international system of weights and measures—including those used in electronics—should find this NBS translation of the BIPM centenary volume of great interest.

Called NBS Special Publication 420, it is available from the Superintendent of Documents, US Government Printing Office, Washington D.C. 20402.

# BOOKS

Just some of the titles from the biggest range of radio and electronics books in Australia.

If the book you require is not listed below it can be ordered from us.

Order Now 1976 Edition A.R.R.L. Handbook—The Standard Manual of Amateur Radio Communication (expected March) \$9.95.

Latest editions of two of the most popular books on the subject:

Radio Handbook (William I. Orr) 19th Edition	\$19.40
The A.R.R.L. Antenna Book (American Radio Relay League)	\$5.50

### Philips Books:

Philips 1974 Pocketbook—Electron Tubes, Semiconductors, Integrated Circuits, Components and Materials	\$2.75
Philips Application Book—Photomultipliers	\$3.45
Philips Application Book—Field Effect Transistors	\$3.45
Philips Application Book—Fast Response Photomultipliers	\$3.45
Philips Product Book—Thyristors	\$6.75
Miniwatt Technical Data—Valves, Picture Tubes, Semi-conductor Devices—7th Edition	\$3.75

### New Books:

30 IC Projects (Herbert Friedman)	\$3.75
Unique IC OP-AMP Applications (Jung)	\$6.35
IC OP-AMP Cookbook (Walter G. Jung)	\$14.90

### De Muiderkerk Publications:

Transistor Equivalents—9th Edition (Entirely revised and extended)	\$5.75
TTL Digital Integrated Circuits Part 1 Series 7400-74132 With Equivalents	\$8.95
Semiconductor Handbook Part 1—Transistors 1st Edition (A. E. C. Van Uitteren)	\$8.95
The World's Radio—Broadcasting Stations & European FM/TV (C. J. Both)	\$8.95

### American Radio Relay League Publications:

Hints and Kinks for the Radio Amateur	\$2.85
The Radio Amateur's VHF Manual	\$5.50
Understanding Amateur Radio	\$5.50
The Radio Amateur's License Manual	\$2.00
How To Become a Radio Amateur	\$2.00
A Course in Radio Fundamentals	\$4.35
Special Communications Techniques for the Radio Amateur	\$4.50
FM & Repeater for the Radio Amateur	\$4.35

### Howard W. Sams Publications:

Television Broadcasting—Tape and Disc Recording Systems (Harold E. Ennes)	\$19.40
Workshop in Solid State (Harold E. Ennes)	\$14.10
Television Broadcasting: Equipment, Systems and Operating Fundamentals (Harold E. Ennes)	\$19.40
AM-FM Broadcasting: Equipment, Operations and Maintenance (Harold E. Ennes)	\$19.40
Television Broadcasting: Systems Maintenance (Harold E. Ennes)	\$19.40
Television Broadcasting: Camera Chains (Harold E. Ennes)	\$18.00
RTL Cookbook—A complete Guide to the Understanding & Using of Resistor Transistor Logic (RTL) Digital Integrated Circuits (Donald E. Lancaster)	\$7.00
Transistor Fundamentals—Volume 1—Basic Semiconductor and Circuit Principles (R. J. Brite)	\$6.35
Transistor Fundamentals—Volume 2—Basic Transistor Circuits (Charles A. Pike)	\$6.35
Transistor Fundamentals—Volume 3—Electronic Equipment Circuits (Martin Gersten)	\$6.35
Security Electronics (John E. Cunningham)	\$6.35
Guide to High Fidelity (Institute of High Fidelity)	\$5.20
Colour TV Servicing Made Easy—Volume 1 (Wayne Lemons & Carl Babcoke)	\$6.10
Colour TV Servicing Made Easy—Volume 2 (Wayne Lemons & Carl Babcoke)	\$7.60
How To Read Schematic Diagrams (Donald E. Herrington)	\$5.70
Transistor TV Servicing Made Easy (Jack Darr)	\$6.35
Handbook of Transistor Circuits (Allan Lytel)	\$7.60
Tube Substitution Handbook—No 17	\$2.20
Know Your VOM-VTVM—Now Includes Vacuum Tube, Solid State, Analog, Digital (Rissa)	\$7.00
101 Ways to Use Your VOM and VTVM (Robert G. Middleton)	\$5.75
101 More Ways to Use Your VOM and VTVM—2nd Edition (Robert G. Middleton)	\$5.75
101 Ways to Use Your Oscilloscope (Robert G. Middleton)	\$5.75
Semiconductor Handbook (Robert B. Torner)	\$7.40
Troubleshooting with the Oscilloscope (Robert G. Middleton)	\$7.00
Transistor Specifications Manual—6th Edition TV Servicing Guide—Arranged by Trouble Symptoms (Leslie D. Deane & Calvin C. Young)	\$5.75
Transistor Colour-TV Servicing Guide (Robert G. Middleton)	\$6.35
Electric Guitar Amplifier Handbook (Jack Darr)	\$7.65
EIA Electronics Multimedia Handbook (Ed. Irving W. Larson) Sponsored by Electronic Industries Assn.	\$6.35

### Babani Publications:

First Book of Transistor Equivalents & Substitutes (B. B. Babani)	\$1.30
Second Book of Transistor Equivalents & Substitutes	\$3.15
1st Book of Hi-Fi Loudspeaker Enclosures	\$1.95
Radio and Electronic Colour Codes and Data Chart	60c
World's Short Medium and Long Wave FM & TV Broadcasting Stations Listing	\$1.95

### Other Titles:

TV Fault Finding—5th Revised Edition (J. R. Davies)	\$3.00
73 Dipole and Long-Wire Antennas (Noll)	\$6.35
73 Vertical, Beam and Triangle Antennas (Noll)	\$6.35
Slow Scan Television Handbook (Don C. Miller & Ralph Taggart)	\$7.10
Basic Television—Principles and Servicing 4th Edition (Bernard Grob) New Edition just received	\$21.80
Colour Television Servicing—Second Edition (Gordon J. King)	\$13.20
Colour Television Theory—PAL-System Principles & Receiver Circuitry—SI Units (Hutson)	\$11.30
Colour Television with Particular Reference to the PAL System (G. N. Patchett)	\$15.35
PAL Colour Television for Servicemen (W. C. Cook)	\$15.00
T.V. Technician's Bench Manual (G. R. Wilding)	\$7.50
T.V. Camera Operation (Gerald Millerson)	\$5.95
The Mazda Book of PAL Receiver Servicing (D. J. Seal)	\$18.40
Pin-Point TV Troubles in 10 Minutes—Check Charts—New TV Trouble-Shooting Technique	\$8.05
Colour TV Repair (Martin Clifford)	\$4.35
The Oscilloscope (George Zwick)	\$6.70
Pin-Point Transistor Troubles in 12 Minutes—Check Charts—New Transistor Trouble-Shooting Techniques	\$9.65
Improving your Hi-Fi (John Earl)	\$9.00
Set Up Your Own Hi-Fi—A Beginner's Guide (R. H. Warring)	\$5.00
Motorola High-Speed Switching Transistor Handbook 9th Edition	\$5.00
Transistor Pocket Book (R. G. Hibberd)	\$6.75
Transistor Manual—Light-Weight Edition—Circuits, Applications, Characteristics, Theory (General Electric)	\$3.95
Basic Theory and Application of Transistors (Dover Publications, New York)	\$3.00
Test Equipment for the Radio Amateur (H. L. Gibson)	\$6.65
Radio Valve and Transistor Data—9th Edition (Compiled by A. M. Ball)	\$3.00
Pickups and Loudspeakers—How To Choose and Use (John Earl)	\$9.00
Audio Technician's Bench Manual (John Earl)	\$8.80
Ham Radio—A Beginner's Guide (R. H. Warring)	\$5.65
Non Linear Circuits Handbook (Analog Devices, Inc.)	\$9.00
Ham Notebook—From the Editors of Ham Radio (Ed. James Fisk)	\$5.10
Manual of Sound Recording—Second Edition (John Aldred)	\$10.50
The All-In-One Tape Recorder Book—A Focal Soundbook (Joseph M. Lloyd)	\$3.50
Introducing Electronic Systems (Ian R. Sinclair)	\$4.50
Introducing Amateur Electronics (Ian R. Sinclair)	\$3.75
Automobile Electrical Systems—2nd Edition	\$1.85
Questions and Answers (A. J. Coker)	\$1.85
Basic Electricity—Revised Second and Enlarged Edition (Prepared by the Bureau of Naval Personnel)	\$5.40
Electrical Calculations (Arthur Mychael)	\$4.45
Radio and Electronic Laboratory Handbook 8th Edition (M. G. Scroggie)	\$18.50
SCR Manual—Fifth Edition—Including Triacs and Other Thyristors (General Electric)	\$5.65
How To Get the Most out of Your Pocket Calculator (Henry Mullish)	\$1.95
Public Address Handbook—A Manual of Sound Reinforcement (Vivian Capel)	\$9.00

### RCA Publications:

SSD-205C RF/Microwave Devices	\$4.50
SSD-206C Thyristors/Rectifiers	\$4.50
SSD-207C High-Reliability Devices	\$4.50
SSD-204C Power Transistors	\$4.50
SSD-203C COS/MOS Integrated Circuits	\$4.50
SSD-202C Linear Integrated Circuits—Application Notes	\$4.50
SSD-201C Linear Integrated Circuits Selection Guide/Data	\$4.50
Solid State Hobby Circuits—68 Useful Circuits for Beginners and Experts	\$4.50
Solid State Servicing—Hi-Fi, Tape Recorders, AM/FM Mono, Stereo, TV B & W, Color Designer's Handbook—Solid-State Power Circuits	\$11.25
RC30 Receiving Tube Manual	\$4.50

For Mail Orders Please add: 80c Local—\$1.50 Interstate

**McGILL'S AUTHORIZED NEWSAGENCY PTY. LTD.**

187 Elizabeth Street, Melbourne.

Phone: 60 1475-6-7



# A.C.E. RADIO

## BSR STEREO RECORD CHANGERS



Improve your hifi system with one of these top quality low cost current model guaranteed turntables.

**STANDARD MODEL:** 3 speed, auto manual, ceramic cartridge, diamond stylus, cueing. \$35.00

C141 as above plus player spindle, larger turntable, stylus pressure adjustment. \$41.95  
C142 as above plus, 4 pole shielded motor, fully adjustable tone arm counter weight, anti-skate and bias control. Heavy duty t'able, magnetic cartridge, diamond stylus. \$49.95  
DELUXE C142 as above plus heavy weight dynamically balanced deicast turntable. \$59.95

Postage, N.S.W. \$1.85, Vic. & S.A. \$3.50, W.A. \$5.50.

## BSR STEREO PLAYER MODEL P-128

Latest design speed auto or manual operation. 11in heavy weight deicast turntable driven by fully shielded 4 pole dynamically balanced 240V motor. Noise suppressor. Silicone damped cueing device. Square section brushed aluminium pick up arm. Adjustable counterbalance. Calibrated stylus pressure control. Antiskate bias compensator fitted with magnetic cartridge, diamond stylus. \$55.00  
Postage NSW \$1.85, V. Q. SA, T \$3.50, WA \$5.50

## MAGNETIC CARTRIDGE

Stereo, freq. response 15-25000Hz, 1/2" mounting diamond stylus. Only \$5.95.

## GUITAR AMPLIFIER



50 watts RMS solid-state guitar amplifier, PM125 4 inputs, 2 channel with separate volume, bass and treble controls; speed and intensity controls for vibrato. Remote foot switch with plug and lead. Black vlynex carry cabinet. Fully constructed and ready for operation off 240VAC. \$135.00

**12" PLESSEY 50 WRMS**  
12U50, 20, 11000 Hz, RES45Hz. \$38.95  
12Ux50 Twin 20, 13500Hz, RES45Hz. \$45.95

## P.A. AMPLIFIERS

Solid state, rugged modern design metal cabinet. Manual, circuit included. 240V 50 watt RMS. Freq. 50Hz. 20kHz inputs for Mic, Pu, Radio, Aux. 2 Hi Imp, 1 Hi Mic. 1 Lo Mic, 100V-70V line, 4, 8, 16 ohms. \$115.00

15 watts RMS. 240V-12VDC powered. Freq. 50Hz-15kHz. Inputs for Mic, Pu, Radio, Aux. 100V-70V line, 4, 8, 16 ohms. \$69.95

## REFLEX HORN SPEAKERS

In/out door, rugged, lightweight, attractive, 8 ohms.

6" dia. 10 watt 8 ohms \$15.00  
8" dia. 10 watt 8 ohms \$19.50  
12" dia. 15 watt 8 ohms \$22.50  
P-P NSW \$1.50. Interstate \$2.50.

## SPEAKER FLEX

Twin 7/010. Striped. \$9.50 100m. Post & Package: NSW \$1.50 Interstate \$2.00.



## GARRARD

Model SP 25 Mark 4, the newly released latest model—a beautiful machine. 3 speed, 4 pole motor. Aluminium turntable. Fully balanced and CALIBRATED P.U. arm. Bias comp. cue & pause control. Click suppressor. Auto set down.

Super Special \$59.95  
Base & Perspex Cover \$29.00  
Pack and Post N.S.W. \$1.50. Interstate \$2.50

## PEAK KA-200 STEREO AMPLIFIER

6 + 6 watts rms, excellent freq. response, all silicon T'sistors, 8-16ohms, stereo headphone outlet, in/out tape, input magnetic/cer. cart, brushed aluminium panel, teak cabinet, top quality, guaranteed. \$65.00. P.P. NSW \$2.50. Interstate \$3.50.

## TV-FM BOOSTER

The Power Booster is designed to operate either one, two or three sets off one aerial for improved reception. SPECS. gain one set 10db 54-88mhz. 6.5db 174-216mhz. Two sets 5db. 54-88mhz. 2db 174-216. Three sets. No signal loss 54-216mhz. Input/output 300 Ohms \$23.95  
Power 240v 50hz Pack and Post \$1.50

## REVERBERATION DEVICE

Folded spring line, Hi. Imp. 28V. 19ma. Drive power in 530 mv. Max. out. 20 mv. Delay time. 300Hz 2 sec. \$19.50. P-P \$1.50.

## MICROPHONE STANDS

Telescopic, Heavyweight floor model. 1.7 meters. \$21.75.

## MINIATURE 3 CORE POWER CABLE

240V 170 watts 23/0076. Flexible P.V.C. \$22.50 per 100m.

## RED ROTATING DISTRESS BEACON

For car, truck or boat; fits with heavy duty suction cap, 12 volt 2 amp. \$9.95. P-P NSW \$1.50. Interstate \$2.50.

## SANYO BATTERY CHARGER FOR NICKEL CADMIUM BATTERIES

Will charge 4 penlight or 4 C type or 2 D type simultaneously. Complete with sturdy battery holder case and data. \$25.95.  
P.P. N.S.W. \$1.50. Other States \$2.75.  
Rechargeable Ni-Cad batteries  
Type A Penlight, \$1.70, 4 for \$6.00.  
Type C, \$2.90, 4 for \$10.50.  
Type D, \$3.65, 2 for \$6.80.  
P.P. N.S.W. \$1.00. Other States \$1.75.

## KENWOOD

QR-666 Communication Receiver  
6 Brands, 170KHz-30MHz AM, SSB, CW  
Send S.A.E. for full technical data. \$290.00

TS-520 SSB Transceiver \$545.00

## PLAYMASTER 143

High Performance 12.5 + 12.5 watts Stereo Amplifier. For full Particulars Ref. Sept./Oct. 74 Issues EA. Complete Kit Top Quality Components \$72.50. Fully constructed, thoroughly tested \$87.50.

## 15" BASS SPEAKER

V.C. dia 2". Excellent for Organ, Guitar or Sound System. 50 watts. 8 ohms. \$47.50.  
Post & Package: N.S.W. \$2.50. Interstate \$3.50.  
Goodmans Audio M, 18"—P. 8 ohms 100 watts. \$115.00.

## MUSICOLOUR II



Magical Colour Organ operates in conjunction with your home stereo or PA system—simple to connect and operate. 3 channels, 1,500 watt max load per channel.

Complete kit of parts \$59.50  
Constructed ready to operate \$69.50  
P & P \$2.50  
Interstate \$3.50

## GARRARD MODEL AP76 TRANSCRIPTION RECORD PLAYER

240V 50Hz 4 pole 3 speed auto setdown. Counter-balanced tubular p.u. arm Bias Compensator. Adjustable Stylus Force. Large die cast turntable. Fluid damped Cue and Pause. Auto-repeat. Mag. Cart. Super special \$65.00.

## SOUND 4 CASSETTE CAR STEREO.

Auto eject, fast forward & rewind, Indicator Light, separate tone, vol, bal, controls, 9 watts. 12 volt 12 mth. warranty. \$64.00 P.P. \$2.50

## DELUXE TWO-WAY CAR STEREO SPEAKERS

Rear Mount \$21.00 pair  
Door \$19.50 pair  
P.P. \$1.50

## 18 AMP. 6-12 VOLT BATTERY CHARGER

Hi-Lo rate for boost or bank charging \$59.95  
8 Amp Model \$48.95

## SPEAKER SALE SUPER SPECIALS

MSP 7 x 5 RBC/8 Ohms \$4.50  
MSP 6" x 4/15 Ohms \$2.25  
MSP 6 x 4/4 or 3.5 Ohms \$1.70  
Rola C4G/15 Ohms \$1.60  
Rola C3G/15 Ohms \$1.40  
Rola C4D/3.5 Ohms \$1.50  
Rola 5 x 4/15 Ohms \$1.60  
Rola 9 x 6 Twin 8 Ohms \$5.50  
Rola 8M/2 Ohms \$3.50  
Magnavox 6 x 4 SIC Midrange 33 Ohms \$2.25  
6 x 4 S2/3.5 Ohms \$1.70  
6 x 4 S1/33 Ohms \$1.50  
5 x 3/33 Ohms \$1.25  
Magnavox 8XJ Twin 27 Ohms \$3.50  
Magnavox 8 PIX Twin 33 Ohms \$3.50  
Magnavox 7 x 5 27 Ohms \$1.50

Philips ADO160/T8 1" Dome Tweeter. Per pair \$22.50.  
P.P. N.S.W. \$2.00. Interstate \$2.75.

## MINI 12VDC RELAY

DPDT 500 OHMS 22 x 16 x 20 mm. In plastic can. C.B.M.T. \$1.75.


## MULTI-CELLULAR HORN TWEETER

2-18 KHz 30 watts, 8 ohms \$12.95. P.P. N.S.W. \$1.50. Inter. \$2.50.  
30 watts, 8 ohms fully enclosed mid-range \$12.95. Pack & Post: N.S.W. \$1.50. Interstate \$2.50.

## C56 PROFESSIONAL

Programmed Length Hi-Fi low noise guaranteed Cassettes in hard pack. 10 for \$8.50.  
P.P. N.S.W. \$1.50. Interstate \$2.50.

## PLAYMASTER 3-45L LOUDSPEAKER SYSTEM

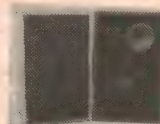

Features the mighty 8-30 woofer, 6J midrange and the incomparable Philips ADO16/T8 tweeter. This top quality low cost 3 way hifi system is available from stock in either walnut or teak veneer and complies with the specs. as per April '75 EA.

\$75.00 EACH

Special offer. 8-30, 6J and ADO160/T8 \$30.00

Standard 8-30 system. Teak or walnut \$67.50 each

Magnavox 6WR bookshelf system \$32.50 each

## MAGNAVOX WIDE RANGE TWIN-CONE SPEAKERS

8-16 OHMS 30-16,000Hz  
6WR MK5 12W RMS \$9.90  
8WR MK5 16W RMS \$10.75  
10WR MK5 16W RMS \$11.50  
12WR MK5 16W RMS \$13.50  
P & P 0.65

## SUPER SPECIALS:

EM 404 Diodes 400V 1A 20 for \$1.75.  
3A, 20V. Battery charger rectifier \$1.00.  
4000UF 75V C.M.T. electro \$2.00.  
100UF 200V C.M.T. electro \$0.90.  
L.55 FET multimeter \$32.00.  
AWA 11 T'sistor P.B. car radio with speaker LD aerial all mt. hard-ware. Made for Leyland P.76; fits most cars \$54.00.  
Polyester Recording Tape. 7" min. length 1200 ft. \$1.40.  
5" min length 900 ft. \$0.90.  
1-C in T05 can. UA741, 709, 723, 301—\$0.40 each.  
DIL SN76023N 75c each.  
Coax off cuts, 75 ohm. 1/2" & 1/4" dia. Min. length 20 ft. \$2.00 incl. post.  
Magnavox 10P1 8 or 15 ohms \$3.50.  
Magnavox 10P1X 3.5 ohms \$2.95.  
Magnavox 10WR 33 ohms \$4.95.  
Tesla 10 x 6 8 ohms \$3.90.  
Tesla 4" tweeter 4 ohms \$1.75.  
Pack & Post: N.S.W. \$1.00. Interstate \$2.00.

## NEW VALVES ONLY 75c EACH.

6AQ8, 6AD8, 6AM6, 6AK8, 6BH5, 6BQ7, 6BW6, 6BW7, 6AB4, 6CG6, 6CQ6, 6CU5, 6CM6, 6DS8, 6BR5, 6ET6, 6HG5, 9A8, 6T8A, 12AC6, 12AT6, 12AT7, 12AV6, 12AV7, 8LT8, 50EH5, PL81, PL82, PL83, PL84, PL5727, EY86, ECL80, PCL84, EY51, ELL80, M8136, M8137, M8162, 7551, 5963, 75C1, 92AV, 5965, 7247, 85A1, 5842, 6485.  
Please add postage 50c.

## NEW TEST GEAR

240V 50Hz USG-20 RF SIG. GEN. 120KC-500 Mc. 6 bands. RF output. HI NO MV. LO. 100UV. Audio output 400 CPS Internal. \$63.00.  
UAG-22D Audio SIG. GEN. sine and sq. wave. 20 CPS—200 KC. 4 bands. Output volts. 1 MOHM. 6V. 10 MOHM. 5V. \$69.95.  
TC-2 Tube Tester checks 7 Pin Noval. Octal Valves. \$57.50.  
Leader LSG15 solid state RF SIG. GEN. 120 kHz—450 MHz. \$69.95.  
P.P. All units N.S.W. \$2.50. Interstate \$3.50.


## EX PMG GEAR

All stock guaranteed.  
Diodes 200 PIV 200 AMP \$8.50  
200 PIV 100 AMP \$4.00  
Powerstat, Variable Transformer. 240V 50Hz Input. 0-280V 15 amp. \$38.50.



# The Amateur Bands

by Pierce Healy, VK2APQ

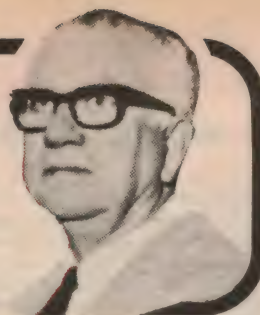

## Amateur satellite report

The amateur satellite program has entered its eighth year of operation. Past achievements, if reinforced by a greater use of the satellite facilities, could favourably influence deliberations on amateur frequency allocations at the 1979 ITU WARC.

The need to publicise amateur contributions through satellite experiments is the theme of the December 1975 AMSAT-Newsletter editorial. It points out that the use of VHF and UHF by amateurs could be questioned at the 1979 World Administrative Radio Conference by countries who are not sympathetic towards the amateur service.

Some of the achievements and firsts in amateur satellite communication have already been featured in these notes. Currently, the facilities of two amateur satellites are being used as educational devices by schools, colleges and universities in Europe and America. Experiments are also being carried out in the transmission of medical data; e.g., electrocardiogram (ECG) signals. Acceptable ECG patterns, closely resembling the original, have been received.

Here are further notes on current and future AMSAT activities.

October 15th, 1975 marked the third birthday of AMSAT-OSCAR VI, outliving its lifetime goal by 300%. The spacecraft continues to operate well, although it is occasionally necessary to reduce the operating schedule as the solar panels gradually degrade with time. AMSAT-OSCAR VI should continue to operate far into the future, providing that telecommand operators are able to maintain regular control over the spacecraft.

AMSAT-OSCAR VII had its first birthday on the 15th November, 1975, and continues to perform well. Like most satellites of comparable complexity, it exhibits some anomalies such as occasional mysterious "mode-jumping", but none which seriously jeopardise the mission objectives.

During 1975, new AMSAT-OSCAR VI telecommand stations were put into operation at the University of Surrey, England, the Technical University of Budapest, Hungary and in California, USA.

In March, 1975, an international AMSAT conference was held, attended by representatives of AMSAT-Canada, AMSAT-Deutschland, Project Australis, AMSAT and the San Bernardino Microwave society. The purpose was to define the AMSAT phase III next generation spacecraft. Phase III spacecraft are intended for high altitude, near synchronous or synchronous-transfer orbits, where communication time and range are much greater than with low orbiting satellites. (A report on that meeting was given in July, 1975, issue of these notes.)

Progress continued on the design and breadboarding of the phase III spacecraft. Plans are for it to carry two transponders, one using 145.9MHz for the uplink and 435.1MHz for the downlink, the other using 435.1MHz for the uplink and 145.9MHz for the downlink. The two transponders would operate alternatively according to a prearranged schedule, much as is done with the two transponders aboard AMSAT-

OSCAR VII. The phase III spacecraft will also contain a microprocessor (already developed) which will function as a command decoder, telemetry encoder (providing Morse code, teletype, or any other code programmed into it), and provide experiment control functions as well.

The preferred orbit is a highly elliptical, high inclination one having an apogee of about 39,000km (24,000 miles), with an inclination of 100 degrees. Such an orbit gives better coverage of the higher latitudes than does a geostationary one, and can be achieved by using an onboard apogee kick motor.

AMSAT-Deutschland in Marburg, Germany, is responsible for the overall phase III spacecraft design and breadboarding, while AMSAT-Canada in Ottawa and Montreal is responsible for prototype and flight spacecraft fabrication. Project Australis will assist in developing ground system equipment, and AMSAT-Washington will arrange testing and launch preparations. The total cost is estimated at between \$100,000 and \$120,000 (US). (This is met from donations, membership fees and the ARRL Foundation.)

In addition to the spacecraft, portable AMSAT satellite terminal equipment is being packaged for use in demonstrations and disaster areas. The terminals are battery operated, and capable of SSB operation with all transponders in OSCAR VI and VII as well as the phase III spacecraft to follow.

In addition to phase III, future projects are being planned. The Japan AMSAT Association is developing a four-watt, two-metre-to-70cm linear transponder which employs state-of-the-art RF power MOSFET techniques. AMSAT-Canada are repackaging the AMSAT-OSCAR VI and VII two-to-ten metre transponder to use thick-film hybrid printed circuit techniques instead of hand wiring. In the United States, a multichannel analog telemetry system is under development, and in England, AMSAT-UK members are discussing a possible fifteen-to-ten metre transponder project.

Reference orbits and operating schedules are:

AMSAT-OSCAR VI—  
Period = 114.9946076 minutes.  
Increment = 28.7486519 deg/orbit.  
Inclination = 101.6015 degrees.

Operating schedule:

2/10 metres on (GNT days), ascending nodes;  
Monday, Thursday, Saturday, descending nodes;  
Sunday (Even days, educational demonstrations only).

AMSAT-OSCAR VII—  
Period = 114.944834 minutes.  
Increment = 28.736208 deg/orbit.  
Inclination = 101.7010 degrees.

Operating schedule:

Even days of year, mode B.

Odd days of year, mode A.  
Wednesday, experimental and bulletin use only.  
General communications not permitted.

Transponder frequencies:

AMSAT-OSCAR VI—  
Uplink—145.90-146.00MHz.  
Downlink—29.45-29.55MHz.  
Beacon—29.45MHz.  
AMSAT-OSCAR VII—  
Mode A uplink—145.85-145.95MHz.  
Mode A downlink—29.40-29.50MHz.  
Mode A beacon—29.45MHz.  
Mode B uplink—432.125-43.175MHz.  
Mode B downlink—145.975-145.925MHz.  
Mode B beacon—145.972MHz.  
Mode A/D beacon—435.10MHz.

At the end of February, 1976, AMSAT-OSCAR VI will have completed 15430 orbits of the earth, and AMSAT-OSCAR VII 5910 orbits.

The board of directors of AMSAT are:—

P. Klein, K3JTE, president; J. King, W3GEY, vice-president engineering; T. Clark, W3LND, executive vice-president; W. Tynan, W3KMY; W. Dunkerley, WA2INB; L. Kayser, VE3QB; C. Dorian, W3JPT. Other officers include R. Carpenter, W30TC, secretary; R. Rosner, WB4UOX, treasurer; W. Hook, W3QBC, asst.-treasurer; Gary Tater, W3HUC, asst.-secretary; R. Zwirko, K1HTV, operations v-president; E. Clammer, W3UN, communication manager; J. Kasser, G3ZCZ, publicity.

New satellite operating award: The purpose of the award is to stimulate a continuing interest in satellite communications by providing recognition of QSO accomplishments, and to provide recognition by AMSAT of special efforts and services by all radio amateurs.

The basic award is available for confirmed satellite contacts with either (1) 20 US states, Canadian call areas, other countries, or a mixture thereof, or (2) six Australian call areas and two countries, or (3) any other requirements as specified by the AMSAT board of directors.

All contacts made via any OSCAR spacecraft using legal transmission mode are valid.

QSL cards or other written confirmation of contacts must show that the QSO was via a satellite.

In lieu of such QSL cards, applicants may submit a list of contacts confirmed by the awards manager of their national amateur radio society or AMSAT affiliate organisation.

All contacts must be made from the same QTH.

Sufficient postage must be supplied for the return of QSL cards sent. The award is free to AMSAT members, and is available to non-members for the nominal fee of \$1.00(US). Please include your membership number.

Endorsements are available for each ten additional areas as defined in section (1) above.

Send applications to AMSAT-Award Program, Box 27, Washington, D.C. 20044, USA.

ORBITAL DATA—In co-operation with AMSAT, an orbital data calendar has been published by Skip Reymann, W6PAJ. The calendar contains all orbits for 1976 for both AMSAT-OSCAR VI and AMSAT-OSCAR VII. Also included is information on the operating schedules and frequencies for both spacecraft, the telemetry decoding equations, plus a step by step instruction on how to determine pass times of the two satellites.

The orbital calendar is available postpaid for \$3.00(US) or 20 IRC's. Overseas orders will be sent airmail. Orders and payment should be made to: Skip Reymann, W6PAJ, PO Box 374, San Dimas, California 91773 USA. All excess receipts over costs benefit AMSAT.

AMSAT membership: Applications for membership should be made to Radio Amateur Satellite Corp. PO Box 27, Washington, D.C. 20044, USA.

There are four types of membership: Individual member—\$10.00(US) per year. Member society—\$20.00(US) per year. Life membership—donation of \$100.00(US) or more. Life member society—donation of \$200.00(US) or more.

Remittance should be made payable to AMSAT in US currency.

All members will receive the quarterly AMSAT Newsletter, and an AMSAT-OSCAR satellite pin for life members.

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent direct to Pierce Healy at 69 Taylor Street, Bankstown 2200.



# A SPLIT SECOND IN ETERNITY



## The Ancients Called It COSMIC CONSCIOUSNESS

Must man die to release his *inner consciousness*? Can we experience *momentary flights of the soul*—that is, become *one with the universe* and receive an influx of great understanding?

The shackles of the body—its earthly limitations—can be thrown off and *man's mind can be attuned* to the Infinite Wisdom for a flash of a second. During this brief interval intuitive knowledge, great inspiration and a new vision of our life's mission are had. Some call this great experience a psychic phenomenon. But the ancients knew it and taught it as *Cosmic Consciousness*—the merging of man's mind with the Universal Intelligence.

### Let This Free Book Explain

This is *not* a religious doctrine, but the application of *simple*, natural laws which give man an insight into the great Cosmic plan. They make possible a source of great joy, strength and a regeneration of man's personal powers. Write to the Rosicrucians, an age-old brotherhood of understanding, for a *free* copy of the book, "The Mastery of Life." It will tell you how, in the privacy of your own home, you may indulge in these mysteries of life known to the ancients. Address: Scribe J.N.B.

## The Rosicrucians

P.O. Box 66,  
Bentleigh, Vic., 3204, Australia

SEND THIS COUPON

Scribe J.N.B.  
The ROSICRUCIANS (AMORC)  
Roland Vigo, 554 North Road  
P.O. Box 66, Bentleigh, Vic., 3204, Australia

Please send me the free book, *The Mastery of Life*, which explains how I may learn to use my faculties and powers of mind.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip Code \_\_\_\_\_

## AMATEUR BANDS

### AMATEUR RADIO IN JAPAN

In mid 1975 there were over 286,000 amateur station licences issued in Japan, and the annual growth rate is between 10-20%. The licensing system in Japan provides for an operator's licence as well as the station licence. The total number of operator licences was just short of 500,000. All licences are issued for life and are not nullified if the holder upgrades to the next class. This means that it is possible to hold as many as four licences.

The four classes of licence issued in Japan are:—  
First class:— Requires a theory test, Morse code test at 12wpm, Japanese Morse test. Entitles holder to all amateur privileges. Total licences 4,800.  
Second class:— Theory test, Morse code test at 9wpm. All amateur privileges but limited to 100 watts antenna power. Total licences 20,100.

Radiotelegraph class:— Theory test, Morse code test of 5wpm. Operation on all amateur bands (except 14MHz), CW only. Antenna power limited to 10 watts. Total licences 437,600.

Radiotelephone class:— Theory test. Operation on all amateur bands (except 14MHz), phone only. Antenna power limited to 10 watts. Total licences 499,300.

The Japanese radio law makes little distinction between amateur and other communication stations and presents quite a challenge to a prospective licensee.

The Japan Amateur Radio League conduct classroom training, divided between theory and regulations, for the radio telephone course and requires about 40 hours' tuition. Passes run at about 85%.

The Ministry of Communication conduct examinations for all amateur licences twice a year. However, in the case of the 10 watt licences, those who complete the JARL classroom training course and gain a pass of 60% or more at the final examination, receive their radiotelephone licence without taking the government test.

Before a station licence is issued the station must be inspected by a government inspector. However, in the case of a 10 watt station a sanctioning system allows the JARL to act as guarantor to the Ministry.

This large amateur population has brought many problems which include serious overcrowding on the 40, 6 and 2 metre bands. More serious is the flaunting of the regulations, complicated by a lack of monitoring. There is no restrictions on the purchase of equipment, and there is frequent use of higher power than that authorised.

The JARL is aware of the many problems and established the Amateur Radio System Research Committee to study the situation and try to solve at least some of the problems. One proposal is a frequency allocation plan which has led to a wider use of VHF and UHF bands.

The use of HF bands by holders of no-code licences, as permitted by Japanese regulations, is based on their interpretation of the term "Harmful interference" in Article 3, section 3, paragraph 93 of the ITU Regulations.

### AMATEUR RADIO AWARDS

Those interested in the various operating awards could find the Radio Society of Great Britain publication "Amateur Radio Awards" a useful reference book. In addition to full details of a large number of certificates, the book also contains countries lists, prefix maps and other useful data.

Available from RSGB publications (Sales), 35 Doughty Street, London WC1N 2AE, England. Price £1.69 (\$2.75 Aus.). Airmail extra. Cheques and postal orders should be crossed and made payable to the Radio Society of Great Britain.

CANADIAN AWARDS: Amateur operators and short-wave listeners, worldwide, are invited to celebrate the XXI Olympiad to be held in Montreal, Canada, in 1976.

Two different and attractive awards will be issued to amateurs and short-wave listeners who fulfill the following conditions:—

World '76 Olympics Award: Work and/or hear amateur radio stations in any 50 countries which will compete at the 1976 Olympics in Montreal, Canada.

## WILLIS TRADING CO.

PERTH G.P.O. Box No. X2217 WA 6001


429 MURRAY ST  
PERTH WA  
21 7609 21 7600



### TR10 CS-1560

The 15MHz dual trace Oscilloscope. Complete with free x10 probes  
Price \$399.00  
\*Plus S/Tax

### KITS

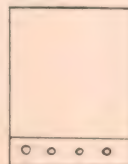

Colour Organs Wired  
\$49.50

Crosshatch Generator  
\$27.00

Hi Power Strobe  
\$27.50

PM143 Kit  
15w Channel  
\$69.00

ET1 440 Kit  
25w Channel  
\$95.00

5 Stage Logic Probe  
7-Segment Readout  
\$12.95

Function Generator  
Module  
\$12.50

### TOOL KIT



Kit Contains:  
Long Nose Pliers  
Flat Nose Pliers  
Cutters  
2 Screw Drivers  
1 Phillips Screw Driver  
Electric Soldering Iron  
Tweezers  
File  
Vinyl Zip Case  
Real Value at \$19.95



### Barlow Wadley

Specifications:  
500 kHz to 30MHz  
Dial accuracy within 5 kHz  
Modes AM LSB USB  
Sensitivity: antenna noise audible at all frequencies  
Price: \$282.00

6 DIGIT  
CLOCK KIT  
Complete  
with Cabinet  
\$32.95



Also Calendar Clock  
with alarm \$45.00



One contact must be with a Canadian station using an "XJ" or "XN" prefix. A special seal will be affixed for a contact with "CZ20", the official amateur radio station on the XXI Olympiad site.

Canadian 76 Olympics Award: Amateur stations have been authorised to use the prefix "XJ" in lieu of "VE" and "XN" in lieu of "VO" during the period 1st August, 1975 and 31st July, 1976. At least one contact must be made with each of the areas XJ1 to XJ8 and XN1 and XN2 for a total of ten contacts. Any contact with XJ0 (VE0) or the special Olympics amateur station will be allowed as a substitute for any missing call area prefix.

For either of these awards send certified log data list and 7 IRC's to:— VE3LSS, Radio Club, Listowel District Secondary School, Mr G. Hammond, 155 Maitland Avenue S., Listowel, Ontario, Canada N4W 2M4.

## WIRELESS INSTITUTE NEWS

The WIA annual federal convention will be held in Melbourne on 7th to 9th May, 1976. Members wishing to submit agenda items or general business items should supply details to their divisional council.

It has been reported by the federal executive that discussions have taken place with the PMC's Department, putting the WIA views in regard to the 1979 ITU WARC. Assurance was given that the WIA would be brought into any discussion, on amateur radio by a preparatory committee formulating the Australian delegation's brief. The question of the accreditation of a WIA delegate, as was the case with the late John Moyle in 1959, is also receiving consideration.

## RADIO CLUB NEWS

**CENTRAL COAST AMATEUR RADIO CLUB:** The Central Coast Award has been achieved by ZL2UK for having made two-way contact with the required number of stations in the Central Coast, defined as the Shires of Gosford and Wyong.

Meetings will be held in the club rooms Dandaloo Street, Kariong on 5th March—business meeting; 19th March—lecture night; 2nd April—election of officers.

Visitors are welcome. For information write to the secretary, PO Box 238, Gosford NSW 2250.

**GOLD COAST RADIO CLUB:** For the second successive year the GCRC were host to the WIA Queensland Division annual convention. Approximately 200 amateurs and interested persons attended. Alderman Clem Jones of Brisbane officially opened proceedings and in doing so congratulated amateurs on the part they played in providing communications during natural disasters in Australia.

Several good lecturers were presented and all told the convention was a success.

The GCRC UHF repeater in operation. Input frequency is 433.1MHz and output on 434.3MHz.

For information on GCRC write to Secretary Mike Adams, VK4ZDA, PO Box 588, Southport, Qld. 4215.

**SOUTH EAST RADIO GROUP:** The SERG newsletter which seemed to have been delayed somewhere, contained notes which may still be of current interest. The call sign VK5BMG has been allocated to the club for use during the "Back to Mount Gambier" celebrations. Approval has been given by TV station SES8, for the SERG repeater to be installed at their transmitter site. Arrangements have been made with the South East College of Further Education for SERG meetings to be held in one of the class rooms.

If intending to visit or pass through Mt Gambier, contact the secretary, Box 1103, Mt Gambier, SA 5290, for information on SERG activities. You will be made welcome.

**SYDNEY DX CLUB:** Is holding a world popularity poll. To enter, list those you consider to be the top ten DX stations and in no more than thirty words state why the number one station was chosen. Entries must be in by the 30th April, 1976. Entry fee is a donation towards the Handicapped Aid Program.


For information about the club contact Adrian Pitt, president, PO Box 204, Roseville, NSW 2069, Australia. Send stamped, self addressed envelope for reply.

**BOX HILL TECHNICAL COLLEGE RADIO CLUB:** Here is a letter received from Mark Tredrea, a 5th form member of the club.

## IONOSPHERIC PREDICTIONS FOR MARCH

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open.

3.76

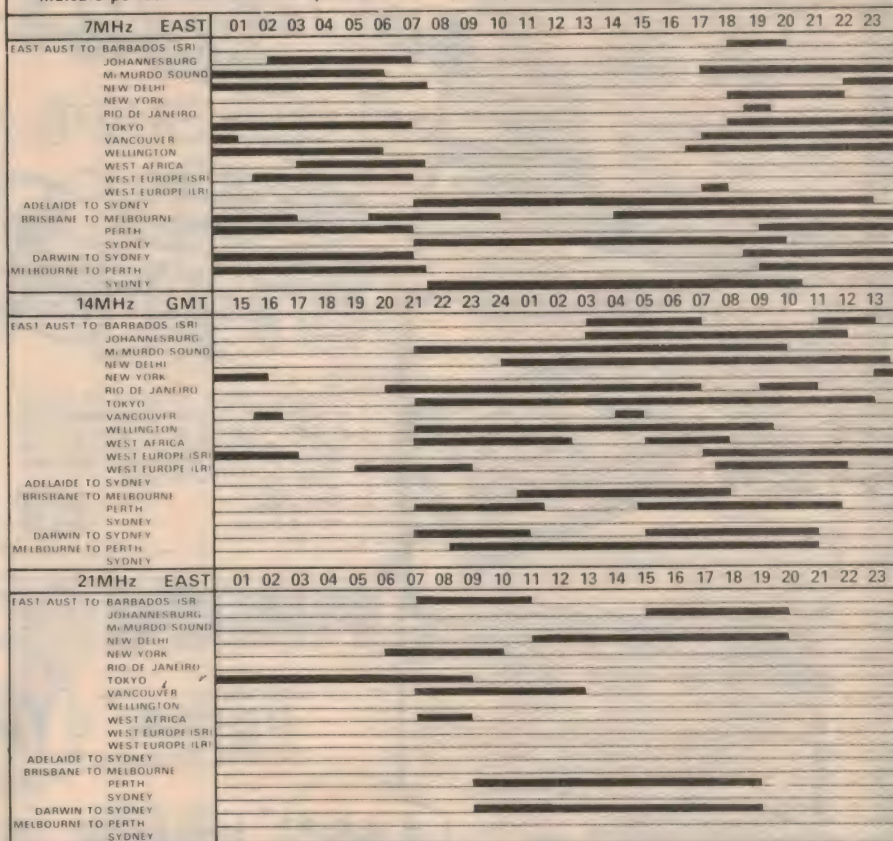

"I have been asked to write to you about our school radio club and particularly our class activities.

"The students in the college radio club total 27. Fourteen are fourth form students and the remainder are fifth form and higher technician students.

"The course I am undertaking is fifth form electronics. This course was introduced this year as a preliminary year to the higher technician section. At the moment there are no amateur radio licensees in the class but several members are studying with the view of obtaining their licence at the end of the year.

"Our class has four hours of radio work per week, two hours' theory and the rest practical, except for the four hours' practical work sessions. We go on the air two hours per week, Wednesday 10 am to 12 noon. The club call sign is VK3BHT and operates on 80, 40, 20 and 2 metres.

"The ambitions of our class are varied—five hope to be telecommunication technicians, two radio technicians, two electricians, three electronic engineers, one scientific instrument maker and one physical education instructor.

"In the two hour practical sessions, the projects our class is undertaking include stereo amplifiers and electronic testing equipment; also repairing television sets, radios and electronic devices."

It is pleasing to receive such letters which indicate the enthusiasm of up and coming amateurs.

The club is supervised by Graeme Scott, VK3ZR, a member of the teaching staff at the college. More about the club and photographs in future notes.

**ST. GEORGE AMATEUR RADIO CLUB:** Seventy-five members and visitors were present at the November meeting of the SGARC. Many of the visitors were from neighbouring radio clubs.

Bill Shakespeare, VK2AGF, gave a down-to-earth resume on the practical aspects of antenna construction.

Meetings are held on the first Wednesday of each month in the Rockdale Civil Defence Headquarters Highgate Street, Bexley at 7.30pm. Visitors welcome.

**INTERNATIONAL AMATEUR RADIO CLUB:** At the annual general meeting held late in 1975 the following officers were elected; R. C. Kirby, WOLCT, president; E. Robinson, F8RU, and R. F. Stevens, vice-presidents; J. Rutkowski, secretary; L. Jarrett, HB9AMS, treasurer. R. Kirby is the director and J. Rutkowski a councillor of the International Radio Consultative Committee (CCIR) of the International Telecommunication Union.

New members of the IARC will be welcome, and a life membership is offered until the 1st July, 1976, for 50 Swiss francs (\$15.00 Aus.). Membership applications should be sent to the Treasurer, IARC, Box 6, 1211 Geneva 20, Switzerland.

## YOU WANT TO BE A RADIO AMATEUR?

### A New Opportunity!

The Wireless Institute of Australia (N.S.W. Division) announces the introduction of a PERSONAL NOVICE COURSE which will commence at the Institute on 17th February, 1976, two evenings per week, extending over a period of 15 weeks. The Course will then continue for a further two terms to cover the full A.O.C.P. Course. Our A.O.C.P. Course by Correspondence is available at any time. A Novice Correspondence Course will be available later.

For further information, write to  
**THE COURSE SUPERVISOR, W.I.A.**  
14 Atchison Street  
CROWS NEST, N.S.W. 2065



# EDGE ELECTRIX YOUR ELECTRONIC WORLD

31 BURWOOD ROAD, BURWOOD, N.S.W. 2134 TEL: 747 2931

## ELECTRONIC KITS ★

CRYSTAL RADIO KIT

**4.50**

No soldering — easy to construct. Ideal for Junior to learn about crystal radio.


## SUPER

2 TRANSISTOR RADIO KIT

**\$6.60**

A great beginner's kit — fun to build, no soldering and a practical gift.

## 20 SIMPLE PROJECTS IN ONE KIT

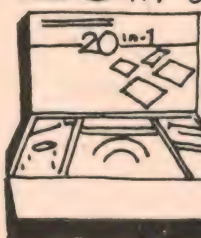

No soldering — no tools • Morse Telegraph set • Water purity tester • Transistor radio and many many more.

**\$12.40**


## 65 IN ONE KIT

ONLY **\$19.50**

- Transistor Radio
- Harpsicord Chimes
- Burglar Alarm
- Water Level Alarm
- Fire Alarm
- Electric Siren
- Solar Light Meter

Plus 58 other practical projects.

## 150 IN ONE KIT

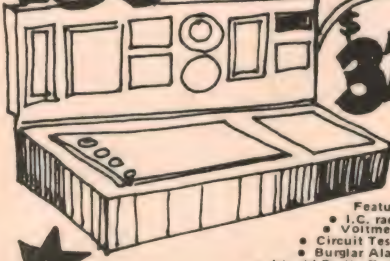


**\$31.50**

- Features
- I.C. radio
- Voltmeter
- Circuit Tester
- Burglar Alarm
- Liquid Purity Tester
- IC Record Player Amp
- Morse Code Light Signal

Plus 143 more great projects.

## Coral

SPEAKER KITS

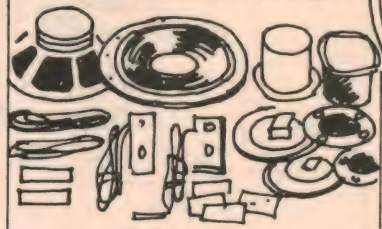

Why pay \$200 to \$300 for a 4 or 3-way pair of top class speakers? Here's what to do — buy the kit (pair) complete with all bits and make or buy your own cabinets. They really sound good.

8" 3 way **\$33.00**  
10" 3 way **\$55.00**  
12" 4 way **\$77.00**


## PHILIPS GREAT KITS

KIT NO 4A  
2 x AD 8066 W8  
2 x AD 5060 SQ8  
2 x AD 130T8  
2 x 3 way Cross Over

**\$120.00**

KIT NO 7A  
2 x AD 12100 W8  
2 x AD 5060 SQ8  
2 AD 160 T8  
2 x 3 way Cross Over

**\$165.00**

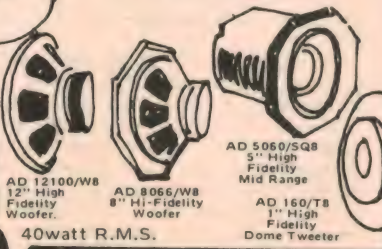

AD 12100/W8  
12" High Fidelity Woofer.

AD 8066/W8  
8" Hi-Fidelity Woofer

AD 5060/SQ8  
5" High Fidelity Mid Range

AD 160/T8  
1" High Fidelity Dome Tweeter

40watt R.M.S.

## PHILIPS 8" 2WAY SPEAKER SYSTEM WITH CABINETS AD8K40



**\$129.00**  
**GREAT**

All you need is a screwdriver to assemble this pair of Philips Speakers, 12" x 18" cabinets (supplied — 40 watts RMS a side, 8" Woofer and a Philips dome for each. The sound? everyone knows how good Philips speakers are!

## MAIL ORDER SPECIAL

### E.A. & ETI KITS

E.A. FM & AM TUNER  
\$135.00. With front panel but less case.

### ETI KIT 440

\$99.00. Including metal work.

### CROSS HATCH GENERATOR

\$22.00. Without front panel.

### SPEAKER SPECIAL

Magnavox 830 \$13.95.

### INNERBOND \$1.80 yd.

### SEMI CONDUCTOR SPECIALS

2N3055  
1 OFF \$1.10 each  
10 to 99 .95c each  
100 .80c each.

NE555 .70 each  
MW 741 DILI 72c ea.  
LM309 \$1.20 ea.

### MILUX CAR RADIO

Manual 6 Transistor with inbuilt speaker — lock aerial \$21.50.

### MICROPHONE SPECIAL

DM17 DYNAMIC  
Suits most tape recorders. \$3.80.

PLEASE RUSH ME

I ENCLOSE A CHEQUE FOR ..... +\$5. P&P  
(BALANCE OF P&P TO BE RETURNED)

PLEASE FORWARD INFORMATION ON.....

NAME.....

ADDRESS.....



# Shortwave Scene

by Arthur Cushen, MBE



The External Service of Radio Laos, broadcasting from Vientiane, has been heard with a service in English on 7145kHz at 1330GMT.

A new external service has been introduced by Radio Laos at Vientiane. The station is using the frequency of 7145kHz at 0400-0630GMT, 1100-1400GMT and 2300-0130GMT. The programs are in Thai, Vietnamese, Cambodian, French and English. The English broadcast is best received 1330-1400GMT on 7145kHz, and has been reported by John Mainland of Wellington, N.Z. Other transmissions are 0600-0630GMT and 0100-0130GMT.

According to the BBC Monitoring Service, the Domestic Service closes at 1430GMT and is broadcast on 640, 4245, 5160, 6130, 6200, 6210, 7310, 7480 and 8630kHz. In the past, Laos has been heard on 6130kHz and, according to the 'Down Under DX Bulletin', French has been observed 1230-1300GMT.

## SIGNALS FROM UGANDA

Three frequencies have been heard carrying the new External Service of the Uganda Broadcasting Corporation from Kampala. Reception on 9515kHz has been noted 1600-1730GMT with a transmission to South Africa. English news is broadcast at 1700GMT followed by a commentary or economic talk, and at 1715GMT popular music. The station when closing at 1730GMT asked for reports to the External Service, Uganda Broadcasting Corporation, PO Box 2038, Kampala.

A second transmission 1800-1900GMT to West Africa is on 15325kHz. This frequency suffers interference from Radio Canada, according to John Mainland of Wellington.

The third transmission 1900-2100GMT is on 9730kHz, and has been heard with English announcements at 2030GMT.

## SEOUL USES 7250kHz

Radio Korea, using the new frequency of 7250kHz, has been heard with English at 0900-0930GMT. This new frequency of 7250kHz from Seoul also carried Japanese at 0930GMT, but suffers from severe jamming at 1000GMT. Recently Radio Korea put into service three frequencies for its overseas services: 11850, 9600 and 9640kHz. The latter has long been the main channel for programs of the Korean Broadcasting System. The new outlet is not received as strongly as other frequencies, with 9640kHz still being the best signal for the English service, after the BBC leaves the same frequency at 0915GMT.

## SANAA ON NEW FREQUENCIES

Radio Sanaa in Yemen has recently been heard on three frequencies during a period of testing for a new channel. John Mainland of Wellington, NZ, reports hearing the station on 7265kHz with an Arabic news bulletin at 0515GMT. Later the station was observed to use 9765kHz at the same time.

Our reception has been on the new frequency of 9780kHz, and transmissions were observed from 0300 to past 0600GMT. Reception is fair, but there is considerable sideband interference from the Voice of America on 9770kHz. The signals during the transmission around 1830GMT give better reception, and

at this time a march, station identification and news in Arabic is presented. Signals suffer at this time from sideband interference from Radio Moscow on 9775kHz, which has been heard broadcasting in Portuguese. It is understood that the Sanaa transmission is from 1345-2200 GMT.

## VERITAS CONTINUES TESTS

Test transmissions from Radio Veritas at Quezon City in the Philippines continue to be received. A broadcast 0100-0200GMT is carried on 15325kHz, with frequent announcements for reception reports. In addition, the station has also been heard on 15310kHz. According to the announcement another test transmission is broadcast 1400-1500GMT on 1187kHz.

Reports from listeners are requested to Radio Veritas Overseas, Box AC373, Quezon City, Philippines. Our reception of broadcasts on 15325kHz has shown good signals with sideband from Radio Australia on 15320kHz. This is also the case when Veritas is using the announced frequency of 15310kHz.

## FREQUENCY CHANGES

Seasonal adjustments to frequencies are made by most international broadcasting stations four times each year, and on the first Sunday of this month, some minor changes will take place. Minor changes also take place on the first Sunday in September, with the major frequency changes occurring on the first Sundays in November and May. On these dates, the schedule valid for the following four months takes account of seasonal reception and several frequency changes are made.

As we are still at the low end of the sunspot cycle, there should be continued use of the lower frequencies, with emphasis on the 49, 41, 31 and 25 metre bands. During our summer, frequencies as high as 13 metres were used by many stations, with fair results. The rise in sunspot count in the near future should mean greater use of higher frequencies, thus spreading stations and resulting in less interference.

## NEW COLOMBIAN

A new Colombian station which is a member of the Radio Super network has been noted on 6122kHz around 0700GMT. The station has frequent network announcements and carries a similar program to Radio Super Bogota on 6065kHz and Radio Super at Medellin on 5955kHz.

The frequency of 6122kHz enables fair reception up to 0730GMT, when there is sideband interference from Finland on 6120kHz. At 0800GMT there is severe interference from the Voice of America, which is using 6125kHz.

## THAILAND'S NEW CHANNELS

Radio Bangkok has been heard on two new frequencies with their English broadcasts. Craig Tyson, Wembley, WA, has heard broadcasts at 0830GMT with an English announcement on 11950kHz which replaces 11905kHz.

Radio Thailand has also been noted on 9650kHz 1040-1140GMT with an English broadcast, according to Bill Vogel reporting in DX Post, Adelaide. This is a frequency change from 9655kHz. English is also broadcast on the new frequency 0415-0515GMT. The station is keen to receive reception reports on these frequencies.

## MEDIUM-WAVE NEWS

GUAM: The Trans World Radio Station on Guam, KTWC on 770kHz with 10kW, has been heard in New Zealand around dusk with transcribed Gospel music.

Another new medium-wave station in Guam is KATB, which operates on 570kHz, and has been heard in Japan around 1720GMT. The address of this station is: PO Box 65, Agana, Guam 96910.

KUAM on Guam, one of the old established stations, has been heard closing at 1500GMT with the "Star Spangled Banner". Reception was mixed with the Japanese station JOLK on 610kHz.

GREECE: According to "Australian DXers Calling", and our own advice from the Voice of America, two stations, Kavala and Rhodes, have increased power from 150kW to 500kW. VOA Rhodes transmits on 1259kHz from 0300-2230GMT, while VOA Kavala transmits on 791kHz from 0200-2200GMT. Both stations can be heard around dawn.

## LISTENING BRIEFS EUROPE

POLAND: Radio Warsaw, using 7125kHz, has provided good reception at 1600GMT with a program in English. This includes a news bulletin, a press review, and other features.

HOLLAND: The 'Happy Station' program of Radio Nederland has been well received by E. L. Haynes of Northcote, Victoria on 15260kHz. The transmission, from 1400-1520GMT, is also carried on 11740, 15415 and 17810kHz.

GREECE: Athens Radio on 7140kHz opens in Greek at 0800GMT. The transmission 0800-0850GMT is beamed to the Azores and carried on the 100kW transmitter. Athens has also been heard on 9615kHz at 1400GMT in Greek by the BBC Monitoring Service, and this appears to be a new transmission.

## AFRICA

ZAMBIA: Radio Zambia on 9580kHz has a news bulletin in English at 1600GMT, but reception is spoilt by a transmission from the BBC. The broadcast from London in Finnish also opens at 1600GMT, however it is possible to hear Radio Zambia broadcasting from Lusaka when conditions are favourable.

MALAWI: The Malawi Broadcasting Corporation is using 7130kHz for its broadcast from Blantyre and has been heard at 1615GMT. At this time local language programs are carried, but there is interference from Radio Moscow. At 1628GMT Deutsche Welle opens in Persian, making further reception impossible.

## ASIA

MALAYSIA: Radio Malaysia at Kuching, Sarawak, in a verification gives the following schedule, according to "Australian Calling DX-ers". The station operates on 4950kHz with 10kW from 0800-1600 and 2200-0100GMT, 7160kHz with 10kW from 2330-1445GMT and 9605kHz with 10kW from 0330-0730GMT.

SRI LANKA: The broadcast of 'DX Monitors International', which is conducted by Adrian Peterson and broadcast over the Sri Lanka broadcasting Corporation, Colombo, is heard on Sundays around 0420GMT. In this area, reception is best on 15425kHz. However, this frequency is also used by the ABC in Perth, and consequently there is some interference.

## AMERICAS

HONDURAS: Some months ago we reported the reception of a new station operating on 6185kHz with the slogan of "Radio Swan". The subsequent verification gave the location as San Pedro Sula and stated that the station broadcast 24 hours a day. The first Radio Swan was located on Swan Island in the Caribbean and broadcast programs to Cuba. Radio Swan has now made a frequency change, and has been heard on 6000kHz around 0700GMT. The address of the Station is: Apartado 882, San Pedro Sula, Honduras.

ARGENTINE: Signals on 6180kHz from Radio Nacional at Mendoza have been observed from around 0800GMT. This station formerly had the call sign "LRM" but is now known as "LRA34". Programs were typical Latin American music with station identification at 0845GMT.

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are in GMT. Add 8 hours for WEST, 10 hours for EAST, and 12 hours for NZT.



**SOUND ANALYSER**

General Radio Co. Type 760A \$75.00

**MUIRHEAD**Decade oscillator. Type DG 38A  
\$100.00**LANDING LIGHTS**

24 volts. Ex R.A.A.F. \$9.50

**P.M.G. TYPE TELEPHONES**

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line.

**\$35.00**

(2 TELEPHONE SETS)

\$1 cartage to rail. Freight payable at nearest attended railway station.

**ALTIMETERS**Sensitive type ex Air Force, made by Pioneer USA. \$37.50.  
Post A. \$1.70. B. \$2.25. C. \$2.40. D. \$2.65.**TEN CHANNELS  
VHF TRANSCEIVER**Types TR 1934 100-125 MHz and TR 1936 125-150 MHz. 28 volt DC operated AM single crystal locks both TX and RX on same channel complete with generator. **\$33.00****MINIATURE  
ELECTRIC MOTORS**

1½ to 3 volts DC. Ideal for model boats, cars, planes, etc. Strong torque. Only

75c each or 10 for \$5  
P & P 40c ea. or 10 for \$1.10.**FREQUENCY METERS**AN URM 32 A 120 KHz to 1000 MHz, with two 40V power supply, \$125.00.  
\$1.00 cartage to rail, freight payable at nearest attended railway station.**ILFORD 17.5 mm  
SPROCKETED  
MAGNETIC TAPE**1000 ft reels brand new original packing  
**\$4.00 ea.** quantity availablePost A. \$1.30. B. \$2.00.  
C. \$2.30. D. \$2.80**No. 62 TRANSCEIVER**With headphones, accessories etc.  
**\$60****TELEPHONE WIRE**

1 mile twin (2 miles) genuine ex-Army Don 8 perfect condition \$35 per drum \$1 cartage to rail freight payable at destination.

**PRISMATIC COMPASSES**

Genuine ex-army Mk 3, liquid damped, as new \$45.00 P &amp; P A. \$1.70. B. \$2.25. C. \$2.40. D. \$2.65.

**MORSE KEY** | **MORSE KEY BUZZERS**  
**\$1.40** | **\$4.25**  
Post 40c. | Post 60c.**HALF INCH RECORDING  
TAPE**Top Grade 2400' on 10½" reels. Ideal Video Experimenting. Only **\$3.50** per reel.P & P A. \$1.40. B. \$2.25.  
C. \$2.70. D. \$3.45**UNI-SELECTORS**4 bank 25 position **\$4** each.  
P & P A. \$1.40. B. \$2.25. C. \$2.70. D. \$3.45**ADLER FREQUENCY  
METER**100 KHz 20 MHz **\$95****4 DIGIT RELAY COUNTERS**

50 volt DC, suit slot car Lap counters, etc.

**\$1.25** each. P & P 60c.**NIBBLING TOOL**

Cuts sheet metal like a punch and die, trims, notches and cuts to any size or shape over 7/16 inch.

**ONLY \$9.95**

Post \$1.10

**NIFE CELLS**

1.2 Volt, fully charged, 4in x 3in x 1in 4 AH.

**\$1.50** each. P & P 60c.**BC221**

Frequency Meters.

**\$35.00****HANDY SIGNAL INJECTOR**

Produces an Audio Signal in rich harmonics. Ideal for Sig Tracing in A.F., I.F., and R.F. circuits. Powered by 4 Penlight Batteries with On-Off Switch and indicator lamp. Size 1½" Diam. 5" Long. Only

**\$6.50**. Post \$1.10.**TELESCOPES**25 x 30 **\$5.95**  
40 x 40 With Tripod **\$8.95**  
60 x 60 With Tripod **\$39.50**  
30 x 60 Prismatic With Tripod **\$34.50**  
P & P A. \$1.70. B. \$2.25.  
C. \$2.40. D. \$2.65.**ZOOM  
TELESCOPES**

60 magnification with a 60mm coated objective lens with tripod.

**\$75.00**

as illustrated

P & P A. \$1.90. B. \$2.75.  
C. \$3.20. D. \$3.95.**WALKIE TALKIES**2-way radio, 7 transistor PMG approved, set of 2 only **\$48.50**

1 watt, 11 transistor \$130.00 set of 2.

P & P A. \$1.80. B. \$2.50. C. \$2.80.  
D. \$3.20**SMALL COMPUTER  
PANELS**3in x 2in containing 2 valves, qty. of resistors, etc.  
ONLY 75c. P & P 60c.**ELECTRONIC FREQUENCY  
COUNTER**Austroic type DFC-4 240V 50 cycle 0-100 KHz **\$150****IMPELLER PUMPS**

New gunmetal body, Stainless Steel Shaft. Neoprene Impeller. Up to 15ft. Lift, suitable for almost any type of liquid. Self priming. Ideal boat bilge pump, sullage drains, etc. Approx size 8" x 5"

¾" **\$23.30**  
1½" **\$31.95**  
2½" **\$33.75**

P &amp; P A. \$1.90. B. \$2.75. C. \$3.20. D. \$3.95.

**RECEIVER No. 210**2-16 M/cs \$65.  
Transmitter No. 11 suits 210 \$35.  
24 volt Power supply to suit above \$15.  
Or complete station with Headphones, Mic, Morse Key, Antenna \$110.**SIGNAL GENERATOR**Palec Model SG 1150 Kc/s to 30 M/cs  
240 VAC **\$37.50**.  
\$1.00 cartage to rail.  
Freight payable at nearest attended railway station.

522 Transceivers 100 150M CS

**\$35.00****5" CRO TUBE** 5 BPI **\$5.50** each.  
Post A. \$1.40. B. \$2.25. C. \$2.70. D. \$3.45.**POSTAGE KEY:**A: NSW.  
B: Vic, Qld.  
C: SA, NT, Tas, New Guinea,  
D: WA.**VALVES****BRAND NEW  
IN CARTONS**

807	\$1.50	CV850	\$1.50
65N7GT	95c	1H6G	75c
5U4G	95c	832	\$5.00
EF50	75c	6X4	\$2.25
5Y3	\$2.25	VR64	75c
2 x 2	75c		

P &amp; P 40c

**PARABOLIC REFLECTORS  
PYREX MIRROR**36" dia. Ideal solar radio optical experimenting also decorating purposes.  
**\$60.00**. Sorry shop sales only.**TELESCOPES  
ZOOM FOCUSING**30 x 30 **\$19.95** — 45 x 40 **\$28.95**  
50 x 50 **\$37.50** — 60 x 60P & P A. \$1.70. B. \$2.25.  
C. \$2.40. D. \$2.65.**SPY TELESCOPES**8 x 17 mag size of a rifle cartridge extends to 8" Only **\$4.25** each, post 60c.**BINOCULARS**

PRISMATIC Coated Lenses. Brand new. Complete with case.

7 x 35 Wide Angle.....	\$35.50
8 x 40 Wide Angle.....	\$39.50
7 x 50.....	\$31.50
10 x 50.....	\$32.50
12 x 50.....	\$33.65
20 x 50.....	\$37.95

P & P A. \$1.80. B. \$2.50. C. \$2.20.  
D. \$3.20**SOLENOIDS**

Plunger Type 12V 300MA. Suit electric camera control, miniature trains, radio, etc.

**\$2.50** P & P 20c

200 MA 24 volt, ½ in push movement.

**\$2.50** P & P 20c.**SELSYN MOTORS  
MAGSLIP**MK 11 ..... **\$5.25** ea.  
No. 19 TWO-WAY RADIOS.  
Power supply, accessories, etc., **\$35**.**3000 TYPE RELAYS**P.M.G. 200 Ohms — 1'500 Ohm  
Coils **\$2.50** each. P & P 60c.**P.M.G. TYPE KEY SWITCHES.**  
**45c** P & P 20c

Cintel Oscillator and Electronic Counter, type 388.

**\$250**SPECIAL lucky dip valve offer, 15 new valves in cartons for only **\$2.95**. We haven't got time to sort them, so you reap the benefit.  
P & P A. \$1.80. B. \$2.50. C. \$2.80. D.**RADAR TRANSCEIVER**X BAND WITH KLYSTRON  
ETC. **\$45.00****MULTIMETER**A compact and handy tester for workshop or lab where quick circuit checks are required  
DC Voltage 5.25K (20,000 OHMS per volt) AC Voltage 10-1000V (10,000 OHMS per volt) DC Current 0.50 UA, 0.25 MA, 0.250 MA. Resistance 0.6 Megohms Capacitance 100 UUF to 1UF. Decibels — 20 to plus 22 DB. Complete with instructions.  
Only **\$17.25** ea. Post \$1.05.**EX ABC RECORDING  
TAPES TOP BRANDS**¼" x 2400' on 10½" reels **\$4.95**  
P & P A. \$1.70. B. \$2.25.  
C. \$2.40. D. \$2.65.**Panoramic Adaptor**E.M.I. type PRA-1 455 variable Kc Course 440-520 Kc  
Centre Freq 520-440 Kc  
Fine Centre Freq 20-0-20  
Filter band with 50, 100, 200 L.F.  
200 H.F. Sweep band width 0-200.**\$75.00**.**CONDENSER LENS**1½" Diam 4½" F.L. 75c 2½" Diam 2" F.L. **\$1.50** each. Or **\$2.50** per pair. P & P 40c**TRANSCEIVERS  
Ex Army**No 10 set, 38 to 55MHz with hand piece **\$22.50**. Battery to suit **\$3.50** extra.  
No C42 set, 36 to 60 MHz complete with 24V power supply, headphone, mic, leads etc **\$65.00**.  
No C45 set, 23 to 38 MHz complete with mast, headphones, mic, 24V power supply etc. **\$95.00**.  
\$1.00 cartage to rail, freight payable at nearest railway station.Hartley double beam oscilloscope. Type 13A with probes.  
Working **\$150.00**

77D x RCA STUDIO RIBBON MICROPHONES Variable pattern &amp; response music or speech. \$80.00 ea. Post A. \$3.30 B. \$4.00 C. \$4.30 D. \$4.80.

Director dumpy levels optical complete with tripod and carrying case ideal for all level work also gives elevation and depression illuminated only **\$85.00****ANTENNA MASTS**Telescopic. 10ft. extending to 27 ft. Complete with nylon rigging, stays pegs and base plate. **\$45.00****15" SPEAKERS**Top grade high fidelity. Dual driver. 20 to 20,000 Hz. 120° dispersion. 15 OHMS 40 Watt rating. **\$75.00****ANALYTICAL SCALES**Brand new. Griffin & George (London) Housed in timber & glass case 16" x 16" x 7". Weighs down to fractions of grams. (No weights supplied.) Usual price \$187.50. Special **\$45.00** ea. Post A. \$2.10. B. \$3.25. C. \$4.00. D. \$5.25.**REPERFERATOR**Genuine Siemens Type 33c **\$65.00****Deitch Bros.**  
**70 OXFORD STREET, SYDNEY 2010**

SORRY NO C.O.D.



# INFORMATION CENTRE

**DIGITAL ALARM CLOCK:** I have just read with interest the letter from R.J. of Melbourne, and your reply, in the December 1975 issue. I have just completed building the same project, and experienced the same problems as R.J. The temperature of my clock chip was high, and I found this to be due to excessive current being drawn by pin 23.

I added a 5k resistor in series with pin 23, and reduced the current drawn from 80mA to 2mA approximately. However, this increased  $V_{SS}$  to 30V, so it was necessary to add a 1k resistor in series with D2. The components were soldered directly to the pattern on the underside of the board. (D.S., WA.)

• Thank you for your comments concerning the Digital Alarm Clock, D.S. We have investigated the problems you have outlined, and also your solutions, and in last month's issue we published a note detailing improvements which can be made to the clock.

**TAPE DECK:** I have recently bought a stereo reel-reel deck mechanism which I would like to use in conjunction with my Playmaster 144 cassette deck (File No 1/RA/31). The deck is unbranded, has 7in reel capacity, has 3 $\frac{3}{4}$ , 7 $\frac{1}{2}$  and 15ips tape speed, provision for a separate monitor head and is wired for 240VAC. The R/P head is stamped 250mH. My queries are: If I arrange suitable switching, could I use the record, replay and erase circuitry of the PM144? If the replay circuit is incompatible (I read your reply to G.B. of Glen Waverley in the September issue), would the tape head preamp described in September 1971 (1/PRE/26) be a suitable link to a Playmaster 136 tape socket? If neither of these alternatives is feasible, would you consider designing a circuit for readers who wish to build their own open-reel deck, if possible with tape-tape transfer to the PM144. (M.S., North Carlton, Vic.)

• Our answers to your questions are No, Yes and No. The Playmaster 144 circuitry is not suitable for open reel decks with high impedance heads. There is little demand for and little advantage in designing an open reel tape recorder. We have designed circuitry for these in the past, the most recent being a hybrid valve and transistor circuit, the Playmaster 119 Stereo Tape Adaptor, September 1967, File No 1/RA/28. Reprints are available from our Information Service at the usual charge of \$2.00.

**GAS DETECTOR:** In the June 1974 issue of your magazine, you presented "An Electronic Gas Detector" (File No

3/MS/47). Mention was made in the article that if there was sufficient reader interest, a more complex circuit may be presented.

I now have need to make a similar gas detector, as presented, but with some additional features: it must have an audible/and/or visible alarm and the unit must be so wired that it will prevent the ignition of a boat from being switched on until the unit has ensured that petrol fumes have not been detected. While the latter requirement seems to present no large problems, the first-mentioned may be a little harder to arrange.

Do you have any plans for the inclusion in "Electronics Australia" of a more complex Gas Detector? (P.M., Beaudesert, Qld.)

• Your plans to build a Gas Detector in a boat do not seem to present any really difficult problems but unfortunately we are not in a position to make practical suggestions. To date, we have had little feedback on the Gas Detector project and so we have no immediate plans to publish a more complex unit.

**HIGH POWER AMPLIFIERS:** With the apparent swing nowadays to amplifiers of preponderous power capabilities, I was wondering if you intend to describe a stereo hi-fi power amplifier of approximately 200-300 watts per channel. I for one would certainly be interested in it, since I have just invested in a new, but inefficient, speaker system, which means that half my modest 34 watt per channel amplifier is wasted, not to mention the

other obvious advantages of going into high power.

I'm sure that there are many readers like me who own a semi-professional pre-main amplifier with the facility to separate the same. It would, therefore, be relatively easy to simply "add-on" a more generously rated power amplifier to such a system. (R.D.D., Cal Gully, Vic.)

• We have no plans at present to describe an amplifier of the size you have quoted. Suitable transistors for use in the output stages of such amplifiers are almost impossible to obtain at economical prices, and so any plans for such amplifiers would have to wait until suitable devices become available.

**CDI PRAISE:** I for one will testify to the desirability of CDI on two stroke engines. Without having done any other servicing to my triple-cylinder, triple ignition coil and triple points motorcycle (which incidentally necessitated three trigger systems coupled to the converter unit) except simply fitting CDI, the results were (1) idling speed lowered from 1200 RPM to a steady 800 RPM (2) greatly enhanced throttle response thus improving acceleration and (3) more power than the bike has ever produced at over 6000 RPM.

I have ideas as to how I could design an automatic electronic ignition advance which is a real necessity for any high revving engine (and which very few motorcycles have) but my design would probably be too crude. So I'm waiting in anticipation for you to produce a project for an automatic electronic ignition advance unit to go with the CDI unit. While we're on the topic of CDI, a unit adaptable to lawn mowers would be useful. How about it? I realise that you might envisage some people ruining their engines but advancing ignition by about 35 degrees BTDC at 8000 RPM is

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

**PHOTOSTAT COPIES:** \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

**METALWORK DYELINES:** Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

**PRINTED BOARD PATTERNS:** Dyeline transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

**REPLIES BY POST:** Limited to advice concerning projects published within the past 2 years. Charge \$2. We cannot provide lengthy answers, undertake special research or discuss design changes.

**BACK NUMBERS:** Only as available. Within last 6 months, face value. 7-12 months, add 5c surcharge; 13 months or older, add 10c surcharge. Post and packing for 60c per issue extra.

**OTHER QUERIES:** Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

**COMMERCIAL, SURPLUS EQUIPMENT:** No information can be supplied.

**COMPONENTS:** We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

**REMITTANCES:** Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

**ADDRESS:** All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.





# Scope Cordless 60w Soldering Tool



## HEATS IN 6 SECONDS, COOLS RAPIDLY WHEN TRIGGER RELEASED

### SOLDERS 100-200\* TYPICAL JOINTS BEFORE RECHARGING

\*Light electrical connections.  
Capacity will vary for lighter  
or heavier joints.

**PISTOL GRIP DESIGN** balances  
weight of cells for comfort  
and tip control.

**FULLY RECHARGEABLE  
OVERNIGHT**, from car, power-  
point or Scope Transformer.

**ABSOLUTE SAFETY**  
No earth leakage currents.  
Solder anywhere with total  
personal and component  
protection.

**Basli Rogers & Co. Pty.  
Ltd., Radio & T.V. Repairs.**  
"I'm delighted with its  
performance and sheer con-  
venience in the workshop or in  
the field. It's light, fits easily in your hand  
and you can solder even with the set on."

**Kevin Ball, T.V. Technician.**  
"In my job I work mainly on circuit boards  
and I'm rapt with Scope Cordless. I've never  
reached a point where the gun can't handle a  
day's soldering. I like the feel of it;  
tremendous balance."

# SCOPE

Distributors to the Electrical Trade:  
**NATRONICS PTY. LTD.** The Crescent, Kingsgrove, N.S.W. 2208

Manufactured by: **SCOPE LABORATORIES, MELBOURNE.**



playing reasonably safe. This is taking four strokes into account, for two strokes the advance would need to be slightly higher. (P.T., Canterbury, Vic.)

● Don't hold your breath, P.T. We would not envisage producing a project along these lines. The ramifications of reliability of the increased number of components and the likely problems in providing quick changeover from the existing system to the electronic and vice versa would greatly outweigh any theoretical advantage. Nor do we think a CDI unit for lawn mowers is really practical. It might give more reliable starting, but for a considerable increase in complexity. Don't forget, you'd need to fit a battery and a suitable charging system.

**HIGH POWER AMPLIFIER:** I must say how pleased I am with the Playmaster 128 Stereo Amplifier (Jan 1970) and its companion 127 Control Unit (Nov 1969) which I built some four years ago. Although both units continue to give sterling service, could some thought be given re updating circuitry? As you will be aware, commercially made high power amplifiers are currently enjoying a great deal of popularity and many enthusiasts wishing to build their own will favour the separate preamp/power amp approach. (T.S., Tatura, Vic.)

● It is gratifying to learn that your Playmaster 127/128 stereo system has given you such good performance. We agree that an updated version may prove a popular project, and will give due consideration to publishing an amplifier of similar power output to the Playmaster 128 in the near future. However, modern design trends now favour the integrated amplifier approach (i.e. power amplifier, preamplifiers and tone controls incorporated into one unit), and this will probably be our design philosophy for the present.


**TAPE COPIER:** I have been approached by a church group with the idea that I should help develop a copier which would make available cassettes of the service within about 15 minutes of the end of proceedings. They have mechanically inclined members who feel confident that they could modify up to a dozen standard Vortex decks to operate at a higher speed for copying. Where they need my help is with the electronics. Could you oblige with a circuit? (S.C., Maroubra, NSW.)

● The usual idea behind such a scheme is to allow churchgoers to take a tape of the service to shut-in parishioners. What is not always realised is that old and ailing folk often cannot cope with a purely audio event which typically lasts for an hour or more. A much more realistic approach is to record the service on a good quality open-reel machine, thereafter editing the tape down to a much shorter format by eliminating lengthy announcements, verses from long hymns, long voluntaries, etc. This involves expertise, a fair amount of somebody's time and, of course, a delay in producing the edited master tape, but the end result can be far more listenable. And, of course, it largely obviates the need for high speed copying, involving only the master and ordinary decks as "slave" copiers.

As far as high speed copying is concerned, there would be far more to it than merely speeding up a conventional deck. We doubt that the Vortex or any other ordinary deck could be adequately modified. High speed copying is normally done on to open reels of tape, which is then cut up and loaded into blank cassettes.

As far as the electronics is concerned, copying at say six times normal speed calls for six times the bandwidth and a proportionate increase in bias frequency. No ordinary heads would be equal to the task and very special amplifier, compensation and bias circuitry would be needed. There's a lot more to it than your group appears to imagine and we think that you would be wise to think it through again.
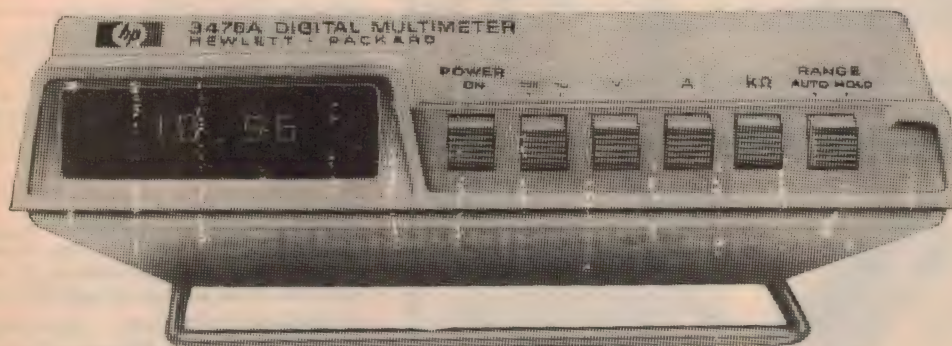
## Autoranging 5-Function Multimeter for \$209



- Auto-ranging with range hold button
- dcV, acV, dcA, acA, ohms
- All functions fuse protected at input
- Weight a low 770 grams for field portability
- Wide range of probe/carrying case accessories available
- 3476A - mains only; 3476B - mains and Ni Cd battery.
- ★ 3476A is \$209 Duty Free or \$261 Duty Paid. Batteries \$47 extra (or \$58 including Duty). Prices valid as at 28/1/76.

For data sheets/quotations on the 3476A phone your nearest HP office.

- ADELAIDE 272 5911
- BRISBANE 229 1544
- CANBERRA 95 3733
- MELBOURNE 89 6351
- PERTH 86 5455
- SYDNEY 449 6566

**HEWLETT**  **PACKARD**

906013



# Marketplace

## FOR SALE

**BRAND NEW** net C = 32 freq. counter in box with warranty & instructions. \$450.00 or nearest offer. Phone Harden 868-201 after hours or write: Mr. Michael Stevenson, "Attunga", RMB 59, Harden, 2587, N.S.W.

**TV MASTHEAD AMPLIFIER** with power unit, 22dB gain, \$32.00, P&P \$3.00. Tweeters, 8 ohm, 80W \$8.00, P&P \$1.50. LED readouts, jumbo 1 inch \$3.90; 3/4 inch \$1.80, P&P 30c. Transistors BC147, 148, 149, 157, 158, 159—10 for \$1.80. AC127, 128, 187, 188—68c each. Diodes IN4004, IN4002, 10 for \$1.50. BA222, 10 for 90c. 1MHz crystal \$11.50, P&P 40c. Primo EMU522 Mics \$19.80, P&P \$2.00. Portable 12V fluorescent lantern with Cig. lighter extension lead, suitable for camping, etc., \$13.00, P&P \$2.00. Electronic Concern, Box 380, Darlinghurst, 2010, NSW.

**PC LAMINATES TO CLEAR**, 3 1/2" x 24" x 1/16", single-sided phenolic, 1 oz copper. \$2.50 for a pack of 5. \$1.00 for P&P in N.S.W. Hobby Hire, 16 Coveney St., Bexley 2207. Tel 50 4361.

**PLAY THREE EXCITING ELECTRONIC GAMES.** Tennis, Football, Basketball. Just plug TELEPLAY Mk III into the aerial socket of your T.V.—B&W or Colour—and you are ready to play. Mains operated. \$115. Reg. Post and Pack \$5.50. Logic Leisure Electronics, Box 390, P.O., Mascot, N.S.W. 2020.

**DISPLAYS:** FNA37 9 digit calculator LED display \$5.50; SP-425-09 9 digit Sperry Gas Discharge Display \$3.50; **POSITIVE VOLTAGE REGULATORS:** 305 up to 40 volts TO-5 \$2.00; 340 T series 5V, 6V, 12V, 15V & 24V volts (specify voltage wanted) TO-220 \$2.25; 376 up to 40 volts mDIP \$1.10. **NEGATIVE VOLTAGE FOLLOWER:** 304 up to -30 volts TO-5 \$1.60. **OPERATIONAL AMPLIFIERS:** 301 TO-5 or mDIP 60c; 307 TO-5 or mDIP 90c; 709 TO-5 or DIP 75c; 741 TO-5 or mDIP 80c; 747 (dual 741) TO-5 or DIP \$2.45; 748 (freq. adj) mDIP \$1.25; 3900 Quad DIP 80c. **VOLTAGE FOLLOWER** 302 TO-5 \$1.10. **VOLTAGE COMPARATOR:** 311 mDIP \$1.50. **CALCULATOR CHIP:** 5005 12 DIG 4 func w/mem \$5.95. **DIGITAL CLOCK CHIPS:** MM5311 28 pin BCD 4 digit mux \$8.95; MM5312 24 pin 1 pps BCD 4 digit mux \$7.95; MM5314 24 pin 6 digit mux \$8.95; MM5313 28 pin 1 pps BCD 6 digit mux \$8.95; MM5316 40 pin alarm 6 digit \$9.95. All parts new & guaranteed; Data sheets supplied upon request with order. **WORLDWIDE ELECTRONICS**, P.O. Box 308, Hornsby, N.S.W. 2077.

**BARGAIN PACK OF CLOSING DOWN STOCK**—103 assorted valves, assorted capacitors, transformers, plugs and sockets and other items too numerous to list. All new, packed and marked. Write for detailed list. Real value at \$420.00. Also 19 stylii and 4 cartridges for \$30.50. All parts are fast moving. Peter Stocks Electrical, PO Box 229, Hughenden, Qld. 4821.

**ICL 1905 Computer parts:** Power supplies, 1972/2 tape unit, teletypes, fans, plugs & sockets, boards. Hadgraft, 17 Paxton St, Holland Park, Qld. 4121.

**WE SELL Construction Plans.** TELEVISION 3D converter, \$25 camera, Kinescoping recorder, VTR Colour Converter, HOB-BYIST: Electronic Microscope, 96-hour music system, voice typewriter, Morse Code to typewriter copier, solid state Tele-type. **TELEPHONE:** Answering machine, pushbutton dialler, phonevision, Autodialler, Car Telephone Extension, legal connector. **BROADCAST:** Special effects Gen., Time Base Corrector. Plans \$7.50, air shipped from our USA research labs. **COURSES:** Telephone Engineering \$52. Security Electronics \$33. Investigative Electronics \$29.50. Super Hobby Catalog plus 1 year's Electronic Newsletter, air mailed \$1.00. Don Britton Enterprises, Suite 28, 280 Pitt St, Sydney, Australia.

**TRANSFORMER BARGAINS**—All 240V pri., r.m.s. values quoted 12V C.T. 1A, \$4.50; 18V 4A, \$10.50; 25V C.T. 1.2A, \$7; 40V C.T. 1.4A, \$10; 70V C.T. 1.7A, \$15.50; plus many others. Send S.A.E. for catalog. Prices include postage. R.K.O. Electronics, 4 Shaw Street, Springvale South, Vic. 3172. Phone 546 6631.

**PRE-AMPLIFIER** English Codar, Brand New. \$30.00. Lockerbie, Cameron St, Merimbula 2548.

**RESISTORS AND CAPACITORS** Packs of 285 resistors. Standard Pack contains 5 each of E12 values 10 ohm to 470K in I.R.H. GL 1/2 metal glaze resistors, (1/2 watt at 70°C. 5%) Computer Pack contains selected quantities. All values included. \$7 per pack. Individual resistors 3c each, 250 or more 2.5c each. Each value is individually packed so no sorting out required! Phillips 1/4 watt carbon film still available, see E.A. November. **CAPACITORS** Ceramic 50 volt circular plate. 10, 25, 47, 68, 120, 270, 470, 680 pf and .001 mf 5c each. .0022 .0033 .0047 .01 .02 .047 8c each. .1 mf 9c each. Ceramic pack contains 80 capacitors being 5 each of values listed. Due to high demand reduced to \$4.50 per pack. Polyester "Green Cap" 100 volt .001 .0022 .0033 .0047 .01 7c each. .022 .033 .047 .068 mf 10c each. .1 and .22 13c each. Polyester pack contains 5 each of these values for \$5.00. **ELECTROLYTICS**, Uprights 1000, 16 volts, 40c, 35 volts, 70c, 2200 mf 16 volts, 55c. Pigtales 1000 10 volts, 35c, 1000 35 volts, 80c 2200 mf 16 volts, 80c, 2200 35 volts \$1.20. Transistors BC549 6 for \$1.00 or 18c each. BC557 6 for \$1.00 or 19c each. Diodes IN914A 10 for \$1.00 12c each. All components brand new from manufacturers or agents. Each value of component individually packed. Post and packing included in all orders over \$6.50. For orders less than \$6.50 add 40 cents for post and packing. 5% discount on orders over \$35.00. 10% discount on orders over \$75.00. Send orders to **RAM ELECTRONICS**, 575 SYDNEY ROAD, SEAFORTH, N.S.W. 2092. Please enclose cheque or money order.

## BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD, CLAYTON, VICTORIA 546 5076

### ATTENTION!!!!


All constructors of Electronics Australia projects  
**BRIGHT STAR CRYSTALS PTY.LTD.**

We have ALL CRYSTALS for past and present projects, including September's Quartz Crystal Drive Unit for clock, 3276-8 KHz "D" spec, GGDF. (See E.A. Sept '75 page 74).

With more than 36 years experience BRIGHT STAR can supply ALL your Crystal needs.
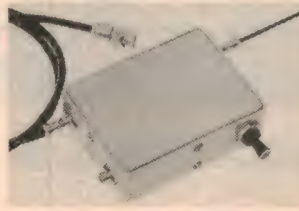
### ALSO AVAILABLE

- \* Wideband Amplifiers.
- \* Crystal Oscillators.
- \* Crystal Clock and Decade Counters. C-MOS, TTL.
- \* Pre Scalars to 250MHz. (See previous advertisements.)
- \* Send S.A.E. for new catalogue.



W. J. MONCRIEF PTY. LTD.  
PERTH. PHONE 25-5722, 25-5902

ROGERS ELECTRONICS  
ADELAIDE. PHONE 64-3296, 42-6666

FRED HOE & SONS PTY. LTD.  
BRISBANE. PHONE 47-4311

PARIS RADIO ELECTRONICS  
SYDNEY. PHONE 31-3273

DILMOND INSTRUMENTS HOBART. PHONE 47-9077

## WANTED

**ADVICE AND CRYSTALS**, headset, etc. To restore a beautiful old china crystal set—also interested in old radios and electrical / electronic devices—contact Ellis D. Fogg, Box 8, Kings Cross, 2011. Phone 31-6479.

## READER SERVICE

**FOR HIRE.** All Test Instruments, free delivery (Sydney Metro Only), free technical advice. Design, repair services also available. Ring **HOBBY HIRE** any time, any day on (02) 50-4361.

**DISPLAY ADVERTS IN MARKETPLACE** are sold by the centimetre from a minimum of 3 cms. to a maximum of 12 cms. Rate \$6.00 per column cm per insertion.

**CLASSIFIED RATES** \$1. per line per insertion payable in advance. Minimum two lines. A convenient form is provided in each issue.

**CLOSING DATE** is six weeks prior to the on-sale date. Issues are on-sale the first Monday of each month.

**ADDRESS** all classified orders, copy, enquiries, etc. to: The Advertising Manager, **ELECTRONICS Australia**, Box 162, Beaconsfield, 2014




# NATIONAL RADIO SUPPLIES

332 PARRAMATTA RD, STANMORE, NSW 2040. PH. 56-7398.


## SERVICE PACK SPECIALS.

## STOCK UP FOR THE NEW YEAR


<b>CERAMIC CONDENSER PACK</b> all different values 100 for \$2.50	<b>MICA PACK</b> A 50 for \$3.00 B 20 for \$1.80	<b>RESISTOR WIRE WOUND Pack</b> 50 for \$5.00 3 & 5 & 10 watt.	<b>WALKIE TALKIE</b>  <b>SANYO</b> The Best   1/2w \$36.00 1 watt \$46.00 5 watt Power \$75.00 27.88
<b>STEREO TURNTABLE KIT</b> with pick up arm & motor \$7.90	<b>RESISTOR PACK</b> Mixed 1 watt & 1/2 watt 100 for \$1.50	<b>POTENTIOMETER PACK</b> 20 for \$2.50	
<b>DOUBLE POTENTIOMETER Pack</b> 10 for \$4.00	<b>VIBRATORS 6V</b> 5211 A.W.A. \$1.00	<b>POLY PACK The Best</b> 50 for \$2.00	
<b>5BP1 OSCILLOSCOPE TUBE</b> still only \$1.50	<b>SELENIUM RECTIFIER 2.5 amp</b> SPECIAL at \$1.50	<b>TRANSISTOR SPECIAL</b> MJ3055-2N3055 \$1.15	
<b>8 ELEMENT AERIALS</b> 406 or 215 \$15.00 by train.	<b>PORTABLE PYE GRAM</b> cabinet only \$3.50	<b>TRANSISTOR SPECIAL</b> BC147, BC148, BC149 10 for \$1.20	
<b>TRANSISTOR</b> 2SC463A equivalent BU105 \$2.60	<b>T.V. BALUN</b> 300 ohms to 75 ohms 80c	<b>B.S.R. AUTO CHANGERS</b> Ceramic cartridge \$41.00 G11204 Magnetic cartridge \$49.00 G11302	
<b>SPECIAL IN VALVES</b> 6CM5 \$1.50      6DX8 \$1.20 6BL8 \$1.00      6BU8 \$1.10 6BM8 \$1.00      6GV8 \$1.10 6Y9 \$1.50      6GW8 \$1.10 6X9 \$1.20      6SN7 \$1.00 6U9 \$1.20      6JW8 \$1.30 1S2 \$1.00      6AL3 \$1.15		<b>MAGNAVOX SPEAKERS</b> 6WR 8 ohms and 15 ohms \$10.75 8WR 8 ohms and 15 ohms \$11.85 10WR 8 ohms and 15 ohms \$13.85	<b>SPEAKERS DUAL IMPEDANCE</b> 8 ohms & 4 ohms 5" \$3.00 6" \$3.20 7 by 5" \$4.20 6 by 9" \$5.20
<b>Please add 15% to all parcels for postage and packing, thank you. For all heavy parcels please state nearest rail station.</b>			

# AUDITEC


PRESENTS THE STATE-OF-THE-ART IN AUDIO:

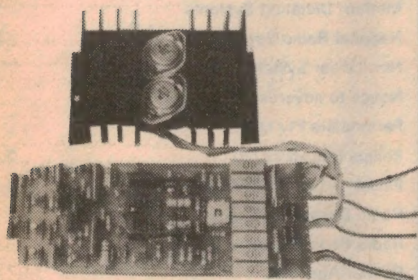

033

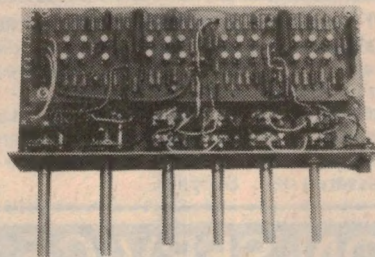

1036

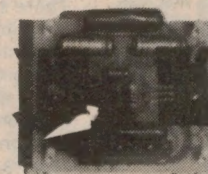

035

*We believe the combination of these modules will build you the best quality audio amplifier currently available at any price! Send the coupon below for full details.*

**Auditec modules are available from:**

**SYDNEY:** ALAN OLIVER ELECTRONICS P/L, 188 Pacific Highway, St. Leonards 2065. Ph.: 43-5305

**BRISBANE:** DELSOUND PTY. LTD., 35 Logan Road, Woolloongabba 4102. Ph.: 91-7048

**MELBOURNE:** ZEPHYR PRODUCTS, 70 Batesford Road, Chadstone 3148. Ph.: 56-7231

**BUNDABERG:** BUNDABERG HI-FI, 244 George Street, Bundaberg 4670. Ph.: 71-3176

**DUBBO:** DUBBO HI-FI, 64 Talbragar Street, Dubbo 2830. Ph.: 82-3793

**TAMWORTH:** HI-FI GALLERY, 186 Bridge Street, Tamworth 2340. Ph.: 65-7788

**ADELAIDE:** KTRONICS, 12 Peel Street, Adelaide 5000. Ph.: 87-5505

**And from: AUDITEC AUSTRALIA**  
P.O. Box 228 Hornsby, N.S.W. 2077  
Phone (02) 47-4166

AUDITEC AUSTRALIA, PO BOX 228, HORNSBY, NSW 2077.  
PLEASE SEND DETAILS OF THE NEW 033, 035 AND 1036 MODULES TO:

NAME: .....

ADDRESS: .....

POSTCODE: .....

EA3/76



# KONTAKT

specialized aids to repairs and servicing



<b>WL</b> degreasing wash	<b>61</b> for new contact protection	<b>90</b> magnetic head cleaner
<b>33</b> conductive graphites	<b>70</b> clear acrylic lacquer	<b>100</b> anti-static coating
<b>SK10</b> soldering varnish	<b>72</b> insulating silicone oil	<b>101</b> de-watering fluid
<b>60</b> corroded contacts cleaner	<b>75</b> freezing spray	<b>600</b> tuner cleaner
	<b>88</b> lubricating oil	

ADELAIDE  
BRISBANE  
HOBART  
MELBOURNE  
PERTH  
SYDNEY

**H. ROWE  
& CO PTY LTD**

A Member of the  
Hecla Rowe Group

There's a KONTAKT spray for every insulating, maintenance, protection, sealing and servicing need. Use KONTAKT for all electrical, radio-TV, tape recorders, switchboards, ignition and mechanical repairs. Where necessary a de-

tachable nozzle is supplied for selective cleaning of individual parts or those which are not easily accessible. Further information and stocks available from your Electrical, Radio-TV or Automotive Supplier.

## SUBSCRIPTION SERVICE



**ELECTRONICS  
Australia**

### Subscription Rates

\$A14.00 per year  
within Australia.  
\$A17.00 per year  
elsewhere.

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher. For publisher subscriptions post this coupon, with your remittance, to Electronics Australia Subscription Dept., John Fairfax & Sons Ltd, GPO Box 506, Sydney, 2001. Subscription will start with first available issue.

Name .....  
Address .....  
Postcode ..... Enclosed is ..... for ..... years

## Advertising Index

	Page
ACE Radio	116
Akai Australia Pty Ltd	5
Apollo Hi Fi Centre	111
Arlunya Pty Ltd	84
Audio Engineers Pty Ltd	18
Auditec Australia	127
Australian Time Equipment Pty Ltd	55
Bright Star Crystals Pty Ltd	126
British Merchandising Pty Ltd	44, 95, 114
BWS Electronics Pty Ltd	50
Classic Radio Service	101
R H Cunningham Pty Ltd	76
Danish Hi-Fi Pty Ltd	6
Deitch Bros	122
Dick Smith Electronics Pty Ltd	42, 62, 63, 99
Diggerman Electronics	108
Dynetics	38
E D & E (Sales) Pty Ltd	113
Edge Electrix	120
Electrocraft	44
Ferguson Transformers Pty Ltd	103
Richard Foot (Aust) Pty Ltd	109
General Electronic Services Pty Ltd	81
Haco Distributing Agencies Pty Ltd	IBC
Hagemeyer (Aust) B.V.	OBC
Harman Australia	16
George Hawthorn Electronics	106
Hewlett-Packard Aust Pty Ltd	125
International Correspondence Schools	54
Interson	36
IRH Components Pty Ltd	70
Jacoby, Mitchell & Co Pty Ltd	22, 75
Lafayette Electronics	105
Lanthur Electronics	114
Marconi School of Wireless	53
McGills Newsagency Pty Ltd	115
Micronics	58
Modern Dictating Systems	110
National Radio Supplies	127
Non Linear Systems	88
Notice to advertisers	47
Parameters Pty Ltd	86
Philips Industries Ltd	2, 66
Plessey Australia Pty Ltd	4, 73
Radio Despatch Service	91
Radio Parts Pty Ltd	30
Ralmar Agencies	11
RCS Radio Pty Ltd	77
The Rosicrucians	118
H Rowe & Co Pty Ltd	128
Royston Electronics	23, 27
Scope Laboratories	124
Peter Shalley Electronics Pty Ltd	60
Sony Kemtron Pty Ltd	IFC, 20
Stanton Pickering	8
Stott's Mayna Sighter	57
Stott's Tech Correspondence College	33
Sulco	14
Video & Hi Fi Centre	45
Warburton Franki Pty Ltd	52
WHK Electronics	90
Willis Trading Co	118
Wireless Institute of Australia	119





## Introducing the revolutionary UD-XL EPITAXIAL cassette




Developed by MAXELL this completely new EPITAXIAL magnetic material combines the advantages of the two materials (gamma-hematite and cobalt-ferrite): the high sensitivity and reliable output of the gamma-hematite in the low and mid-frequency ranges and the excellent performance of the cobalt-ferrite in the high-frequency range. The result is excellent high-frequency response plus wide dynamic range over the entire audio frequency spectrum.

Compared to chrome tape, sensitivity has been improved by more than 3.5dB. Because EPITAXIAL is non-abrasive, it extends to the life of the head. Consequently, the UD-XL delivers smooth, distortion-free performance during live recording with high input. When using UD-XL it is recommended that tape selector be in the NORMAL position.




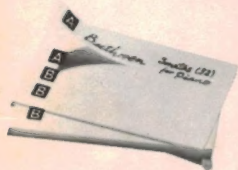Fidelity is also ensured by a precision-manufactured cassette shell with a special anti-jamming rib that provides smooth tape travel and helps eliminate wow and flutter.





Another good idea of the UD-XL cassette is a replaceable self-index label. Simply peel off the old label and put on a new one when you change the recording contents. No more mess on the label.

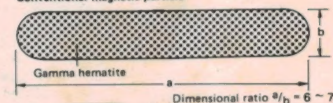Magnetic material structure  
Conventional magnetic particle



EPITAXIAL magnetic particle

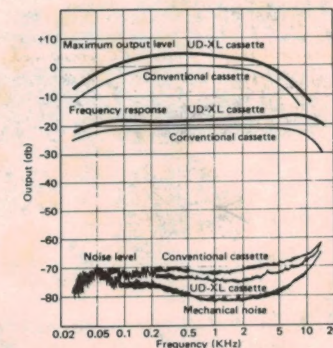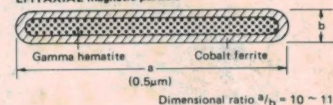

# maxell®

For further information please write to Maxell Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033.

WT.GD. 76M



# TOP DECK.



1669



1668



1667



1655

Whichever cassette deck you finally adopt from the JVC range, you can't lose. All have been designed with the sound connoisseur in mind.


If, however, money is no object and you won't settle for less than one of the best, then may we recommend the 1669 and 1950.

1669 — ANRS — JVC exclusive noise reduction system, separate motors driving the capstan and reels, feather-light operation with servo assisted controls, memory counter with automatic restart.


1950 — Once again ANRS — JVC exclusive noise reduction system, cronus head for greater fidelity and life, independent drive mechanism, plus all the controls built up front.

These are just some of the features that make these one of the best.

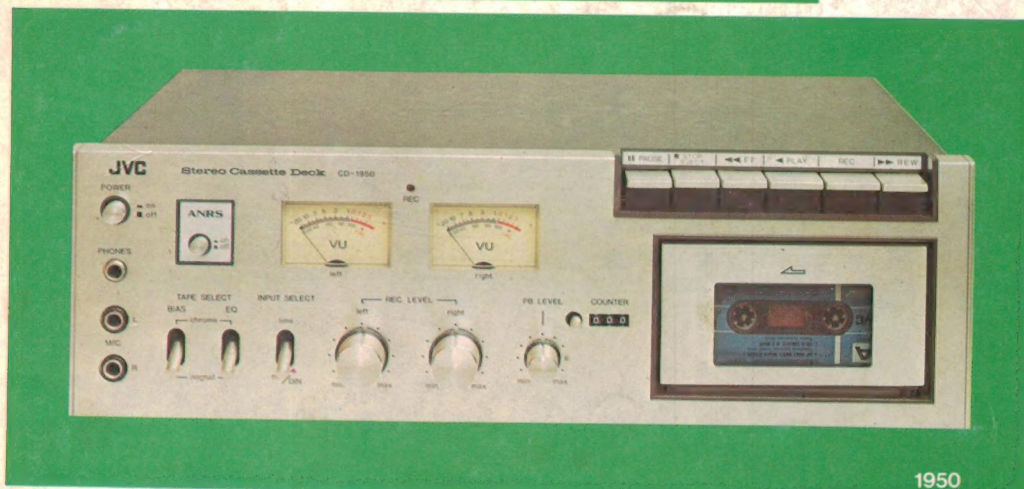But whatever you're prepared to pay, with JVC you can be sure your money is on the top deck.



1950

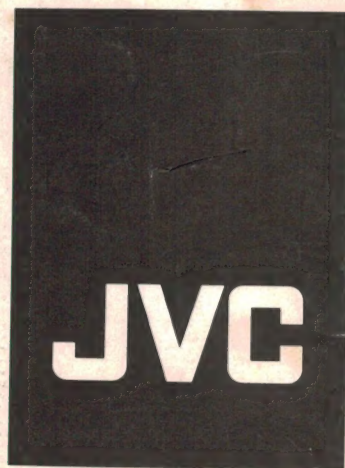

VICTOR COMPANY OF JAPAN LIMITED

Guaranteed and serviced throughout Australia and Pacific Islands by Hagemeyer (Australasia) B.V. Branches in all states.

WT.GD69J